

# **Three-Level Converters – A New Approach for High Voltage and High Power DC-DC Conversions**

*Presented by*

*Xinbo Ruan*


**College of Electrical and Electronic Engineering  
Huazhong University of Science and Technology**

- 1. Backgrounds**
- 2. Derivation of a Family of Three-Level Converters**
- 3. Improved and Simplified Three-Level Converters**
- 4. Buck TL Converter**
- 5. ZVZCS PWM Hybrid Full-Bridge Three-Level Converter**
- 6. Possible of Three-Level Voltage**
- 7. Conclusions**

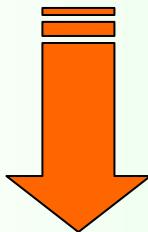- 1. Backgrounds**
- 2. Derivation of a Family of Three-Level Converters**
- 3. Improved and Simplified Three-Level Converters**
- 4. Buck TL Converter**
- 5. ZVZCS PWM Hybrid Full-Bridge Three-Level Converter**
- 6. Possible of Three-Level Voltage**
- 7. Conclusions**

3-phase 380V $\pm$ 20% ac input is rectified to a dc voltage:


- w/o PFC: Vdcmax = 630V
- with PFC: Vdc = 800-1000V




In order to reduce the voltage stress of the switches
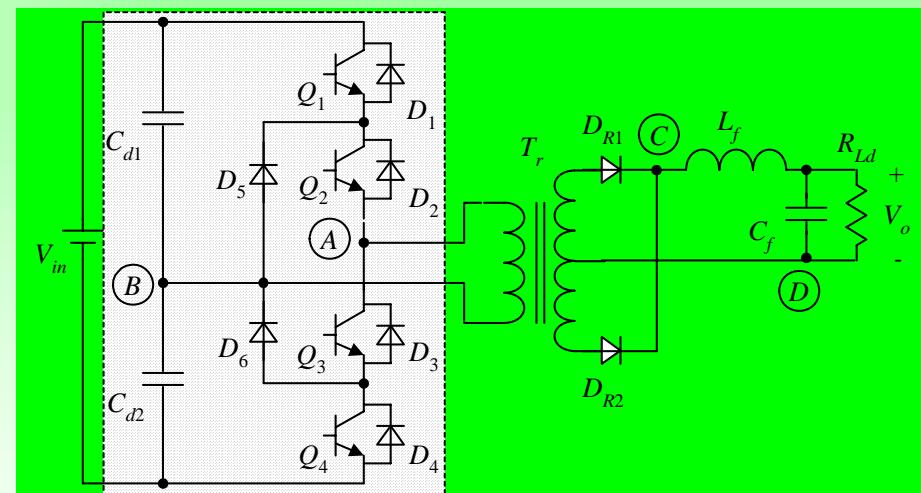
### Three-Level Converter

- ☺ The voltage stress of the power switch is half of the input voltage.



# Derivation of Half-Bridge TL Converter

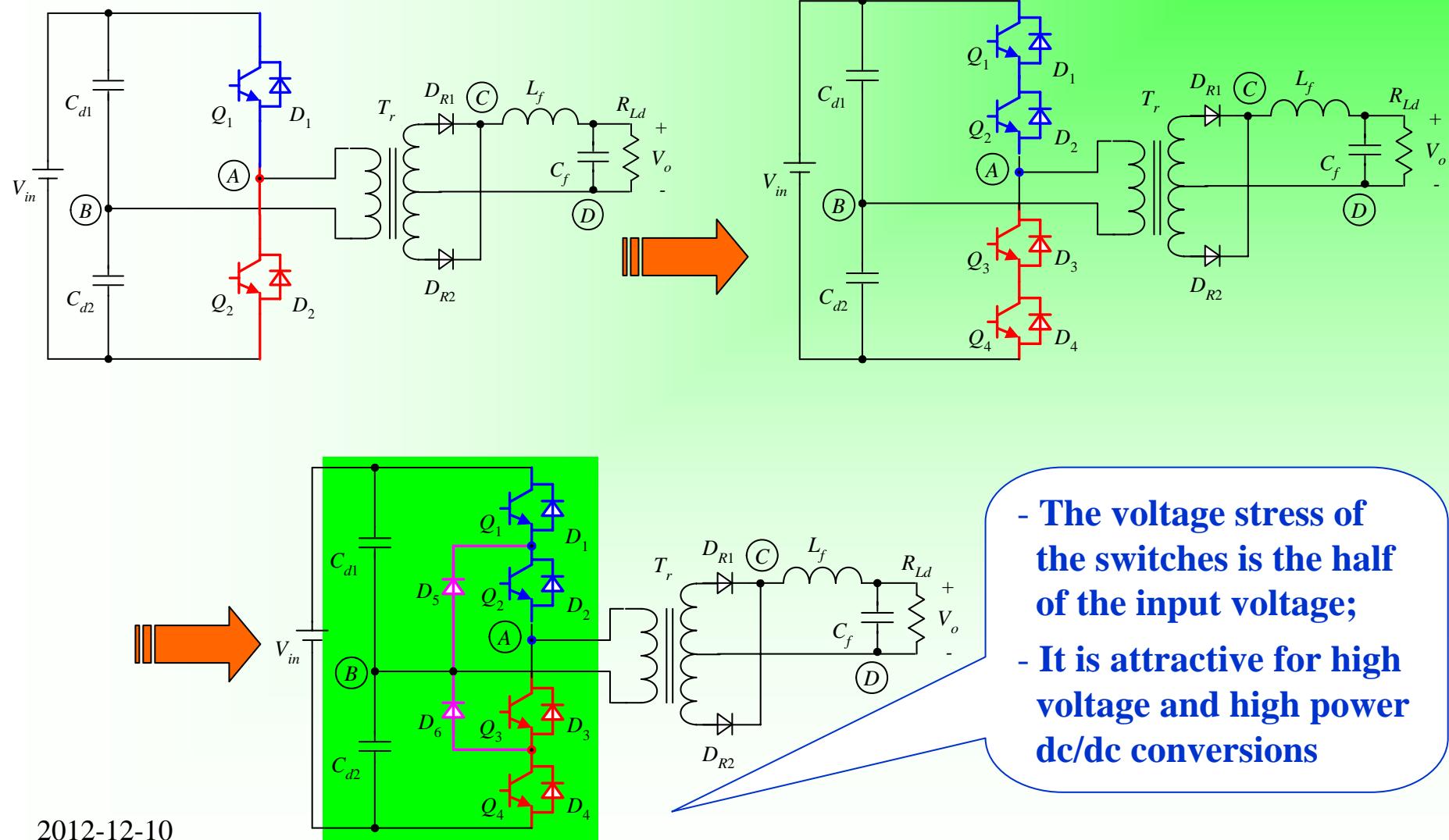


Extend the derivation of Half-Bridge Three-Level converter to all the DC-DC converters


*To reduce the voltage stress*

*of the switches.*

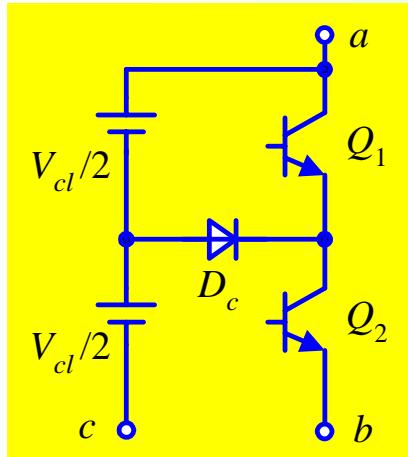1. Backgrounds
2. **Derivation of a Family of Three-Level Converters**
3. Improved and Simplified Three-Level Converters
4. Buck TL Converter
5. ZVZCS PWM Hybrid Full-Bridge Three-Level Converter
6. Possible of Three-Level Voltage
7. Conclusions









**Anode Cell**

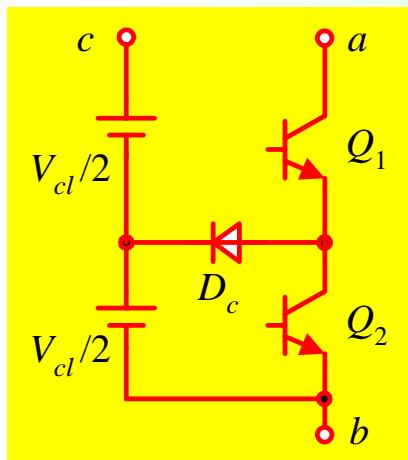

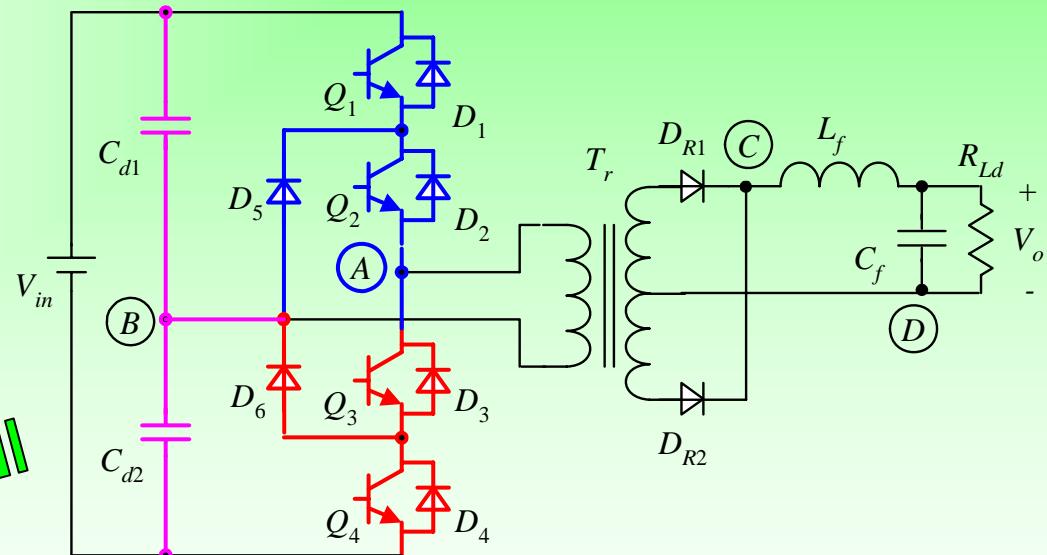
**Cathode Cell**

- Two series switches;
- Clamping voltage source splitting into two equally;
- Clamping diode.




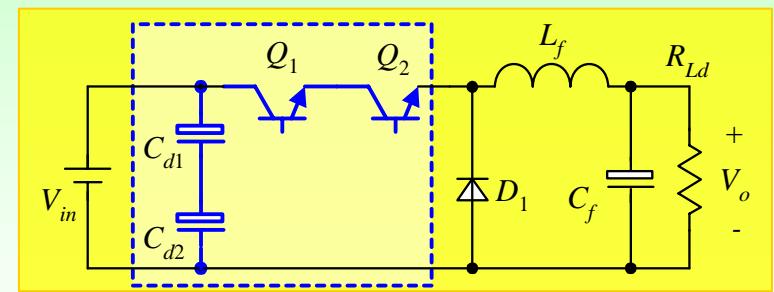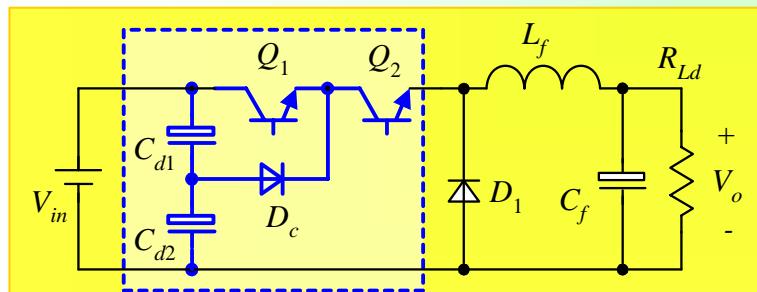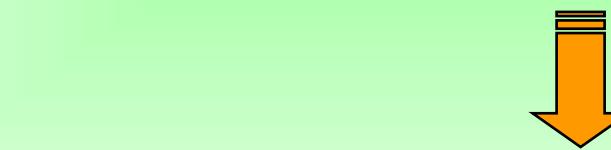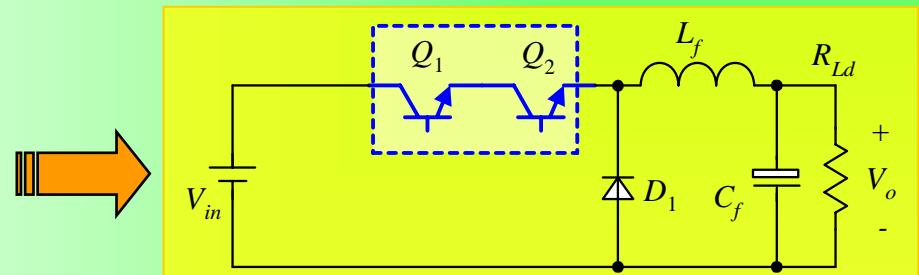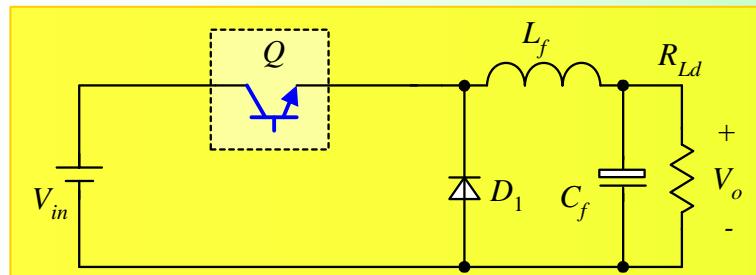


Buck

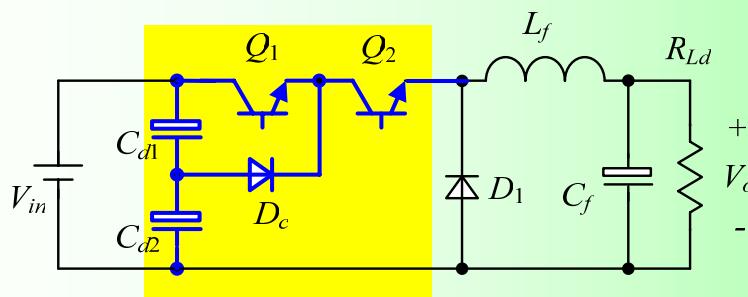


Boost

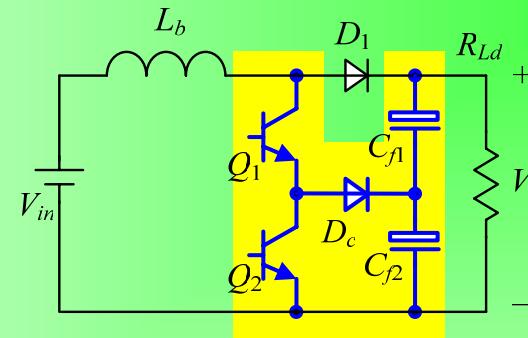


Buck/Boost

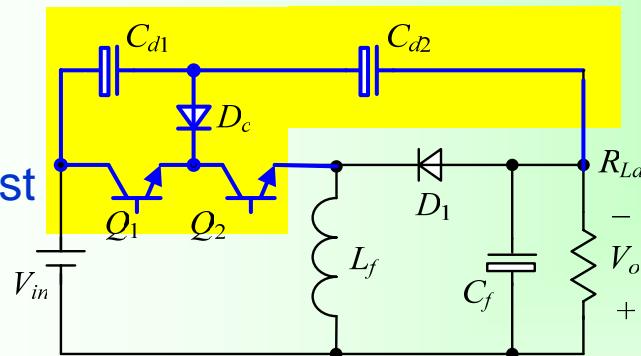


Cuk

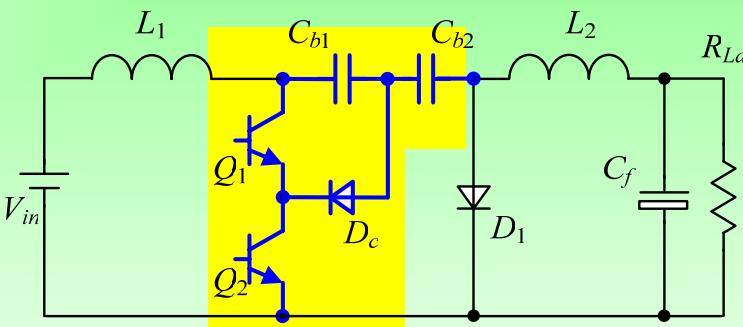


Sepic

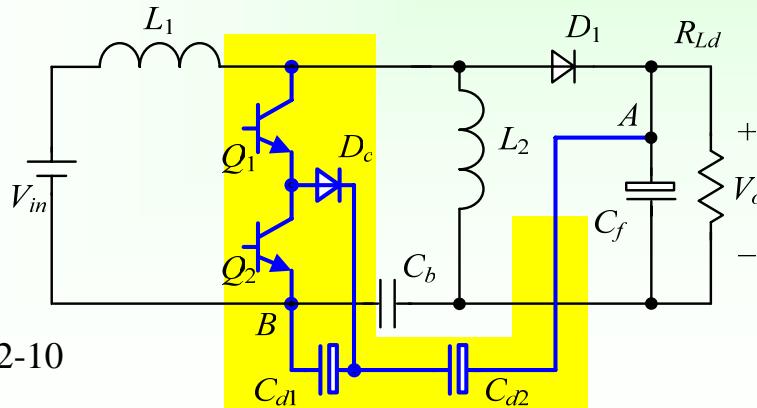


Zeta

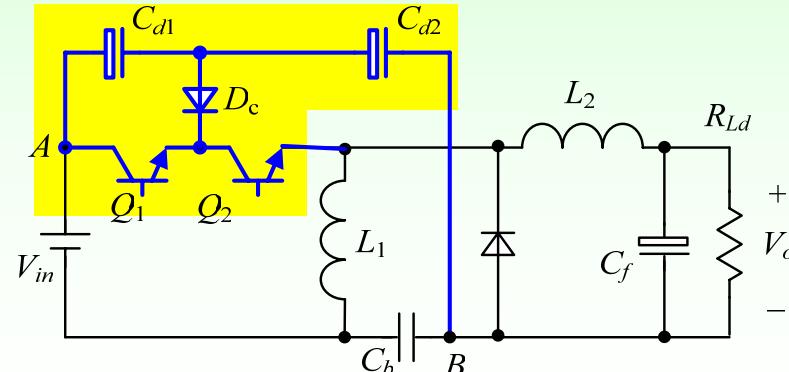


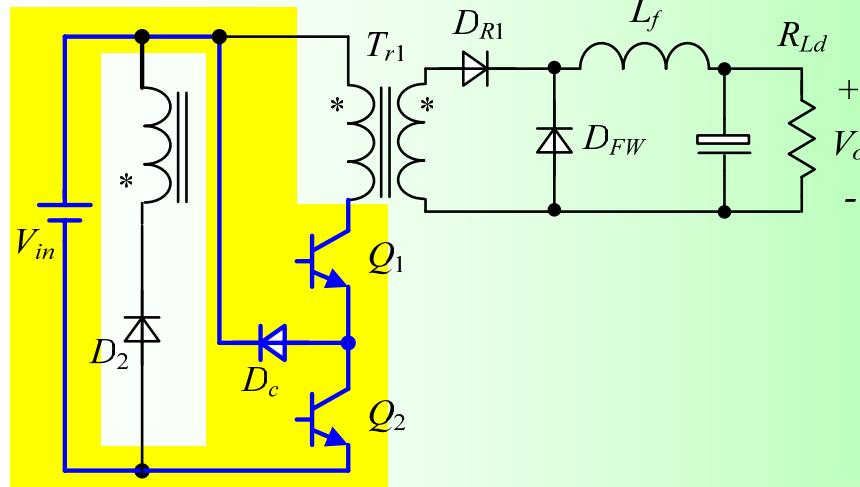


Forward

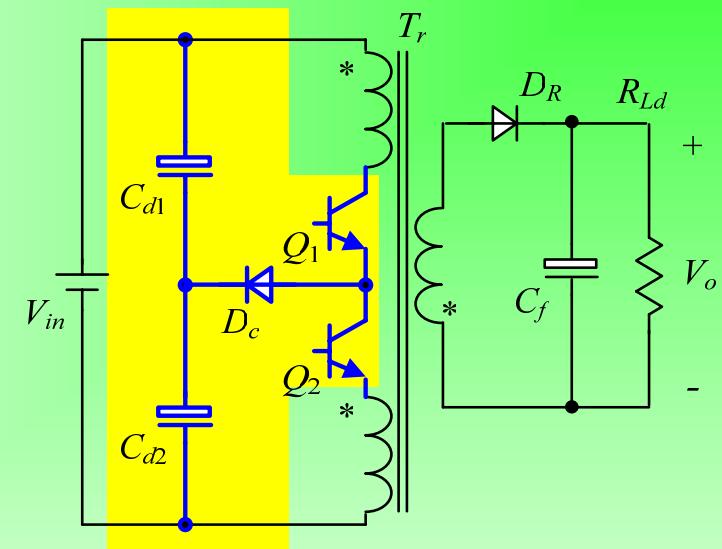


Flyback

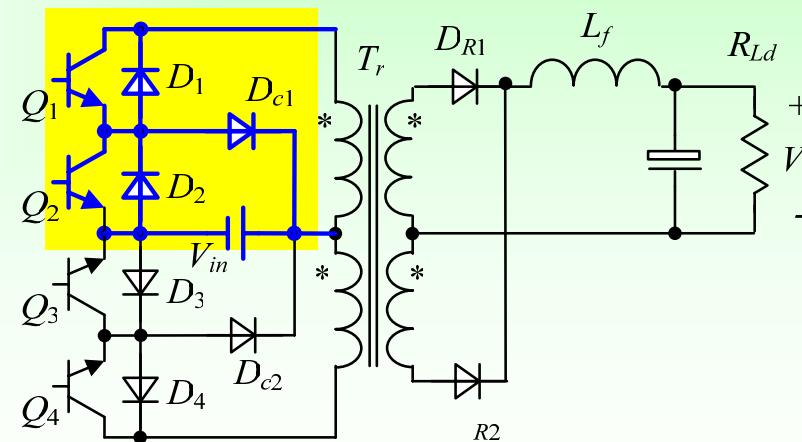

Push-Pull

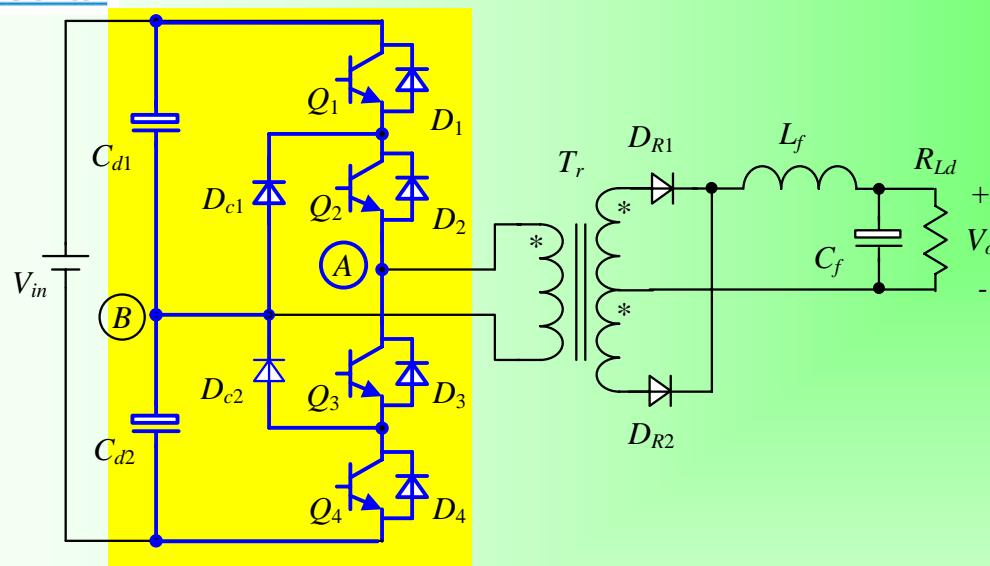


Half-Bridge

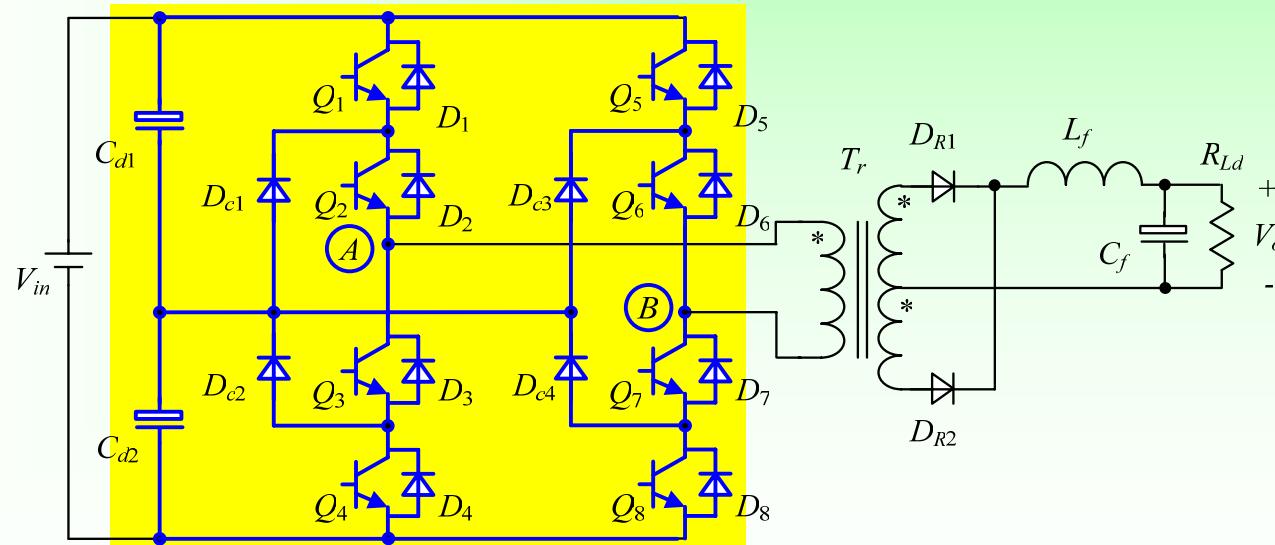




Full-Bridge




1. Backgrounds
2. Derivation of a Family of Three-Level Converters
- 3. Improved and Simplified Three-Level Converters**
4. Buck TL Converter
5. ZVZCS PWM Hybrid Full-Bridge Three-Level Converter
6. Possible of Three-Level Voltage
7. Conclusions

Buck Converter


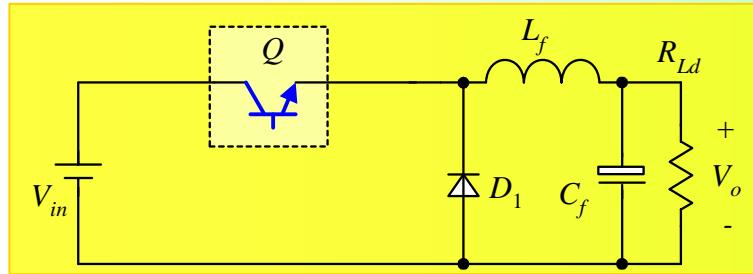


Buck TL Converter

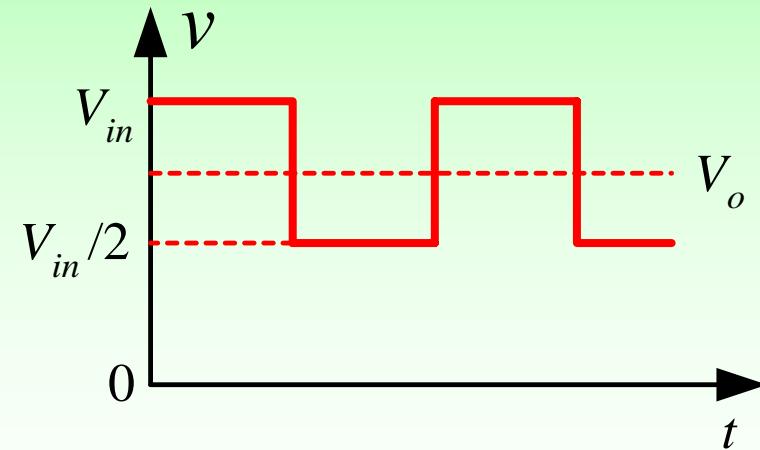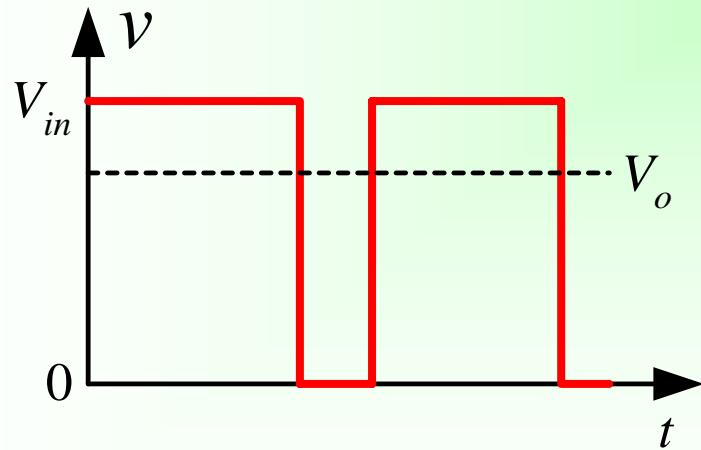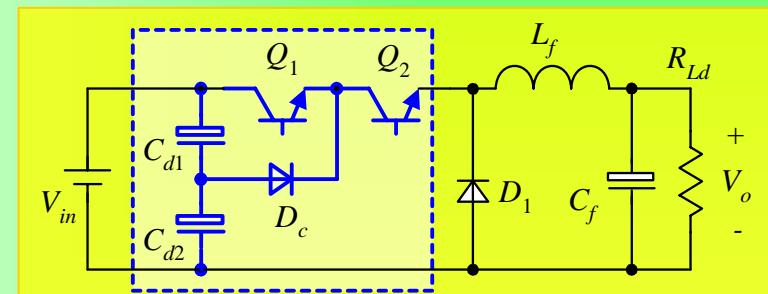


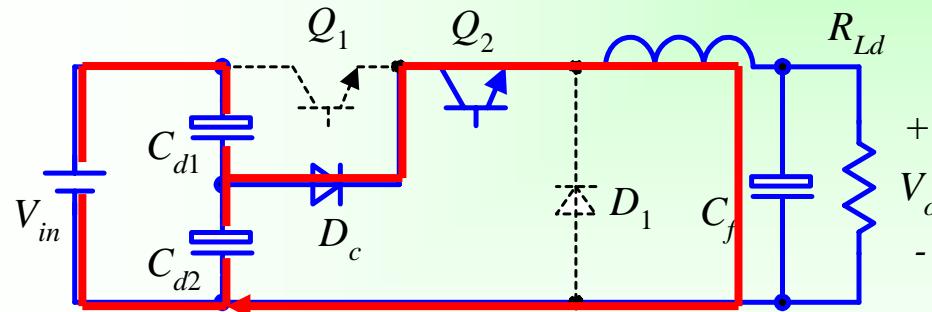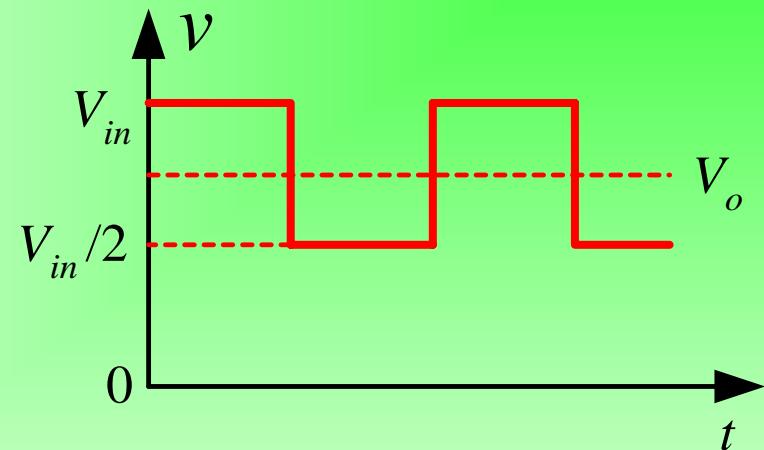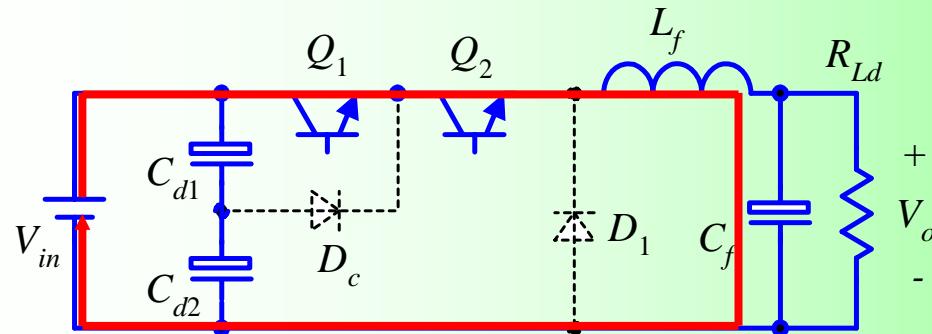



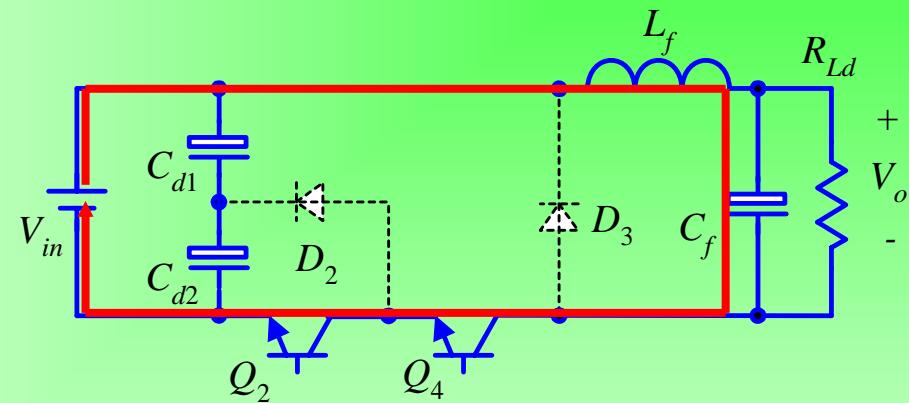
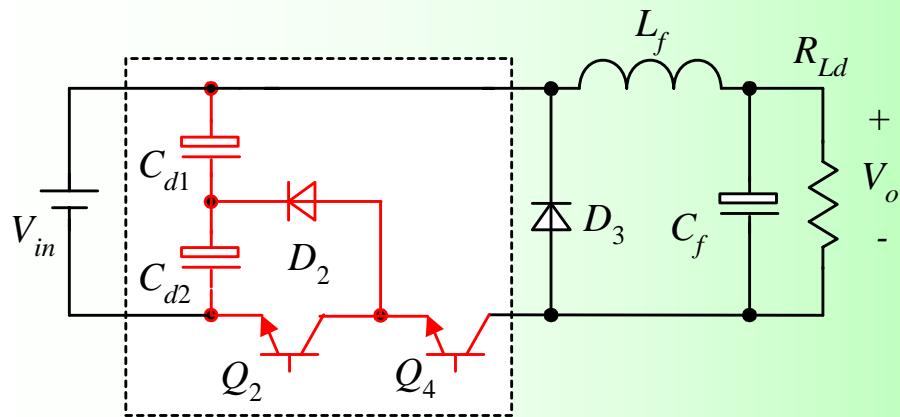
⌚  $C_{d2}$  provides more energy, which results in **unbalance of voltage of the input divided capacitors**




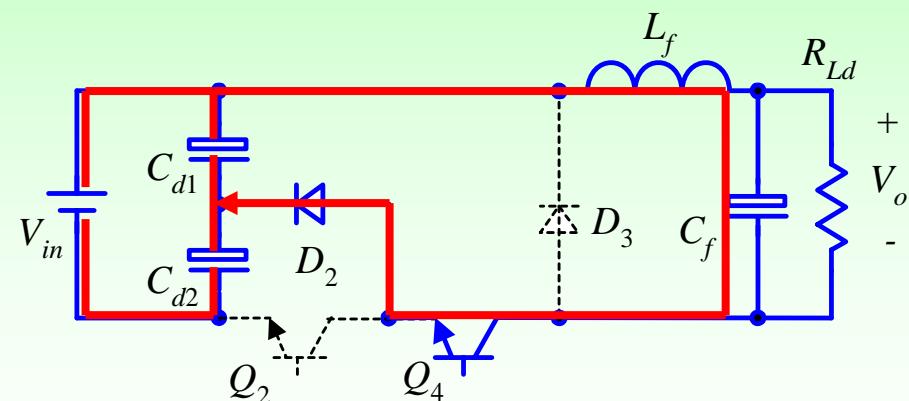
⊗  $C_{d1}$  provides more energy, which results in unbalance of voltage of the input divided capacitors





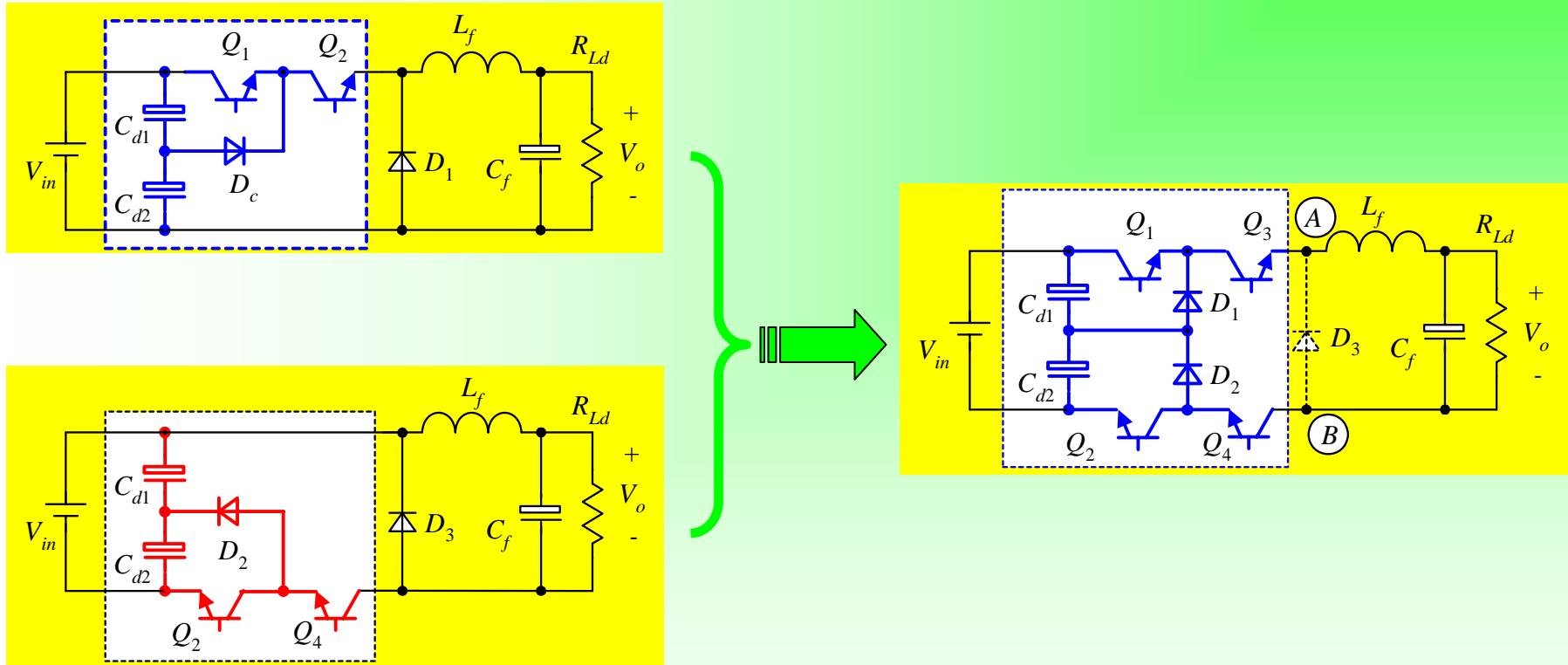

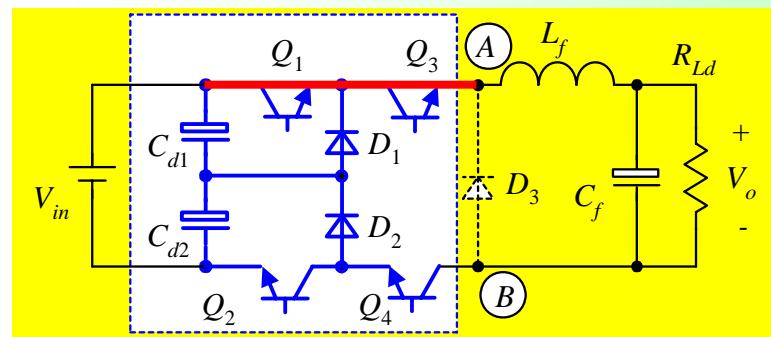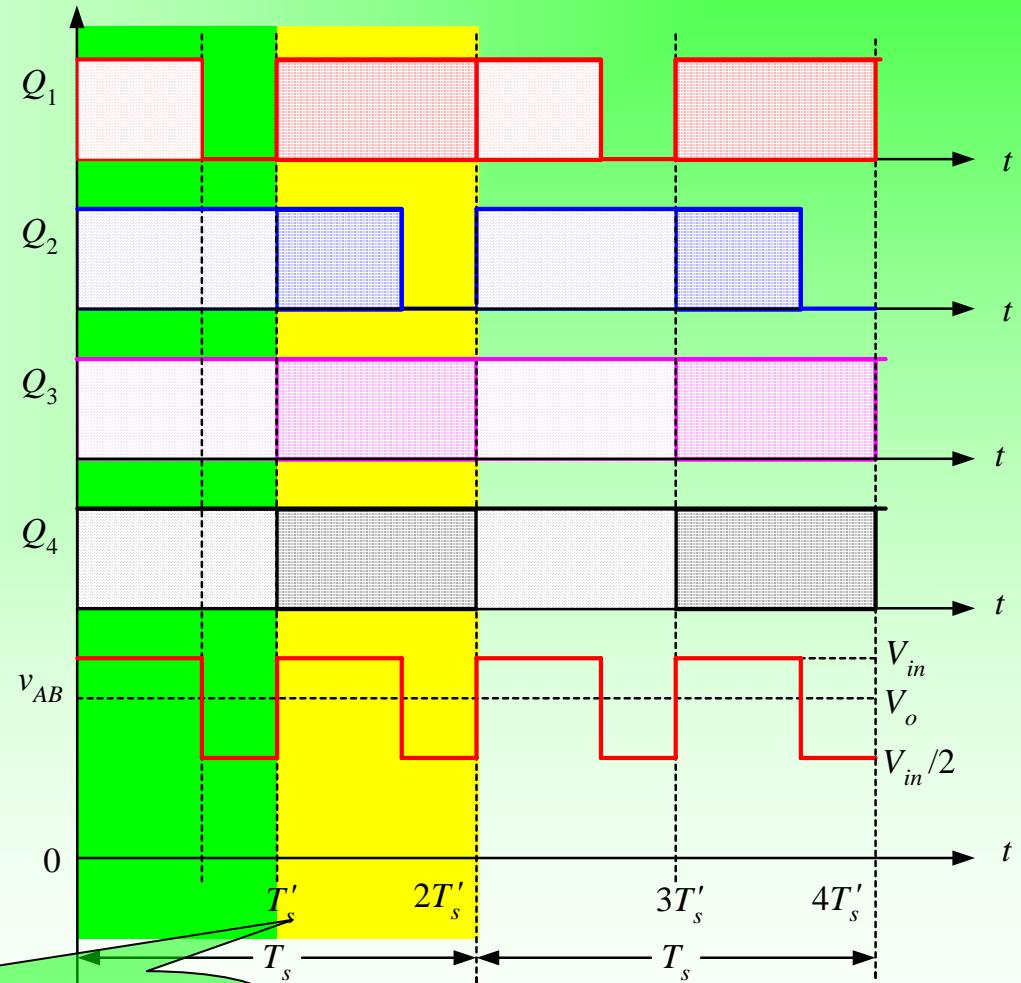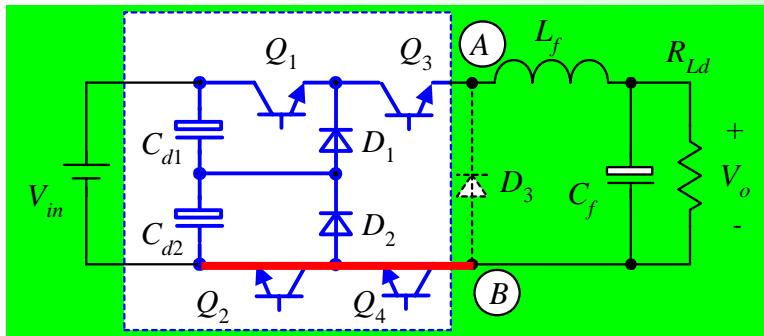

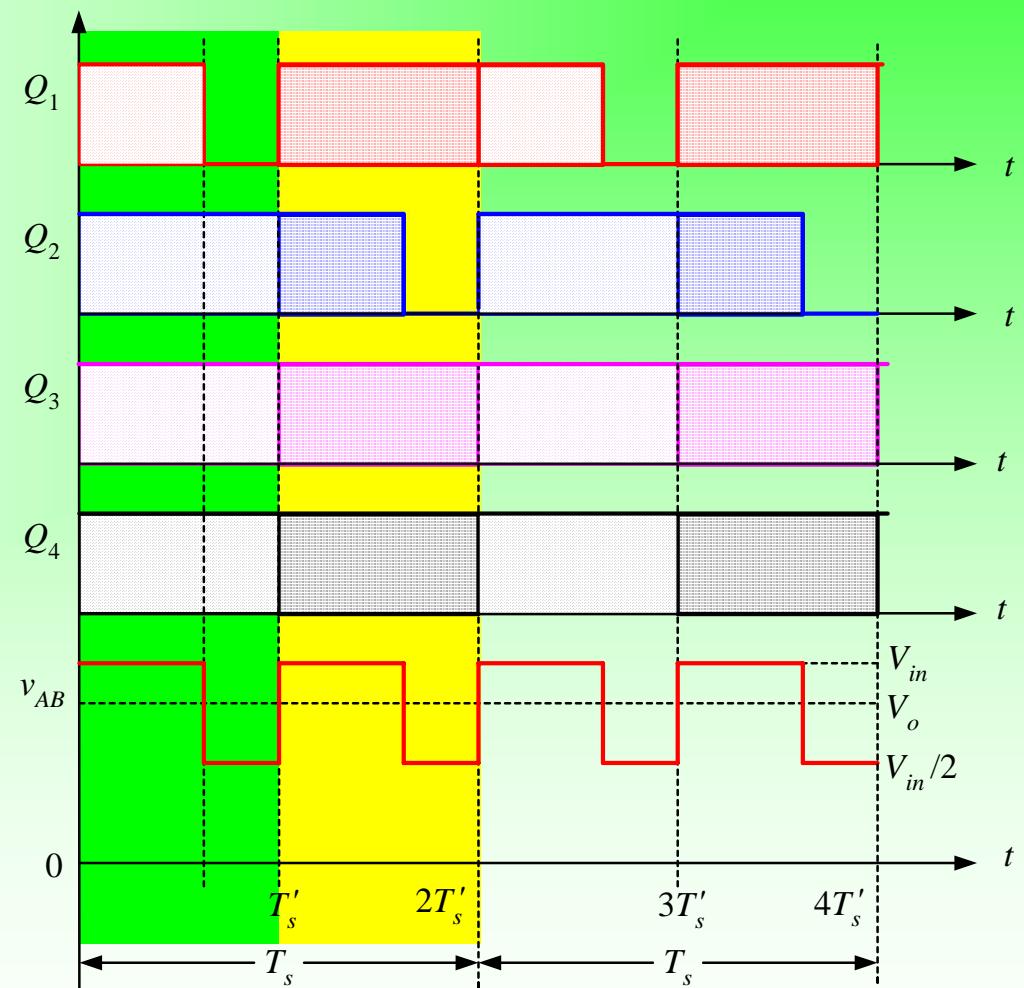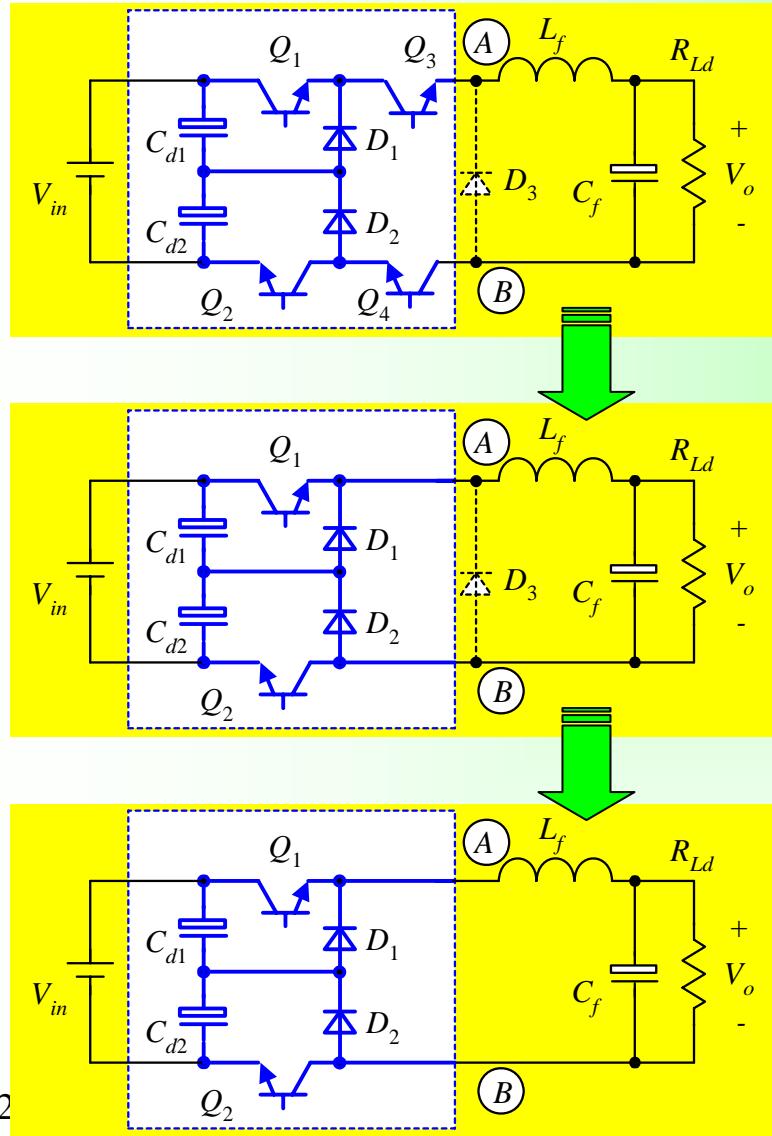
*The voltage of the divided capacitors are Balanced.*



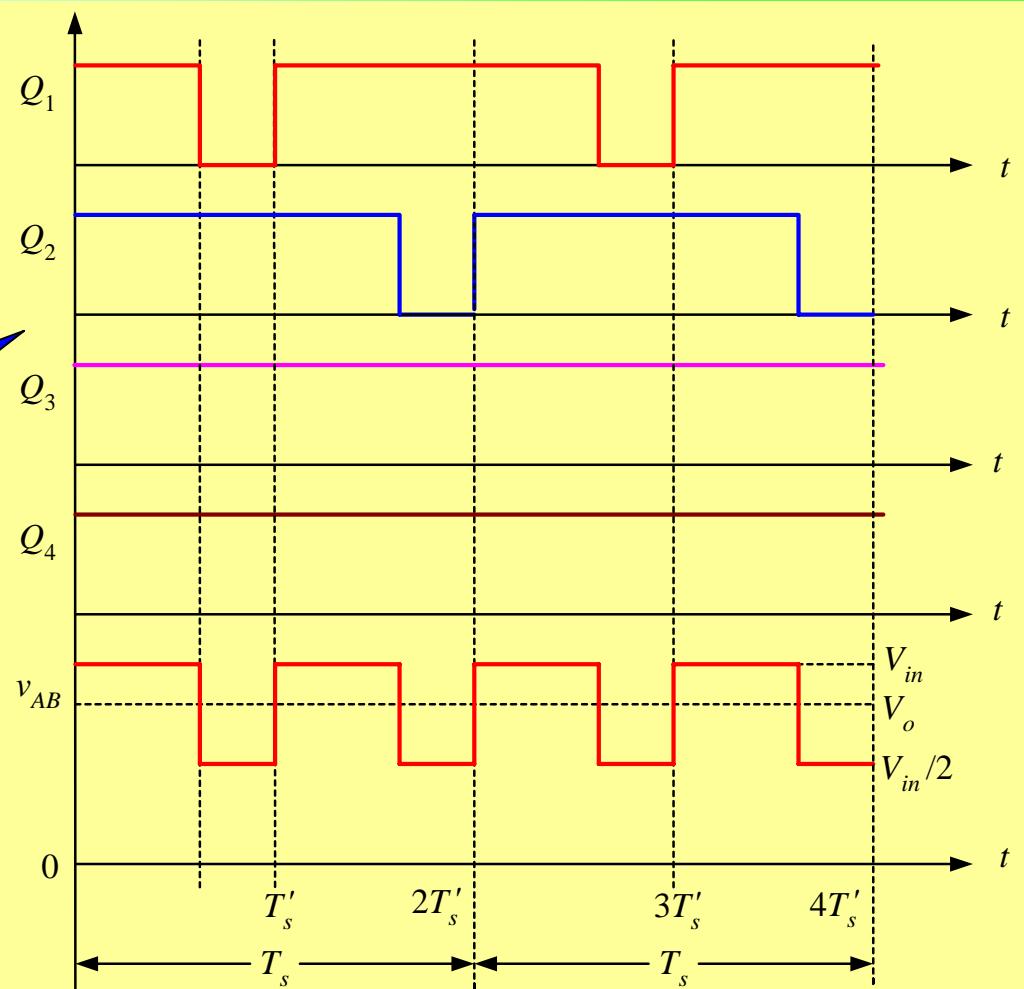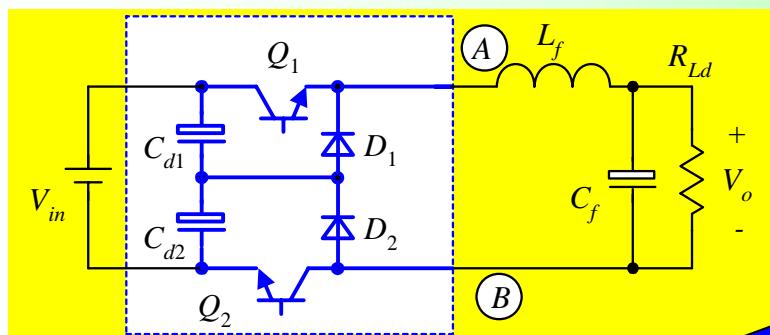


1. The voltage of the divided capacitors are **balanced**;
2. The ripple frequency of  $v_{AB}$  is twice the switching frequency;
3.  $Q_1$  and  $Q_2$  are interleaving switched.


Buck

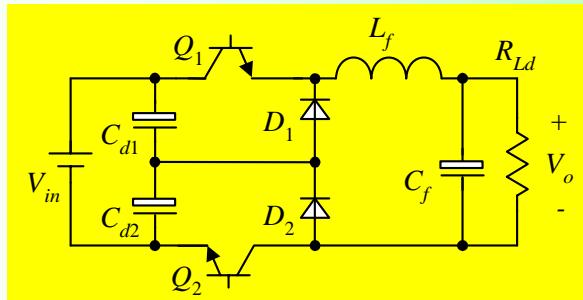


Buck/Boost

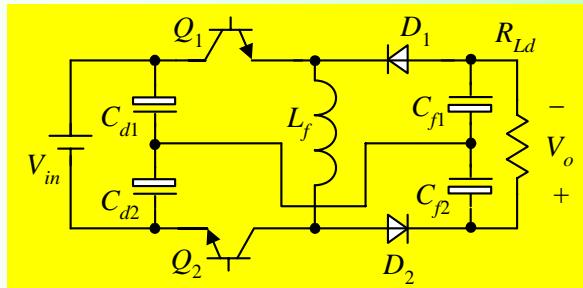


Sepic

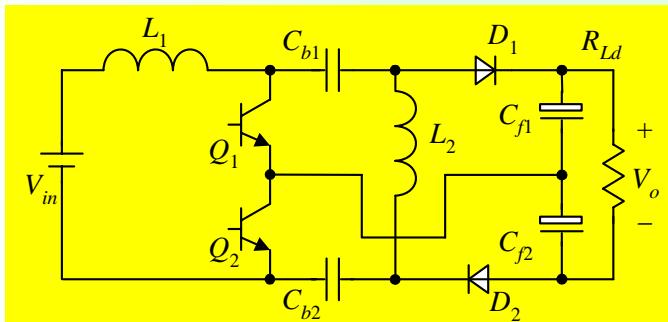


Boost

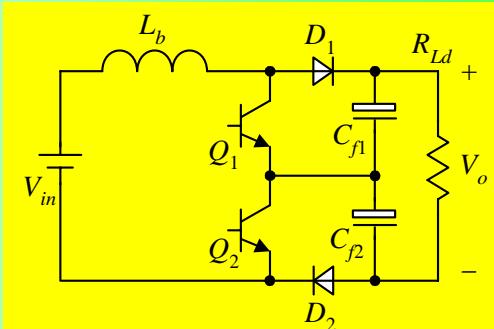


Cuk

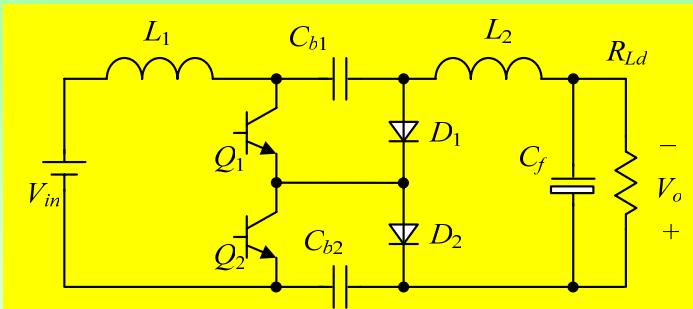


Zeta

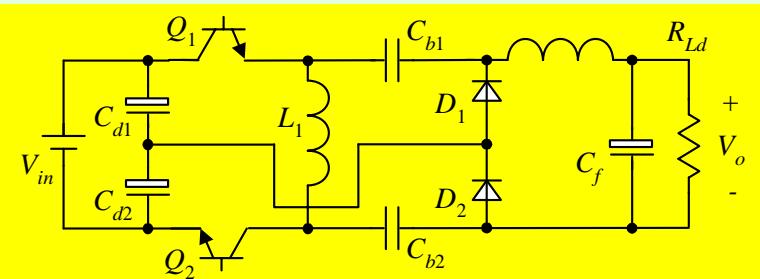


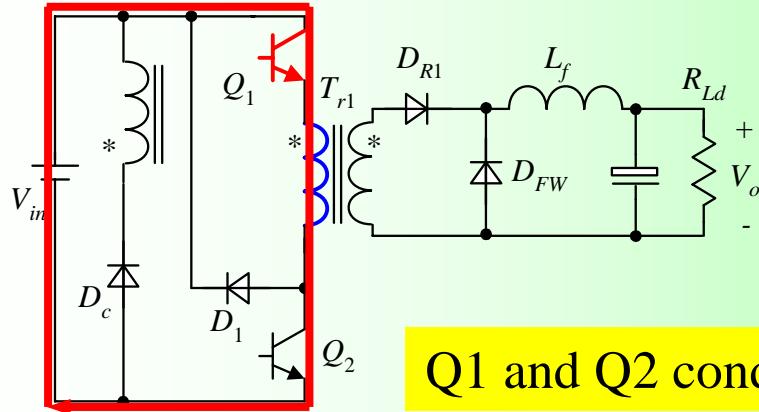


Q1 and Q2 conduct






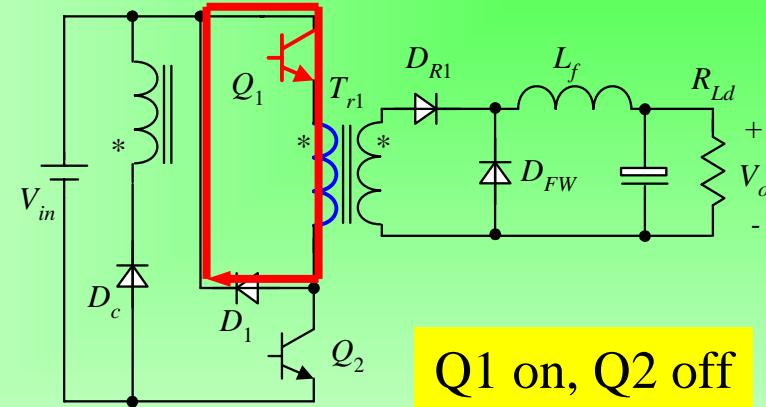


Q1 on, Q2 off



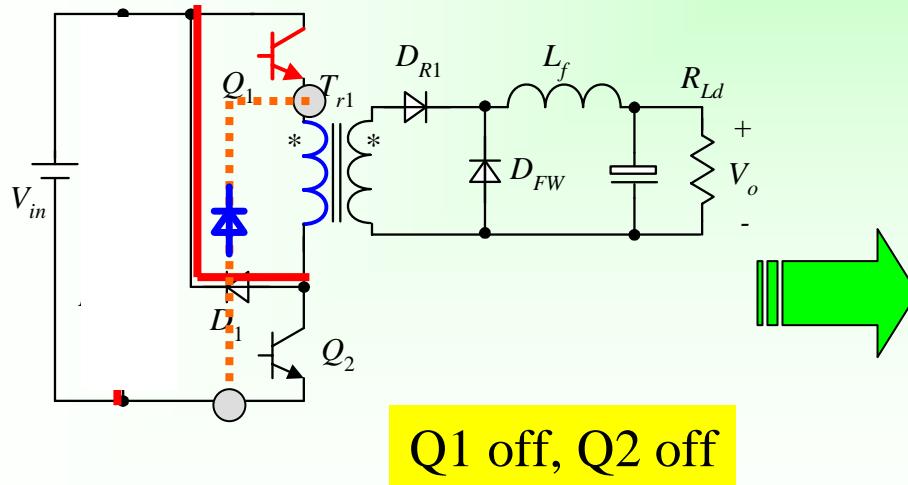


Q1 off, Q2 off


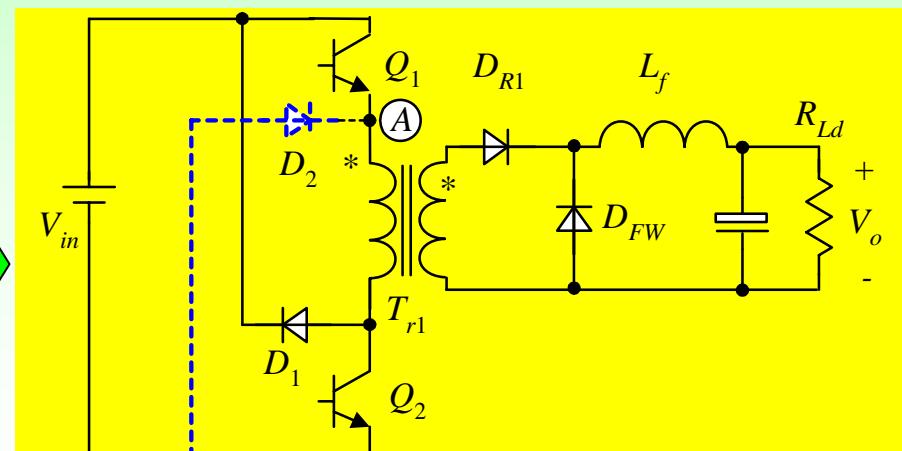


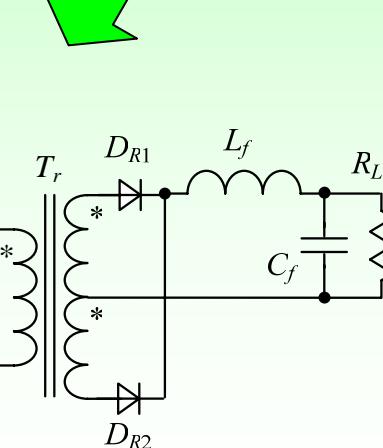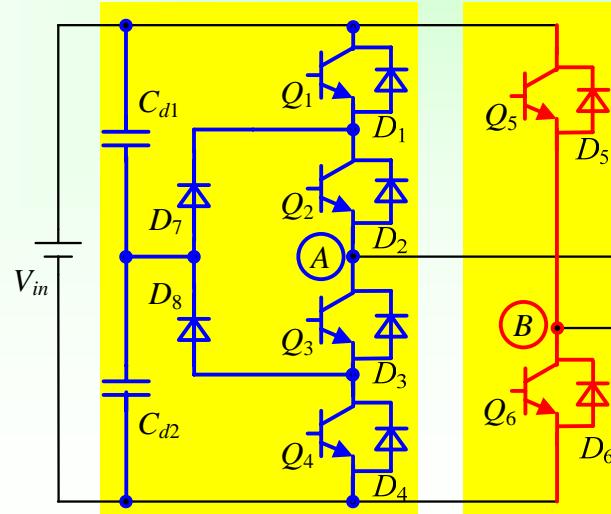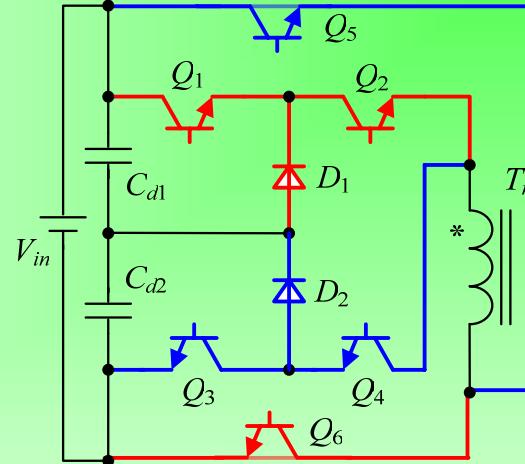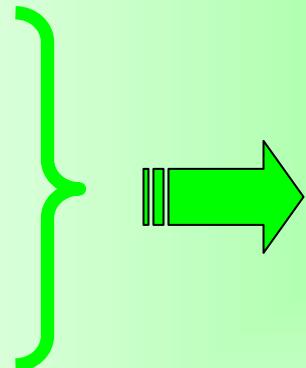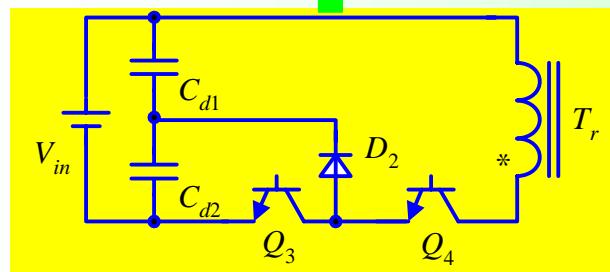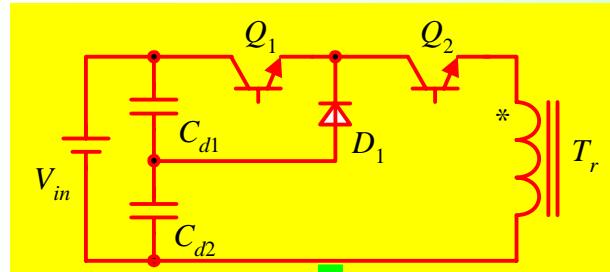

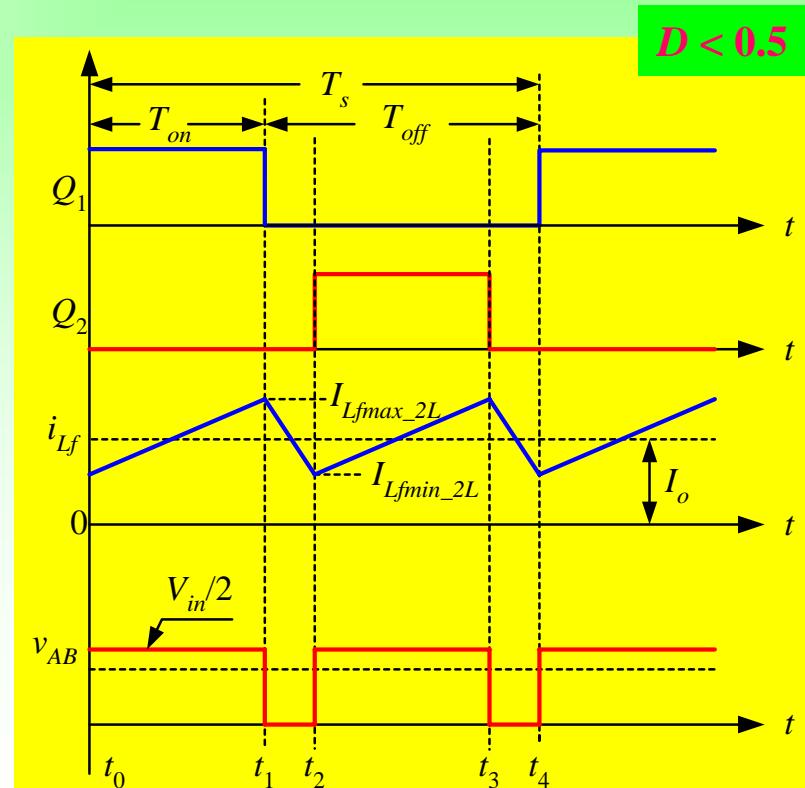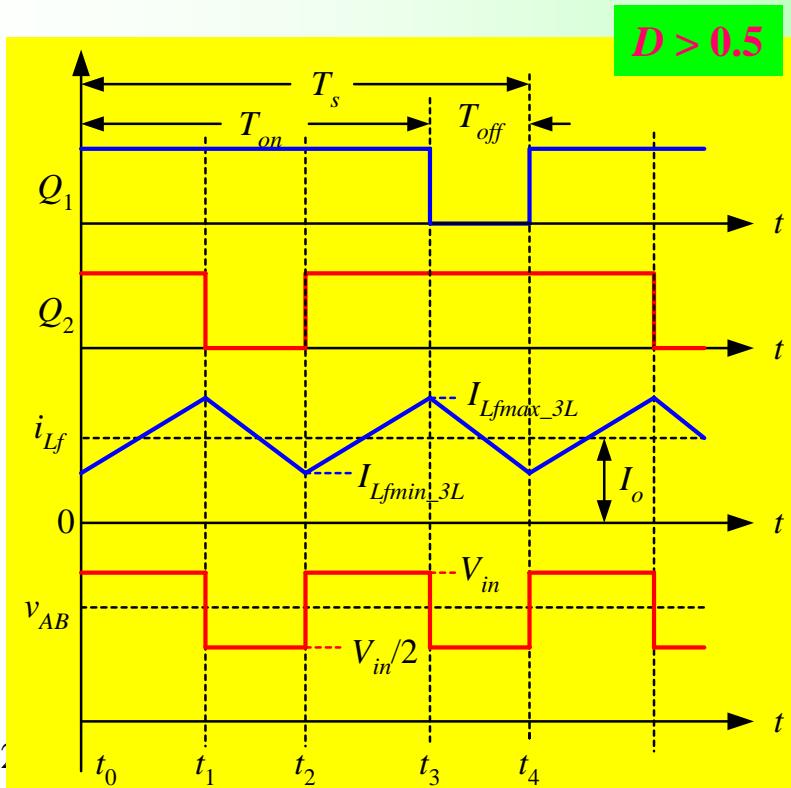
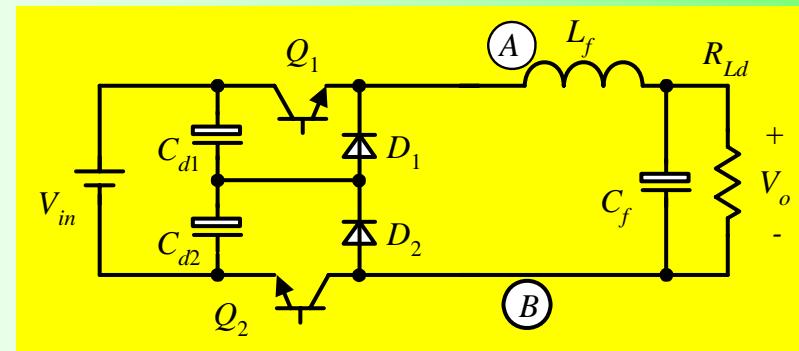
1. Backgrounds
2. Derivation of a Family of Three-Level Converters
3. Improved and Simplified Three-Level Converters
- 4. Buck TL Converter**
5. ZVZCS PWM Hybrid Full-Bridge Three-Level Converter
6. Possible of Three-Level Voltage
7. Conclusions



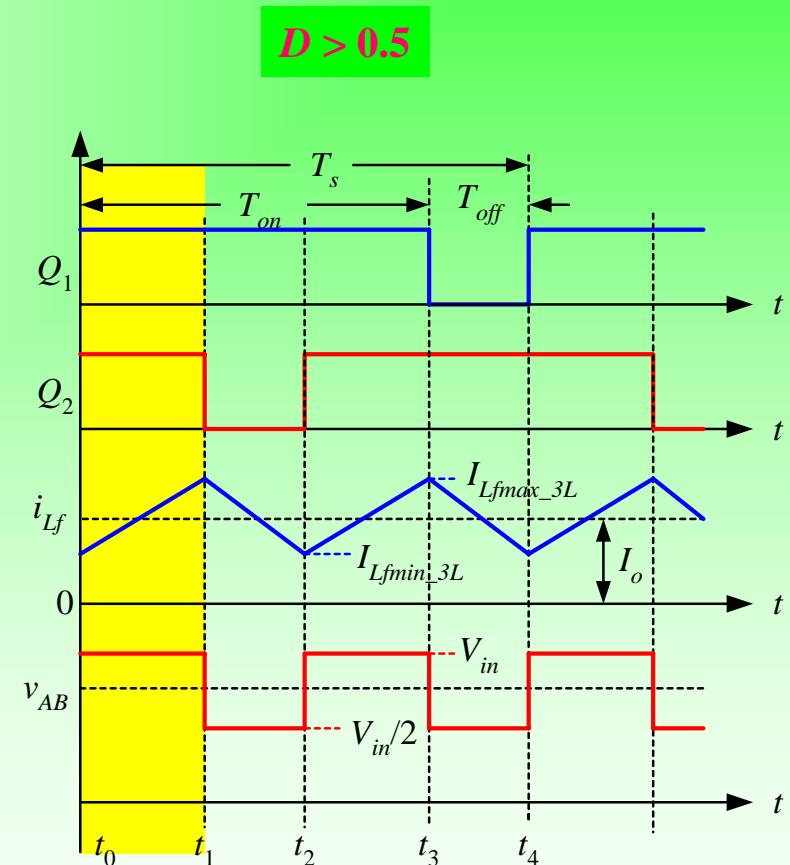
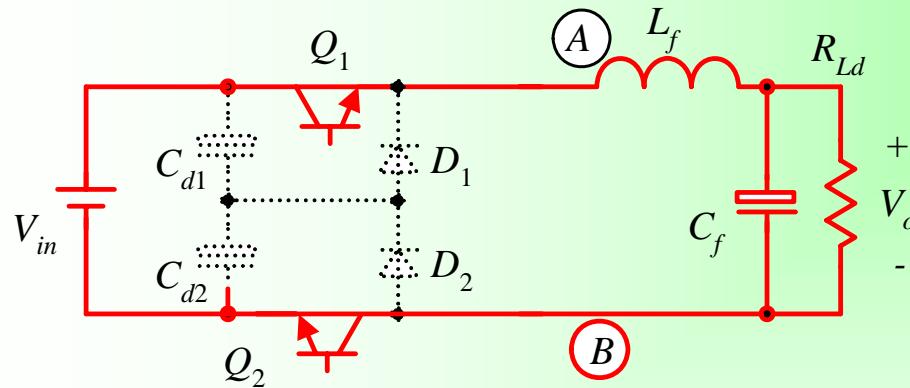
# Operation of Buck TL Converter: D>0.5 (1)



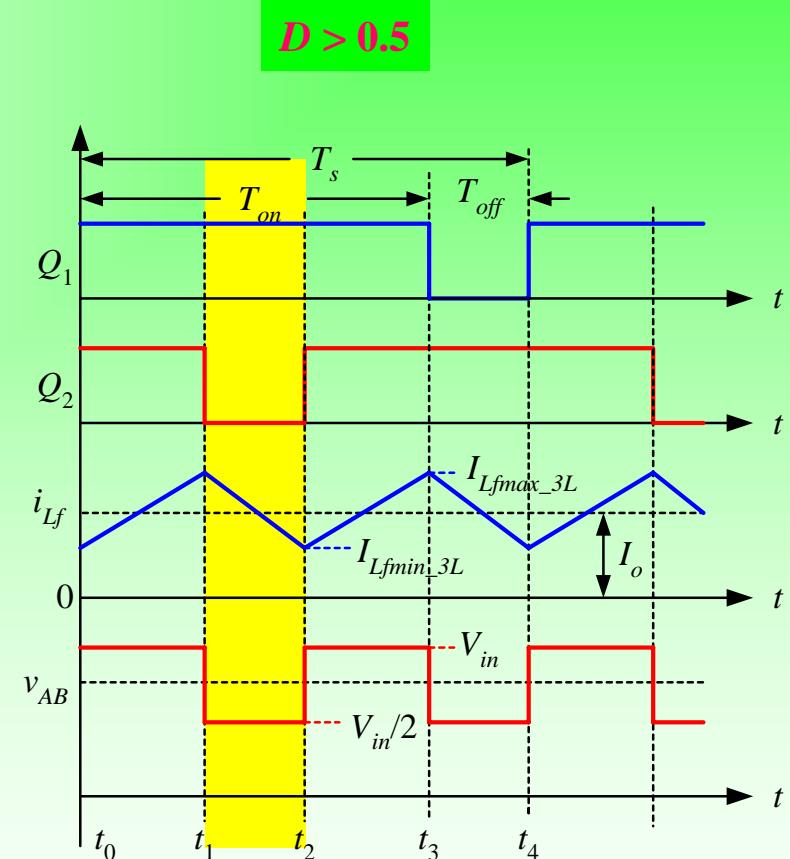
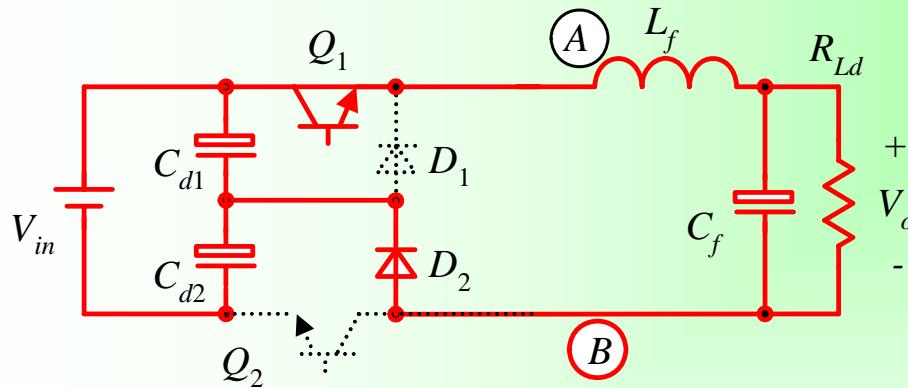
# Operation of Buck TL Converter: D>0.5 (2)



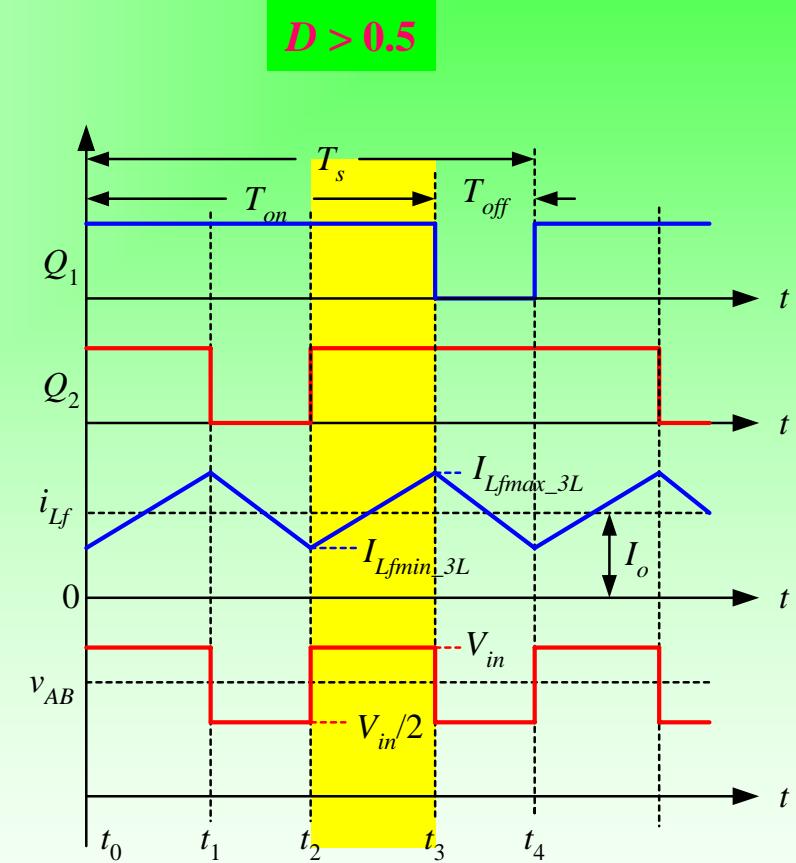
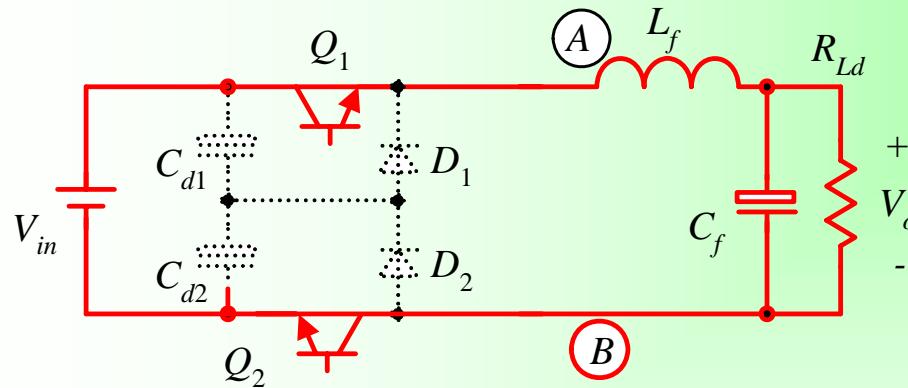
# Operation of Buck TL Converter: D>0.5 (3)



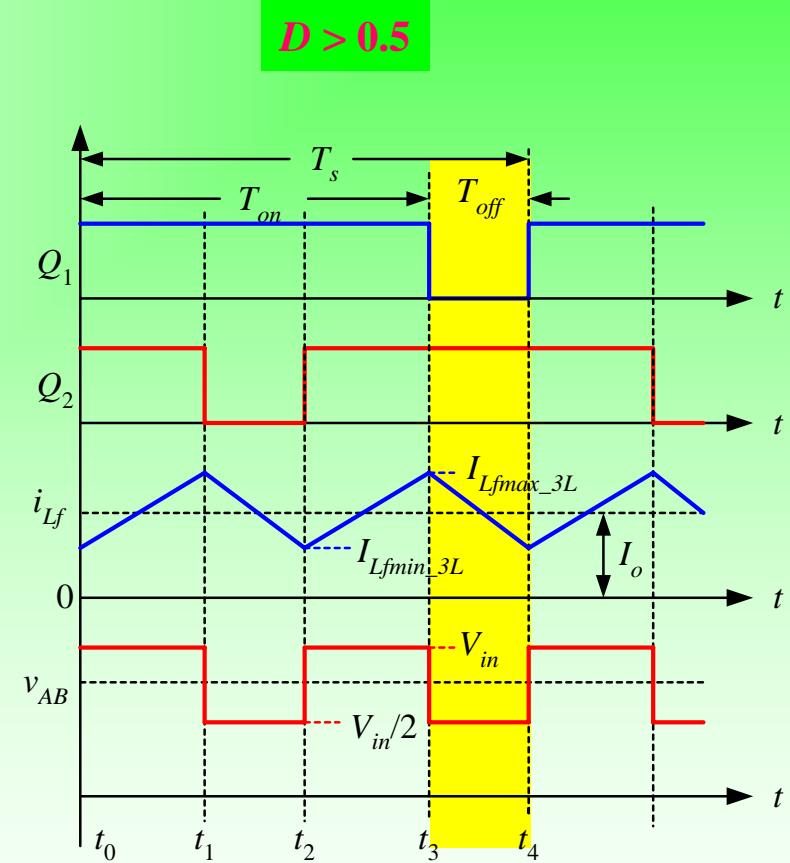
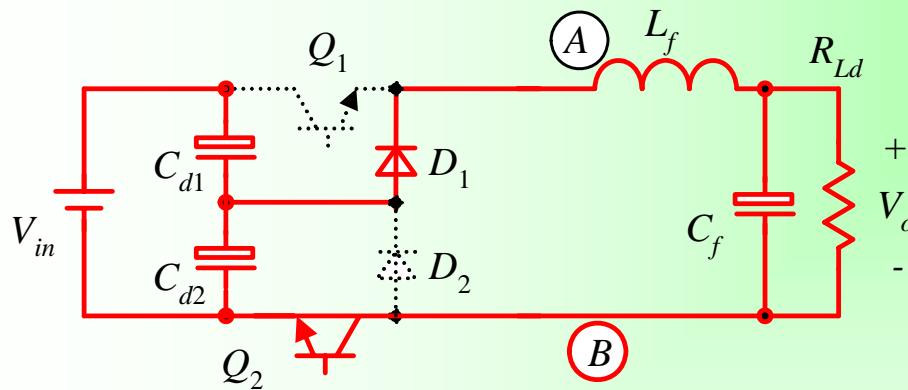
# Operation of Buck TL Converter: D>0.5 (4)



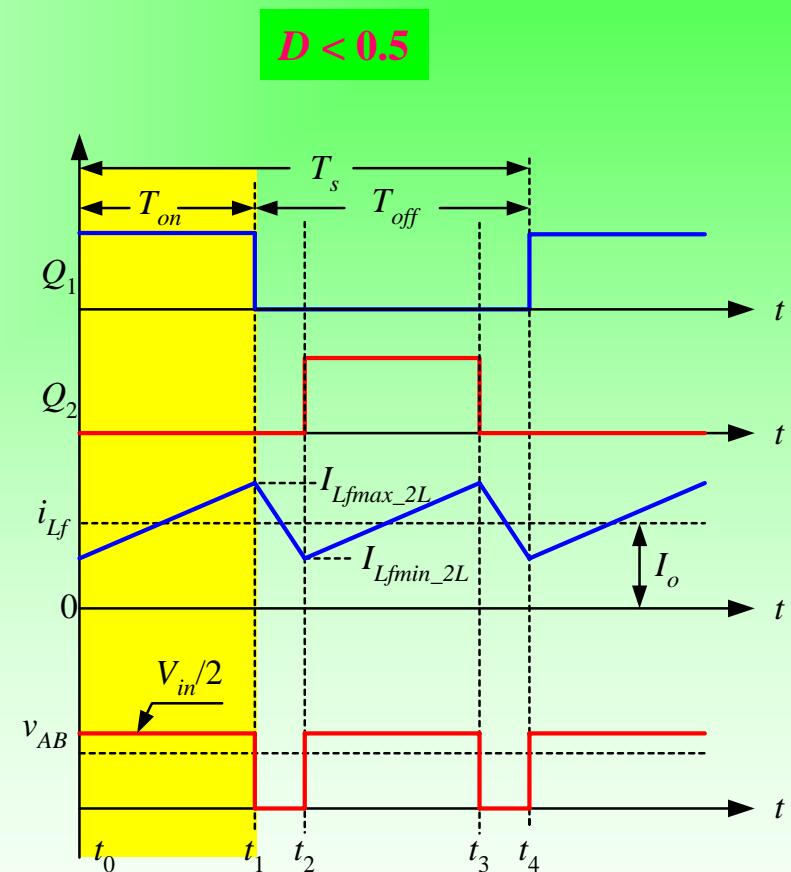
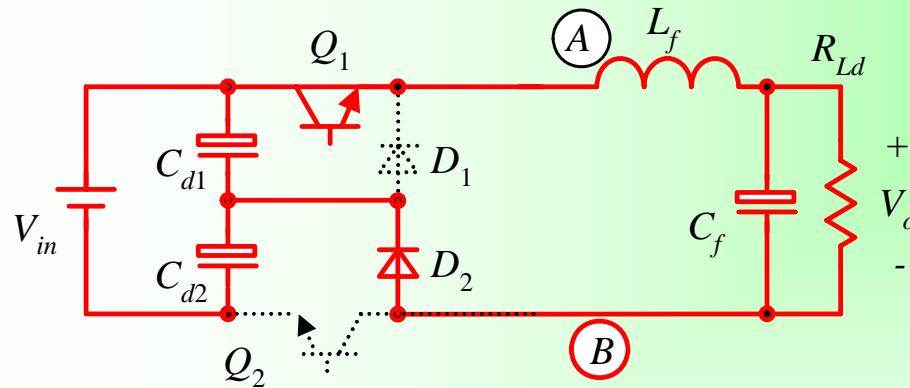
# Operation of Buck TL Converter: D<0.5 (1)



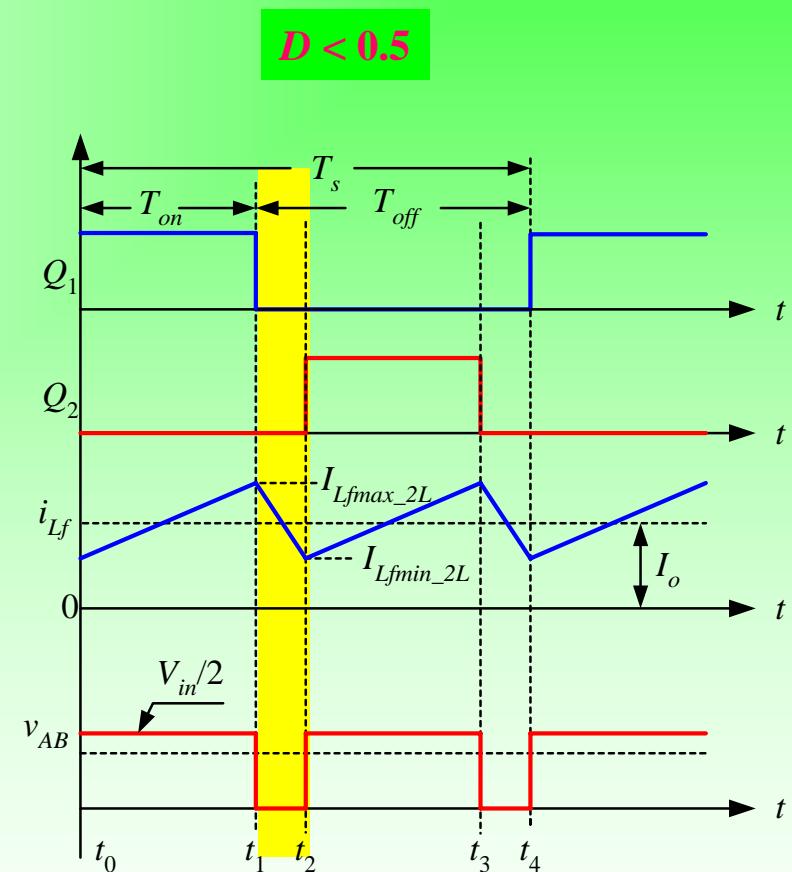
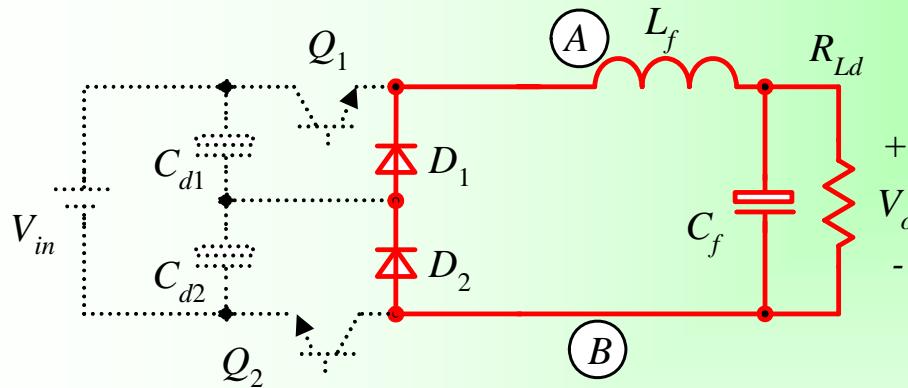
# Operation of Buck TL Converter: D<0.5 (2)



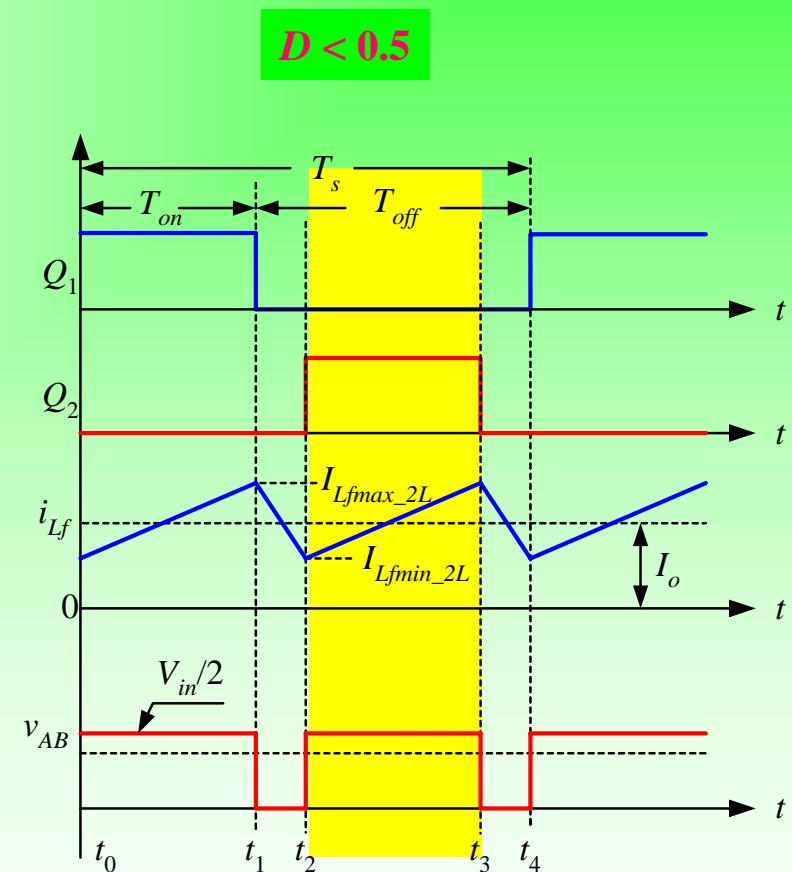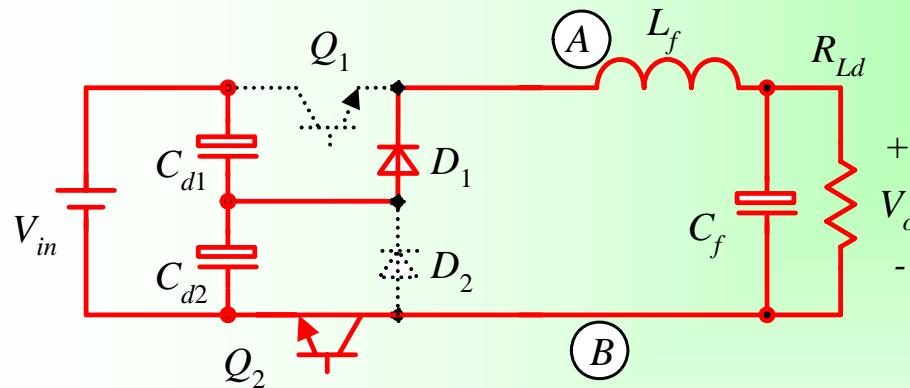
# Operation of Buck TL Converter: D<0.5 (3)



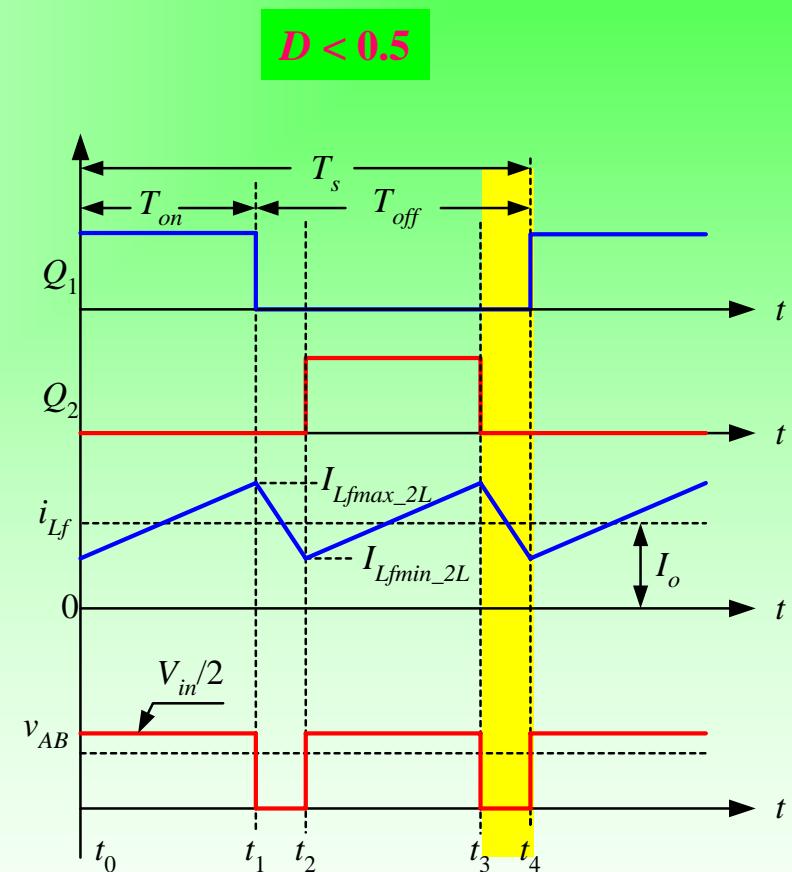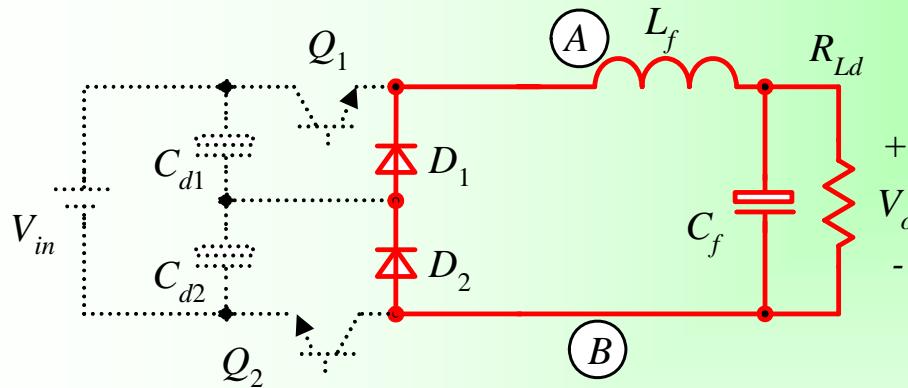
# Operation of Buck TL Converter: D<0.5 (4)




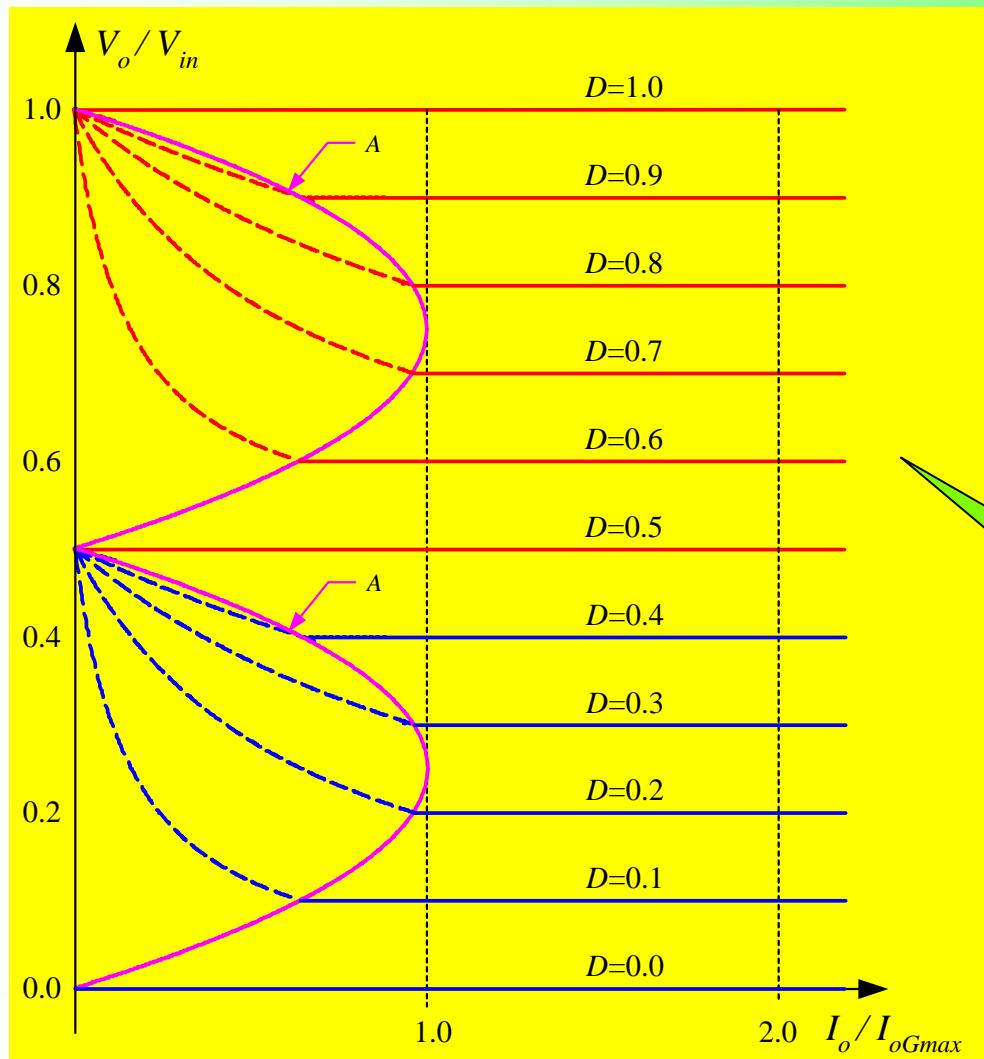

$V_o / V_{in} = D$


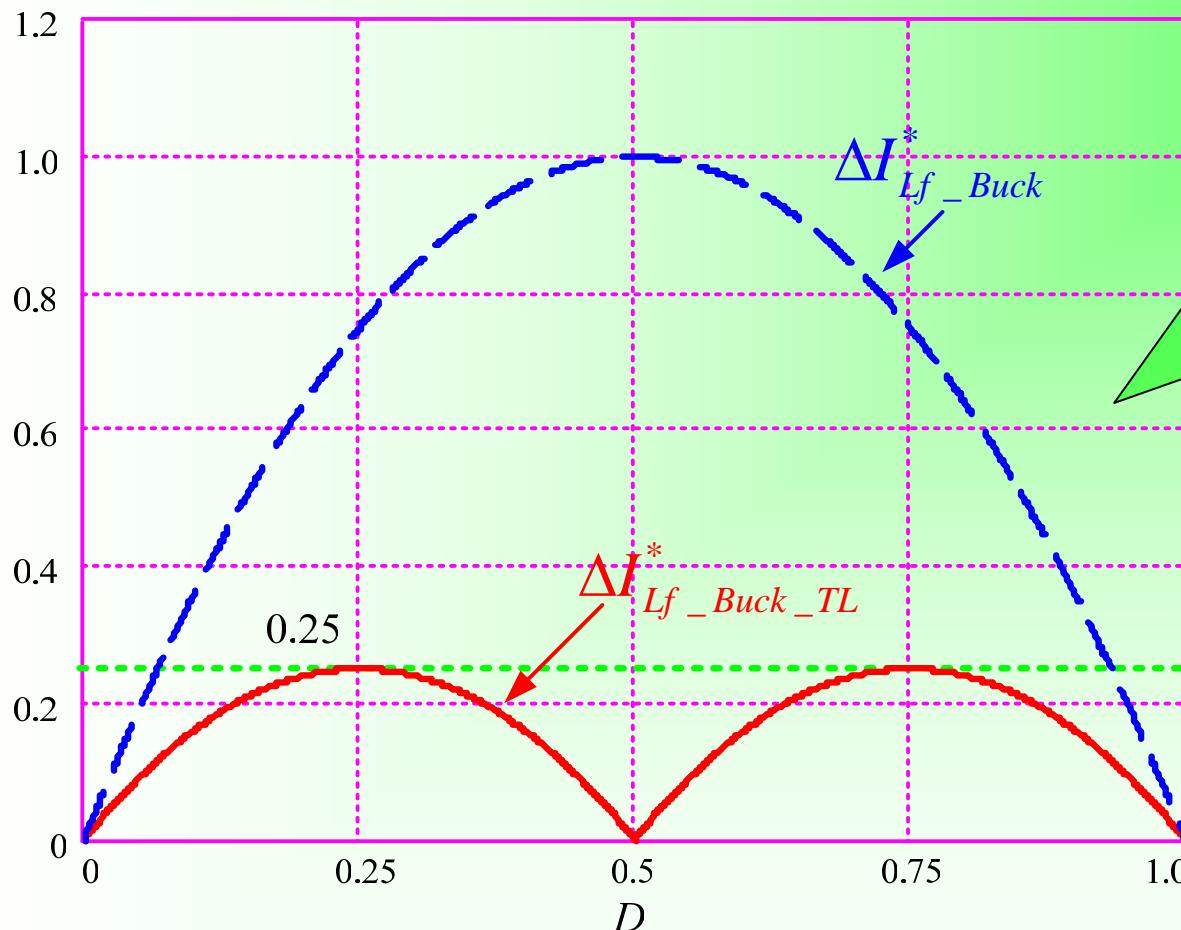


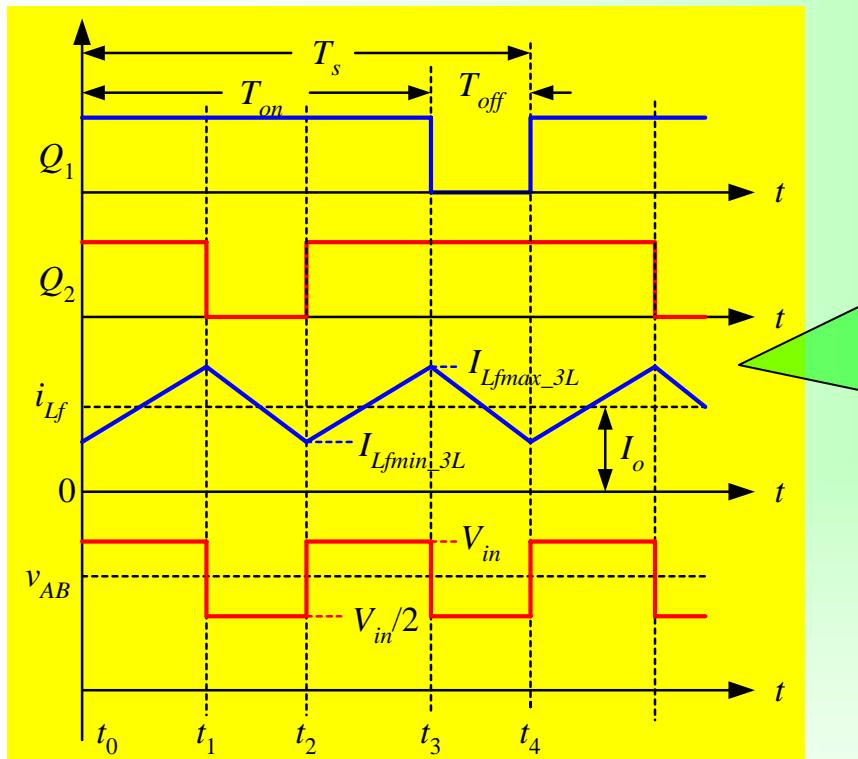The output inductance of Buck TL converter reduces to  $1/4$  of that of Basic Buck converter




The output capacitor in Buck TL converter reduces to  $1/2$  of that in Basic Buck converter


# Unbalanced capacitor voltage

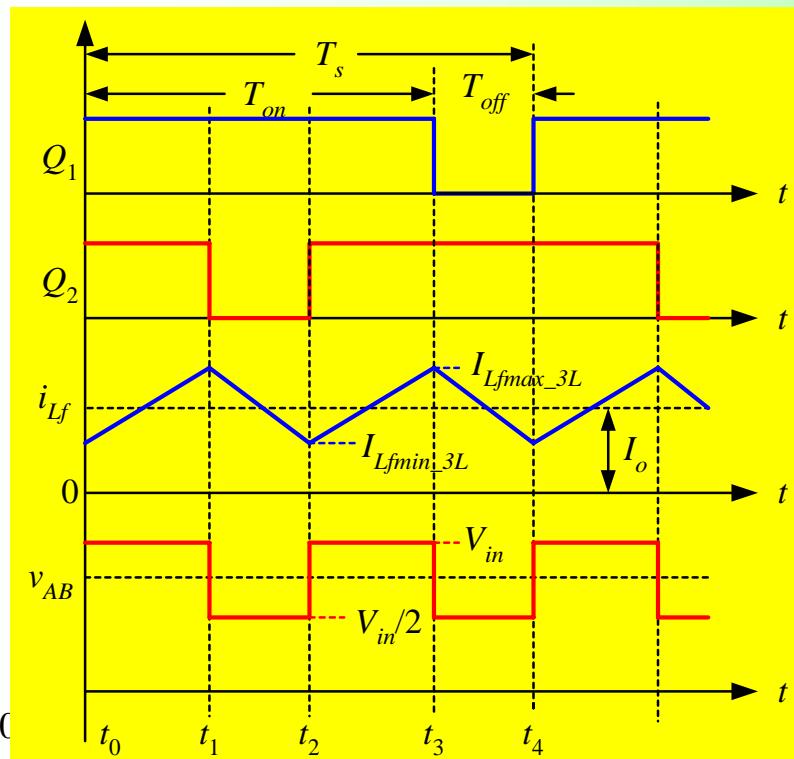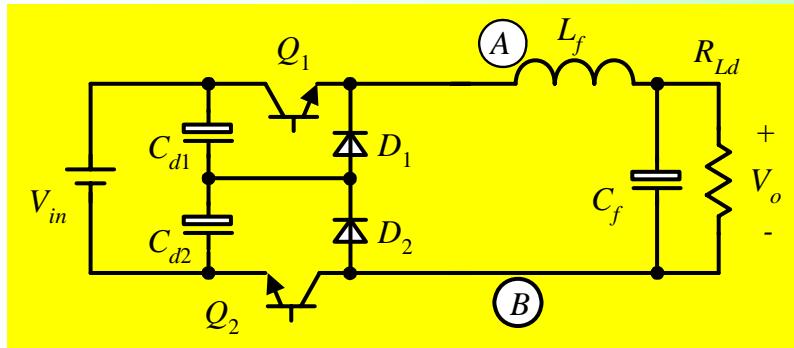

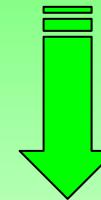
Slight difference of 1) control signal  
and 2) drive circuit




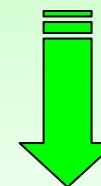Slight difference of duty cycle of the  
two switches




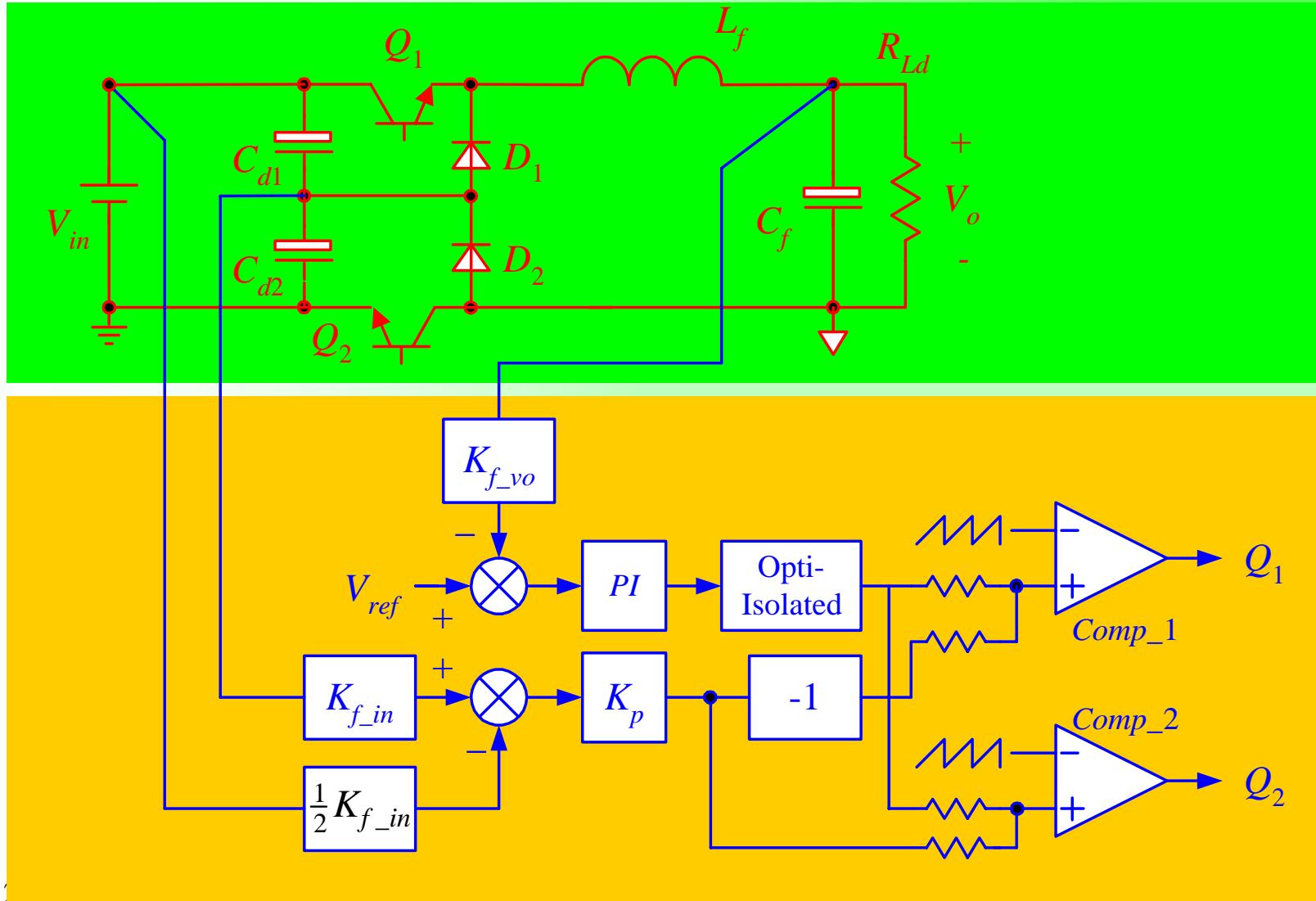Unbalanced voltage of the divided  
capacitors




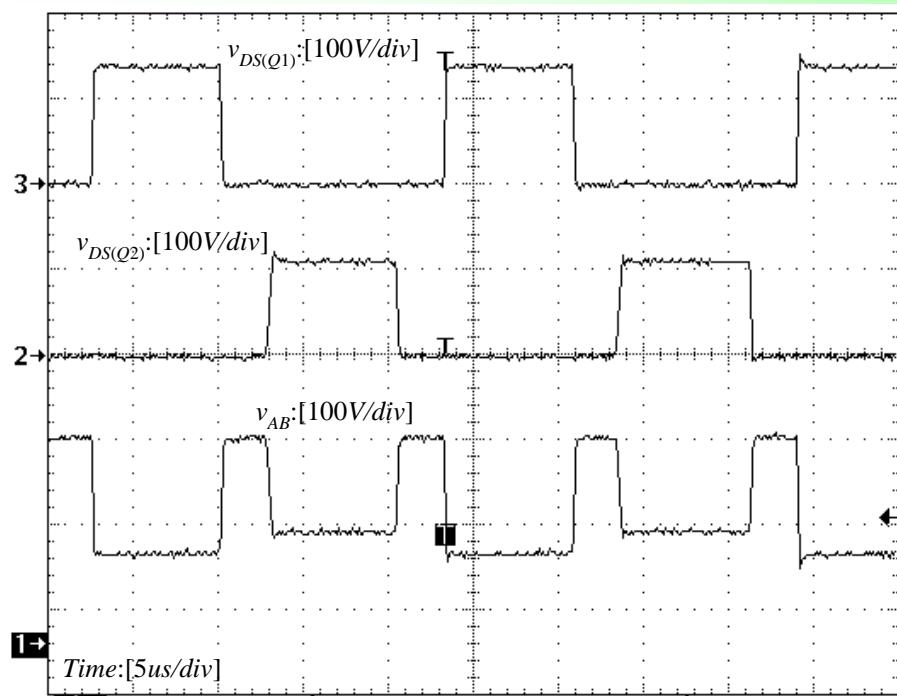


*Without Feed-Forward control*

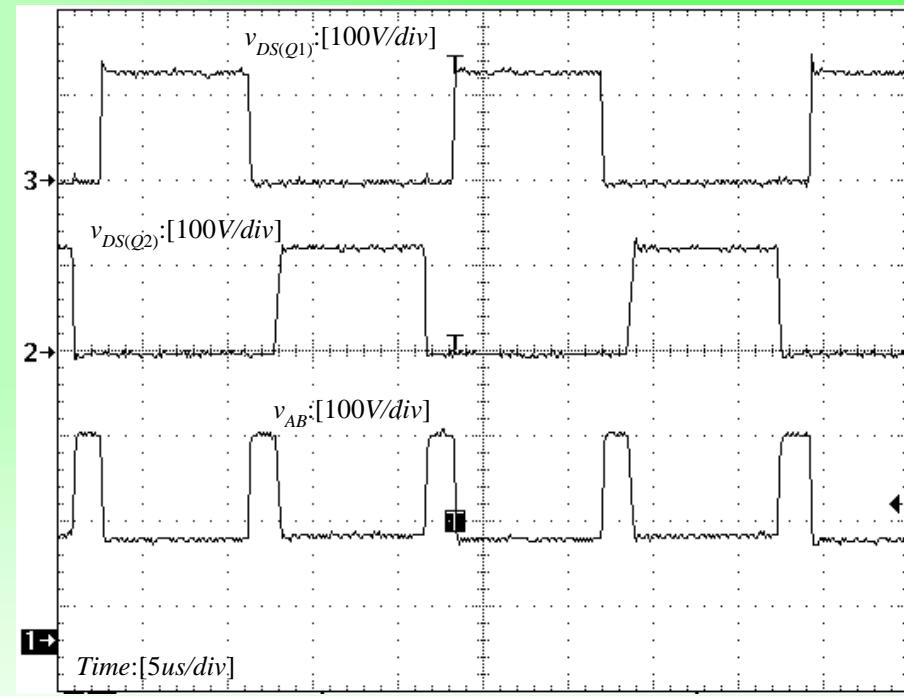



*With Feed-Forward control*

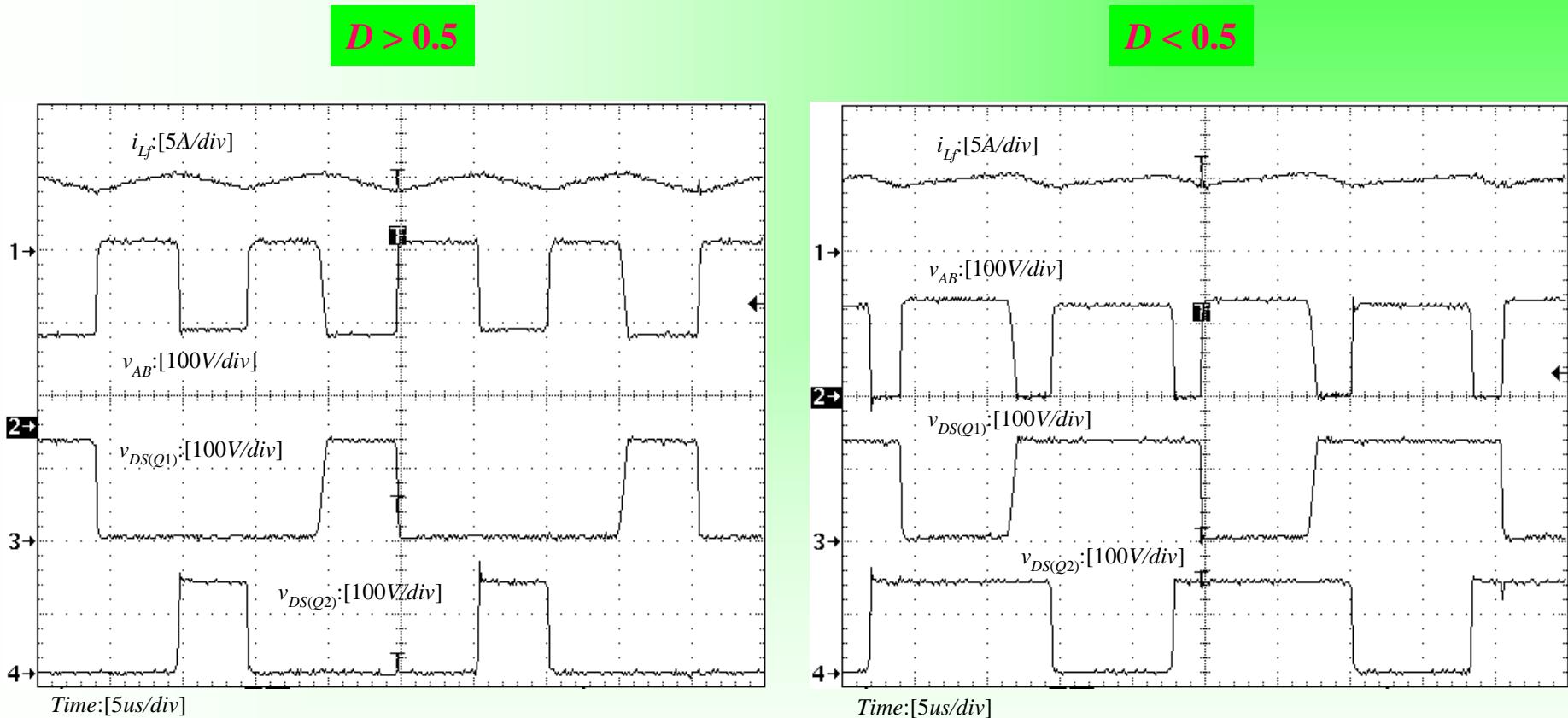


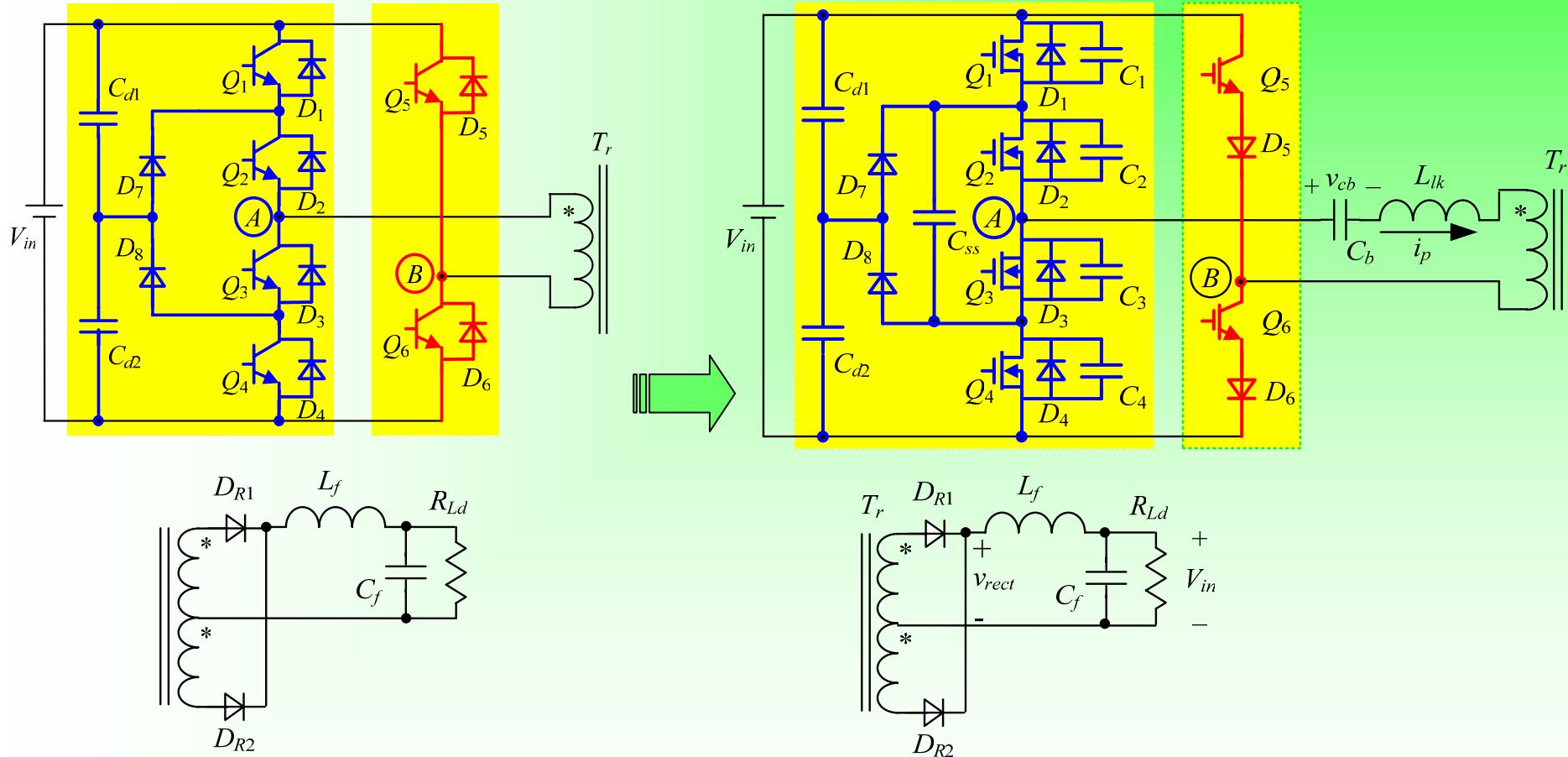1. Backgrounds
2. Derivation of a Family of Three-Level Converters
3. Improved and Simplified Three-Level Converters
4. Buck TL Converter
5. **ZVZCS PWM Hybrid Full-Bridge Three-Level Converter**
6. Possible of Three-Level Voltage
7. Conclusions




# Main Circuit and Key Waveforms

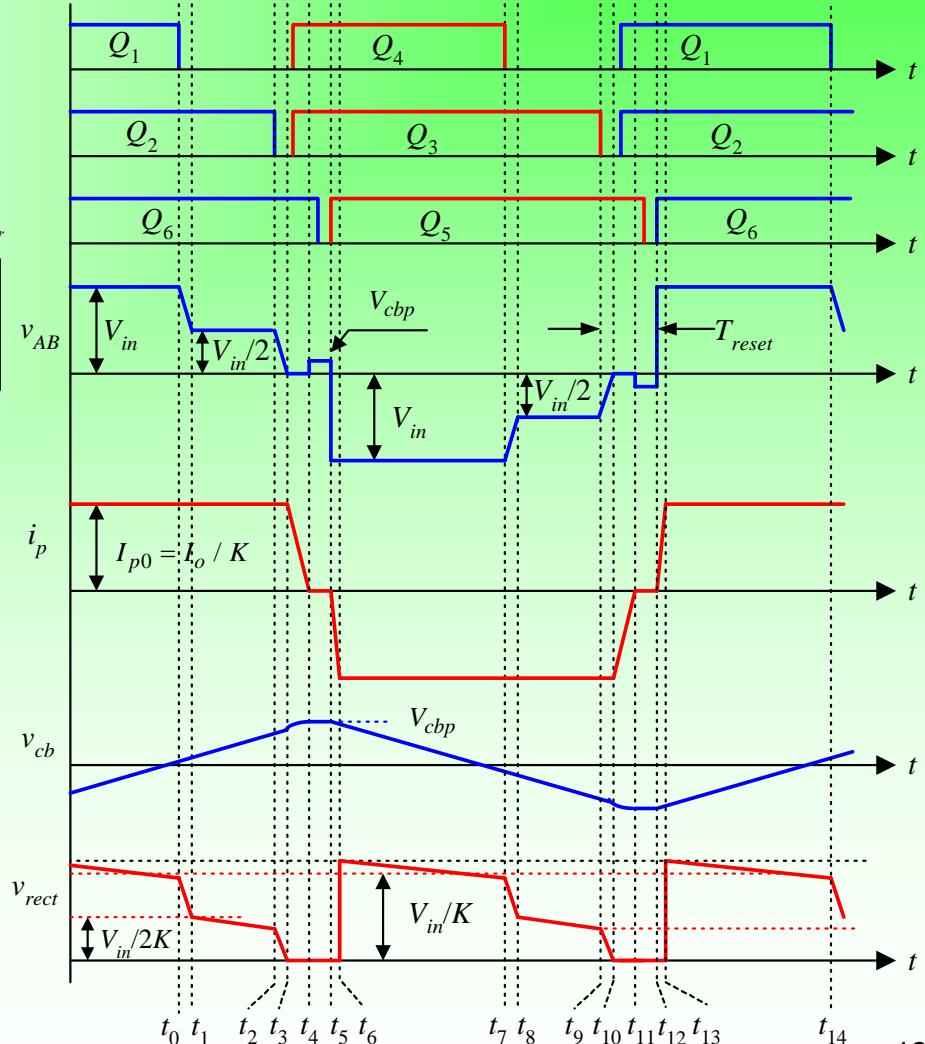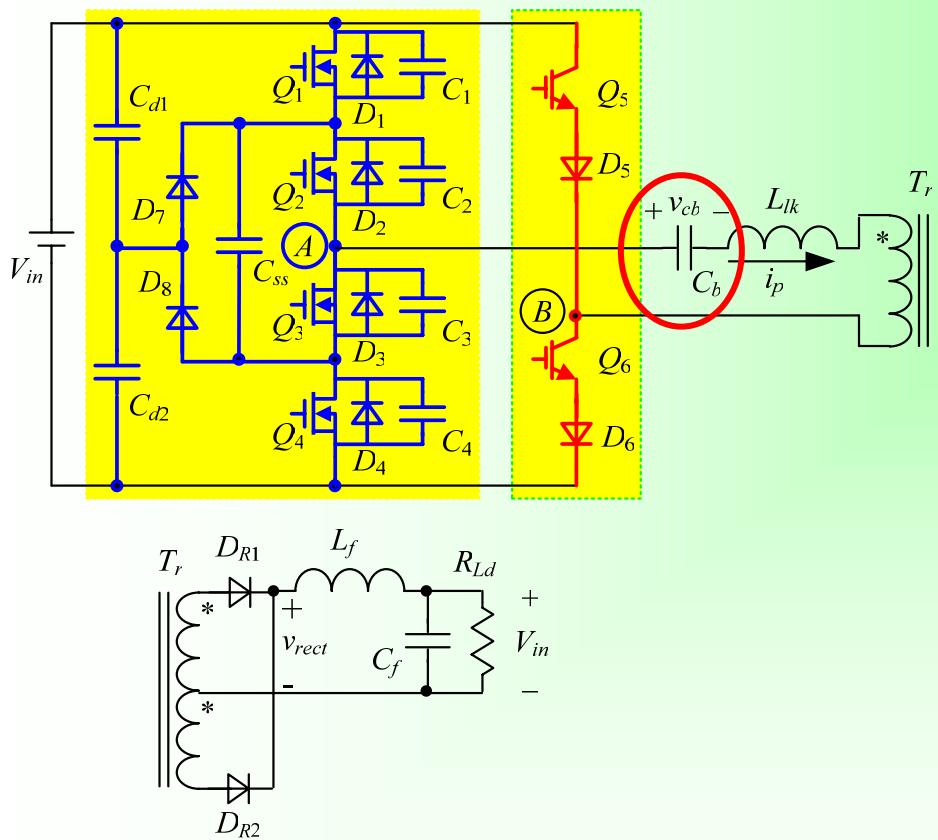


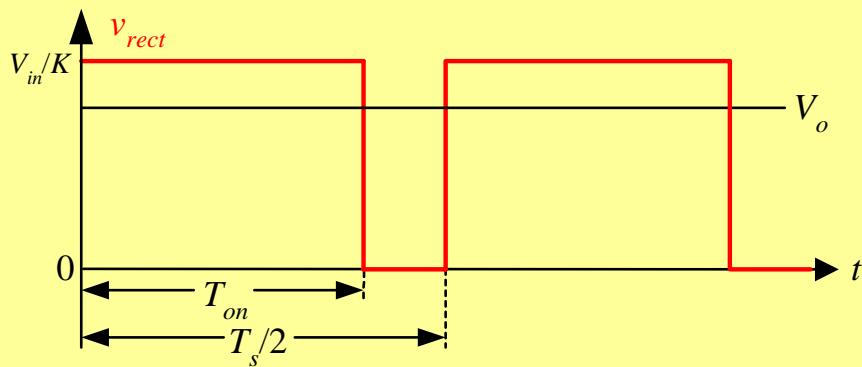


Full-Bridge Converter

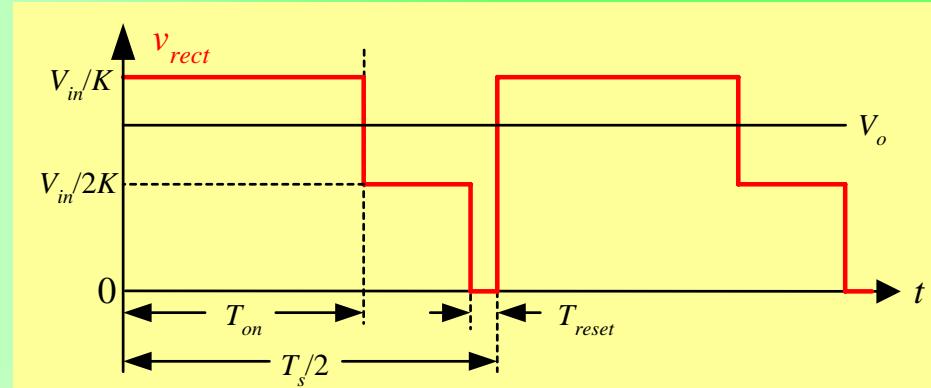


Full-Bridge Three-Level Converter

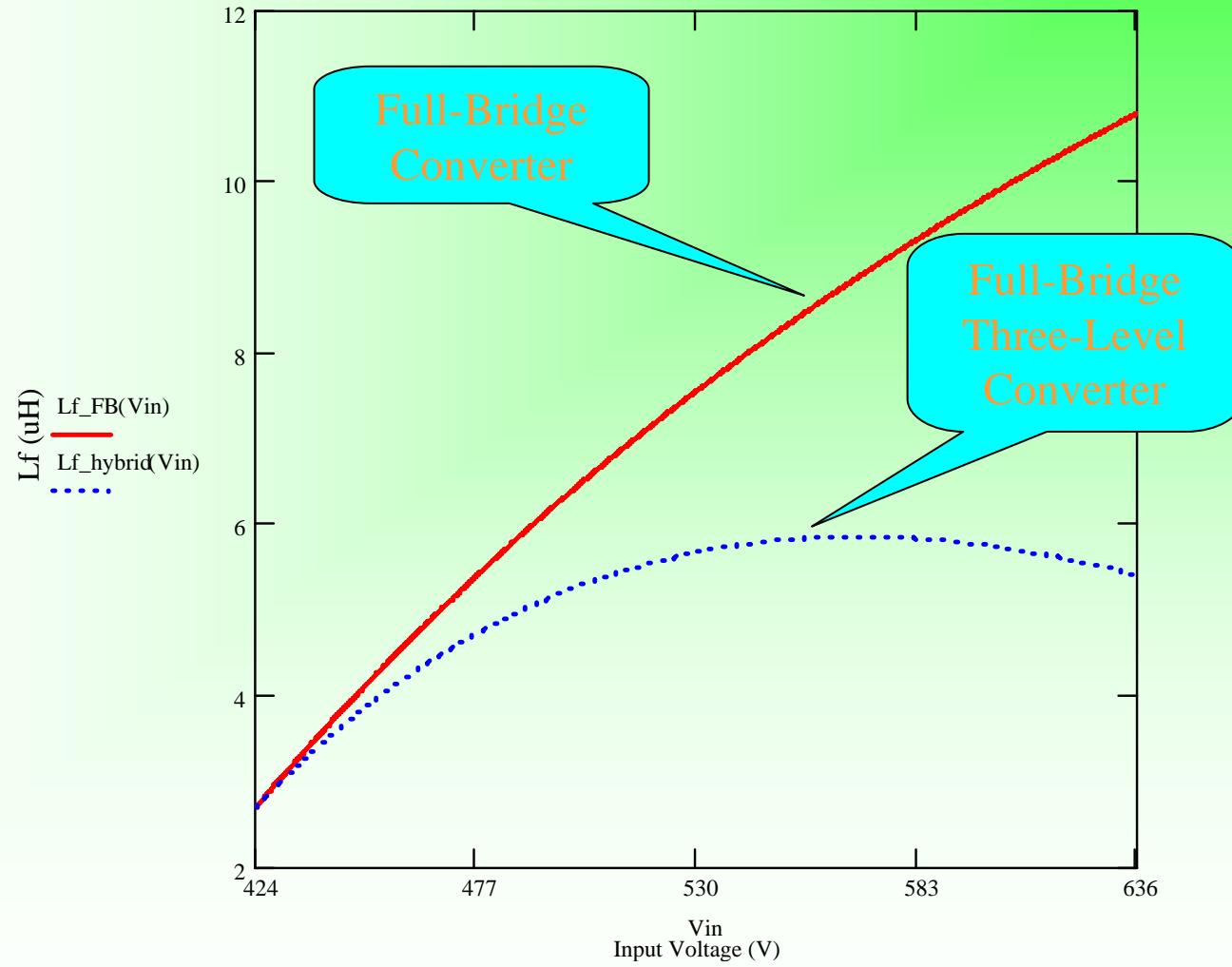


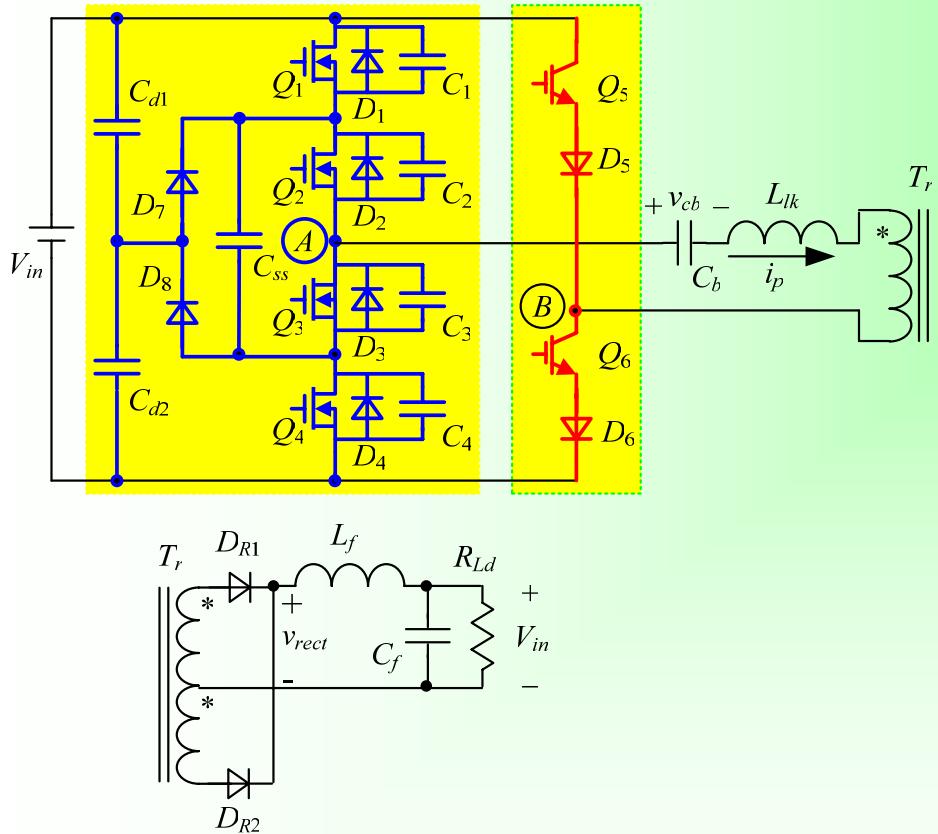



- $V_{in} = 530 \text{ VDC}$  (rectified and filtered from 3 phase 380VAC/50Hz)
- $V_o = 54 \text{ VDC}$ ;
- $I_o = 50 \text{ A}$ ;
- $Q_1(D_1 \& C_1) - Q_4(D_4 \& C_4)$ : IRF460;
- $Q_5$  and  $Q_6$ : CT60AM-20;
- $D_5 - D_8$ : DSEI30-06A;
- Rectifier diode: MEK95-06 DA;
- Ratio of windings :  $K=19:3$ ;
- Leakage inductance  $L_{lk}=6\mu\text{H}$ ;
- Blocking capacitor:  $C_b=1\mu\text{F}$ ;
- Output filter inductance  $L_f=6\mu\text{H}$ ;
- Output filter capacitor  $C_f=6600\mu\text{F}$ ;
- Switching frequency:  $f_s=50\text{kHz}$ .

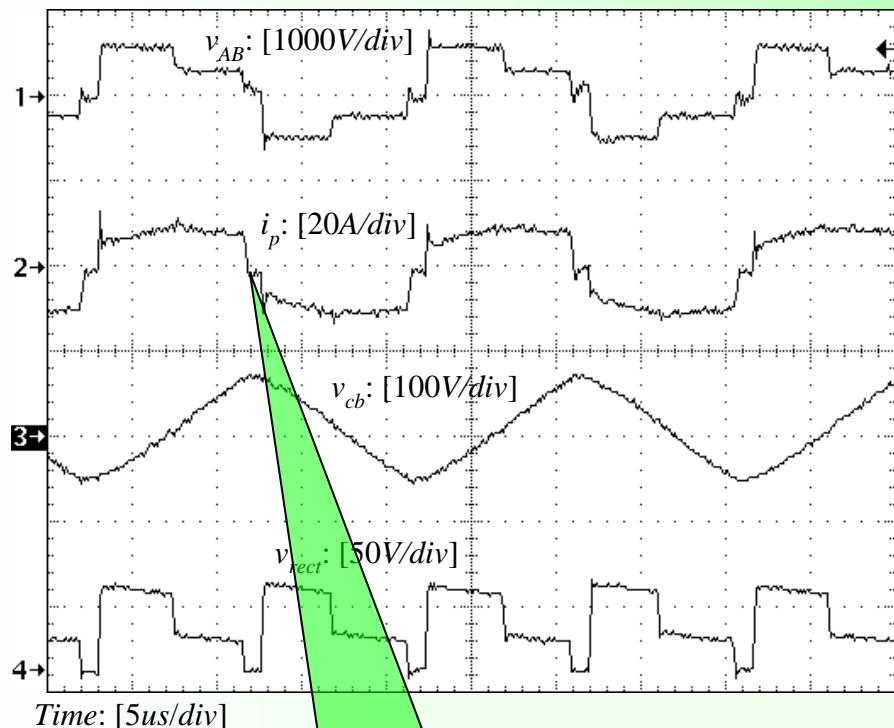

$i_p$  reduce to zero

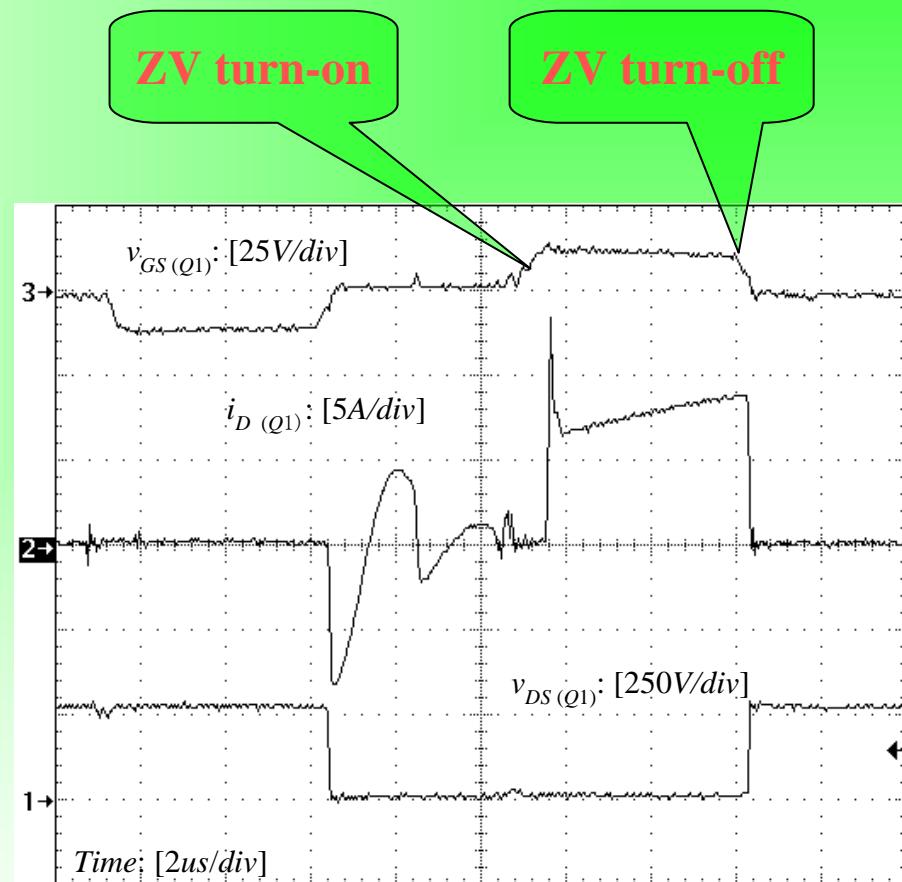


ZVS for Chopping Switches

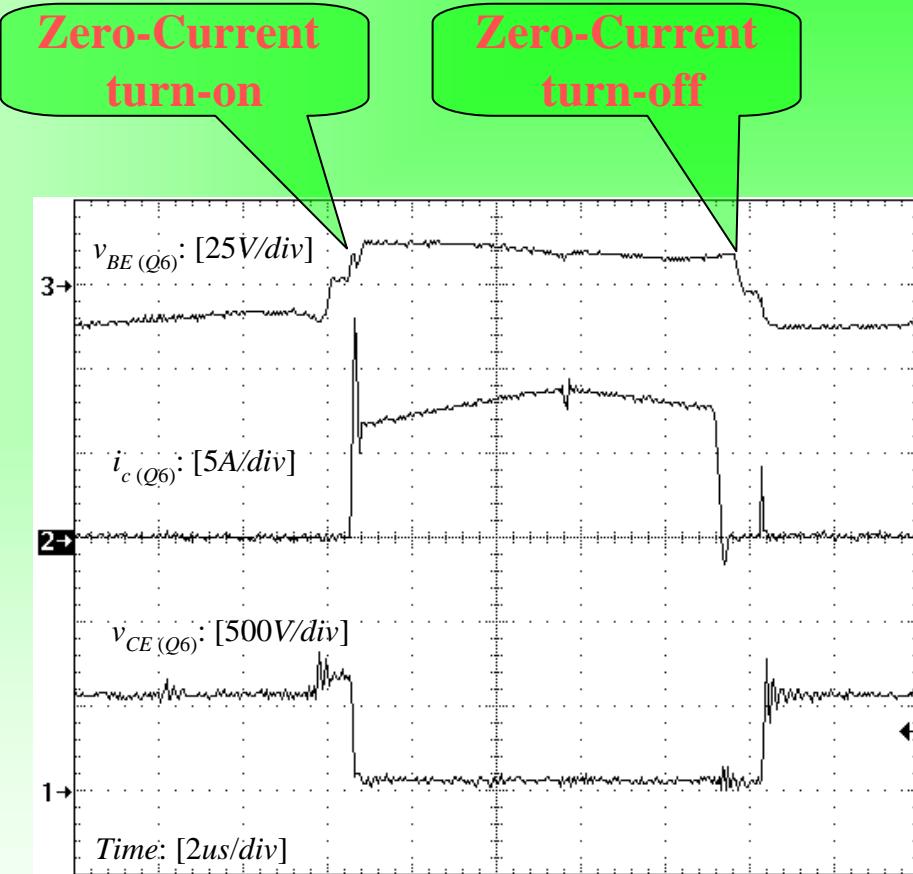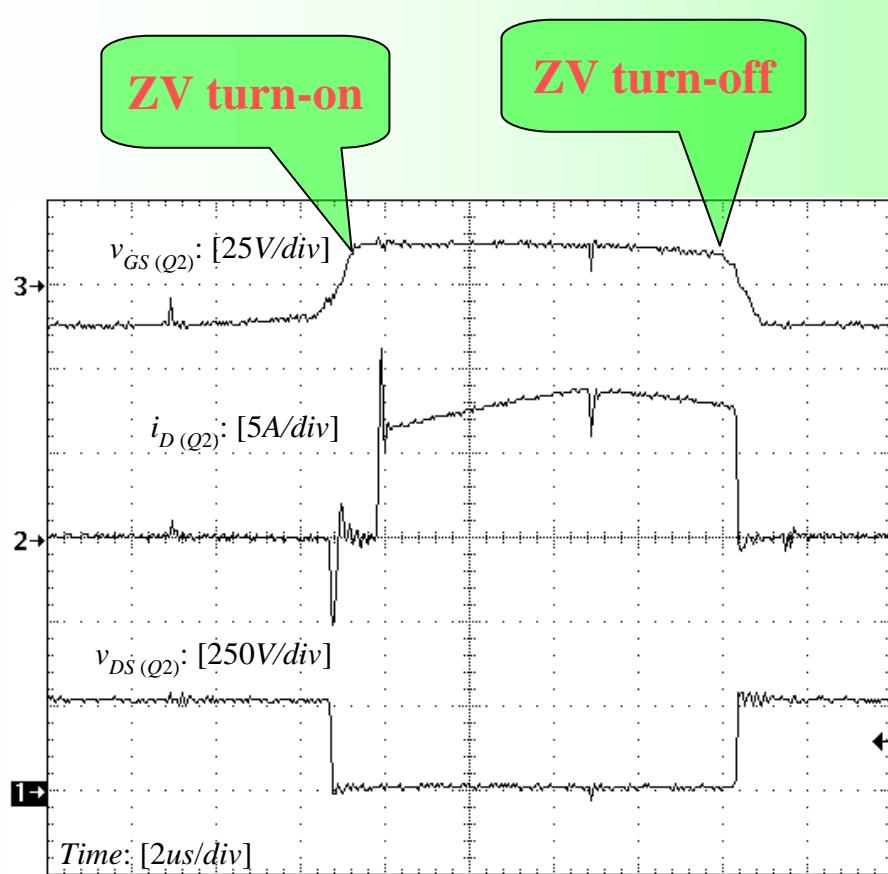


ZVS for leading Switches


ZVS for lagging Switches

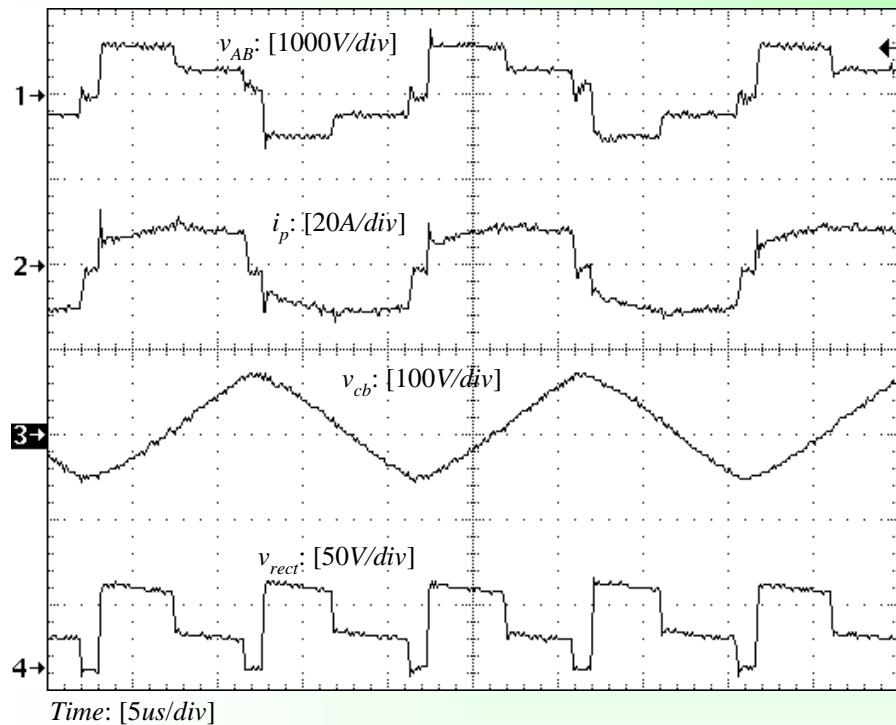


Three-Level Mode


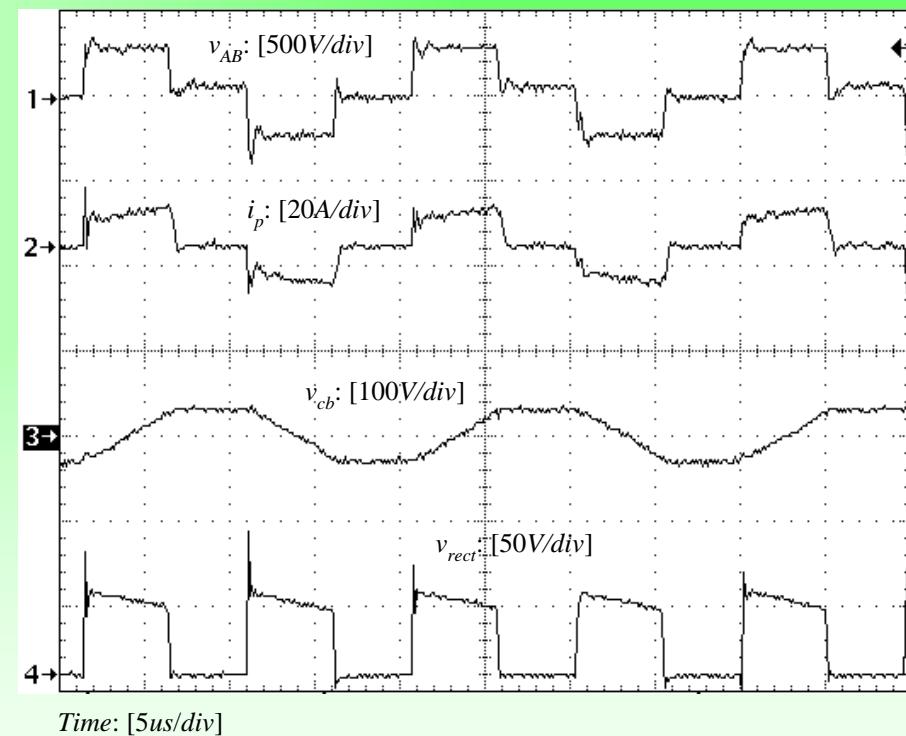


Two-Level Mode


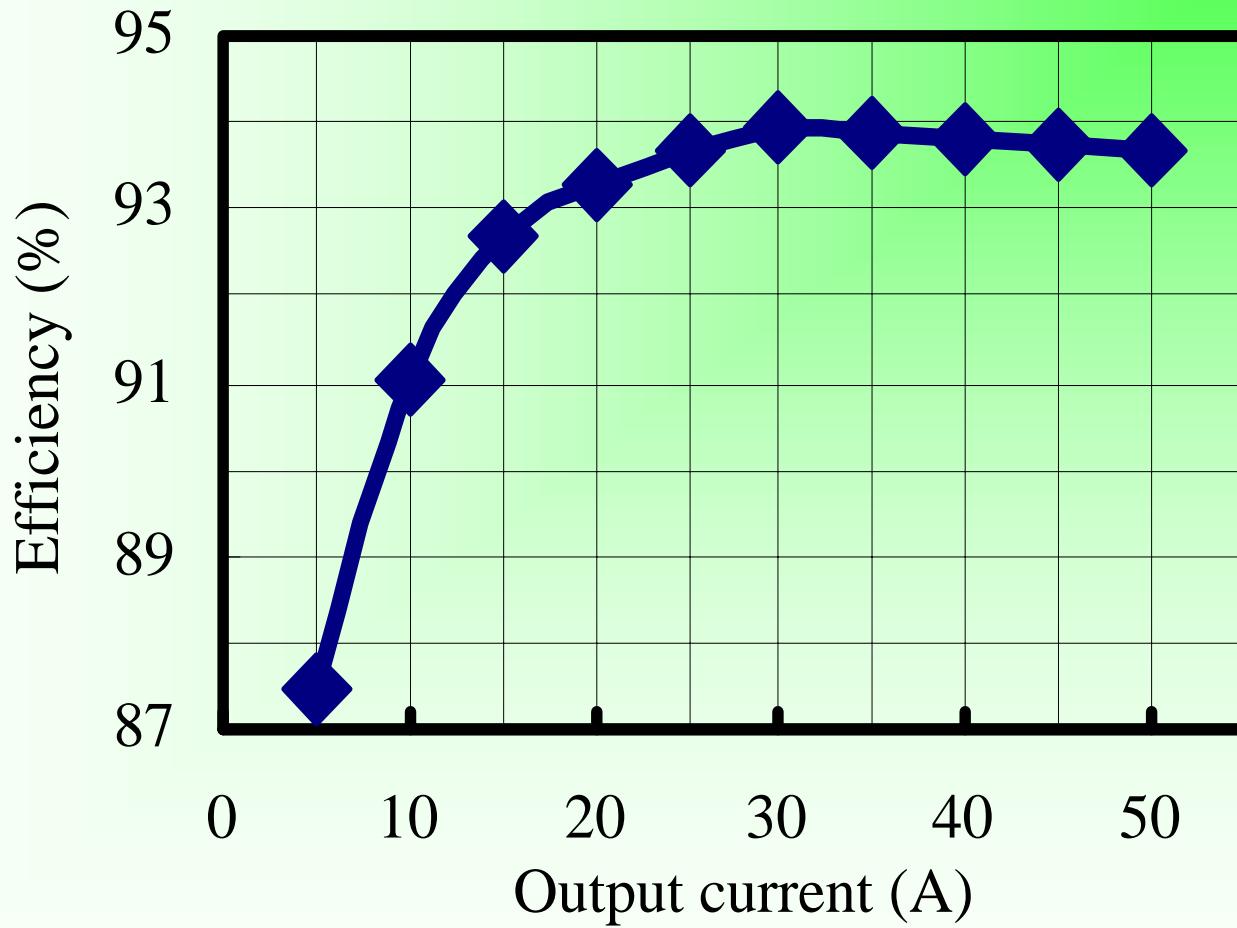


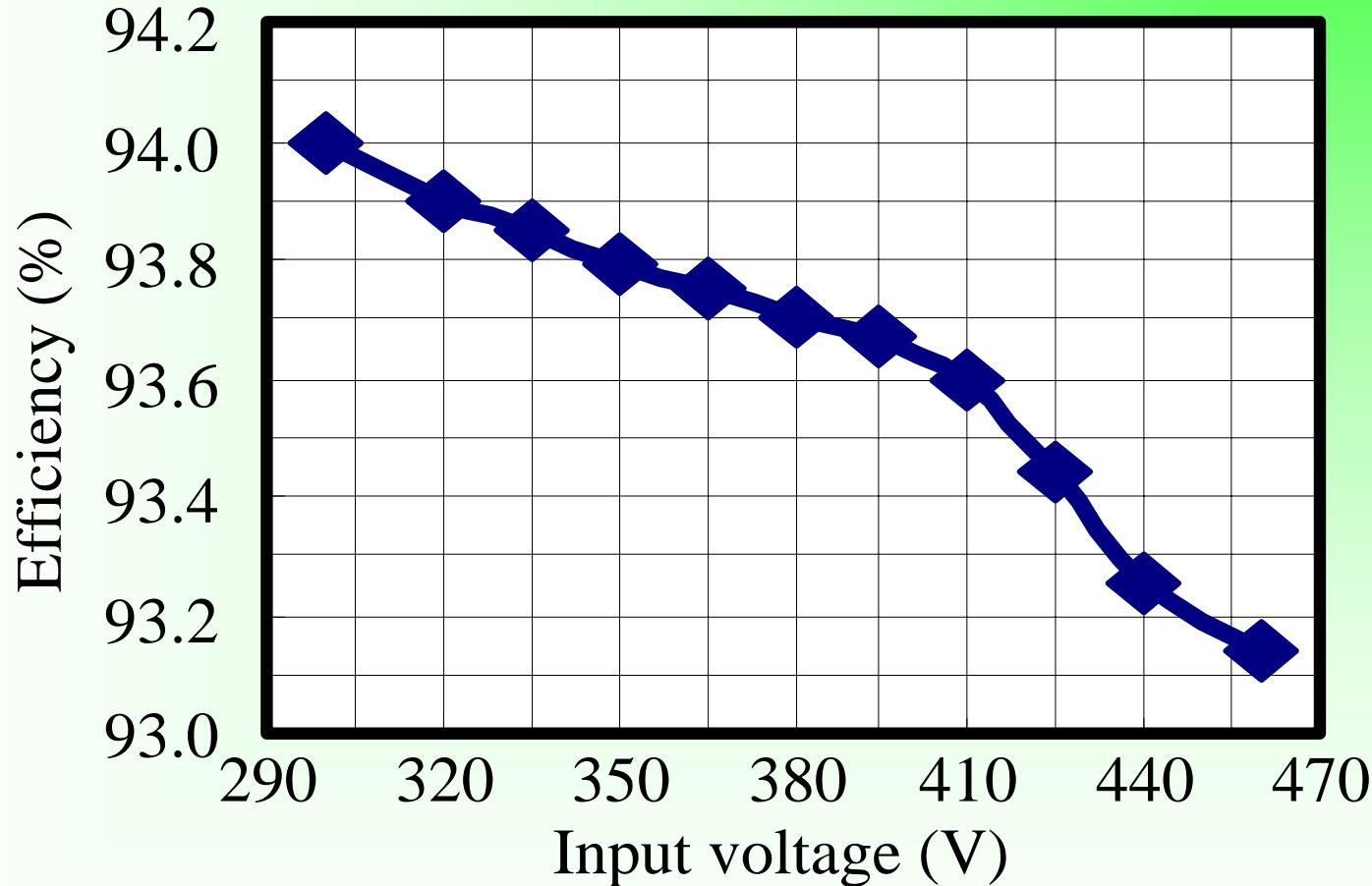


# Several ZVZCS Hybrid FB TL Converters

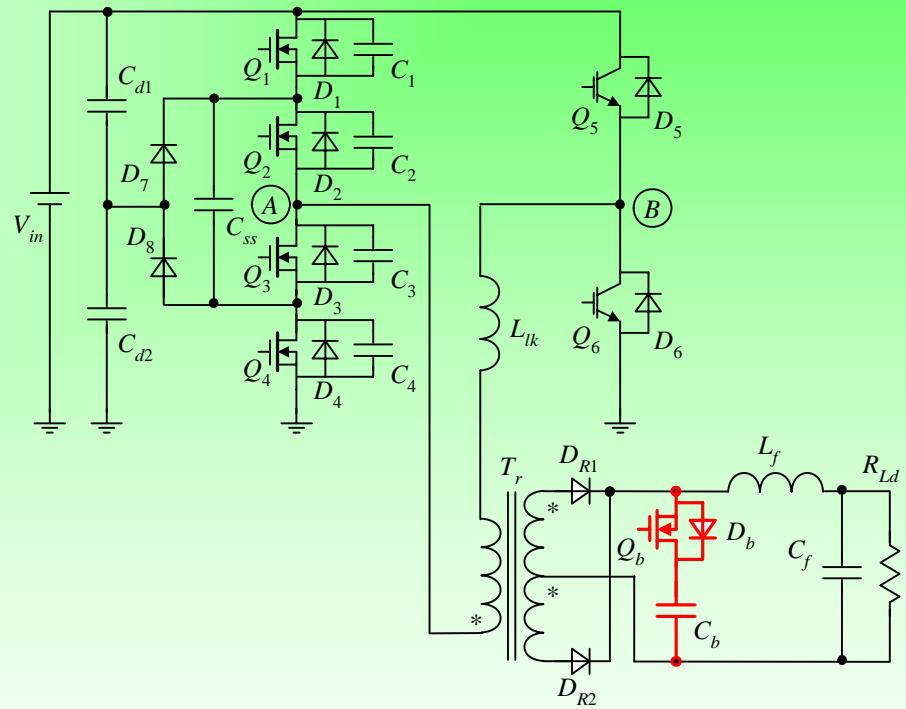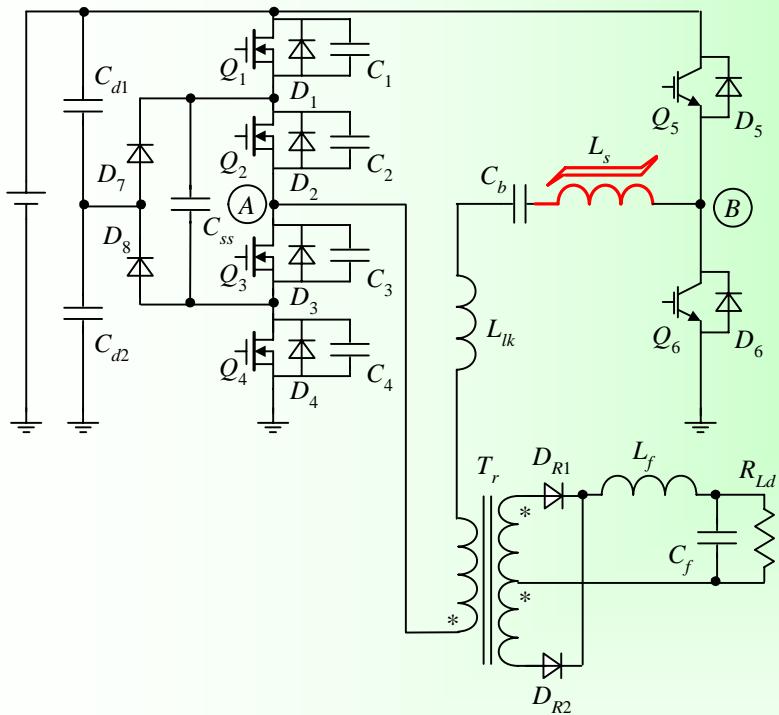

# Several ZVZCS Hybrid FB TL Converters

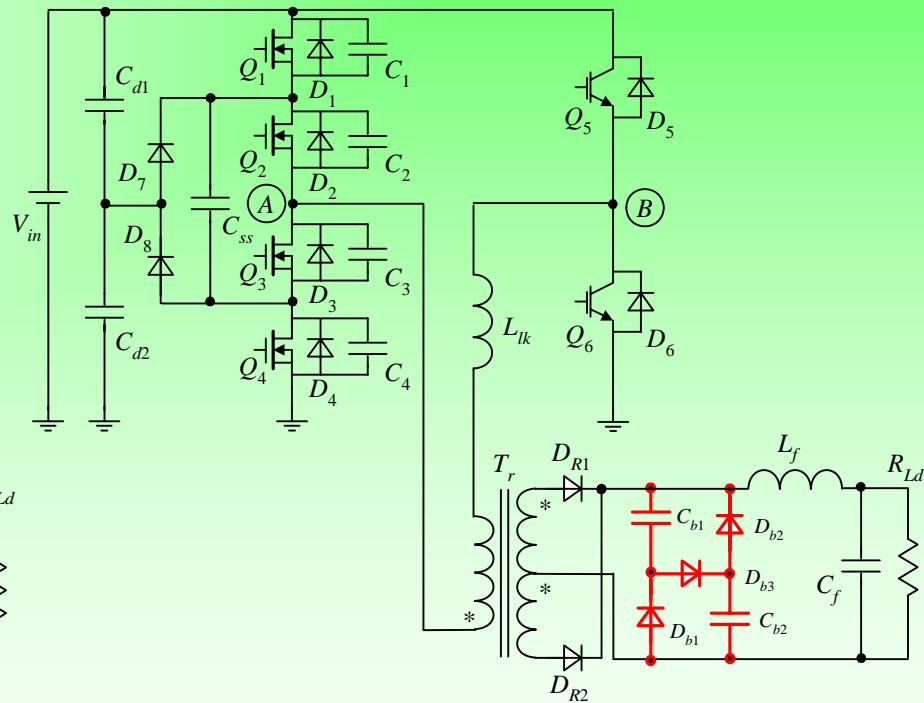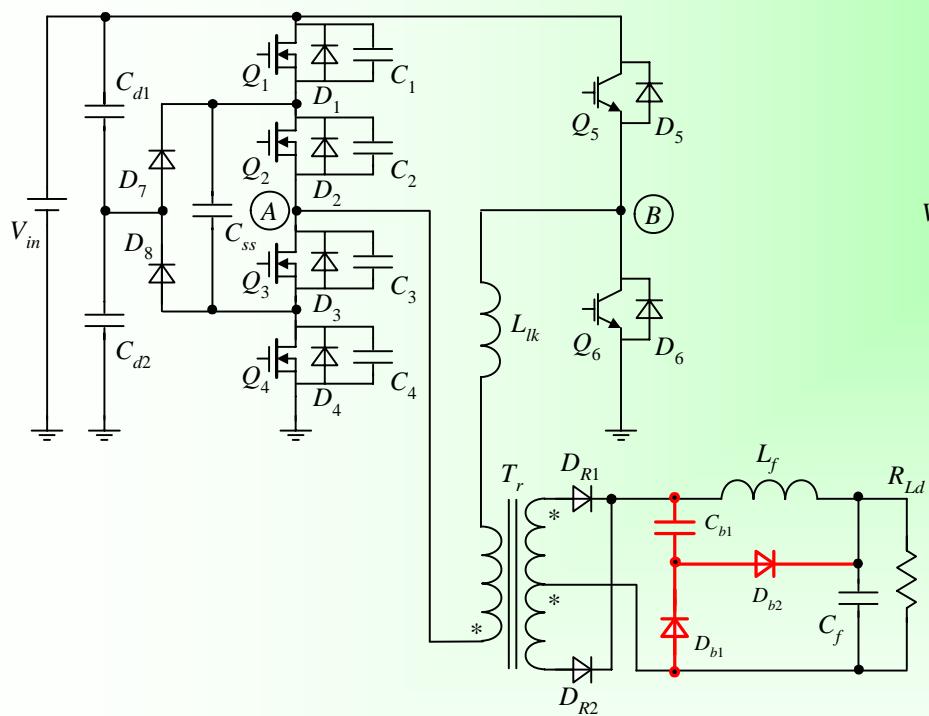

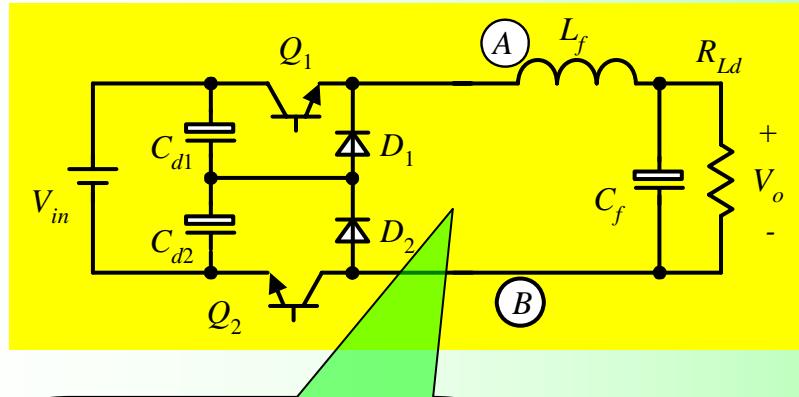1. Backgrounds
2. Derivation of a Family of Three-Level Converters
3. Improved and Simplified Three-Level Converters
4. Buck TL Converter
5. ZVZCS PWM Hybrid Full-Bridge Three-Level Converter
6. Possible of Three-Level Voltage
7. Conclusions




$$v_{AB} = V_{in}, V_{in}/2 \text{ and } 0$$

In order to achieve three-level voltage waveform,


- 1) there should be two divided capacitors.
- 2) The two divided capacitors could power the load simultaneously or alternatively.

# Possibility of Three-Level Voltage Waveforms


Buck

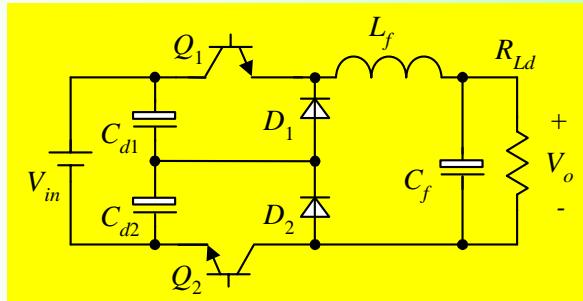


Boost

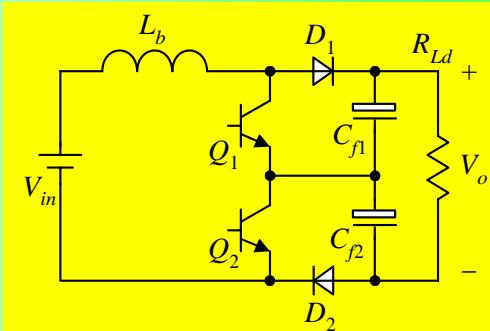


Buck/Boost

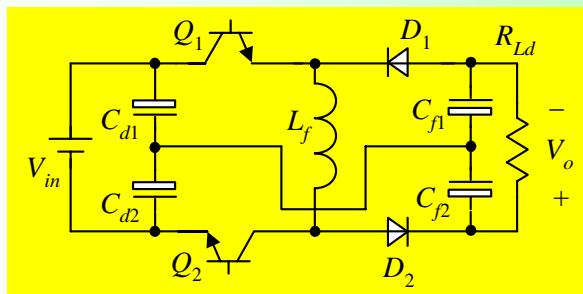


Cuk

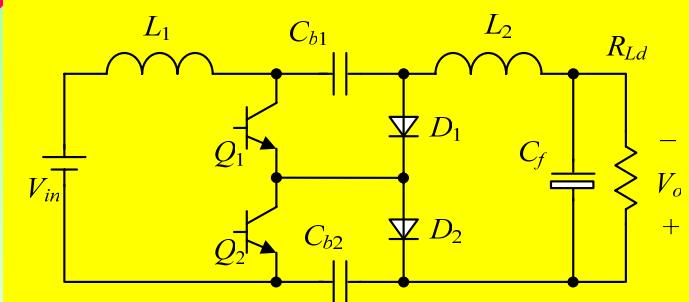


Sepic

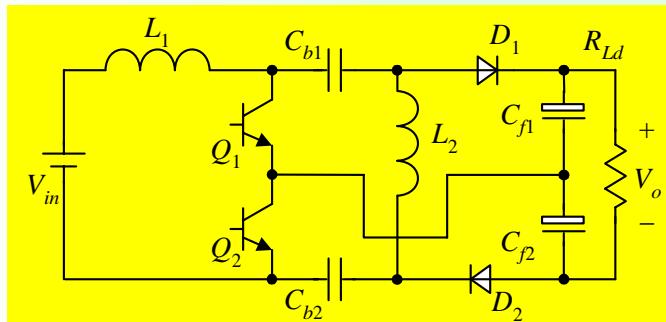


Zeta

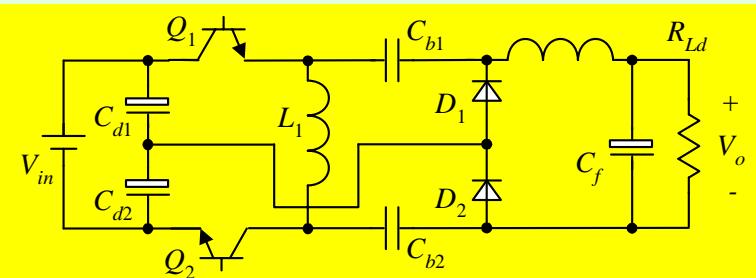
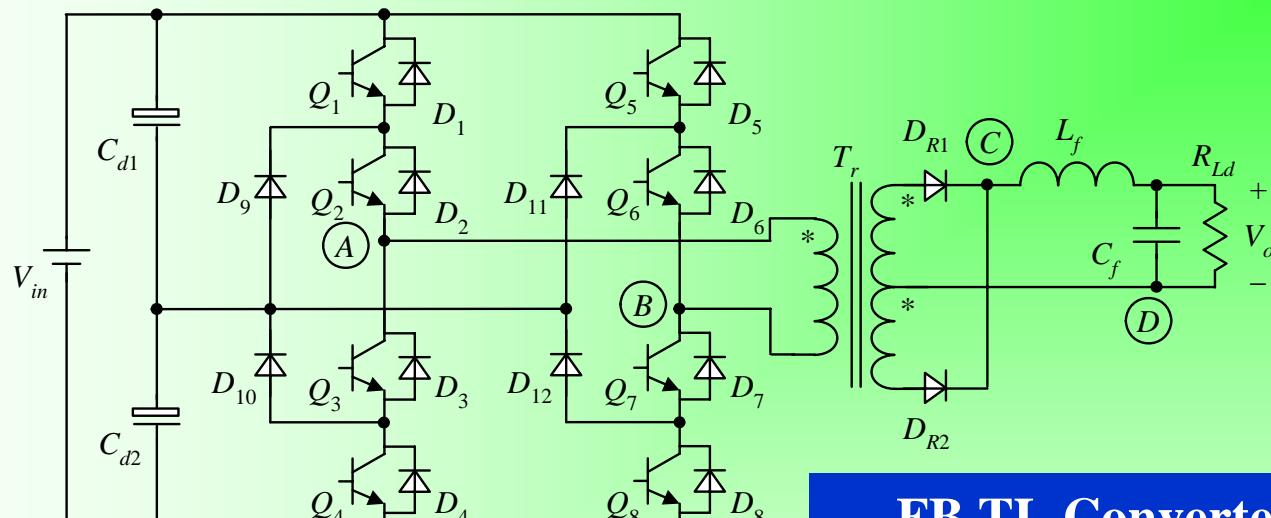
# Possibility of Three-Level Voltage Waveforms




**FB TL Converter**

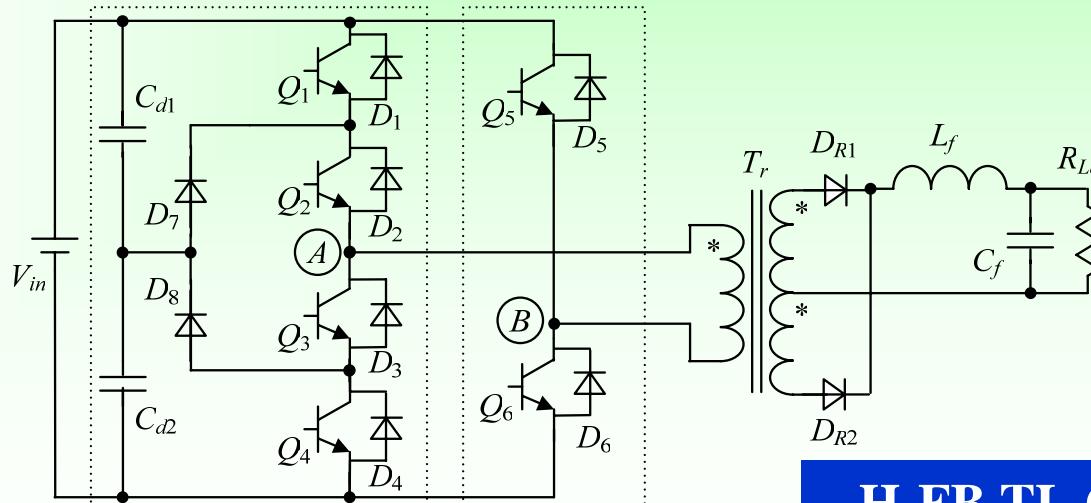


**H-FB TL Converter**

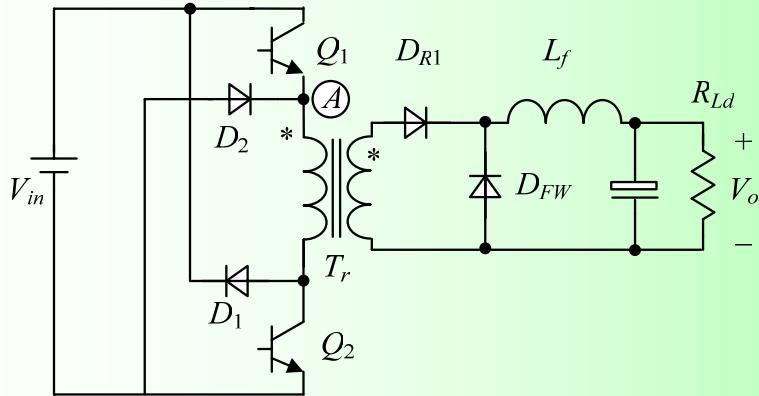
# Possibility of Three-Level Voltage Waveforms




Forward TL Converter

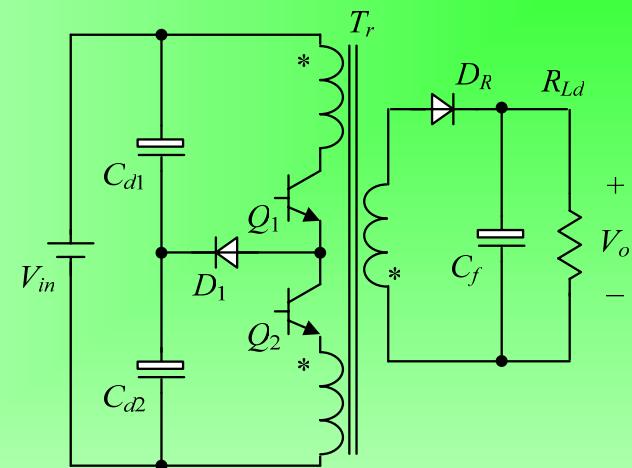

Flyback TL Converter

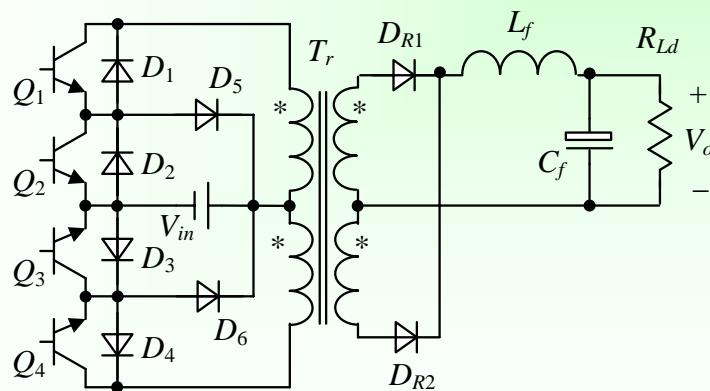

Push-Pull TL Converter

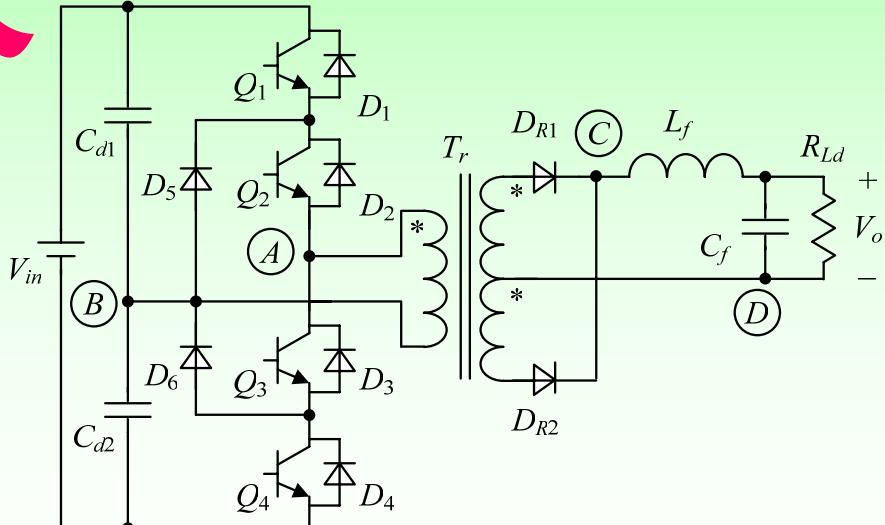

HB TL Converter

## **1. Three-Level Converters**

- A-TLSC and C-TLSC are extracted;
- A family of TL converters are proposed;
- The non-isolated TL converters are improved;
- Forward TL converter is further simplified;
- A hybrid FB TL converter are proposed.

## **2. The advantages of the TL converters**

- Reduction of the voltage stress of the switches;
- some TL converters obtain TL waveform, which can significantly reduce the filter.

## **3. Method to ensure the voltage sharing of the divided capacitors is proposed.**

*Thanks for your attention!*

*Q/A*