

Forward Converters

Presented by

Xinbo Ruan

Aero-Power Sci-tech Center
Nanjing University of Aeronautics & Astronautics

1. Introduction
2. Forward Converter with Reset Windings
3. Dual-Switch Forward Converter
4. Forward Converter with RCD Snubber
5. Forward Converter with Active Clamp Reset
6. Other Magnetic Reset Methods
7. Summary

1. Introduction
2. Forward Converter with Reset Windings
3. Dual-Switch Forward Converter
4. Forward Converter with RCD Snubber
5. Forward Converter with Active Clamp Reset
6. Other Magnetic Reset Methods
7. Summary

- Questions



- Input: 60VDC;
- Output: 48VDC/10A;
- Switching frequency: 100kHz.

Please design a dc/dc converter, determine

- 1) the voltage and current stress on the power switch, and
- 2) the voltage and current stress on the the diode.

Given the ripple current of the filter inductance $20\%I_{omax}$.

Buck: 60V_{in}; 48V/10A output

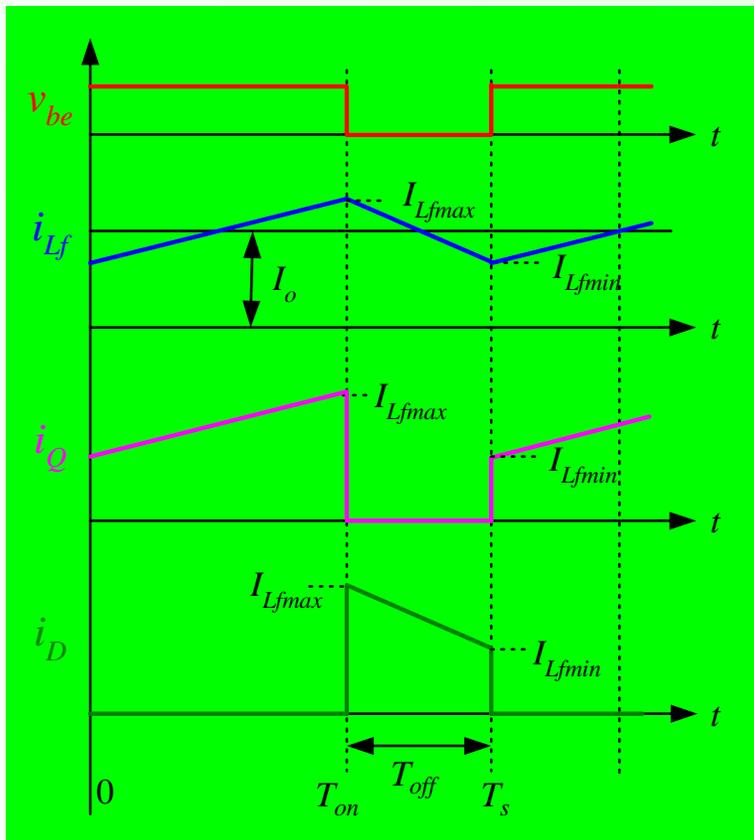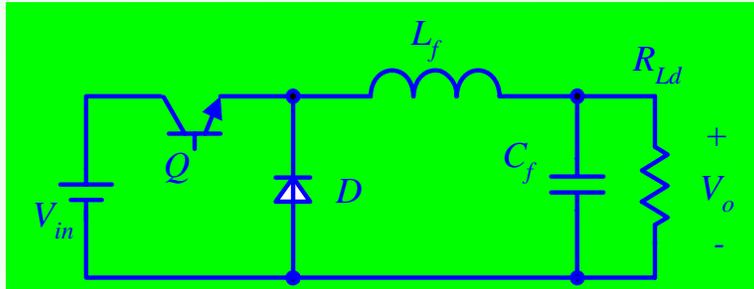

$$V_o = L_f \frac{\Delta i_{L_f}}{T_{off}}$$

$$20\% I_{omax} = 2 \text{ A}$$



$$D = V_o / V_{in} = 0.8$$

$$T_{off} = (1-D)T_s = 2 \mu\text{s}$$

$$L_f = 48 \mu\text{H}$$

$$I_{Q \max} = I_{D \max} = I_{L_f \max} = 11 \text{ A}$$

Buck: 300V_{in}; 48V_{out}/10A

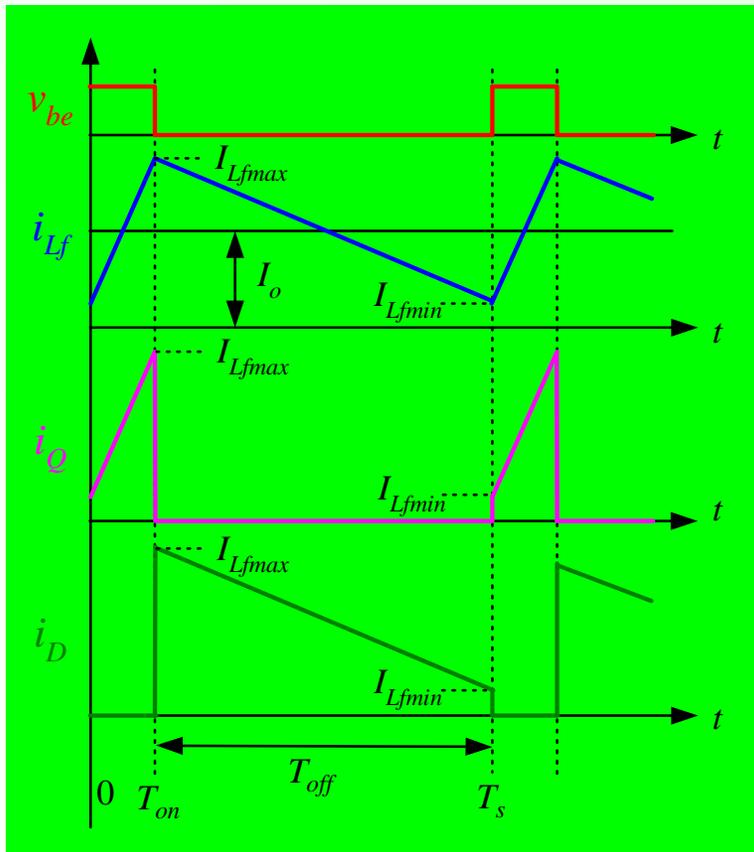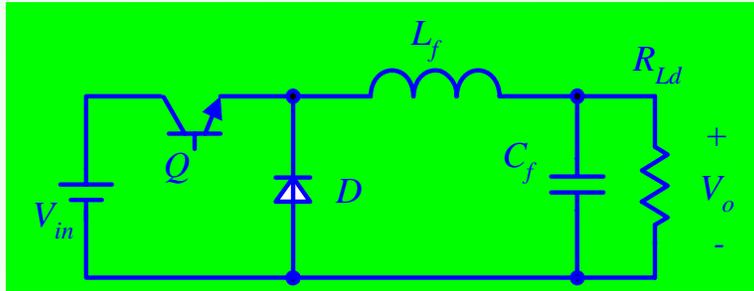

$$D = V_o / V_{in} = 0.16$$



$$T_{off} = (1 - D)T_s = 8.4 \mu s$$





$$\Delta i_{L_f} = V_o T_{off} / L_f = 8.4 \text{ A}$$



$$\begin{aligned} I_{Q \max} &= I_{D \max} = I_{L_f \max} \\ &= 10 + \frac{8.4}{2} = 14.2 \text{ A} \end{aligned}$$

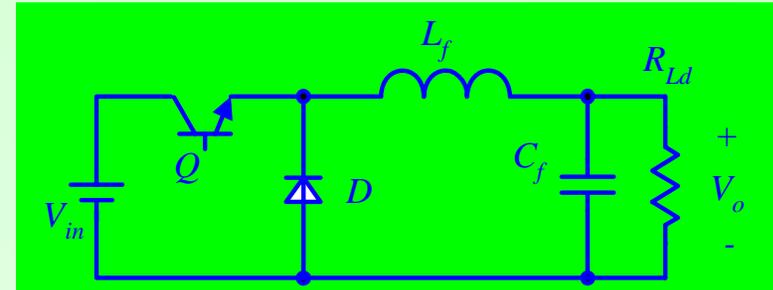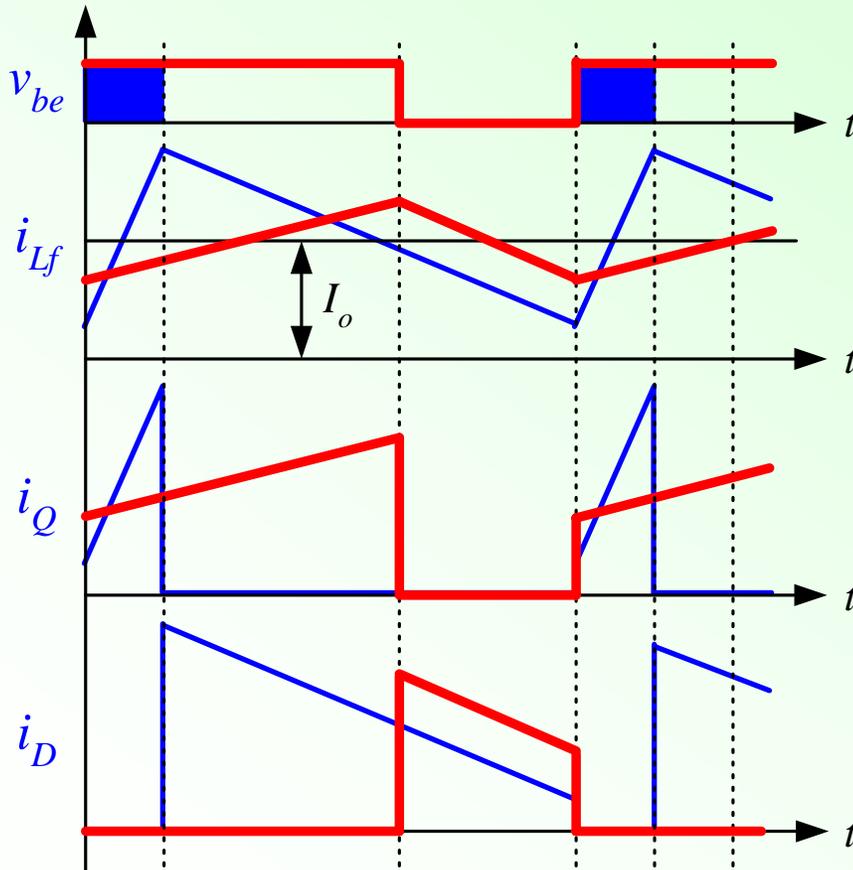Buck: Comparison of Different Input Voltage




Problems:



- ⊗ The current i_o becomes larger;
- ⊗ The switching devices suffer high voltage;
- ⊗ Duty cycle becomes small.
- ⊗ The input is not isolated with the output.

Answer:

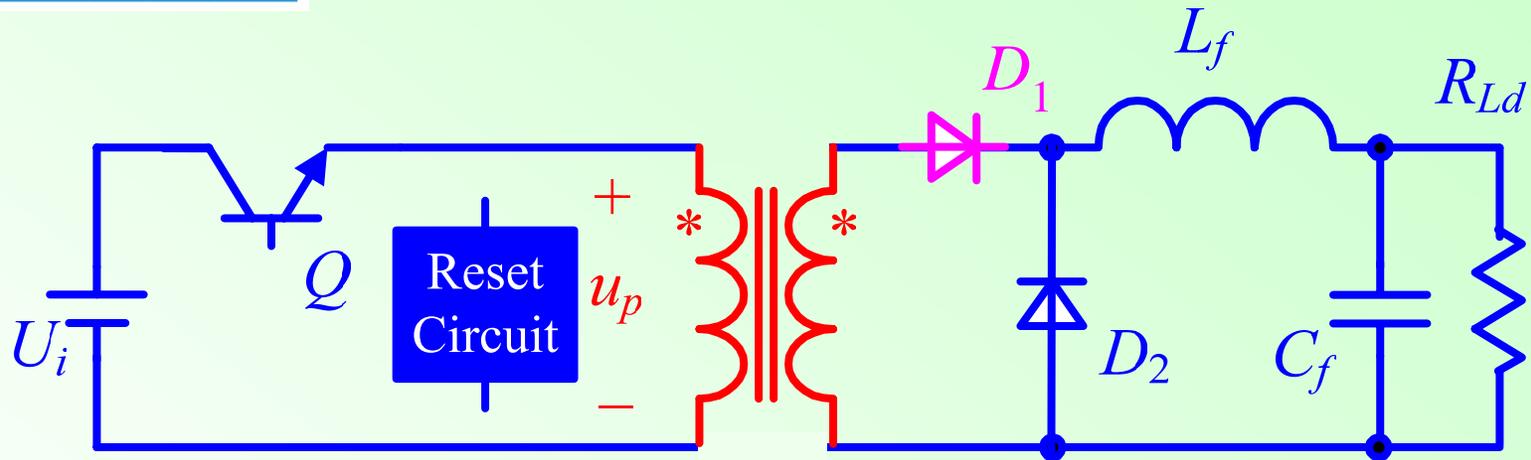The input voltage is not so matched with the output voltage.





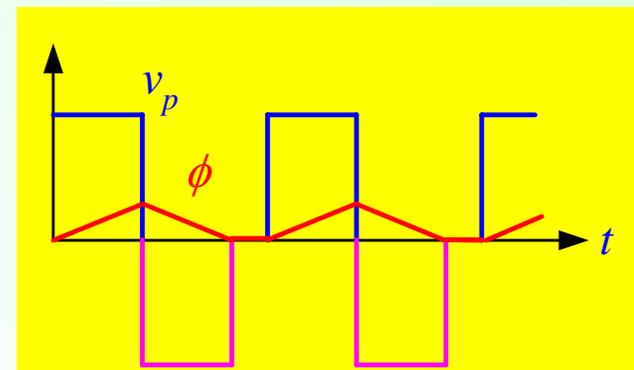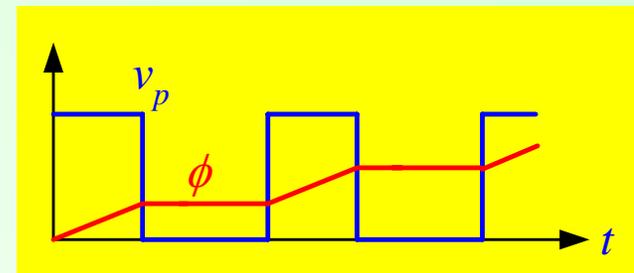
- Step 1: Introduce a transformer;
- Step 2: Magnetic Reset circuit;
- Step 3: Introduce a rectifier diode.




1. Introduction
- 2. Forward Converter with Reset Windings**
3. Dual-Switch Forward Converter
4. Forward Converter with RCD Snubber
5. Forward Converter with Active Clamp Reset
6. Other Magnetic Reset Methods
7. Summary



Another Form of Forward Converter

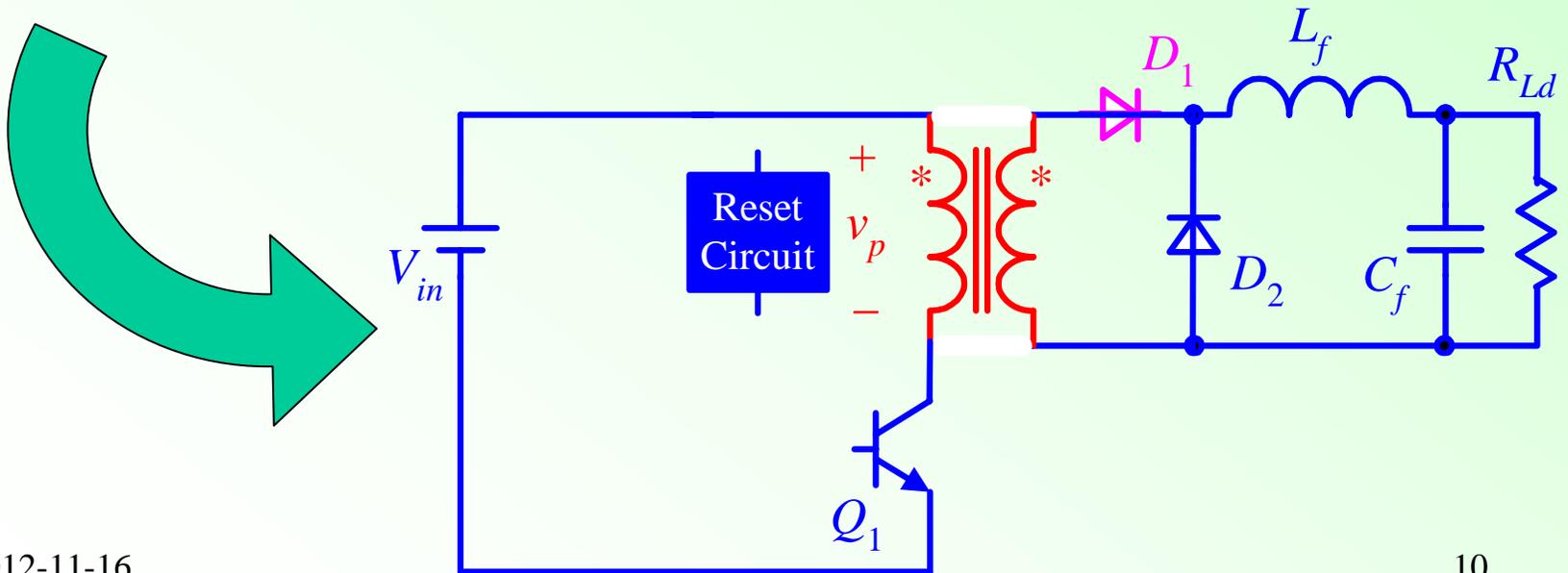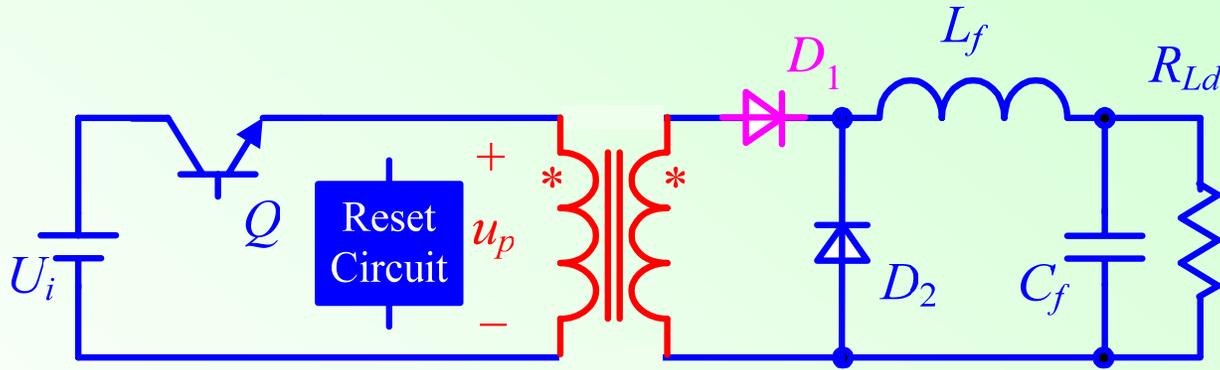

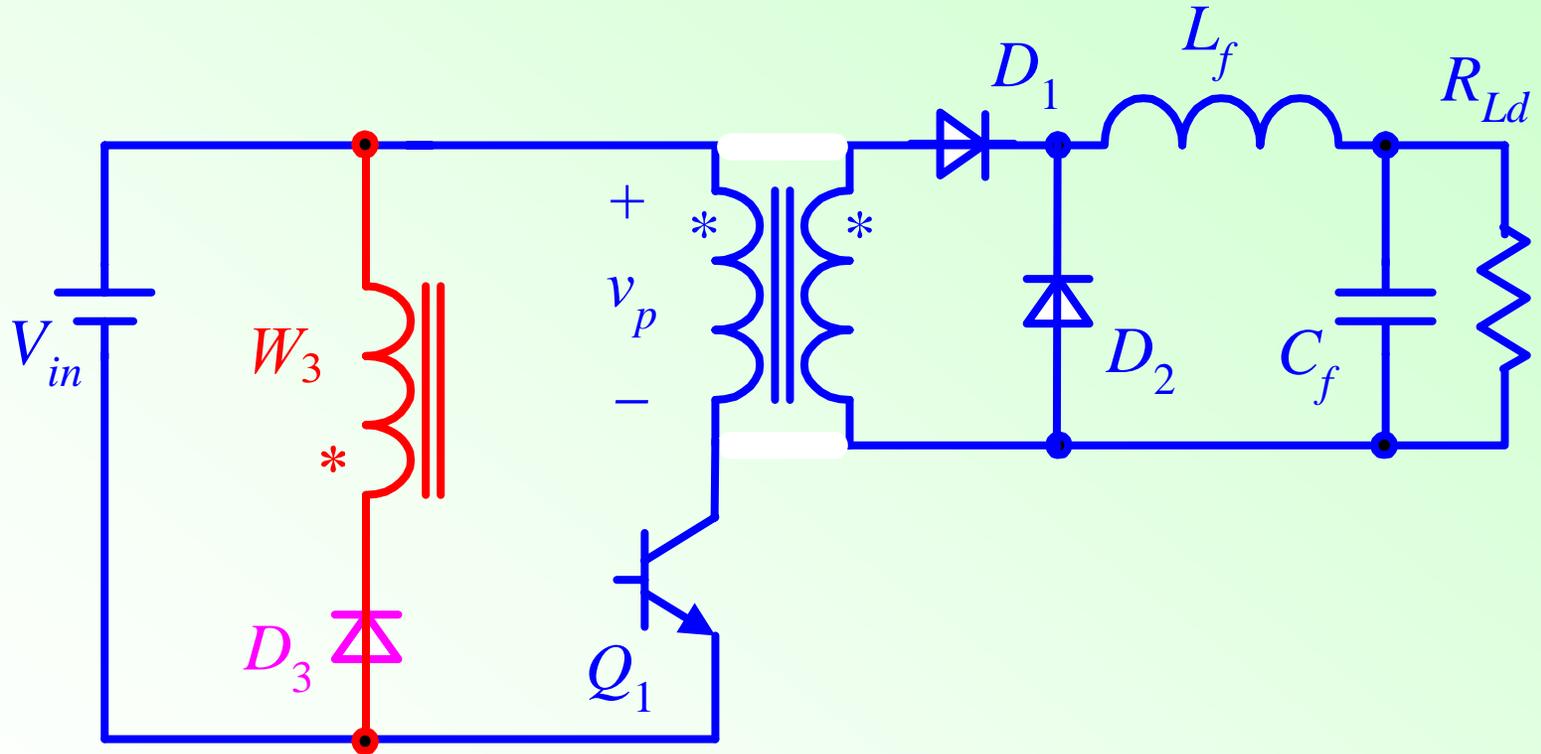

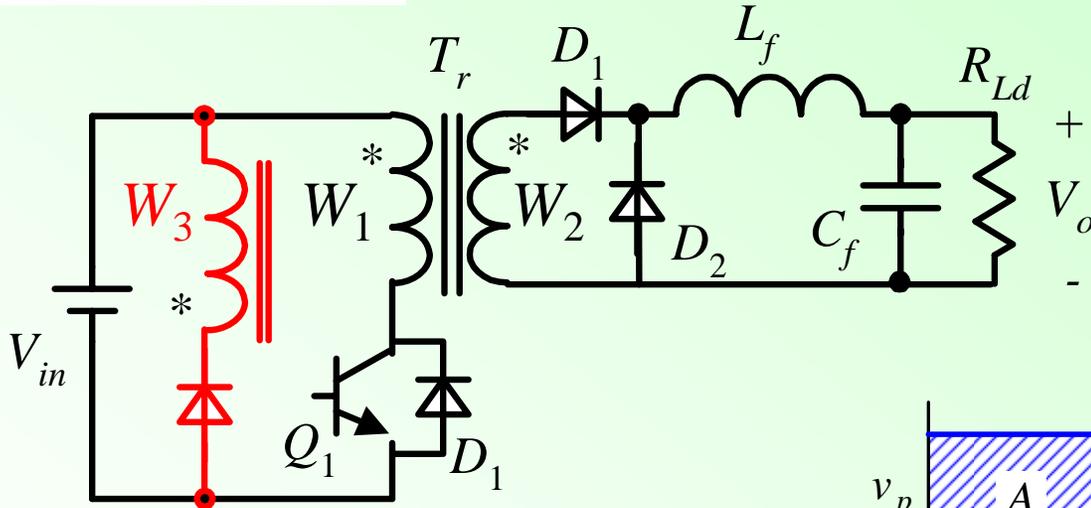


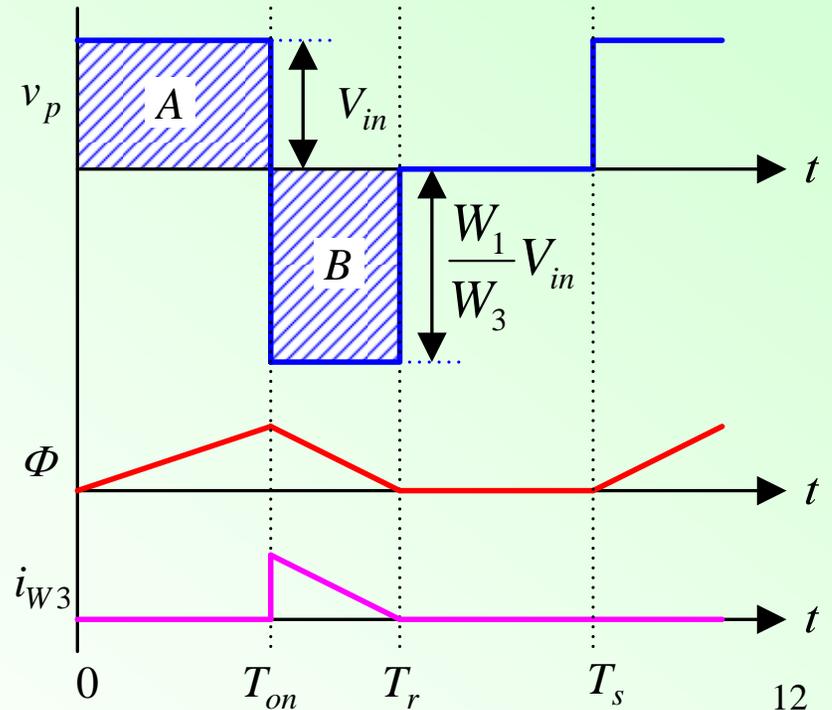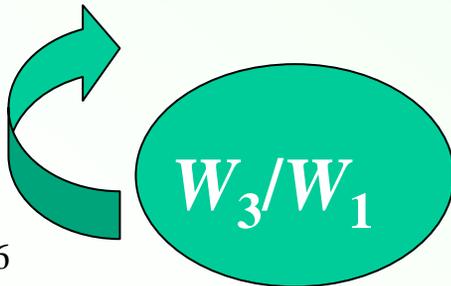1. Duty cycle;
2. Voltage stress of Q_1 .






1. Introduction
2. Forward Converter with Reset Windings
- 3. Dual-Switch Forward Converter**
4. Forward Converter with RCD Snubber
5. Forward Converter with Active Clamp Reset
6. Other Magnetic Reset Methods
7. Summary



Dual-Switch Forward Converters

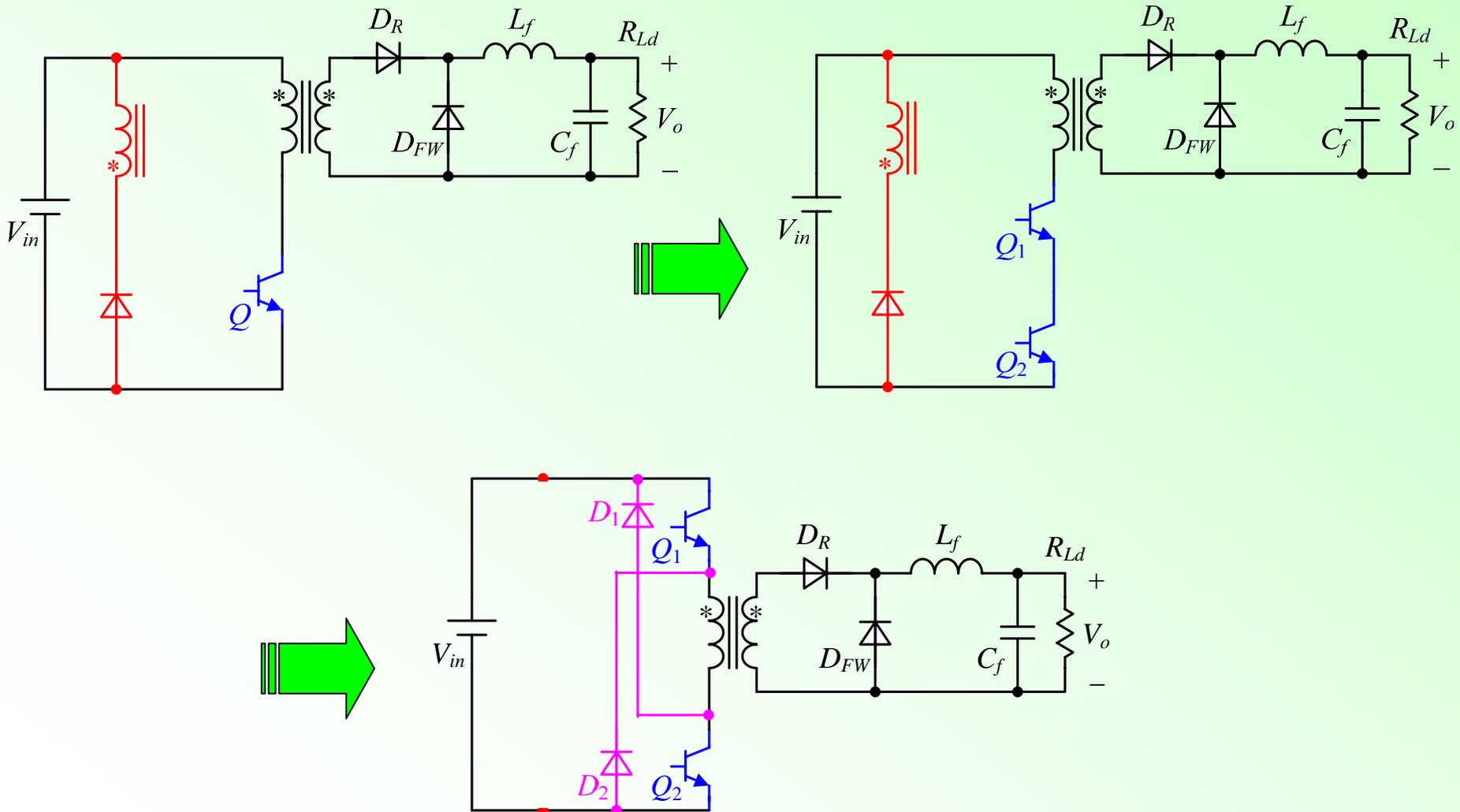

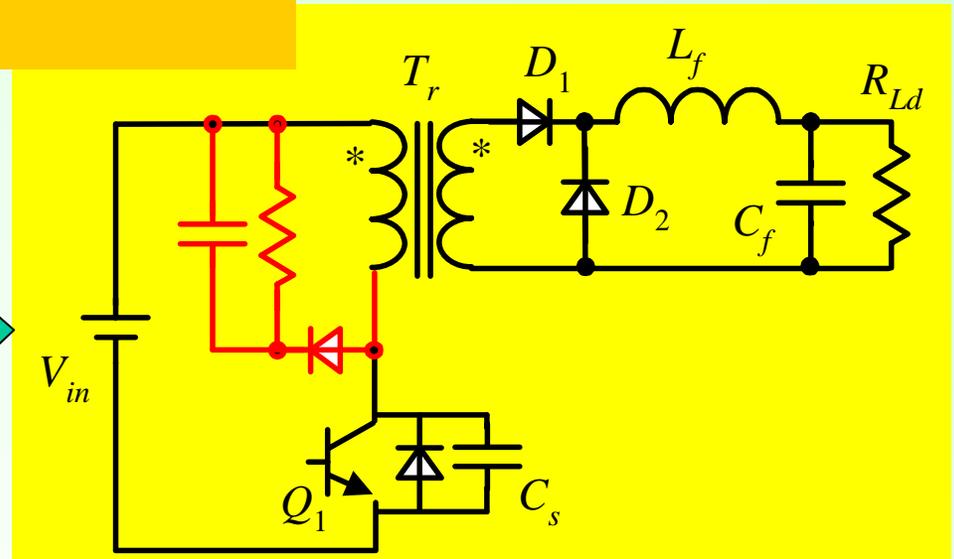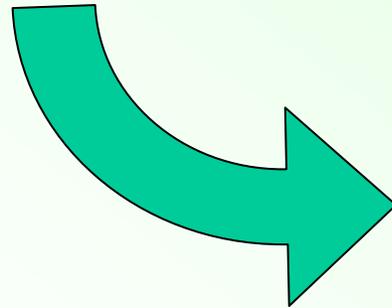
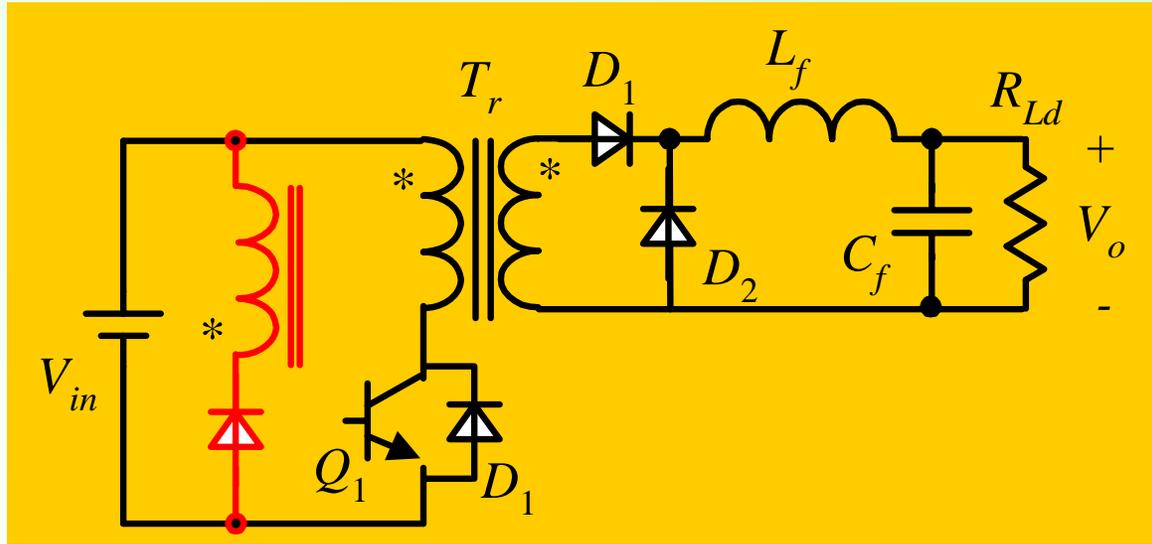
1. Introduction
2. Forward Converter with Reset Windings
3. Dual-Switch Forward Converter
- 4. Forward Converter with RCD Snubber**
5. Forward Converter with Active Clamp Reset
6. Other Magnetic Reset Methods
7. Summary





Operation Principle: $[t_0, t_1]$

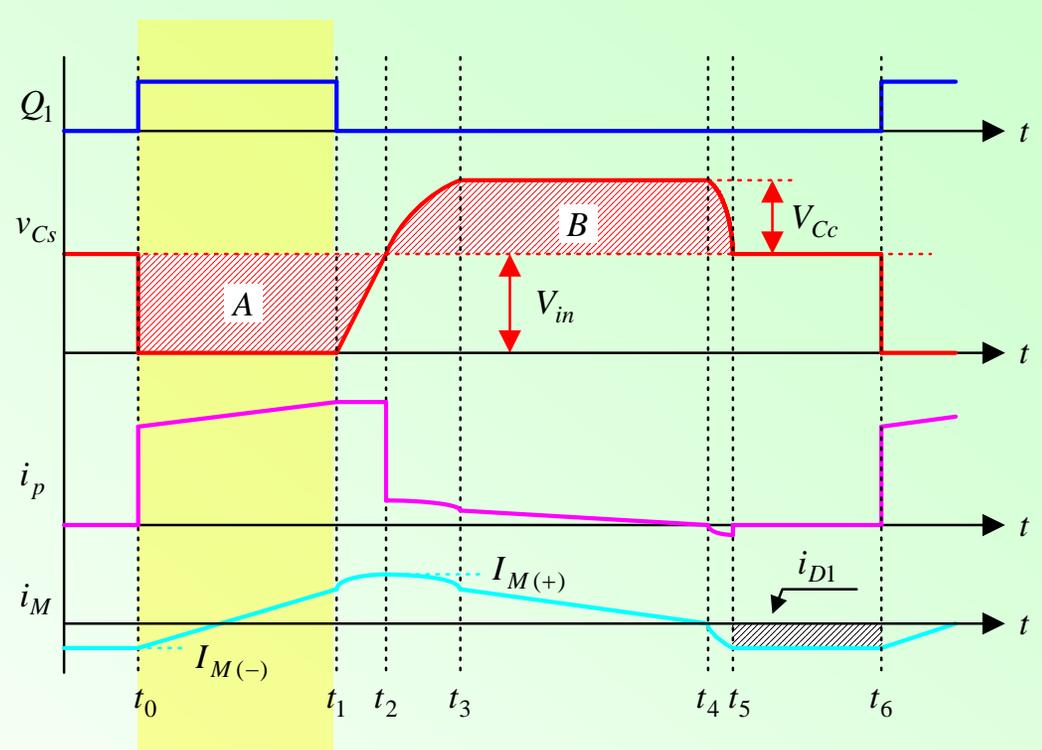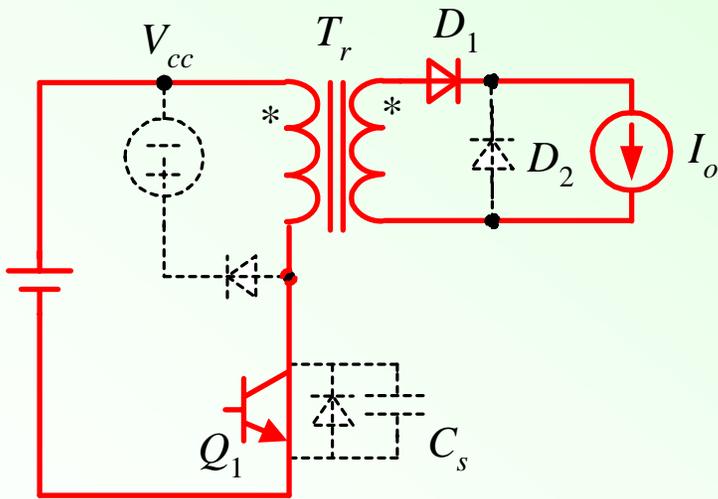



Operation Principle: $[t_1, t_2]$

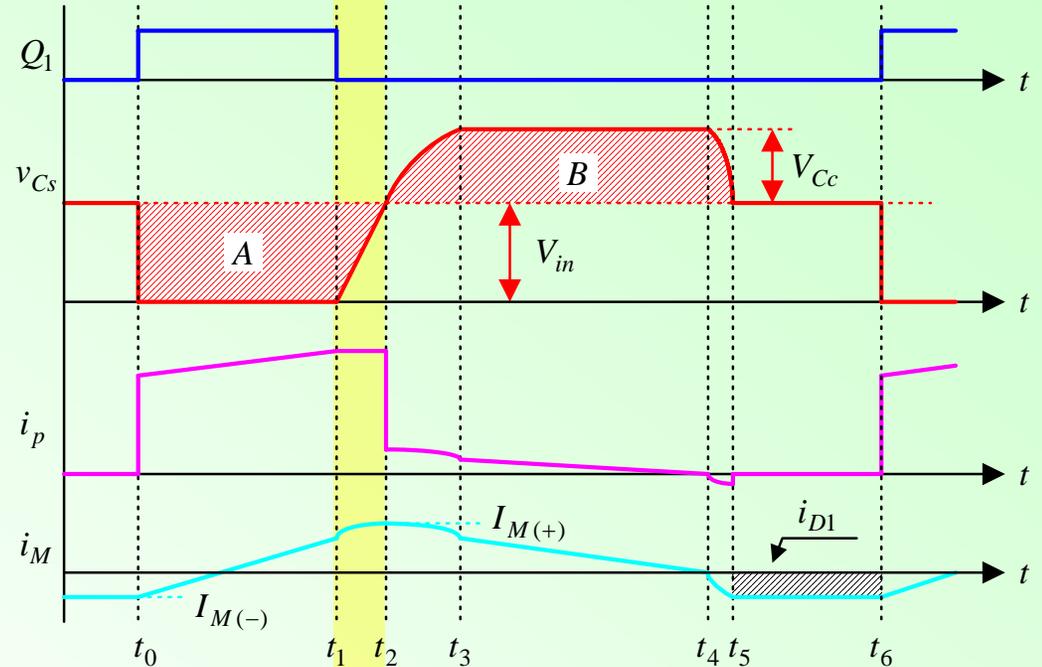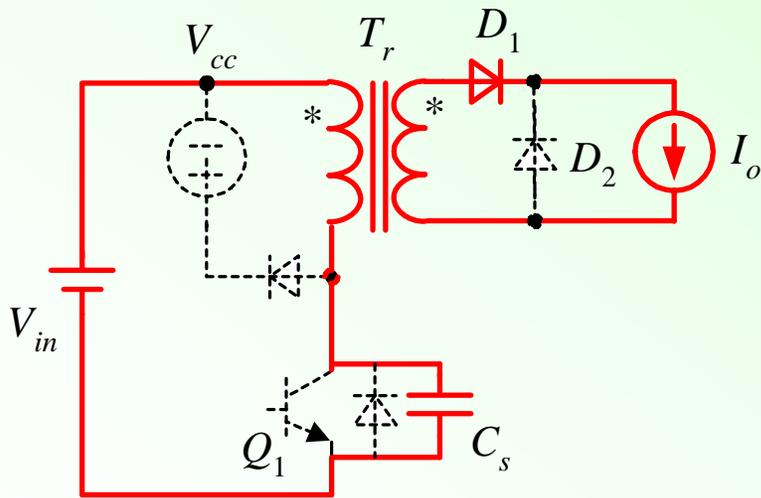



Operation Principle: $[t_2, t_3]$

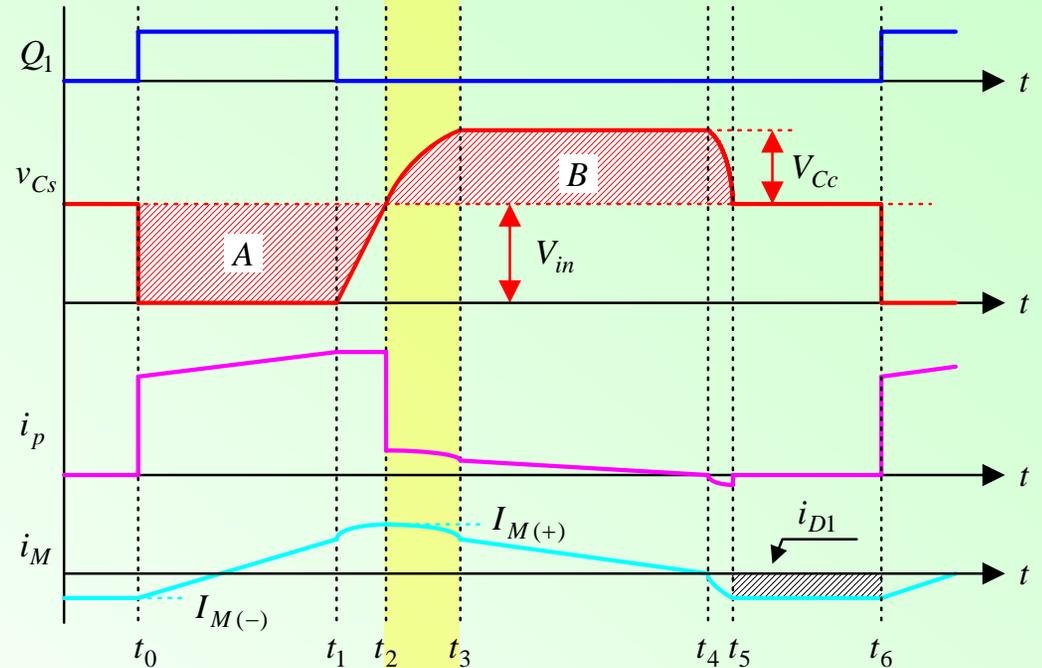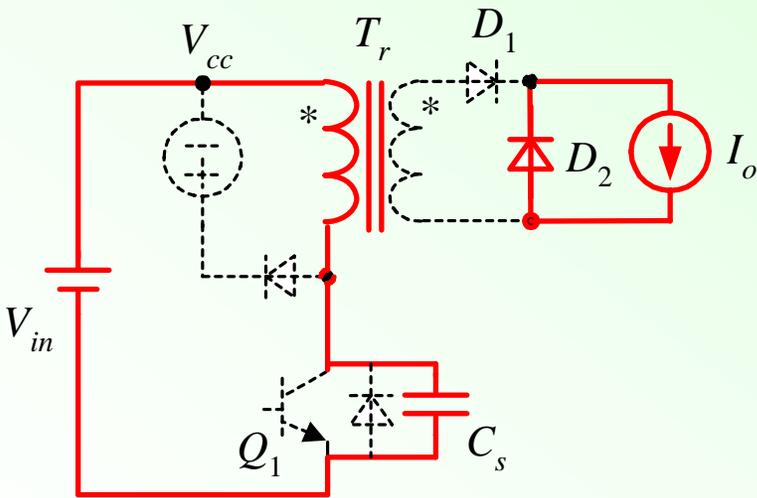



Operation Principle: $[t_3, t_4]$

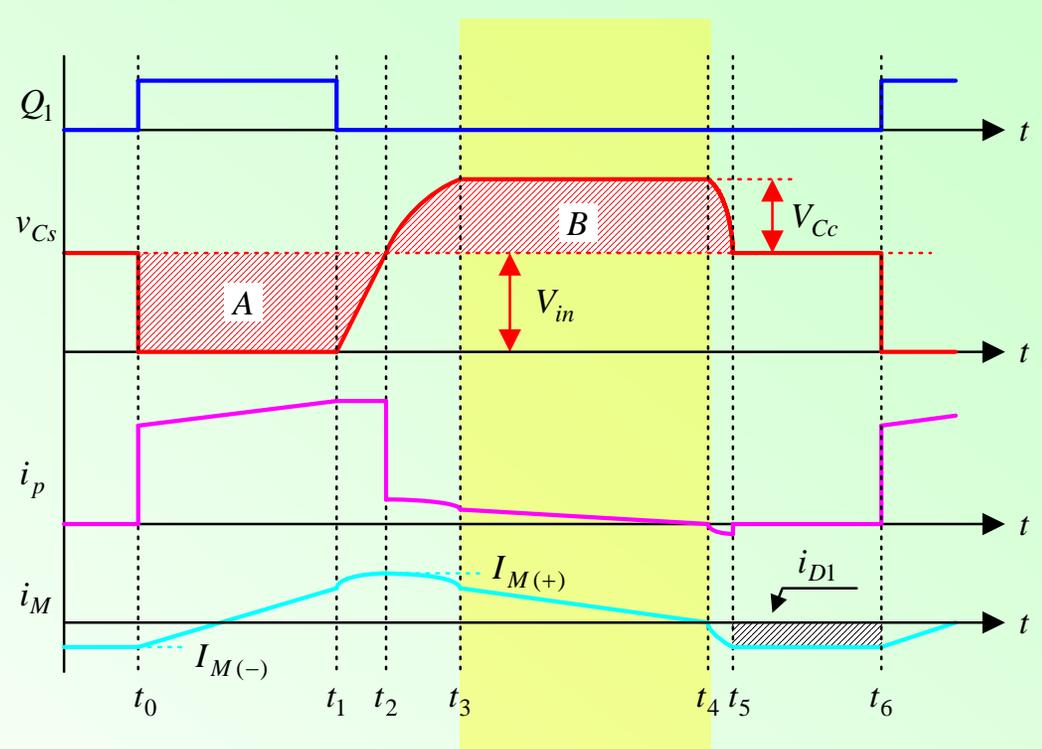
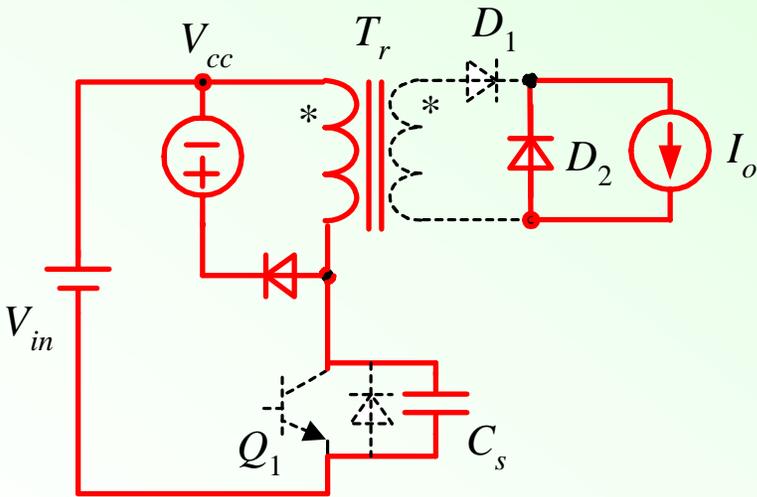


Operation Principle: $[t_4, t_5]$

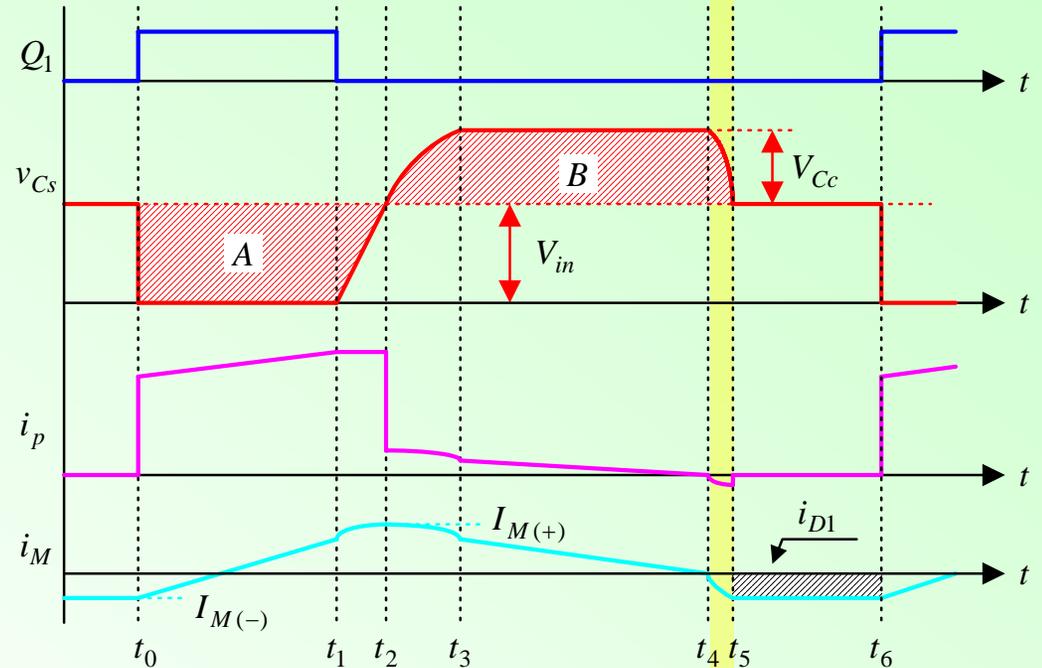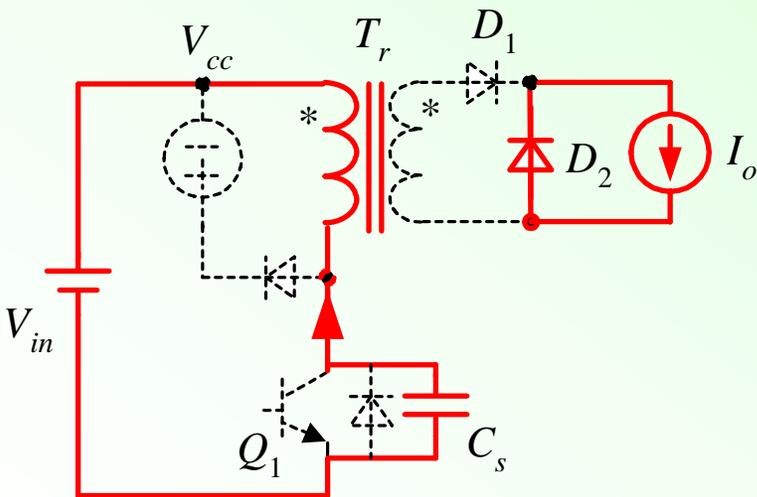

Operation Principle: $[t_5, t_6]$

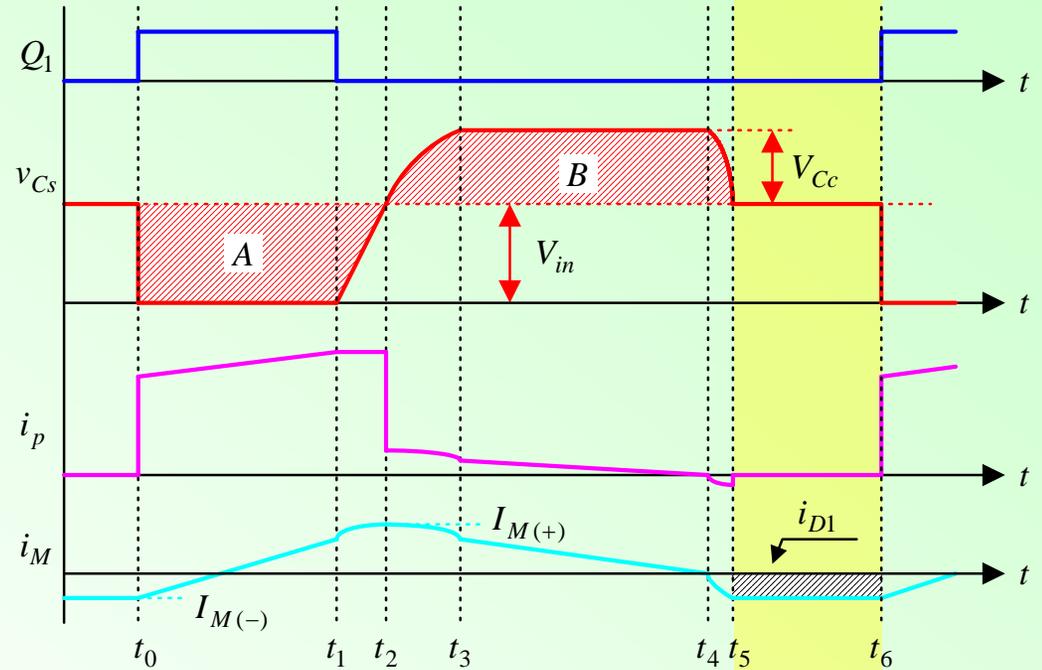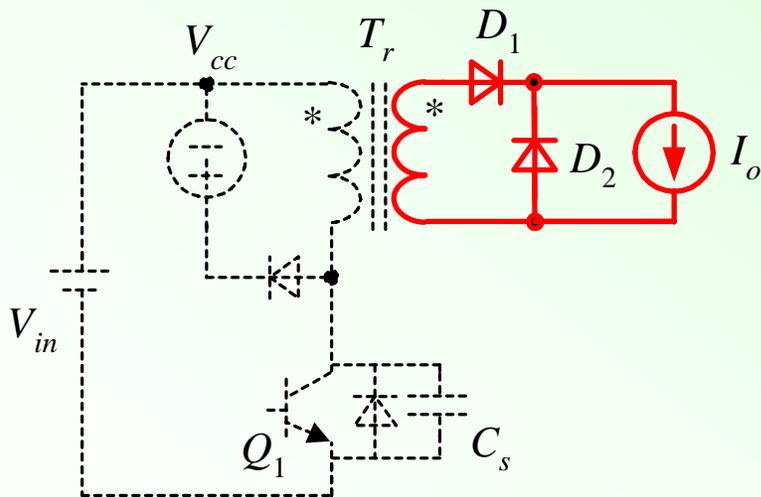

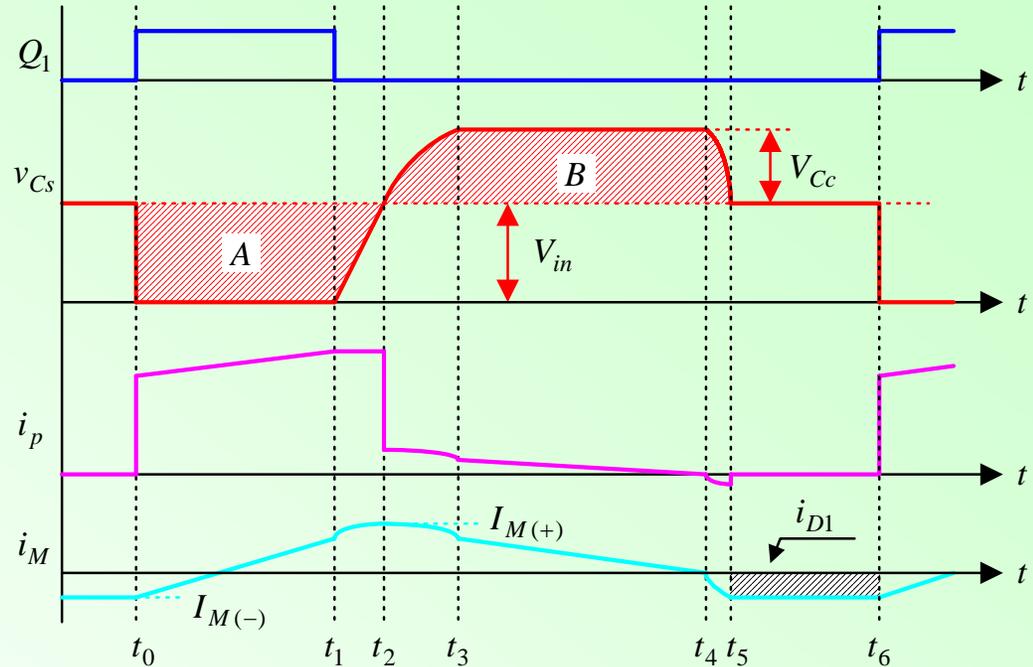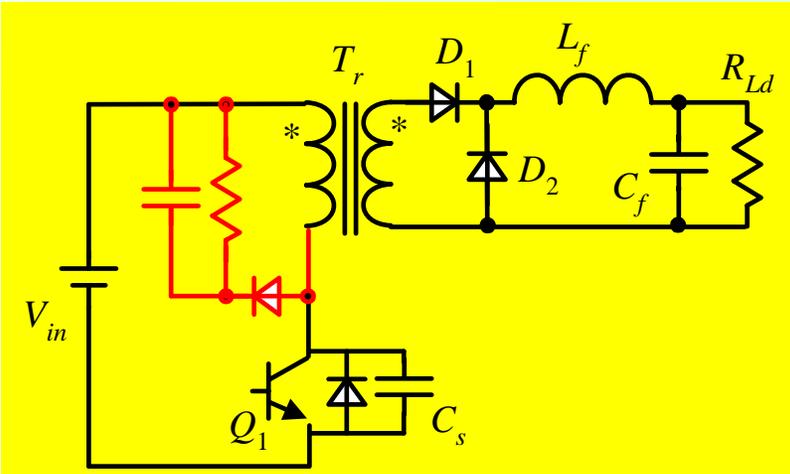

1. V_{cc}

$$V_{cc_min} = \frac{V_{in} D_y}{1 - D_y} = \frac{KV_o}{1 - D_y}$$

$$V_{Q1} = V_{in} + V_{cc}$$

2. R_c

Magnetic Energy

Stored by Junction capacitor


Dissipated in the resistance

3. C_c



$$\Delta V_c \approx 5\% V_{cc}$$

1. Introduction
2. Forward Converter with Reset Windings
3. Dual-Switch Forward Converter
4. Forward Converter with RCD Snubber
- 5. Forward Converter with Active Clamp Reset**
6. Other Magnetic Reset Methods
7. Summary



Active Clamp Forward Converter

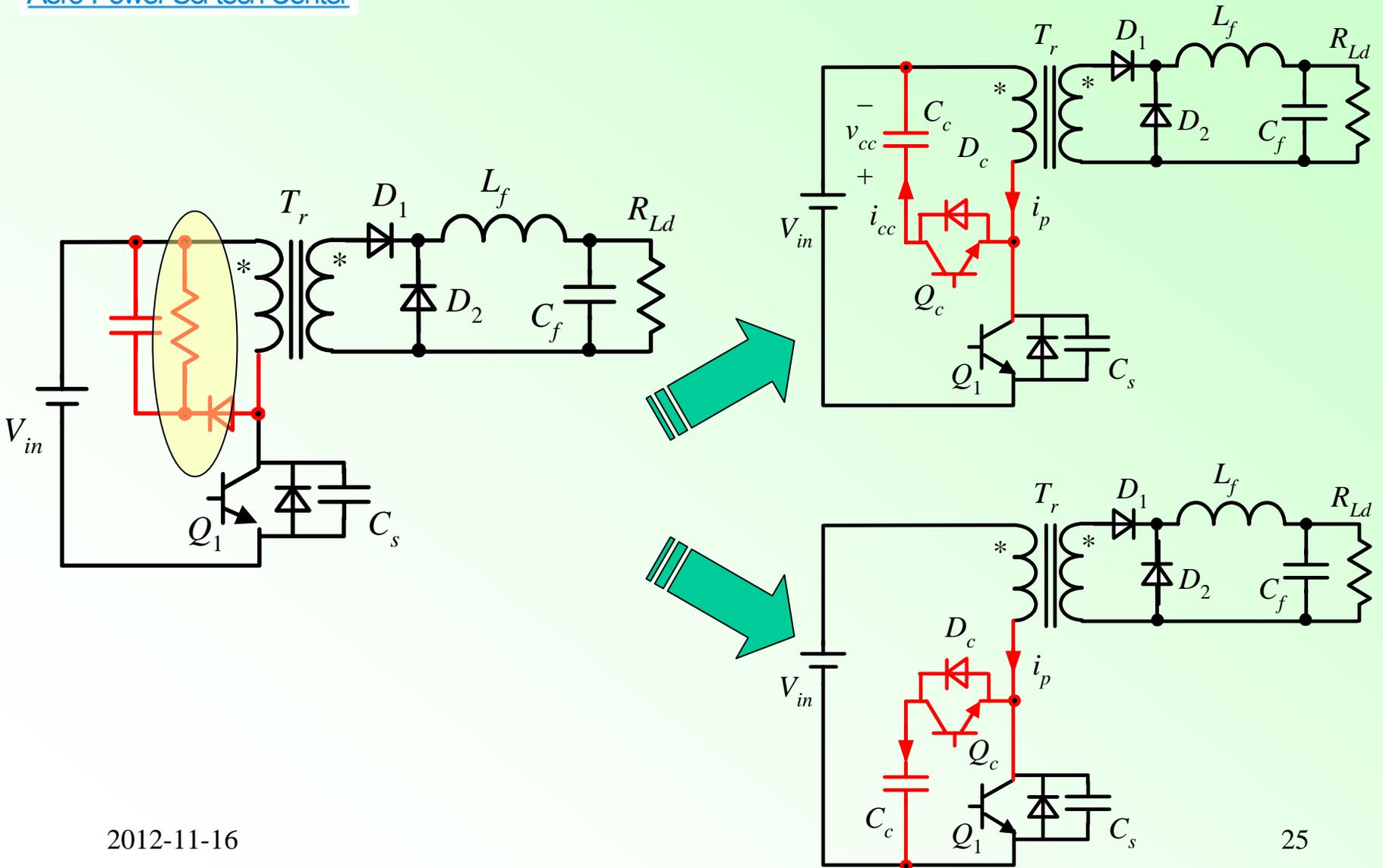



Operation Principle: $[t_0, t_1]$

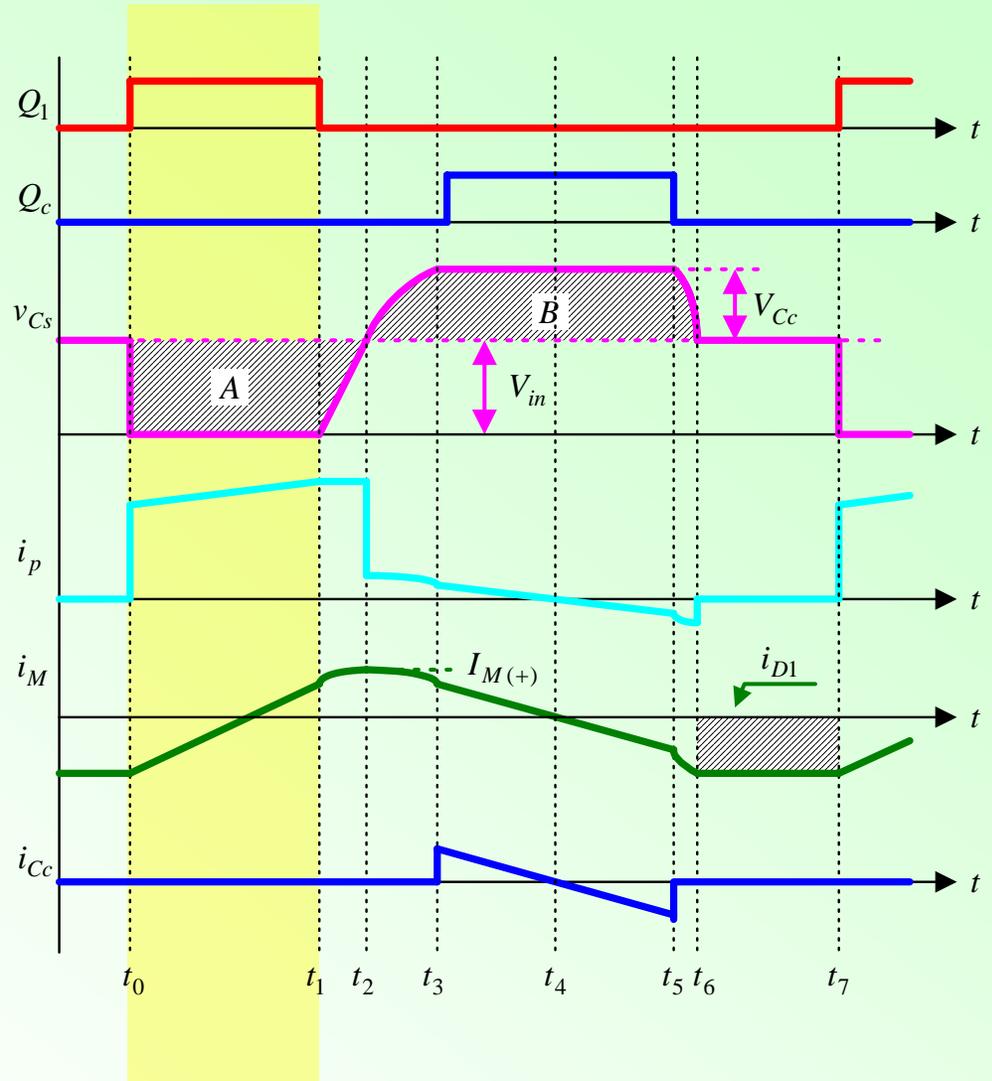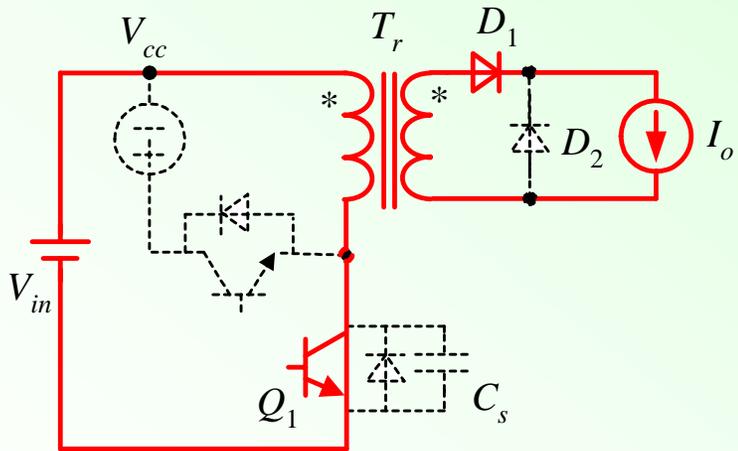



Operation Principle: $[t_1, t_2]$

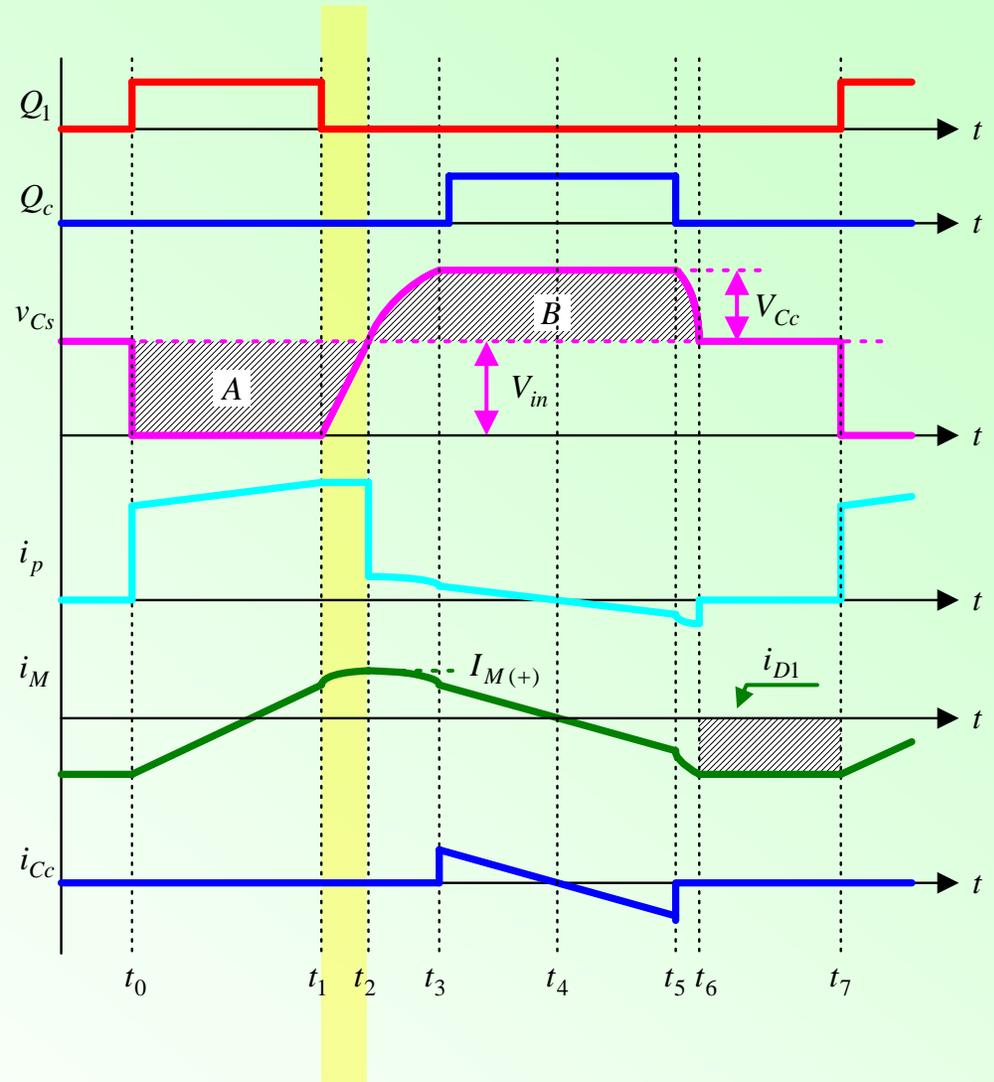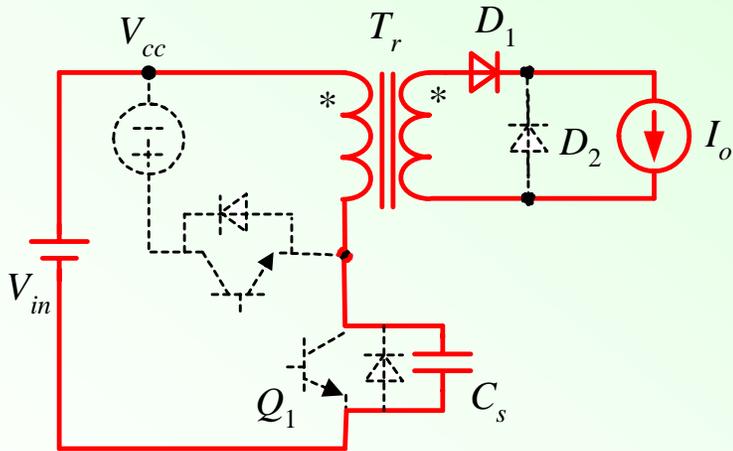



Operation Principle: $[t_2, t_3]$

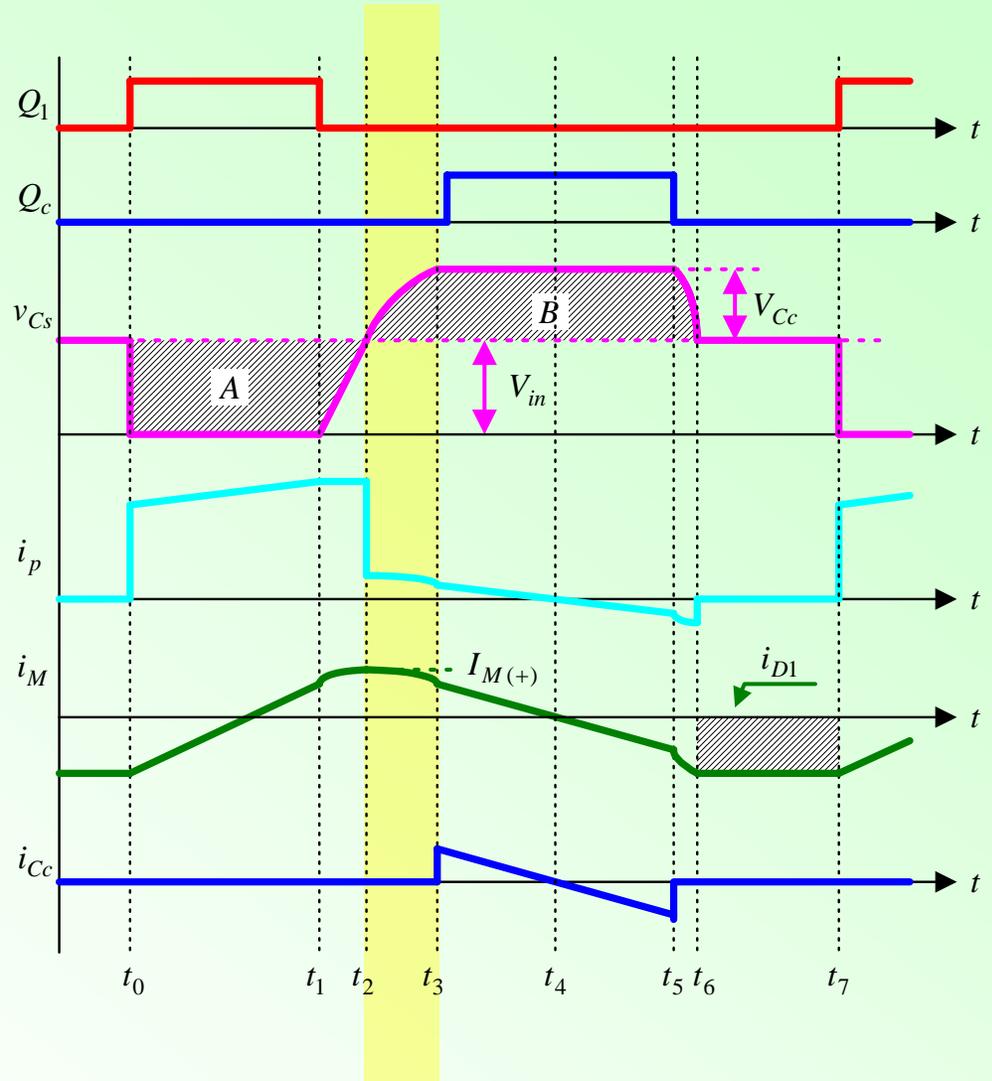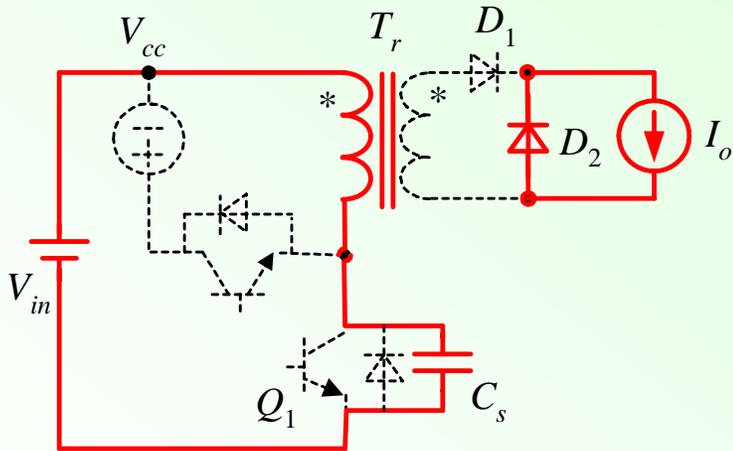



Operation Principle: $[t_3, t_4]$

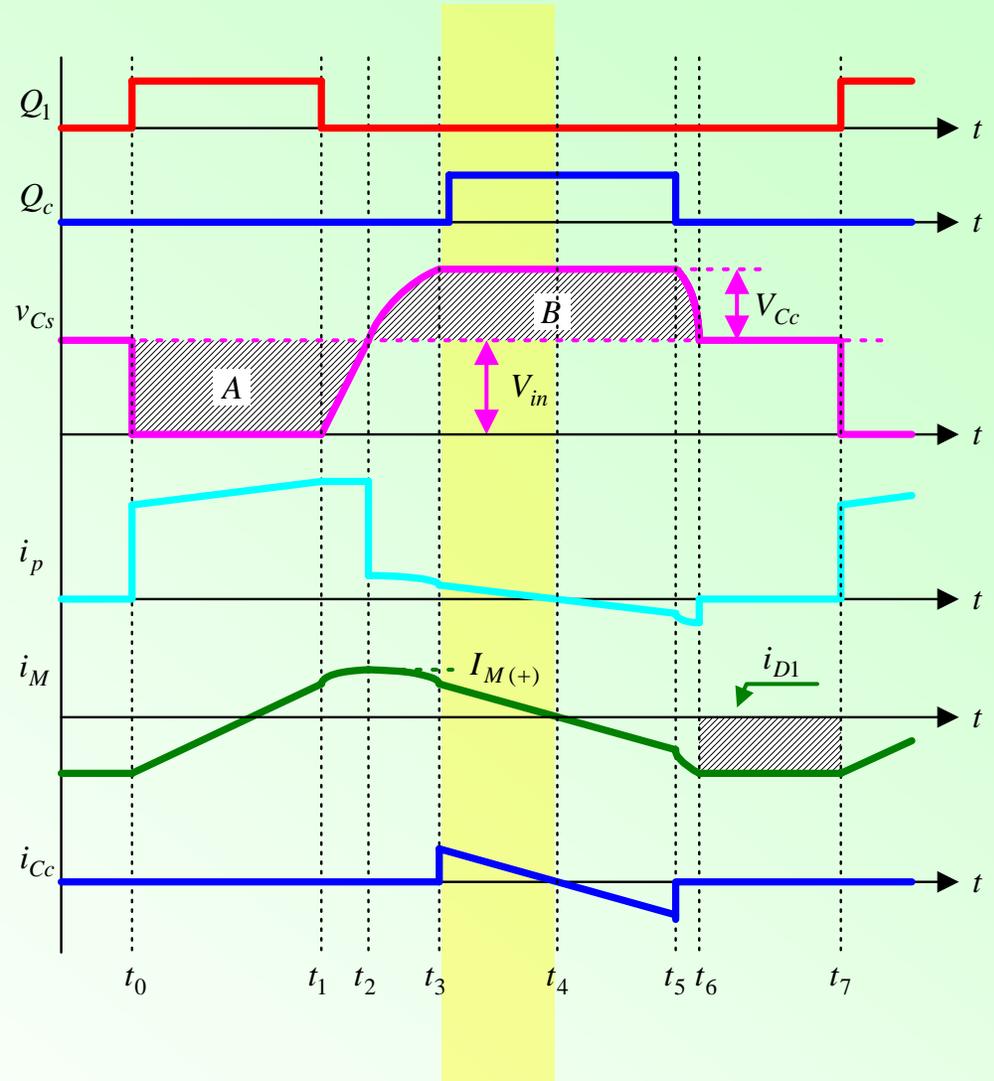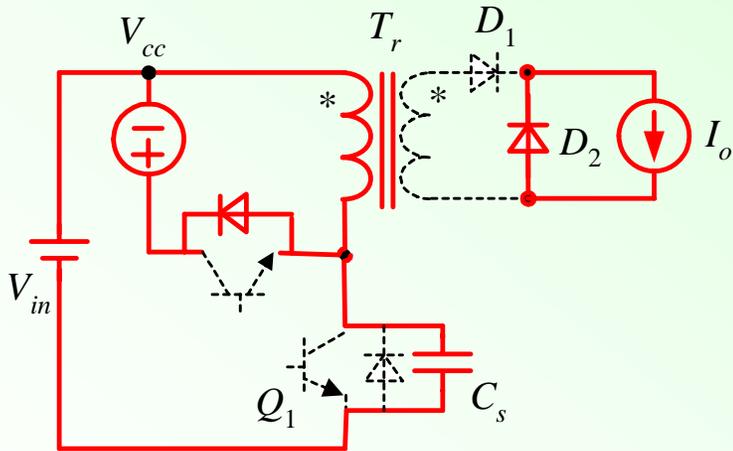



Operation Principle: $[t_4, t_5]$

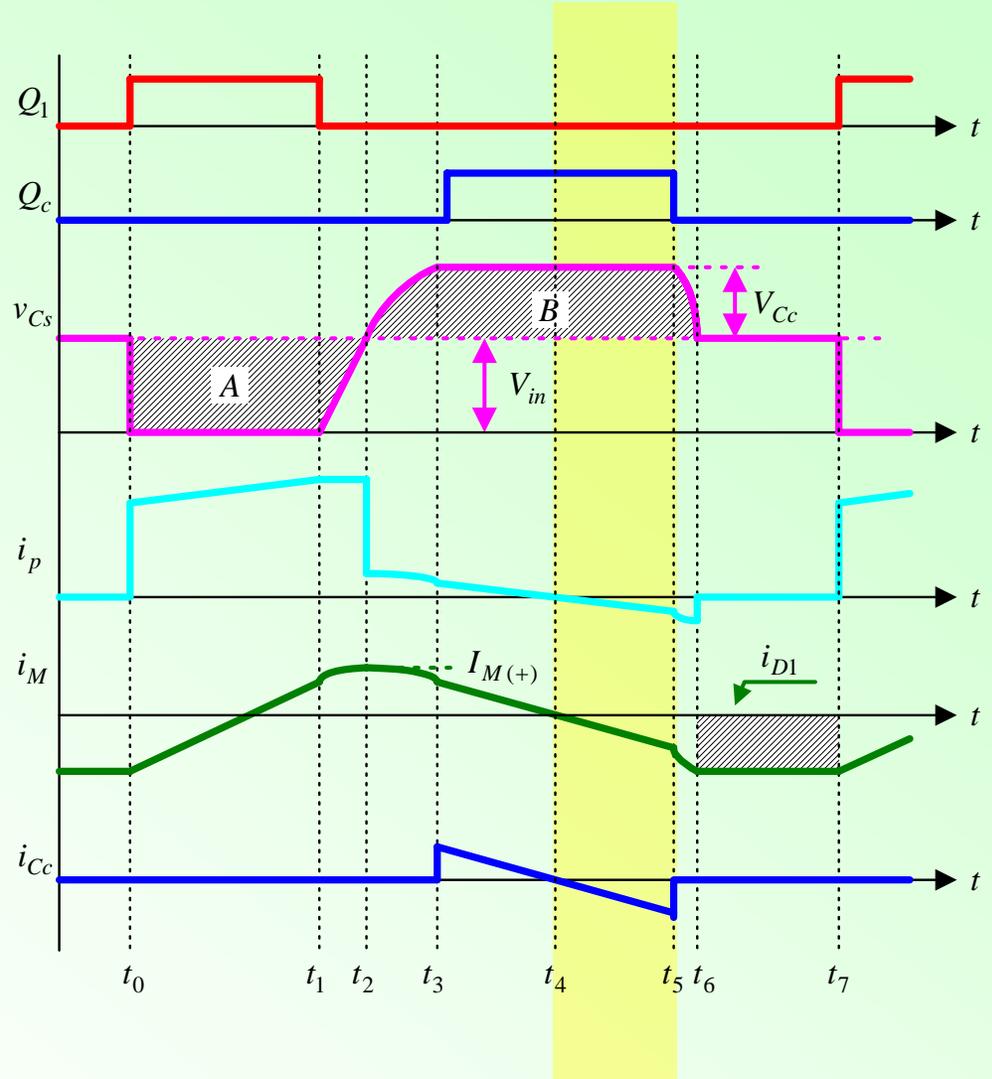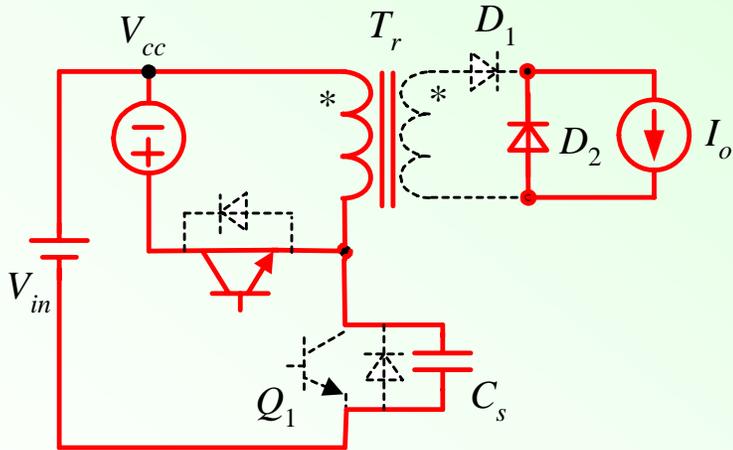

Operation Principle: $[t_5, t_6]$

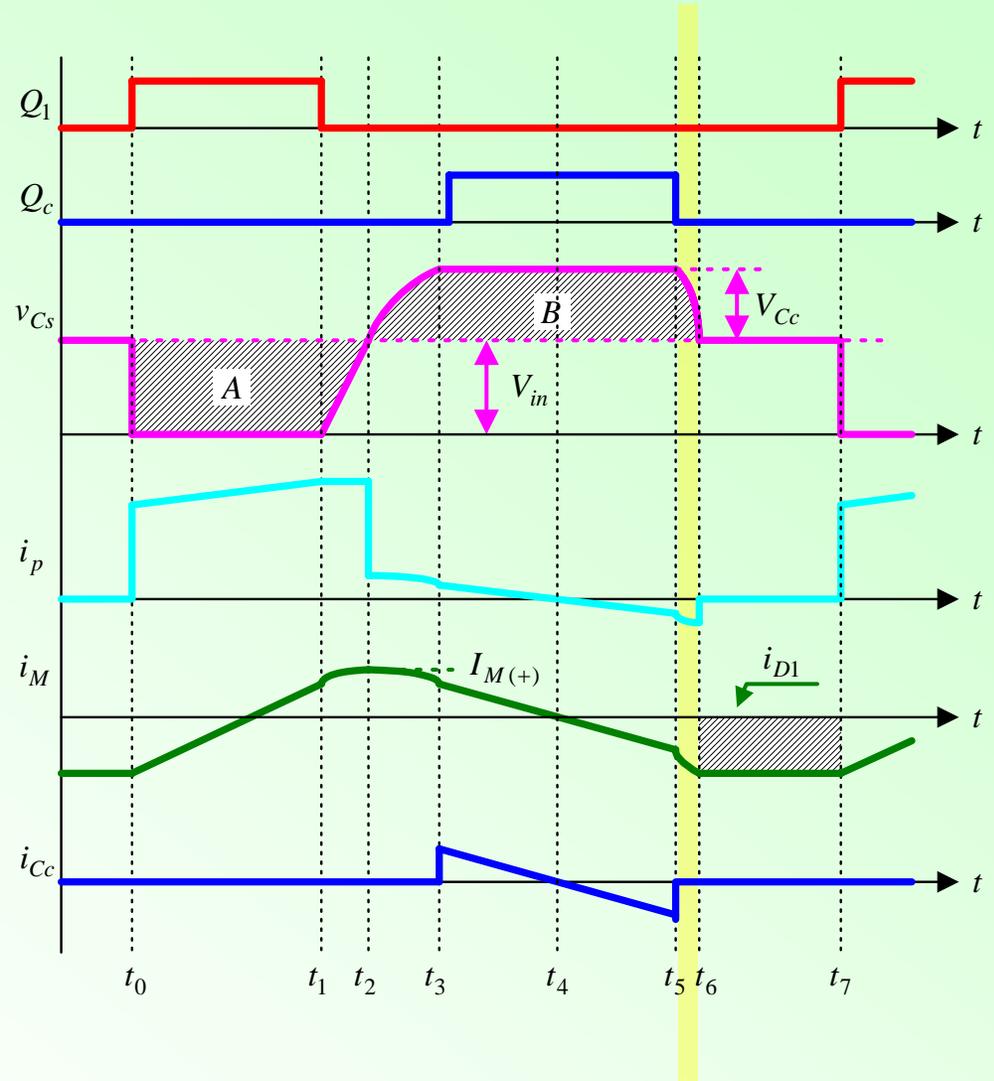
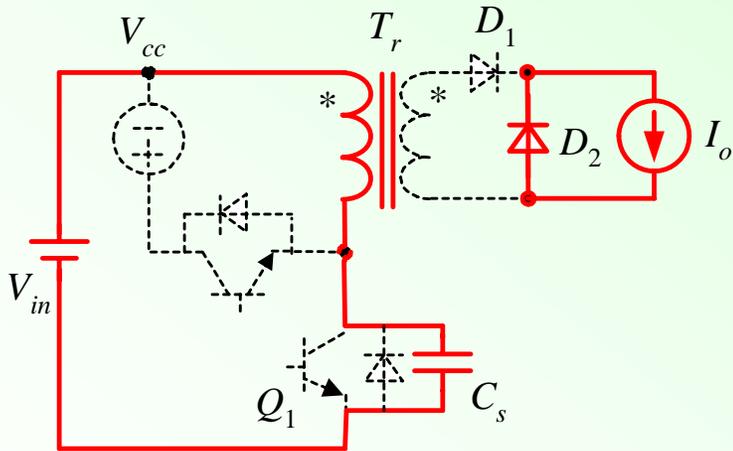


Operation Principle: $[t_6, t_7]$

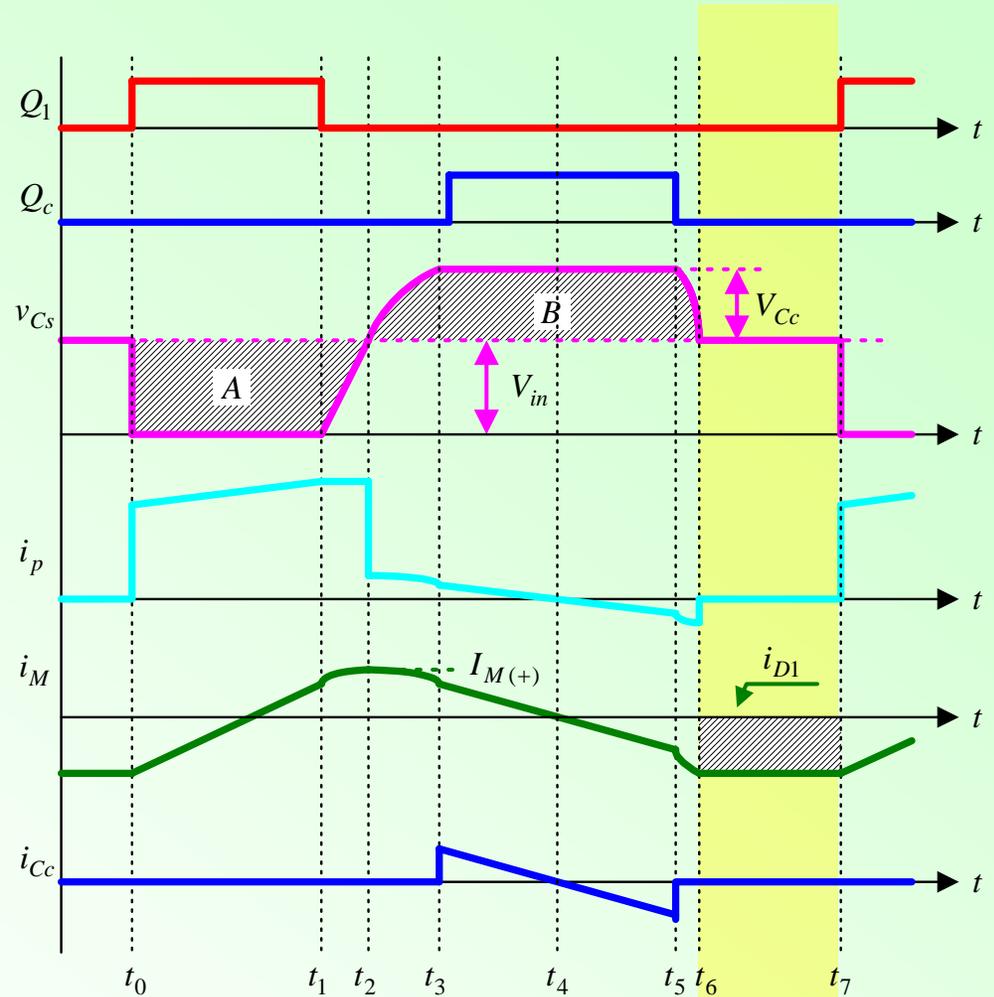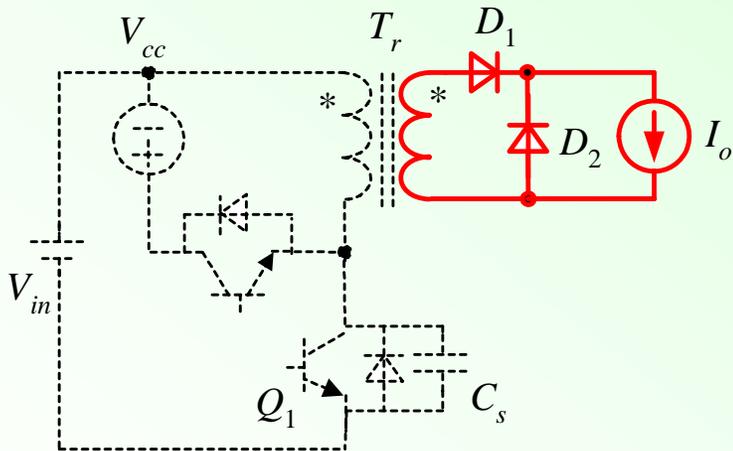

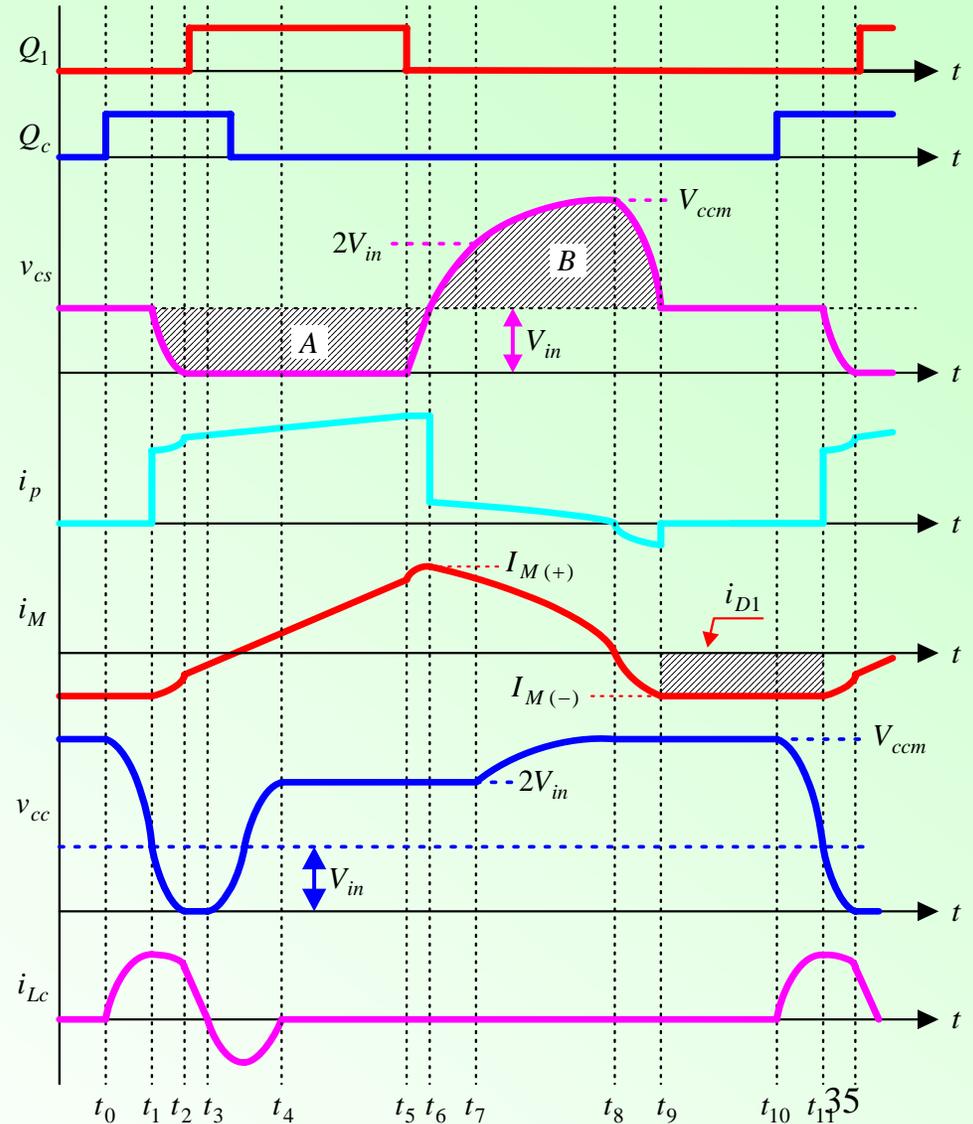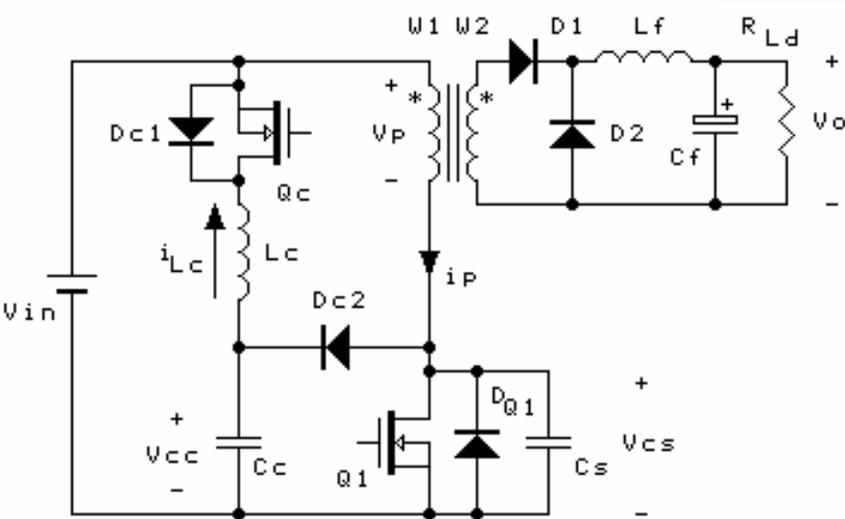1. Introduction
2. Forward Converter with Reset Windings
3. Dual-Switch Forward Converter
4. Forward Converter with RCD Snubber
5. Forward Converter with Active Clamp Reset
- 6. Other Magnetic Reset Methods**
7. Summary

Zero-Voltage-Transition Forward Converter



1. Introduction
2. Forward Converter with Reset Windings
3. Dual-Switch Forward Converter
4. Forward Converter with RCD Snubber
5. Forward Converter with Active Clamp Reset
6. Other Magnetic Reset Methods
7. Summary

Comparison of Reset Circuit

	Reset Winding	Dual-Switch	RCD Snubber	Active Clamp	LCD	ZVT
Topology	Simple	Simple	Very Simple	Simple	Not Simple	Not Simple
Voltage Stress of Main Switch	$2V_{inmax}$	V_{inmax}	$<2V_{inmax}$	$<2V_{inmax}$	$<2V_{inmax}$	$<2V_{inmax}$
Switching of Main Switch	Hard-Switching	Hard-Switching	Hard-Switching	Hard-Switching	Hard-Switching	Zero-Voltage-Switching
Magnetic Core	Unidirectional magnetization	Unidirectional magnetization	Unidirectional magnetization	Bidirectional magnetization	Unidirectional magnetization	Unidirectional magnetization
Duty Cycle	< 0.5	< 0.5	> 0.5	> 0.5	> 0.5	> 0.5
Efficiency	Not so high	high	low	High	Not so high	High
Input Voltage Range	Narrow	Narrow	Wide	Wide	Wide	Wide

Thanks for your attention !

Questions? / Answer!