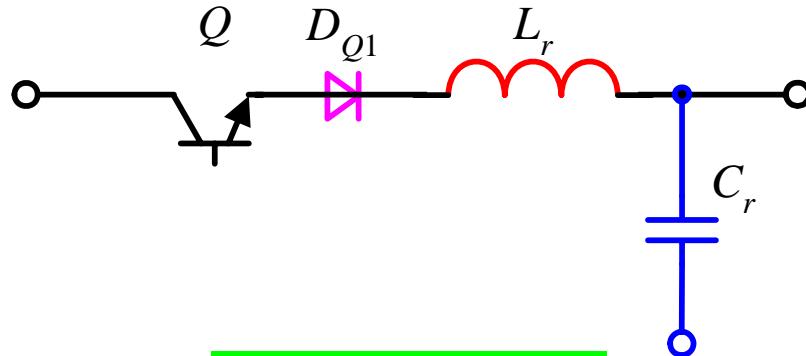


Quasi-Resonant Converters


Presented by

Xinbo Ruan


Aero-Power Sci-tech Center
Nanjing University of Aeronautics & Astronautics




Half-wave mode

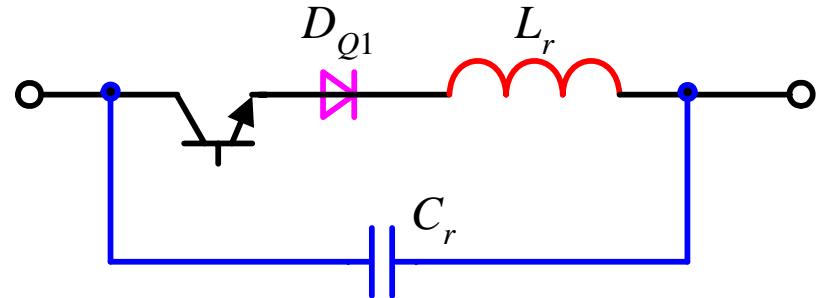


Half-wave mode


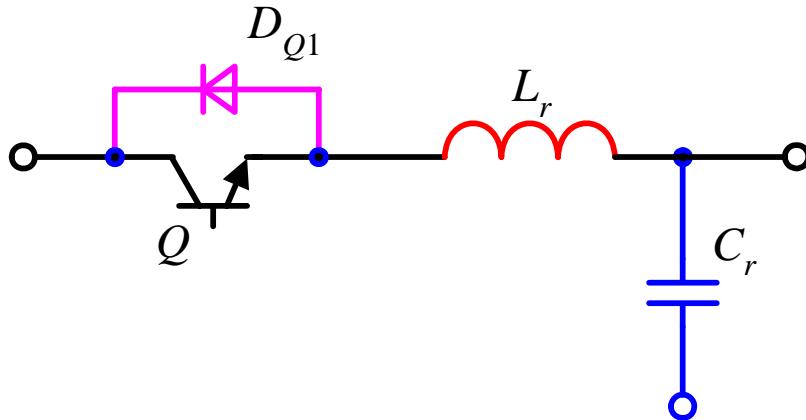




Full-wave mode

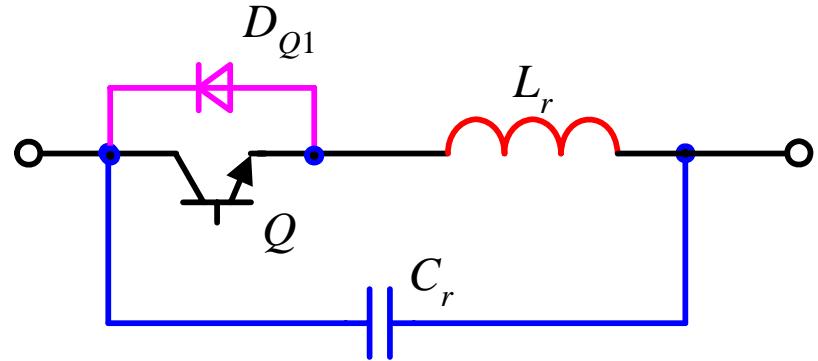



Full-wave mode


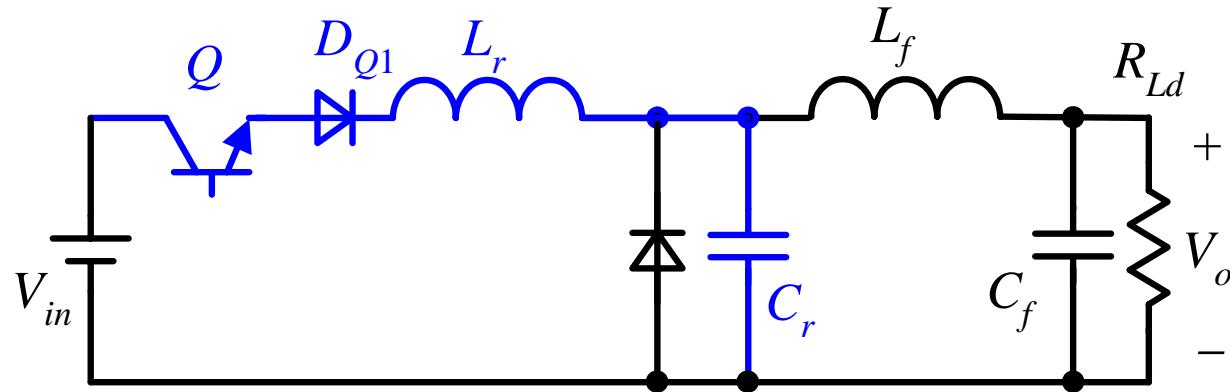


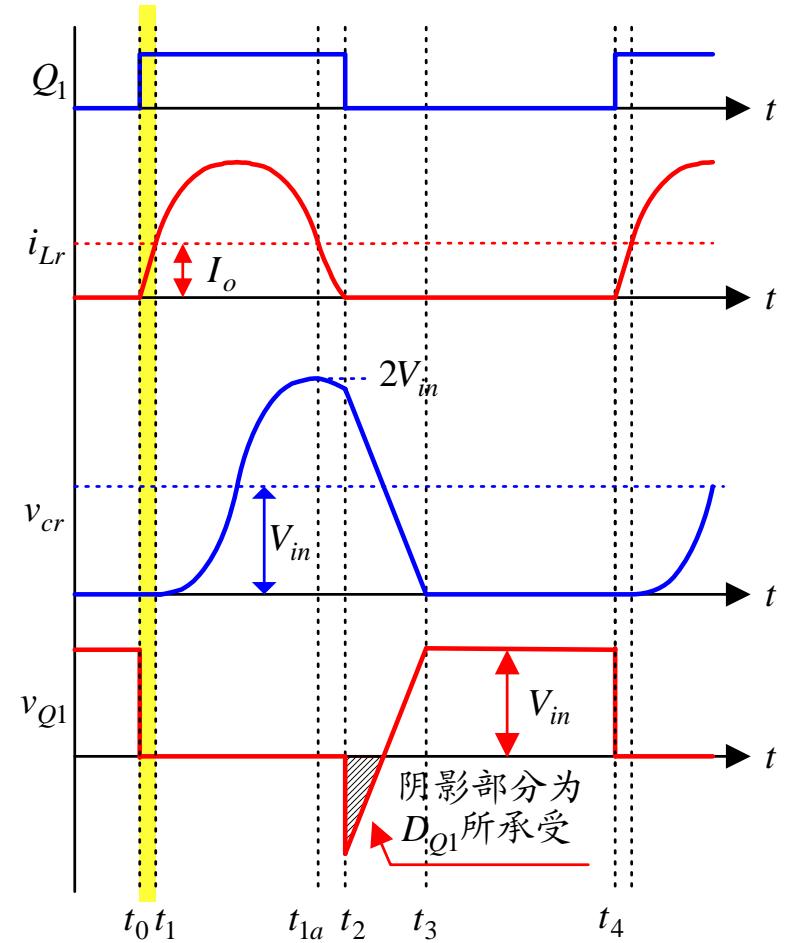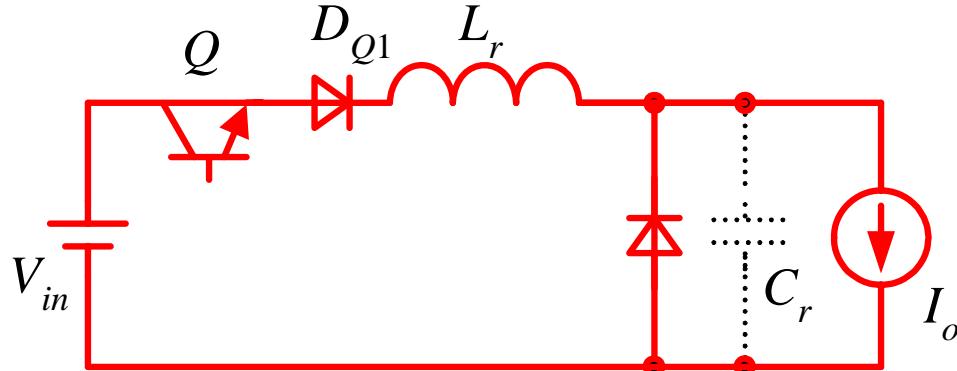


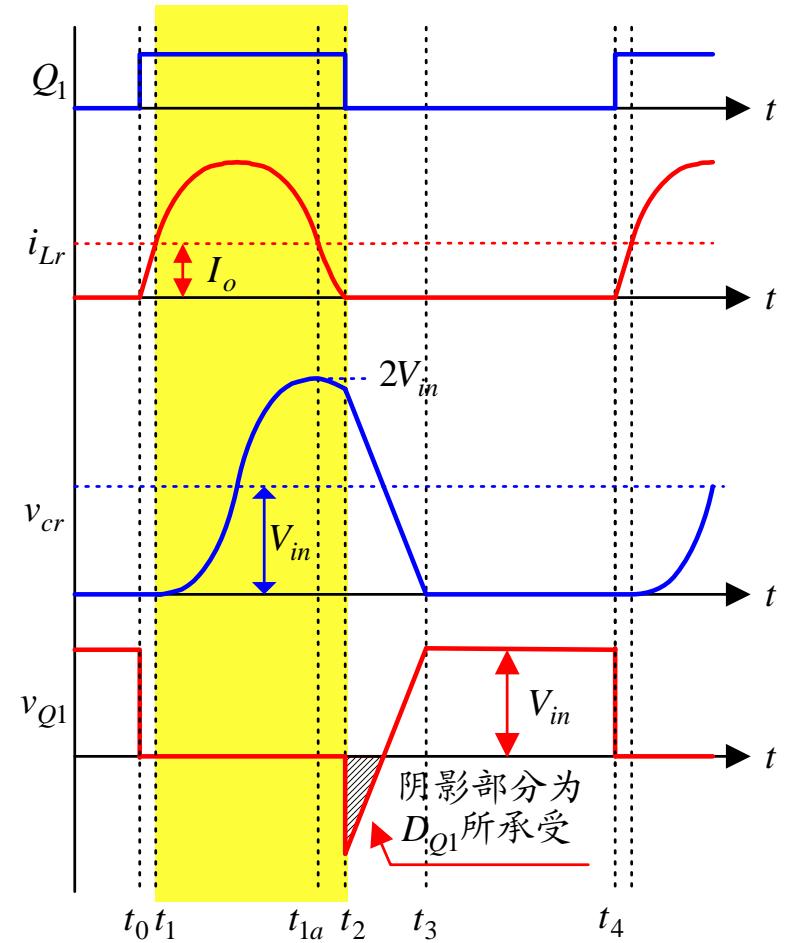
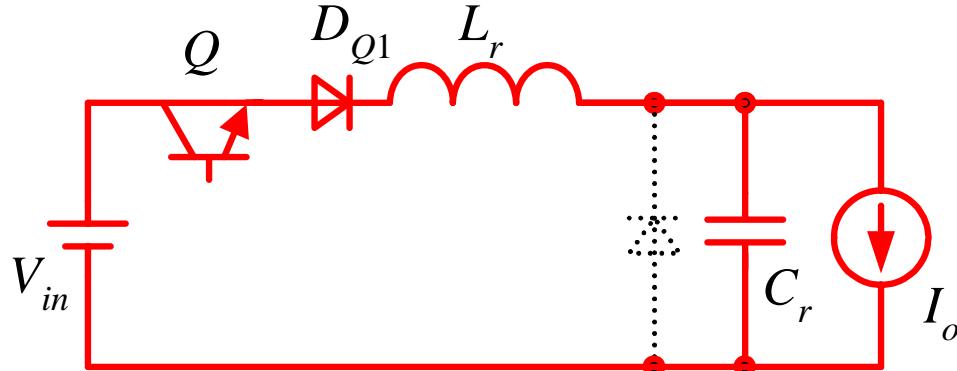




HW ZCS QRC: Discharge Stage

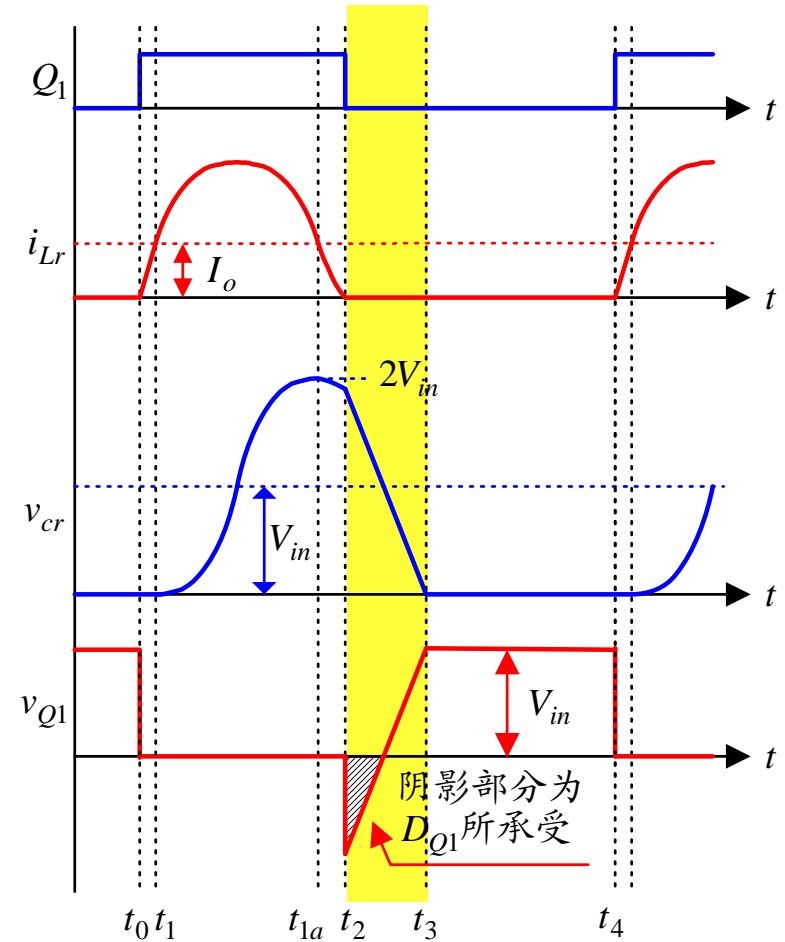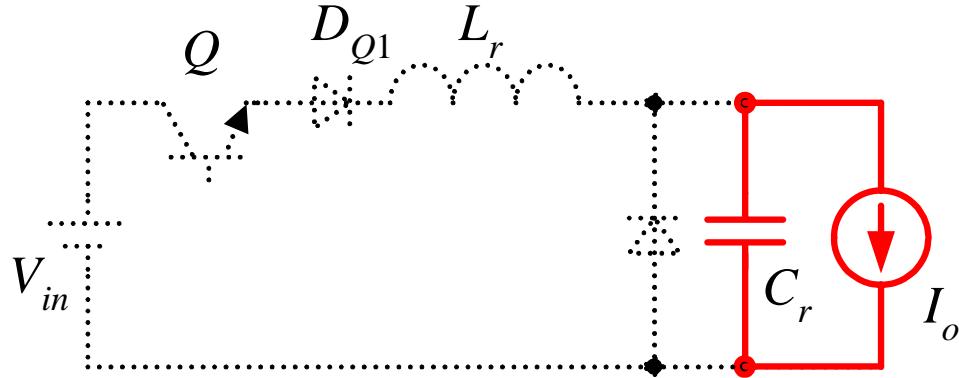

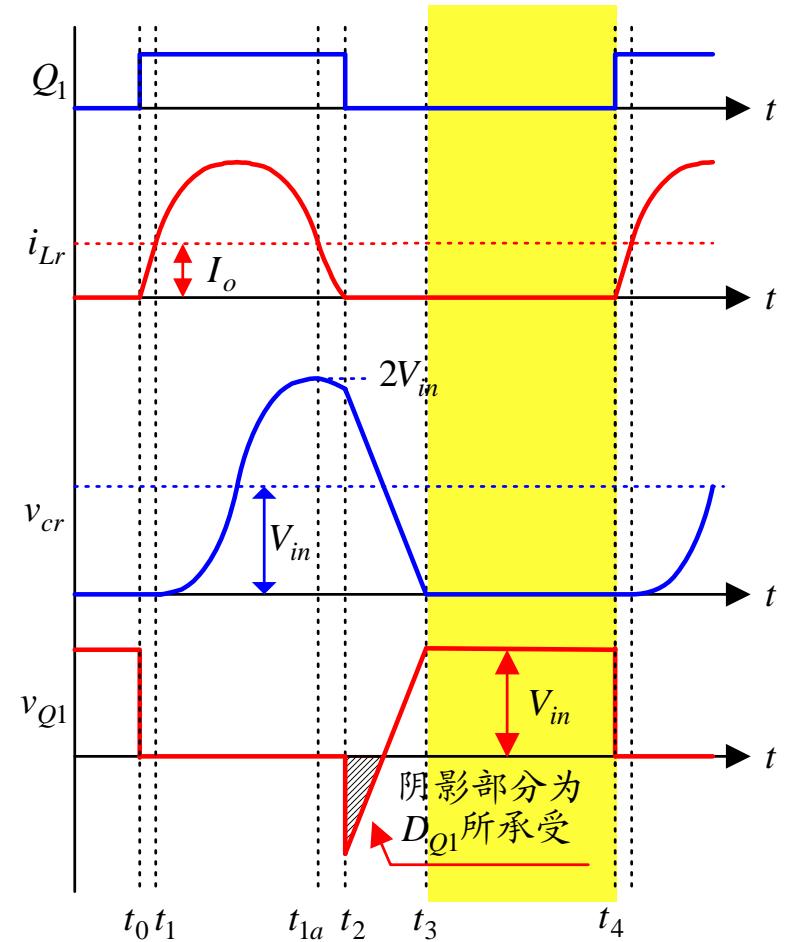
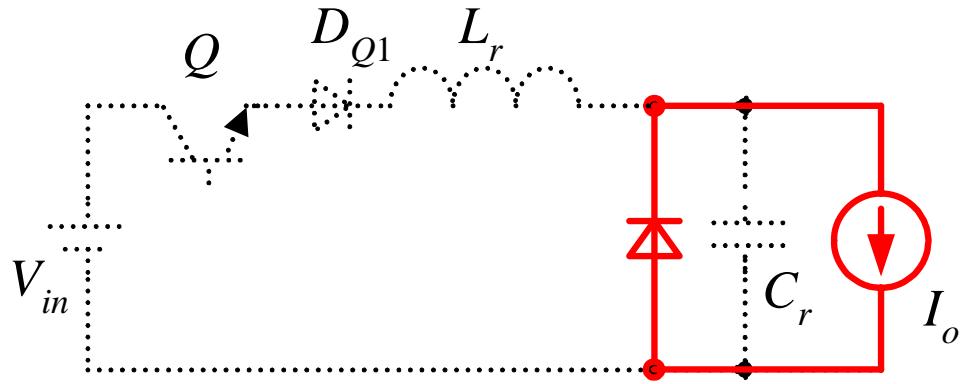


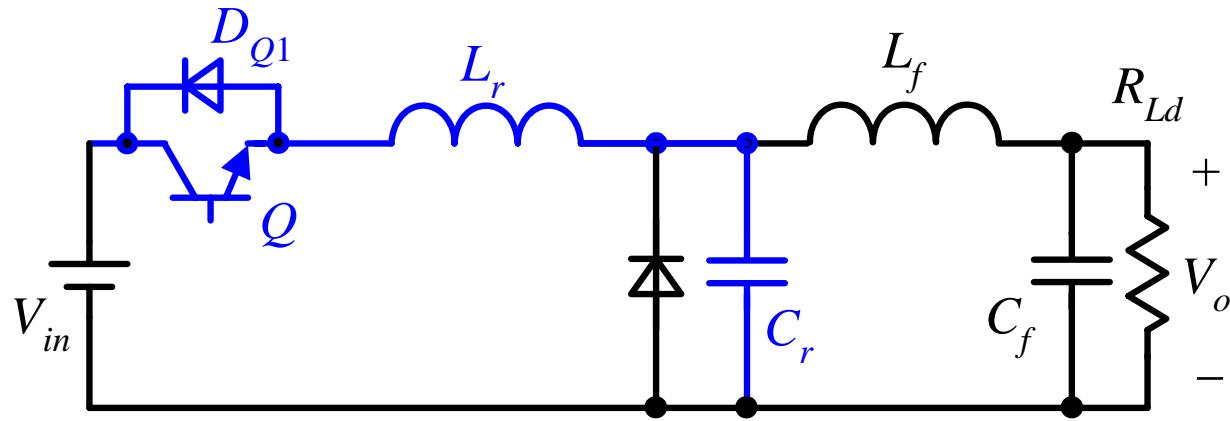

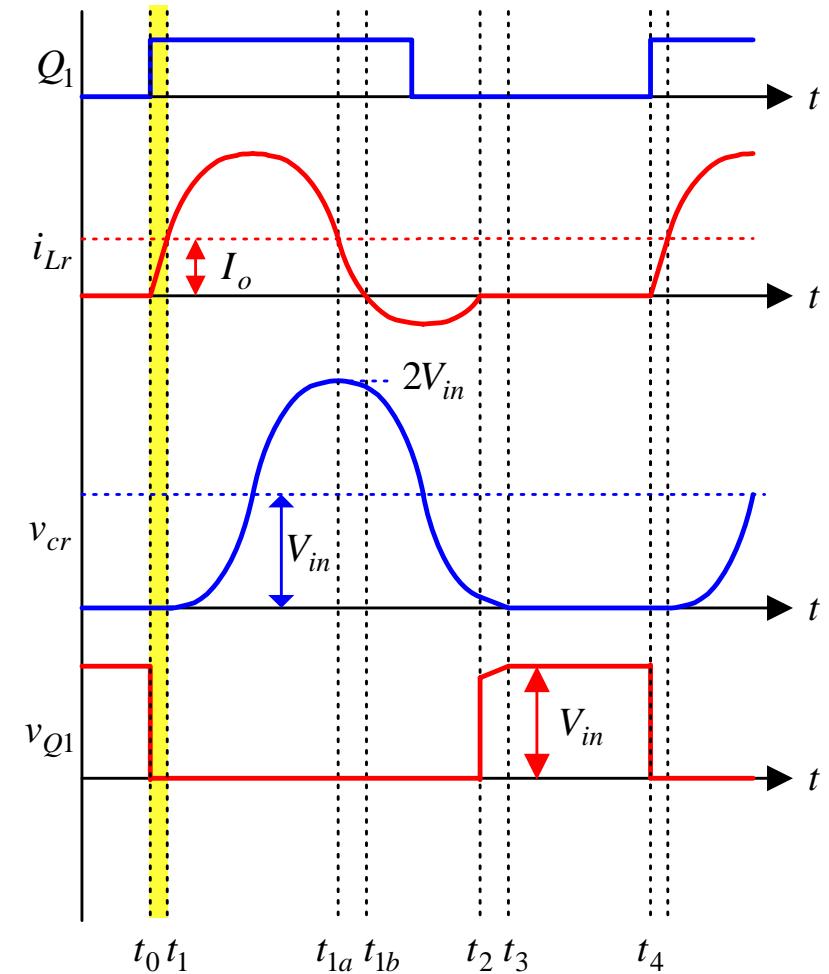
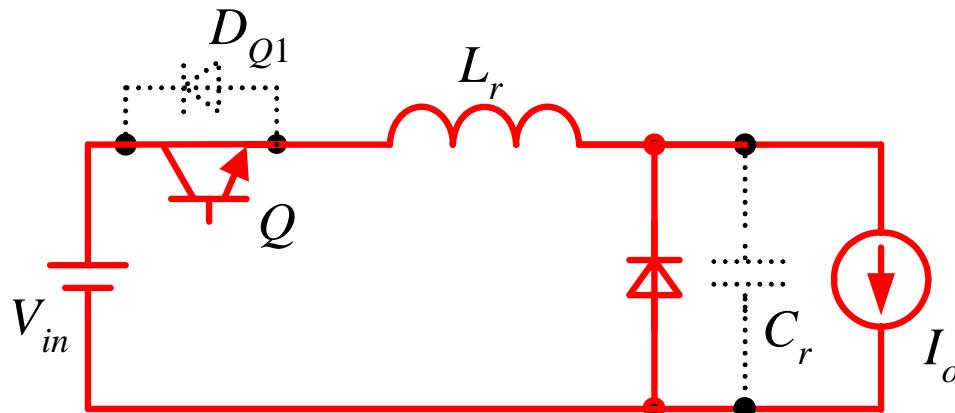


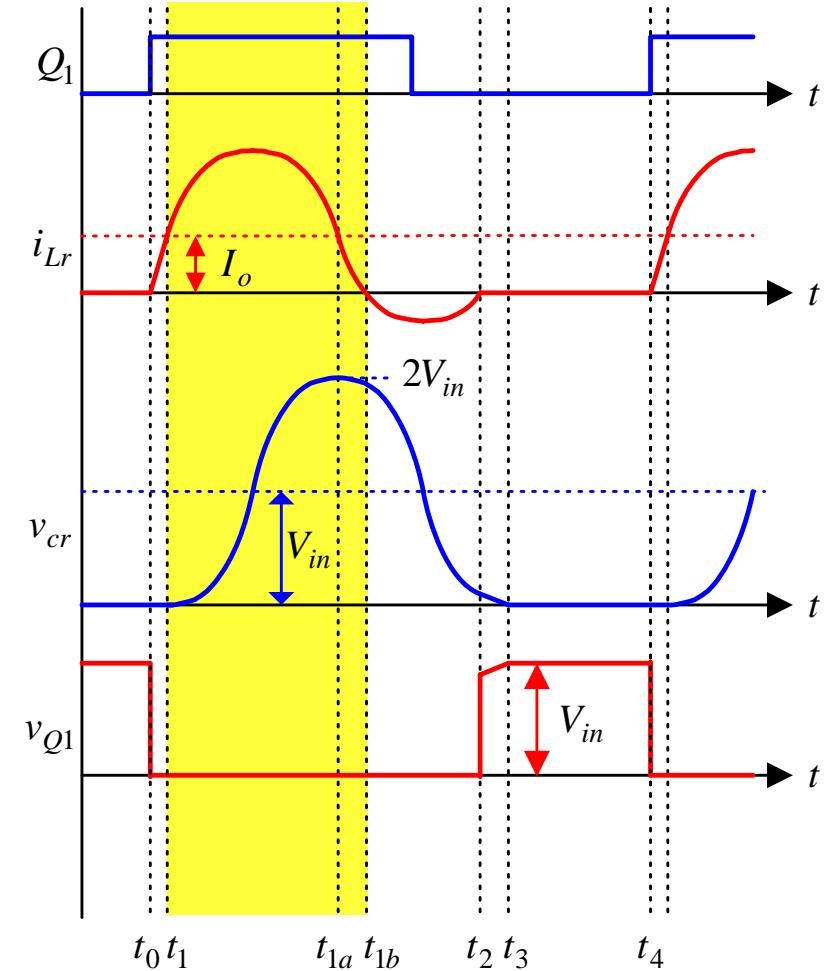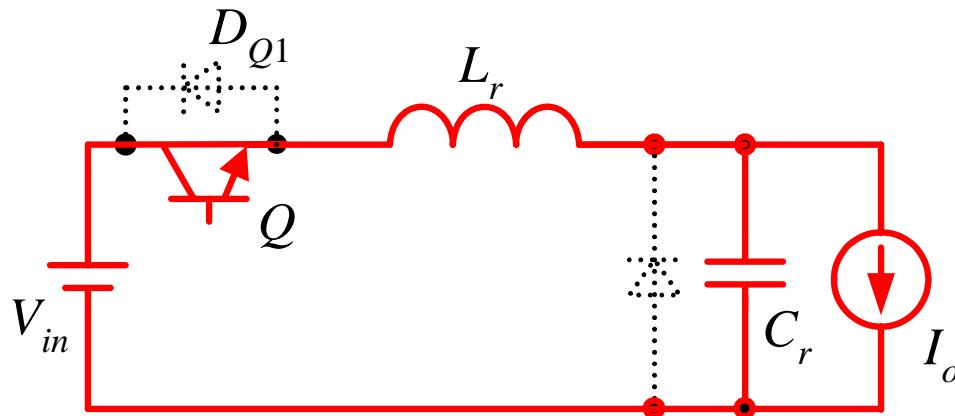



FW ZCS QRC: Resonant Stage (2)

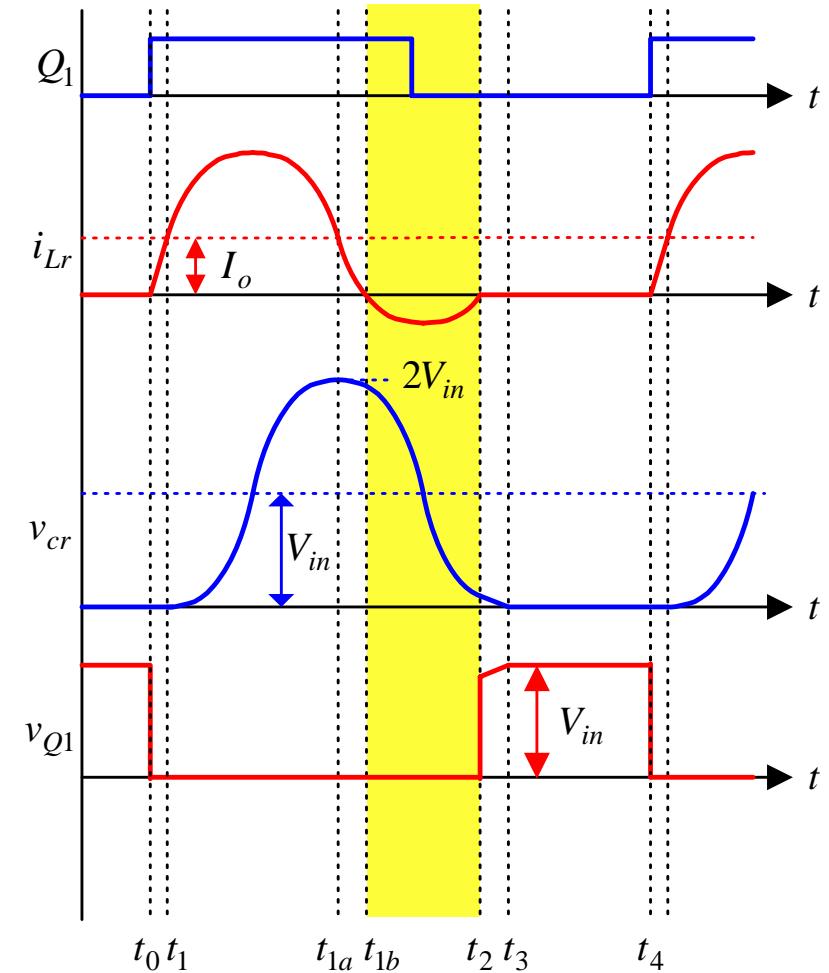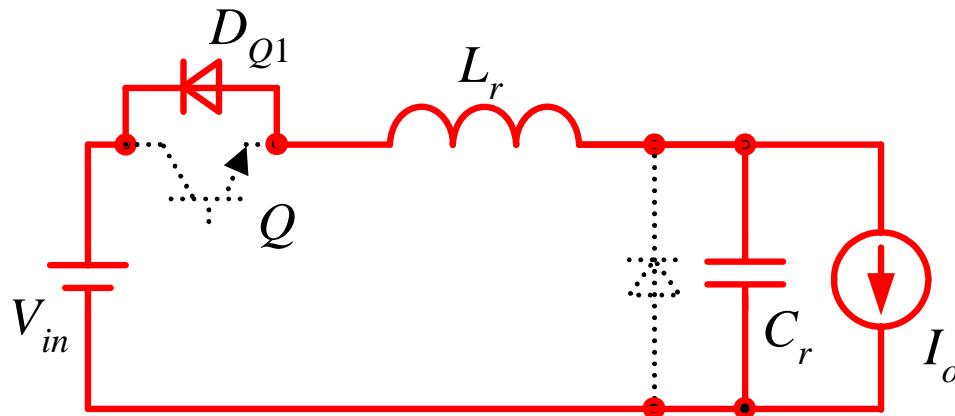


FW ZCS QRC: Discharge Stage

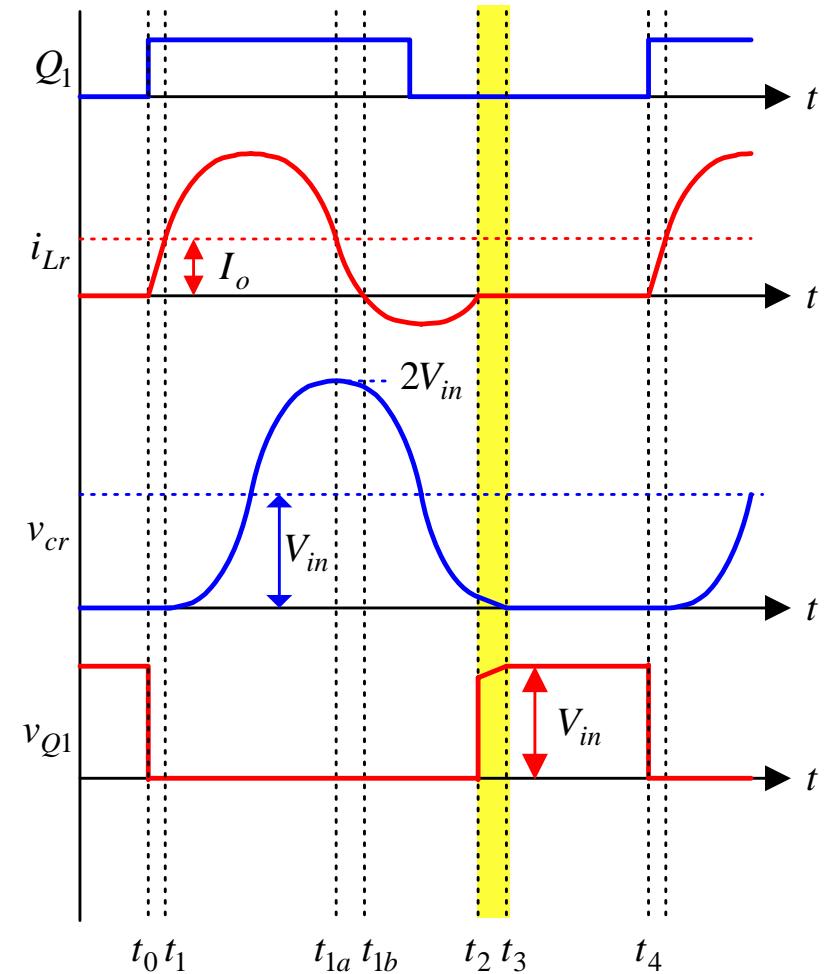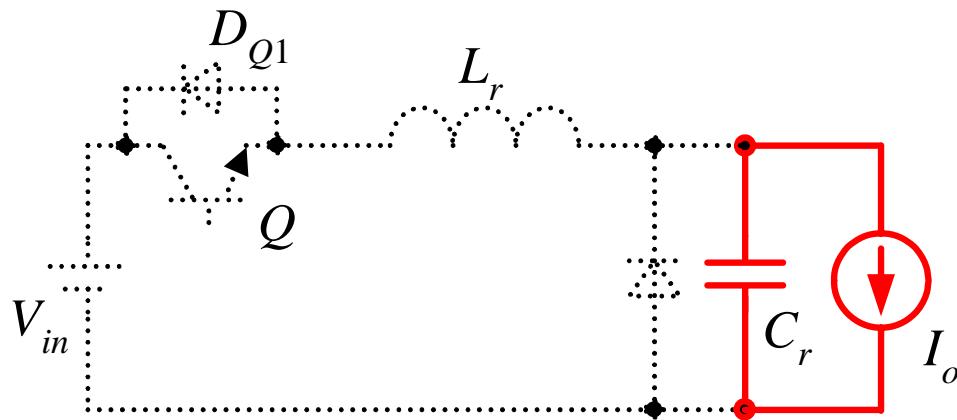

FW ZCS QRC: Freewheeling Stage

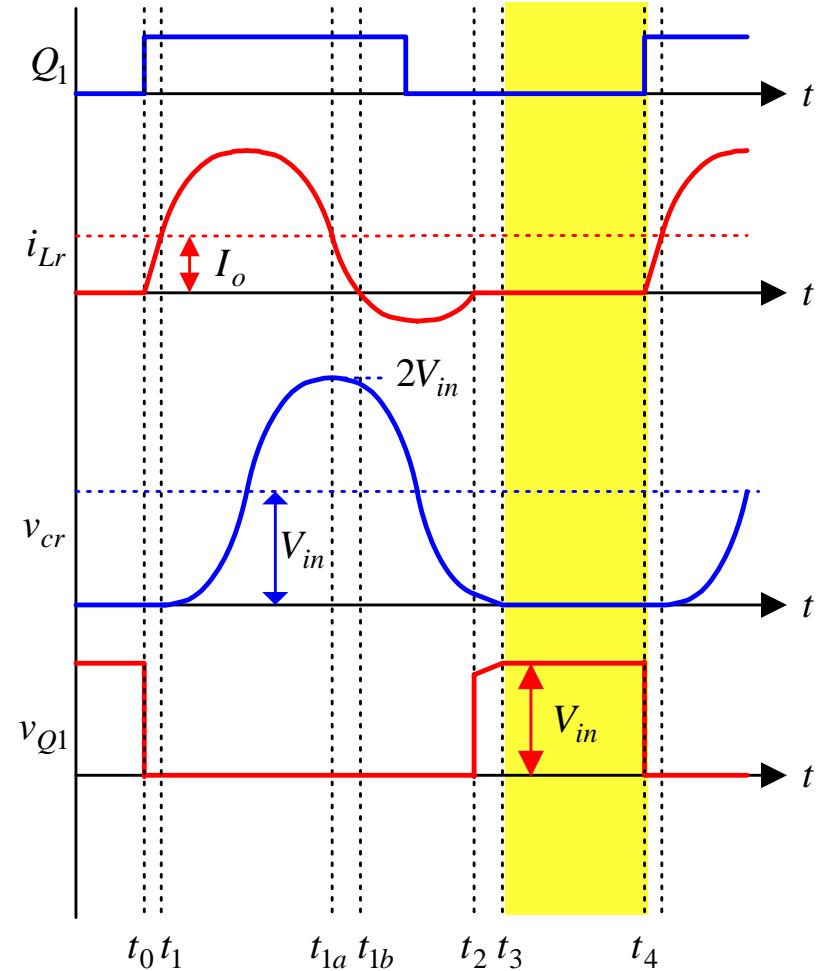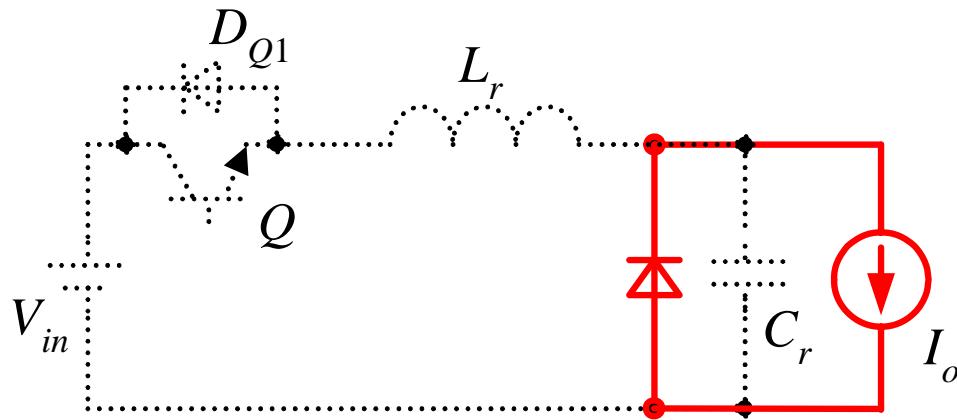


Comparison of ZCS QRC: HW vs FW

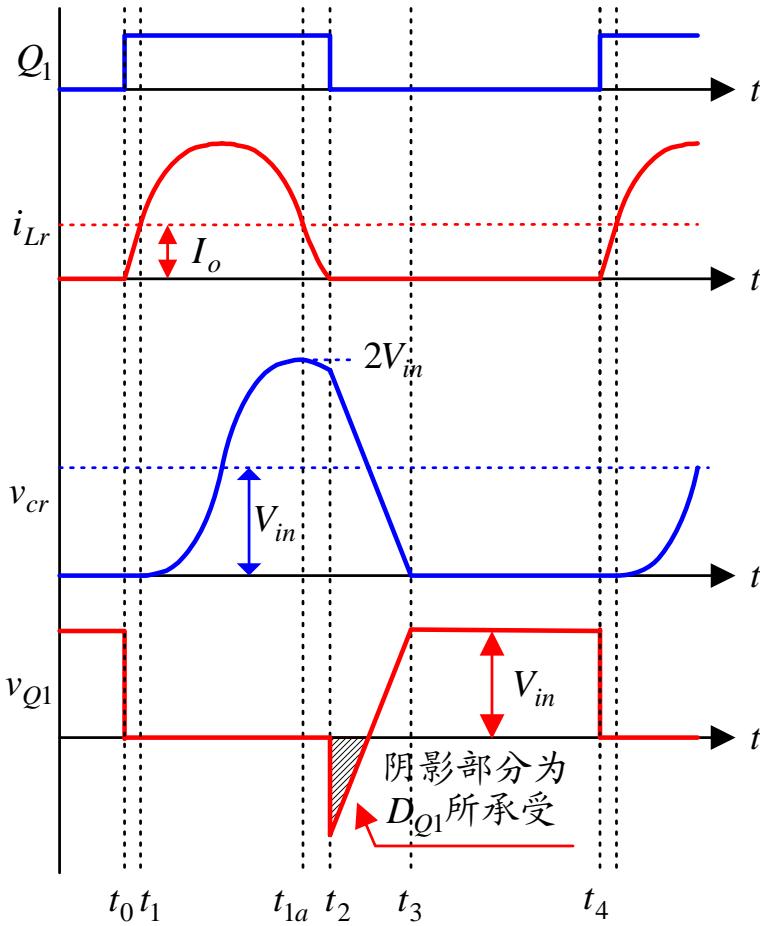

Half-wave mode


2011-10-31

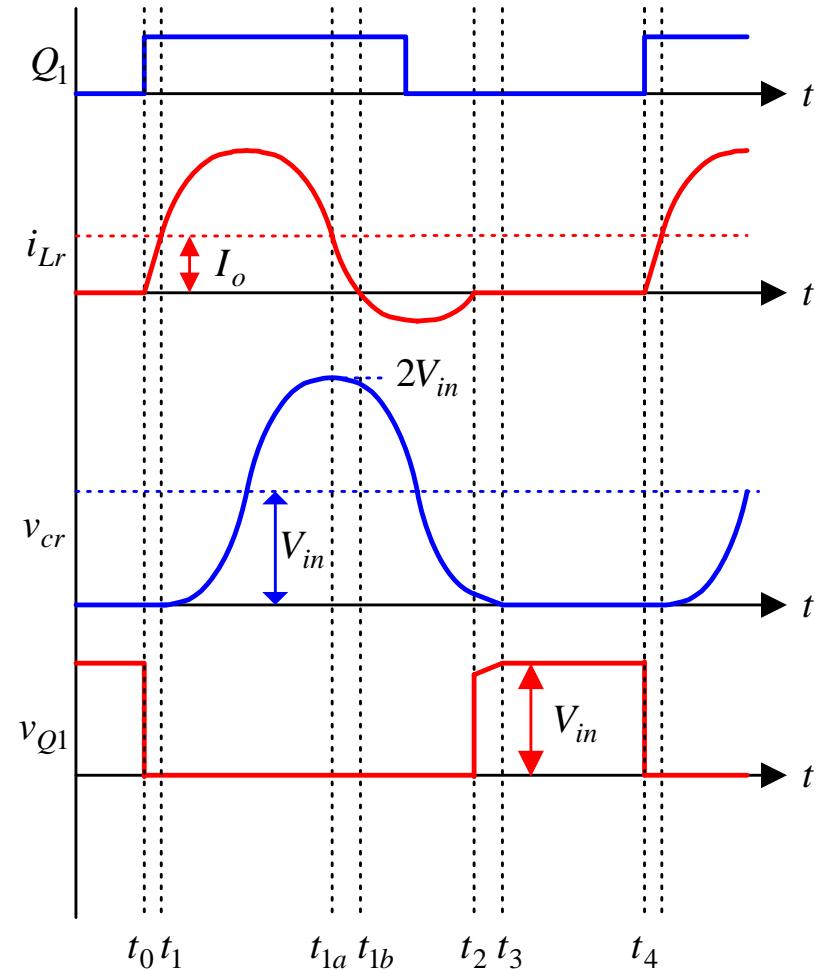


Full-wave mode

14



Output Characteristics of ZCS QRC

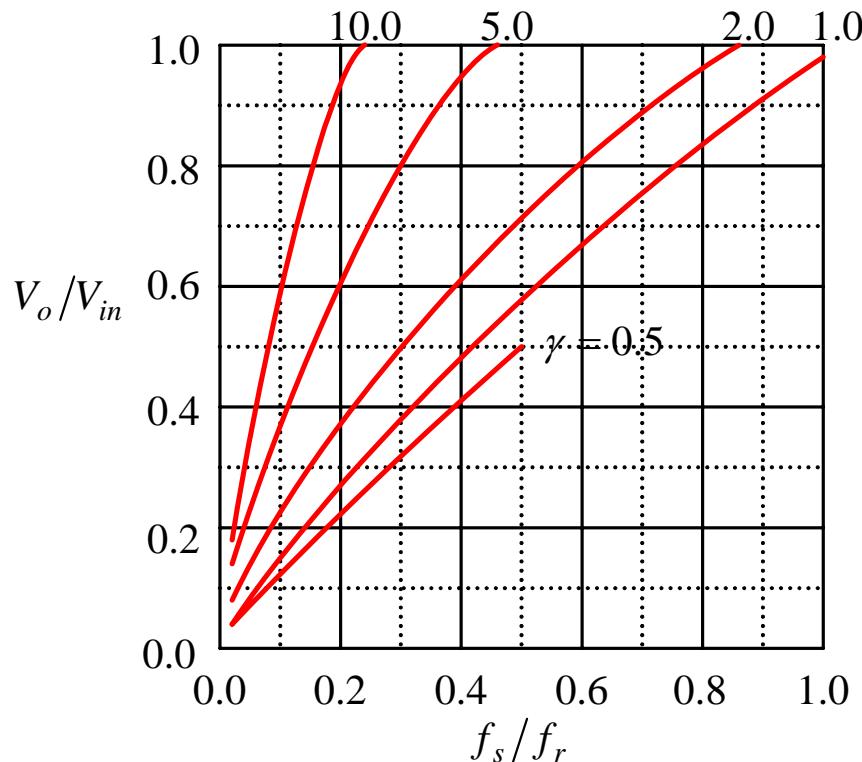



Half-wave mode

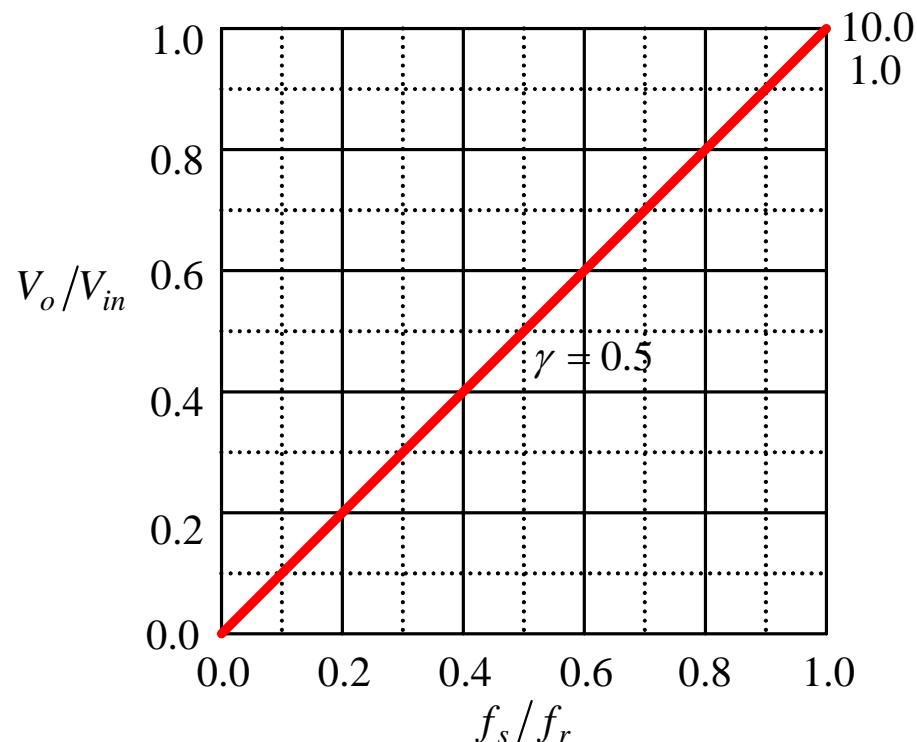


Full-wave mode

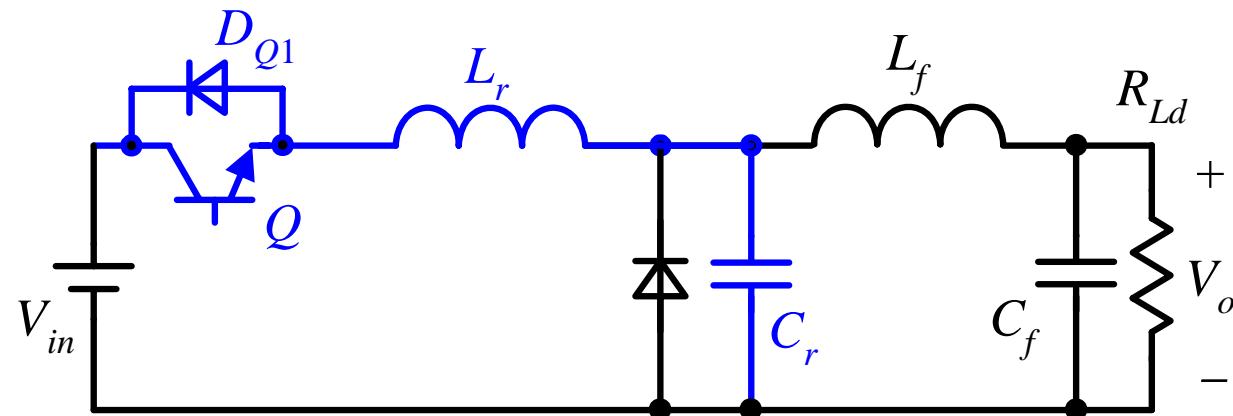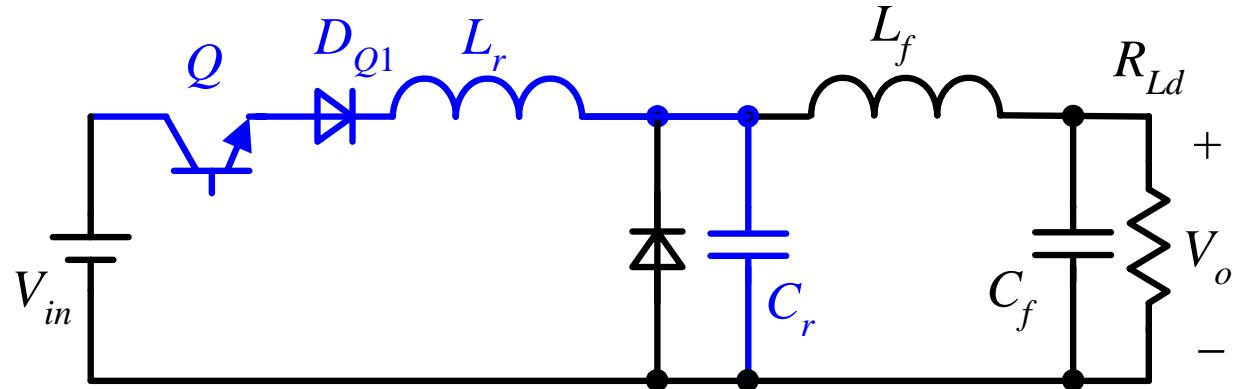


A Family of ZCS QRCs (1)

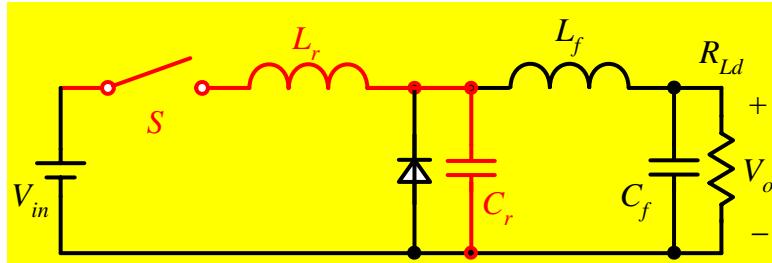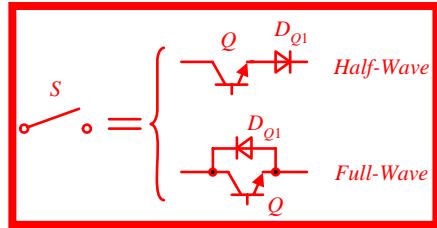


Buck

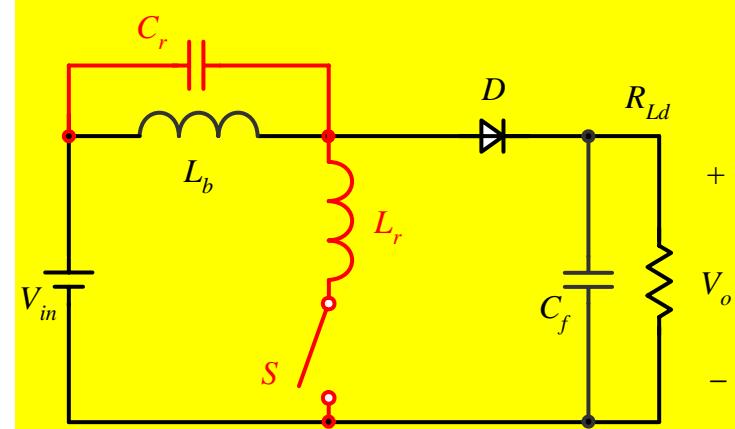

Boost

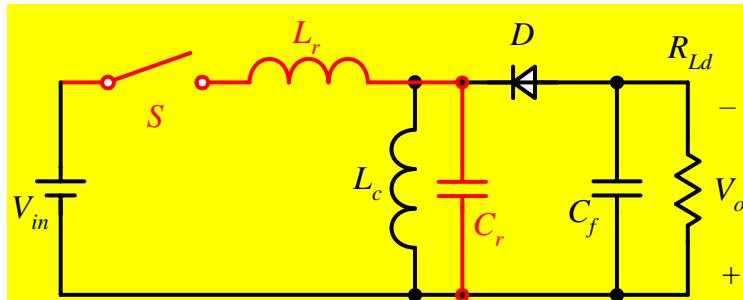


2011-10-3 Buck-Boost

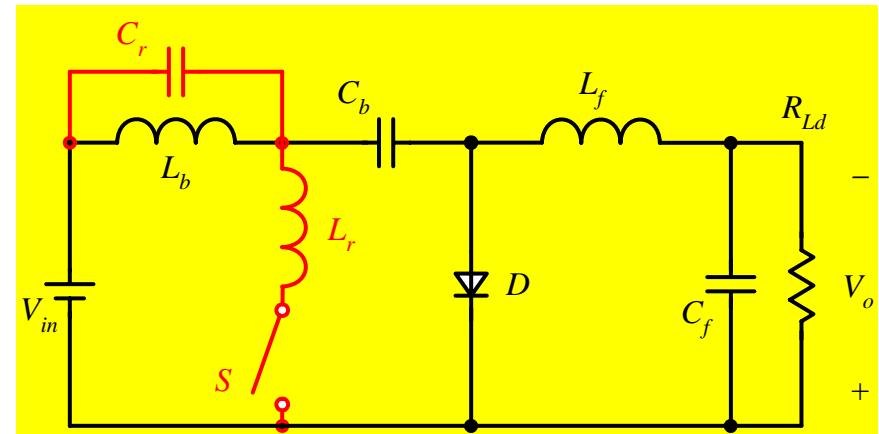


Cuk


A Family of ZCS QRCs (2)

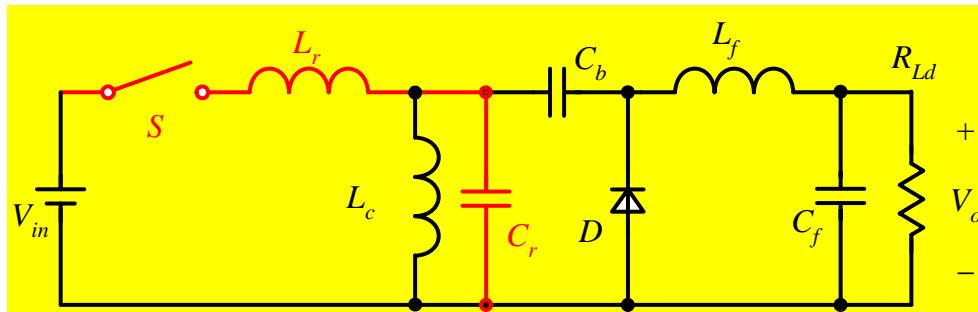

Zeta

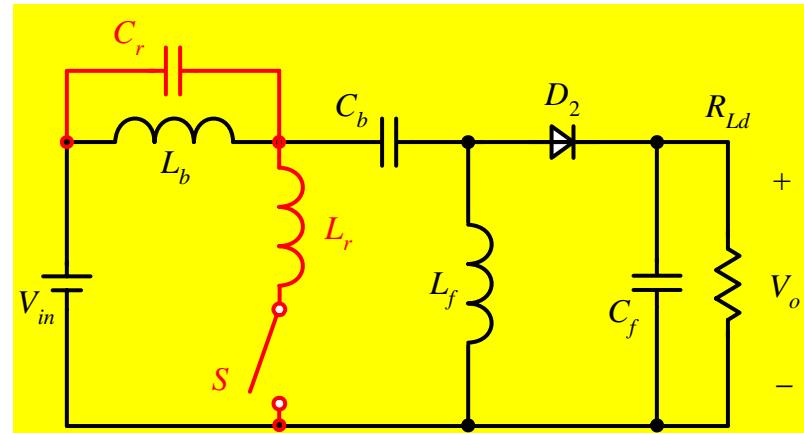


Sepic

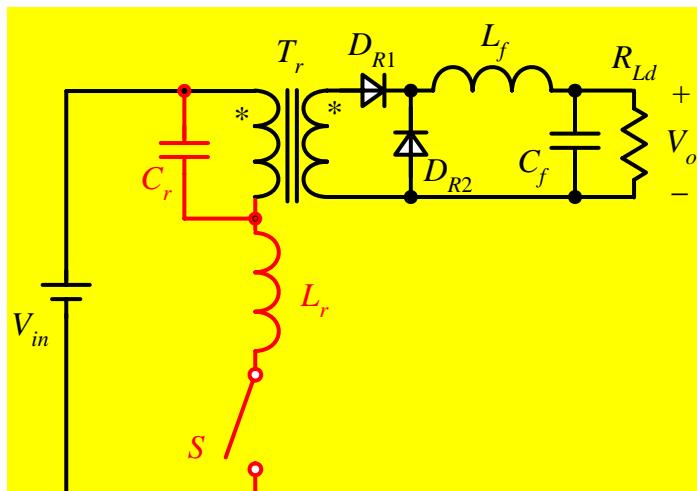


Forward

2011-10-31

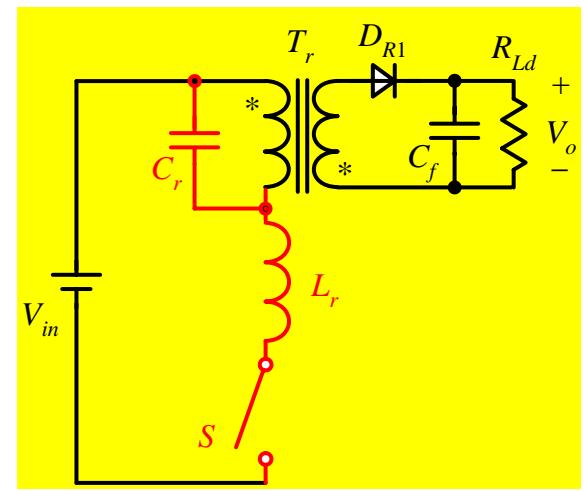


Flyback


18

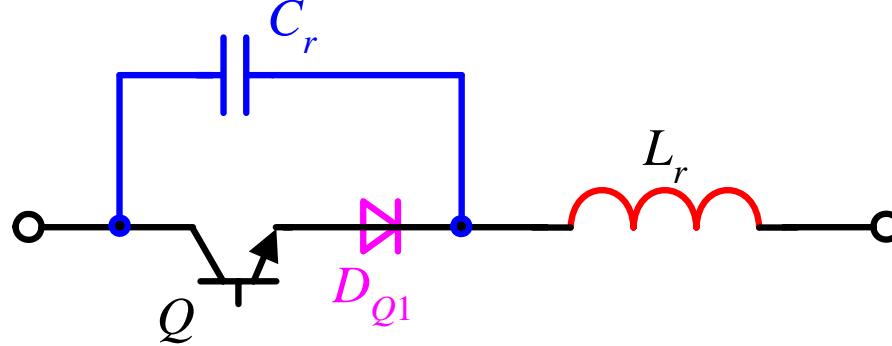


Full-wave mode

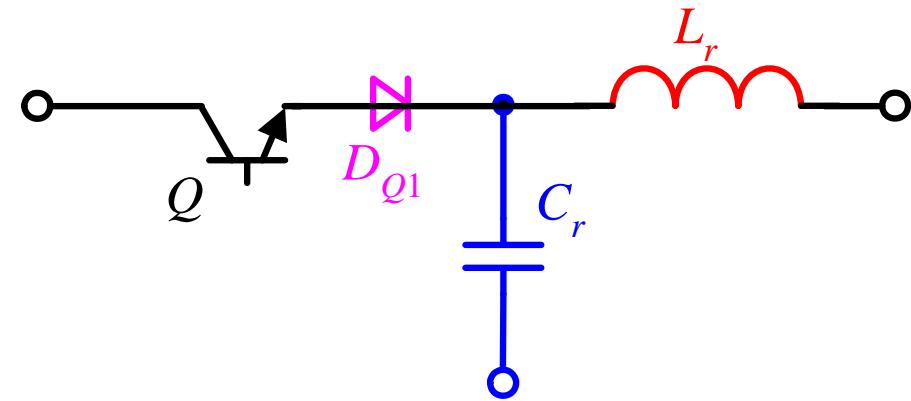


Full-wave mode

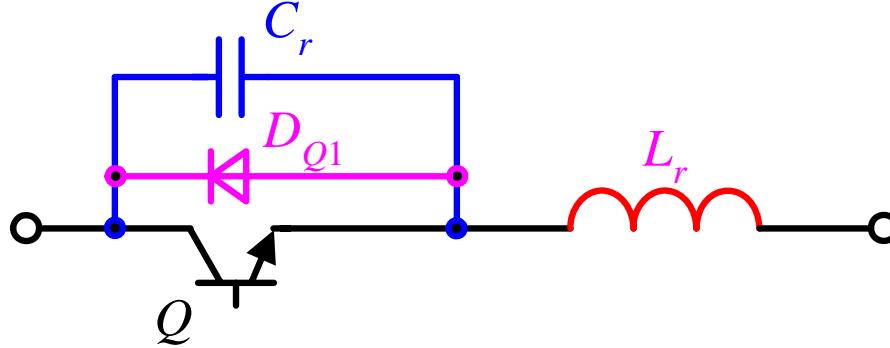



Half-wave mode

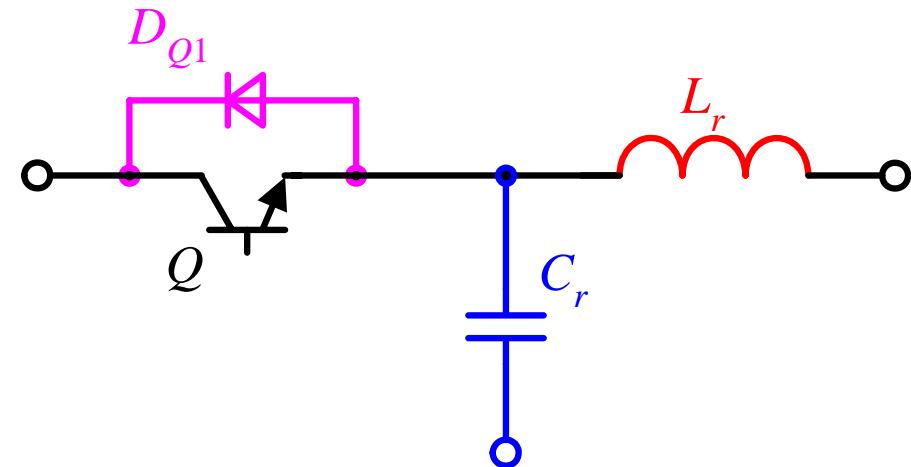



Half-wave mode


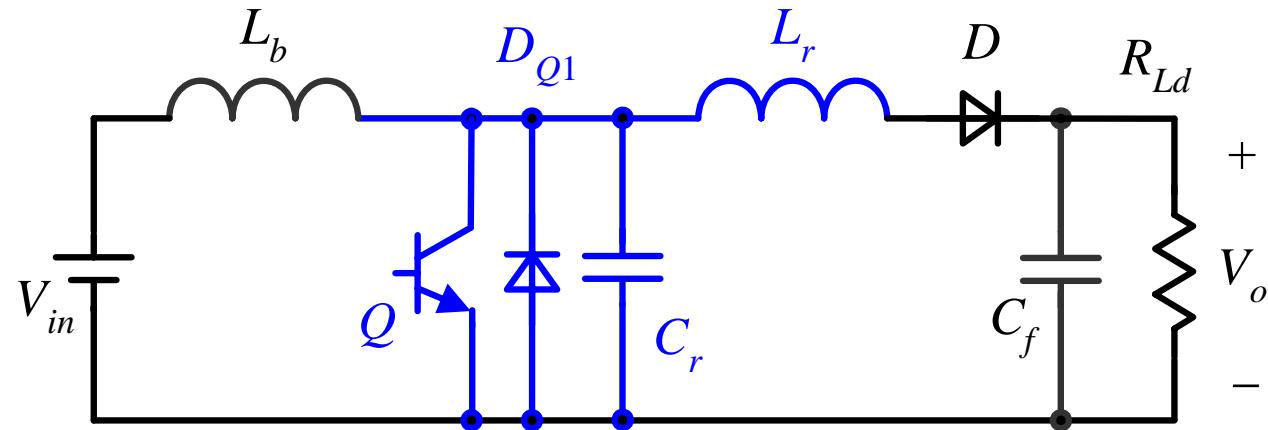




HW ZVS QRC: Linear Charge Stage

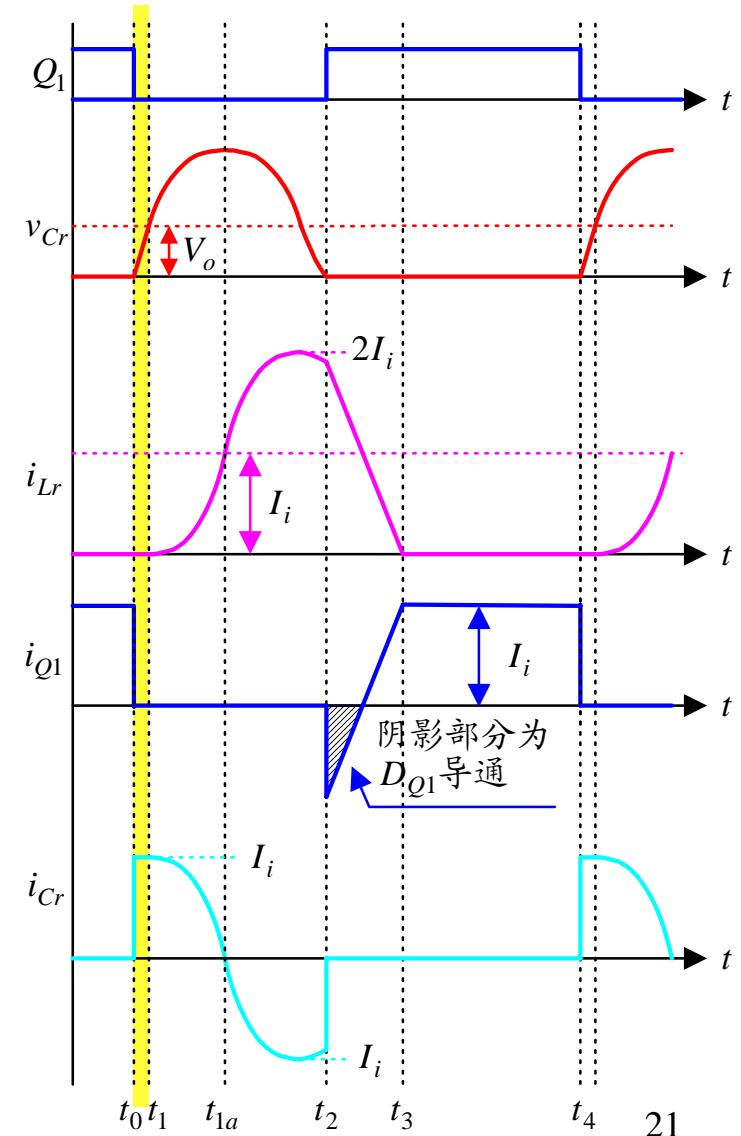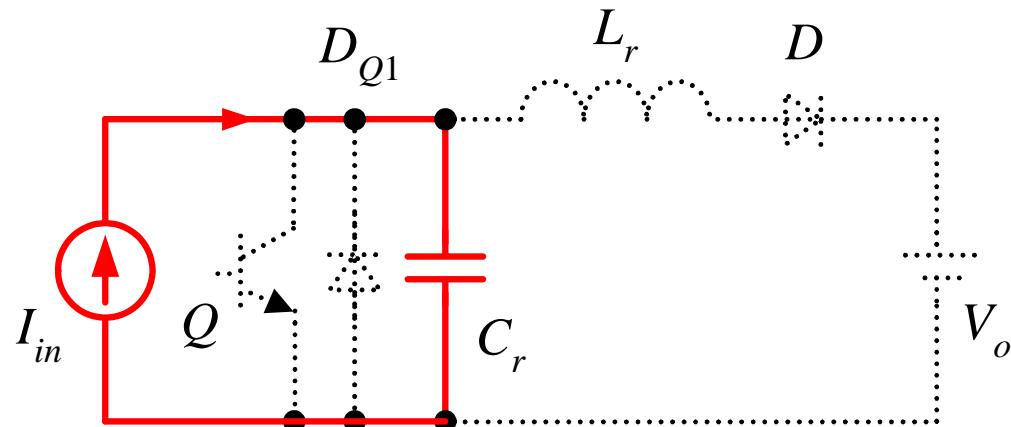




HW ZVS QRC: Resonant Stage

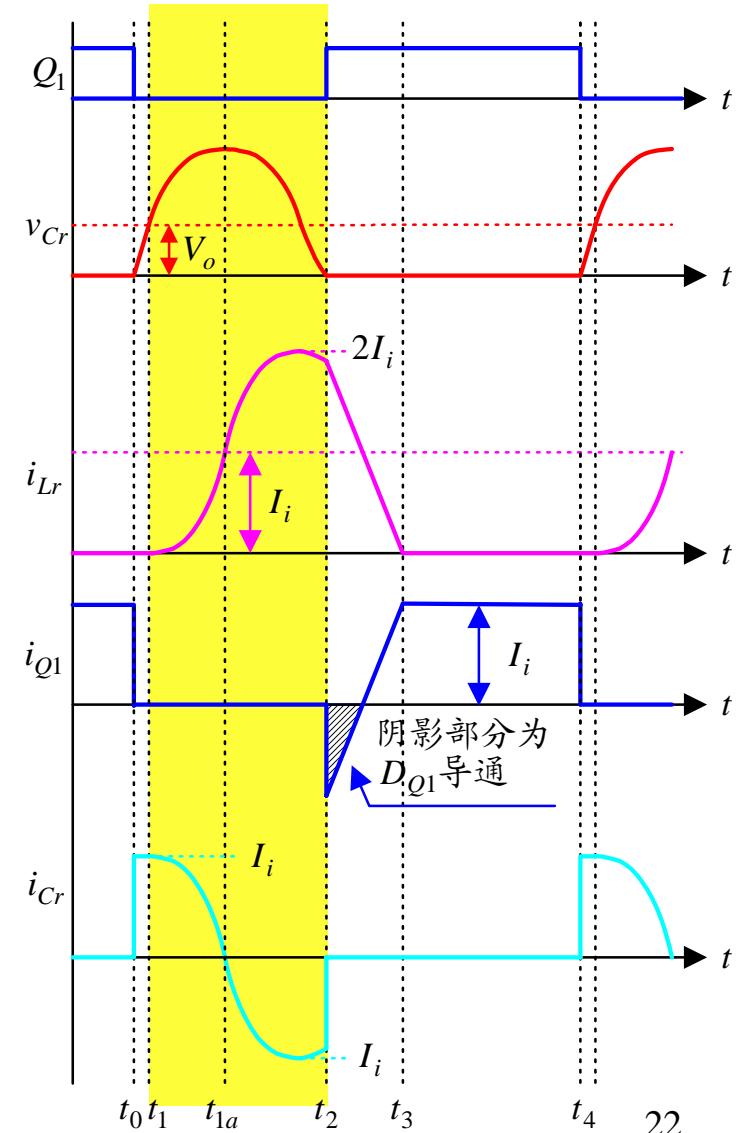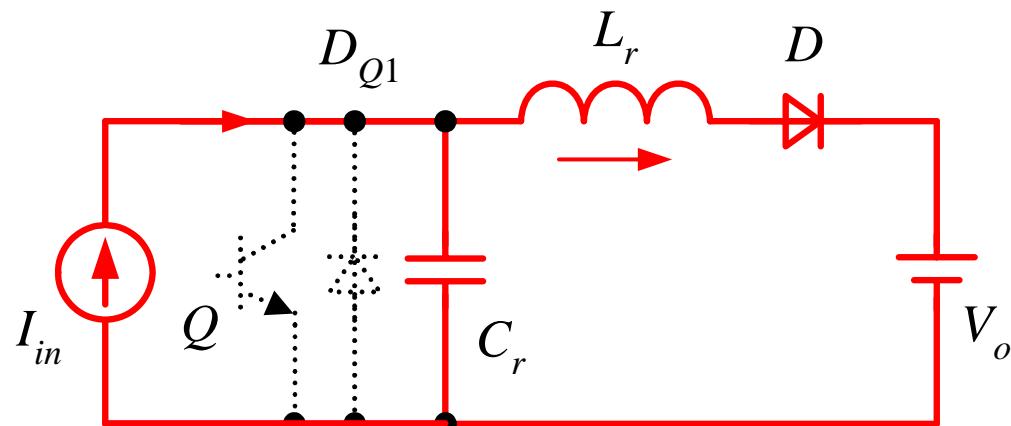

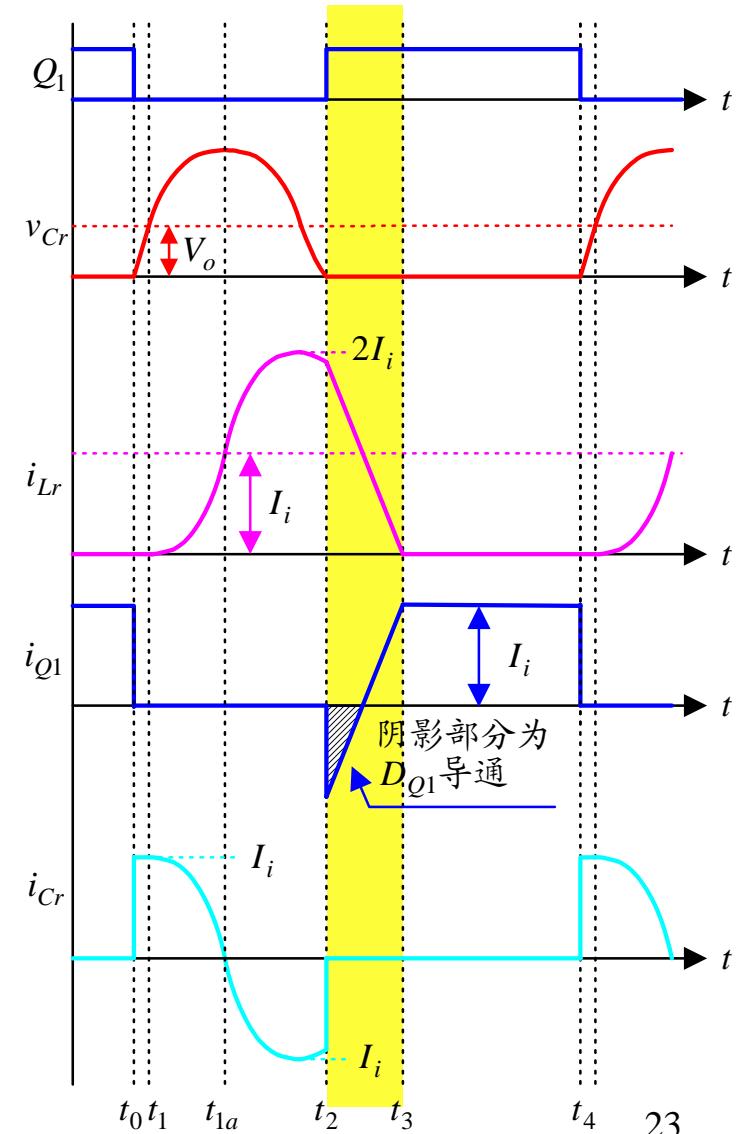
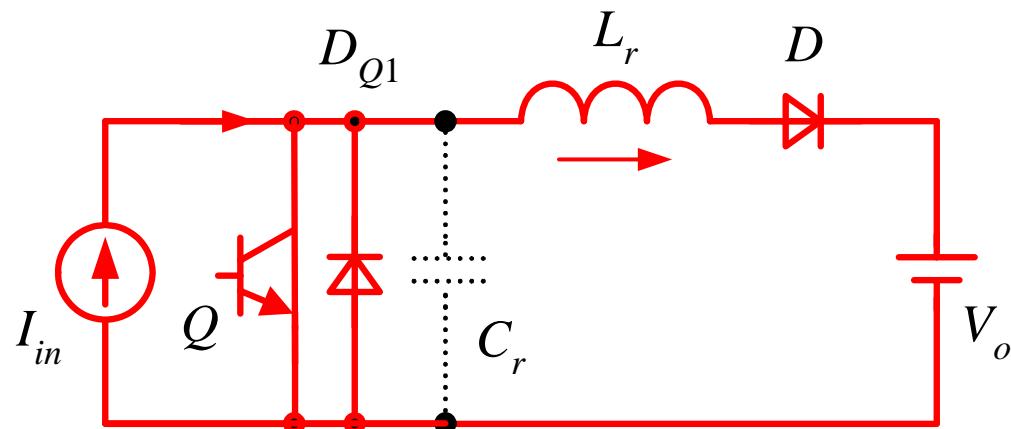


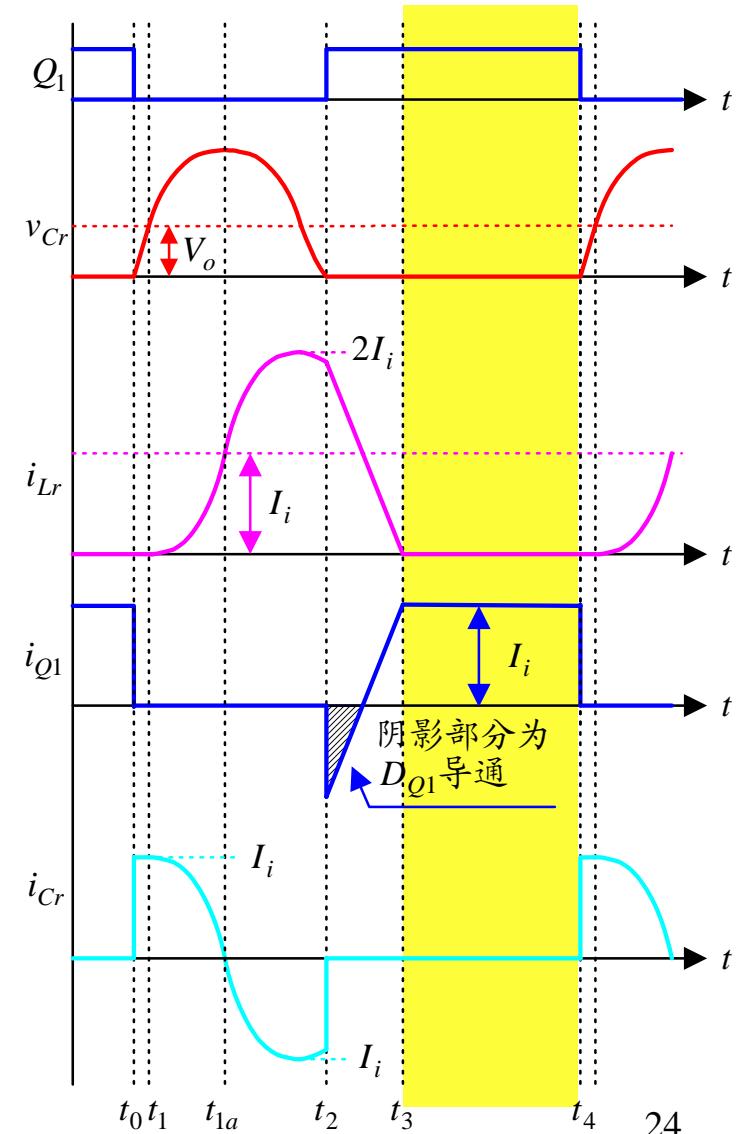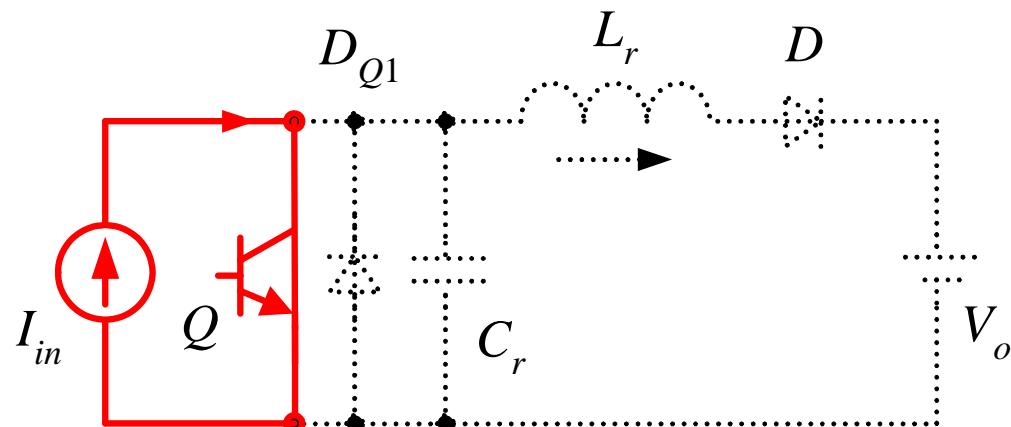


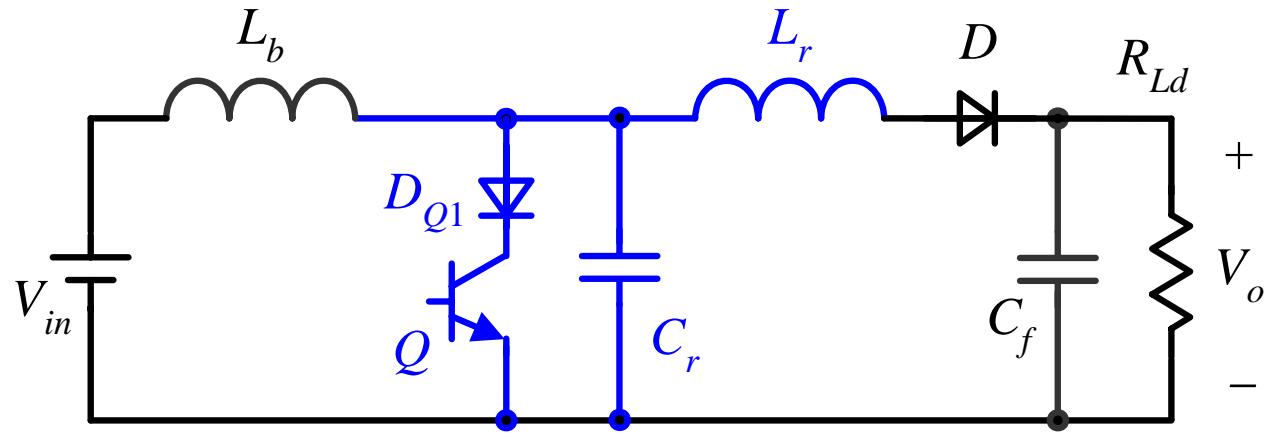


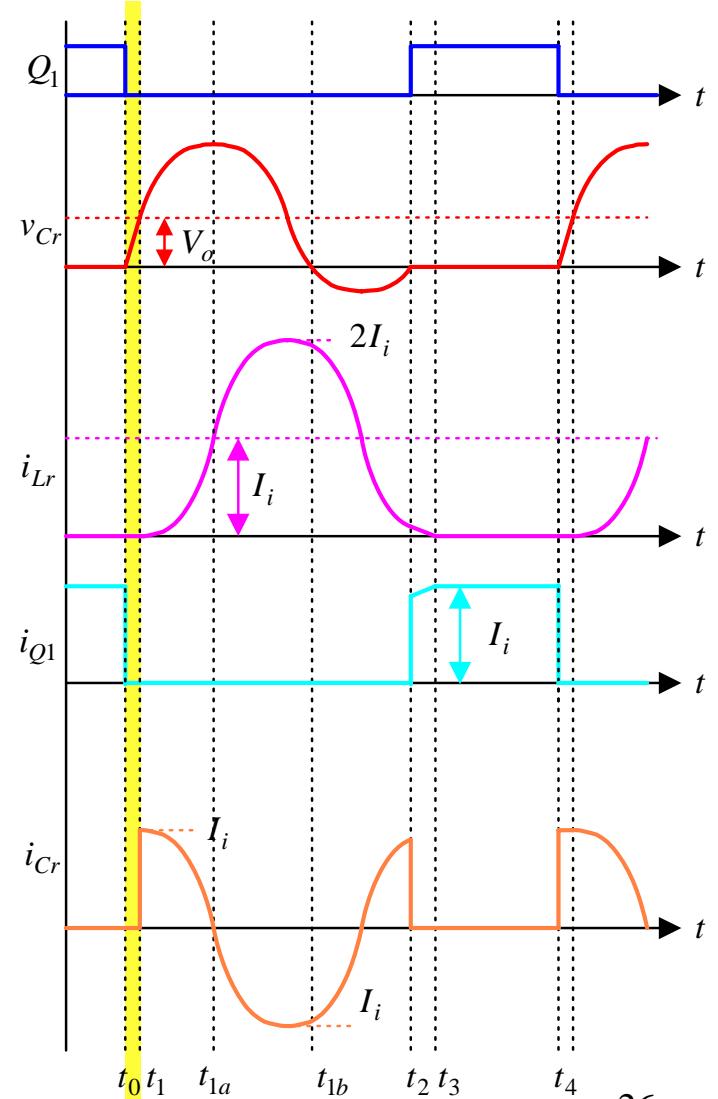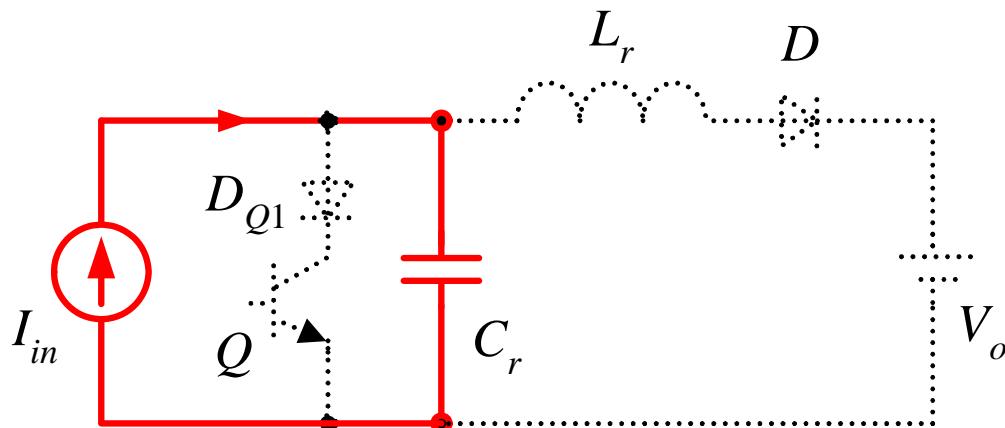



FW ZVS QRC: Resonant Stage

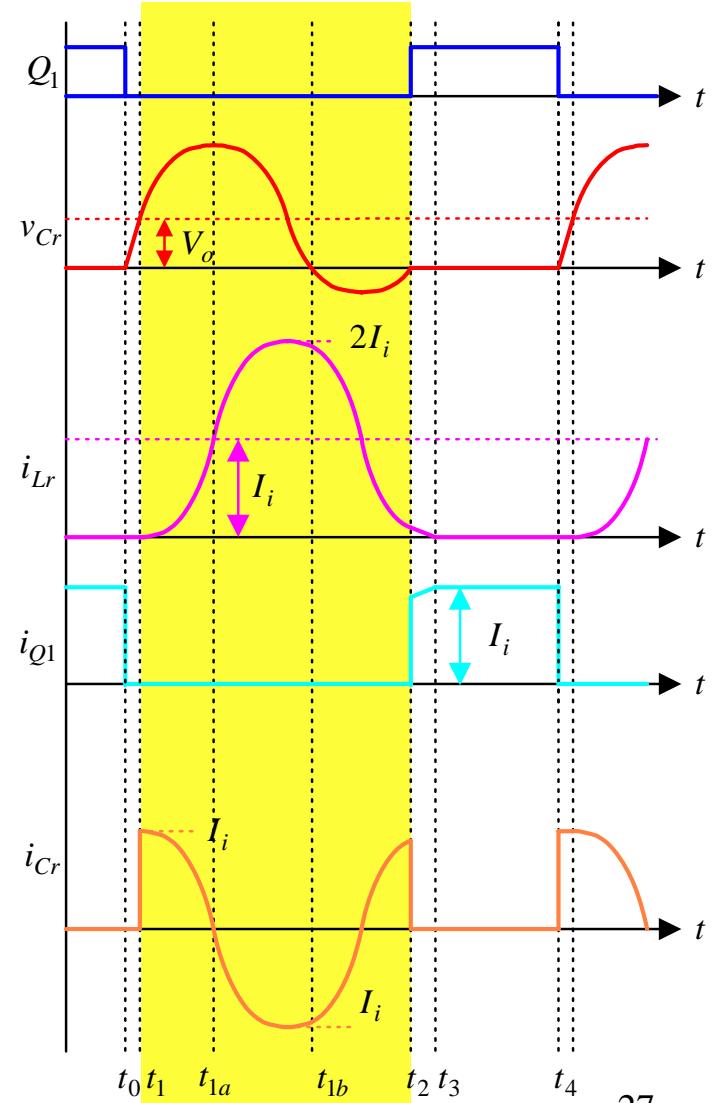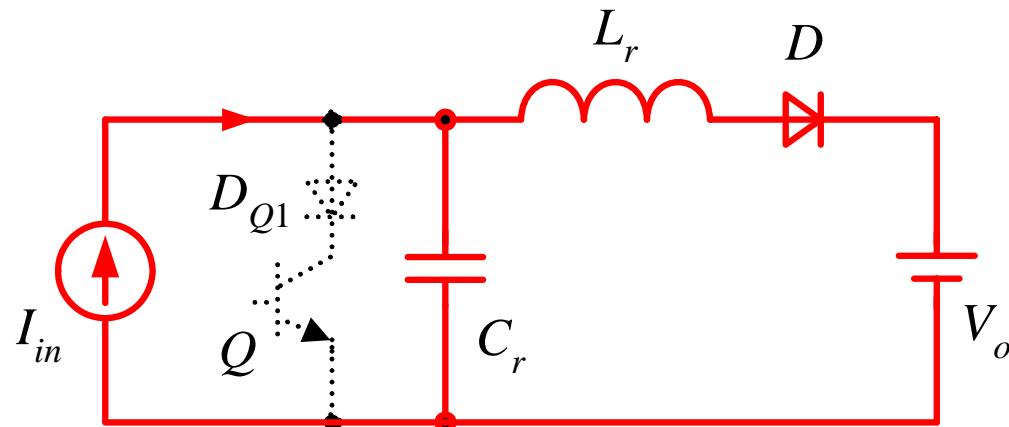


FW ZVS QRC: Discharge Stage

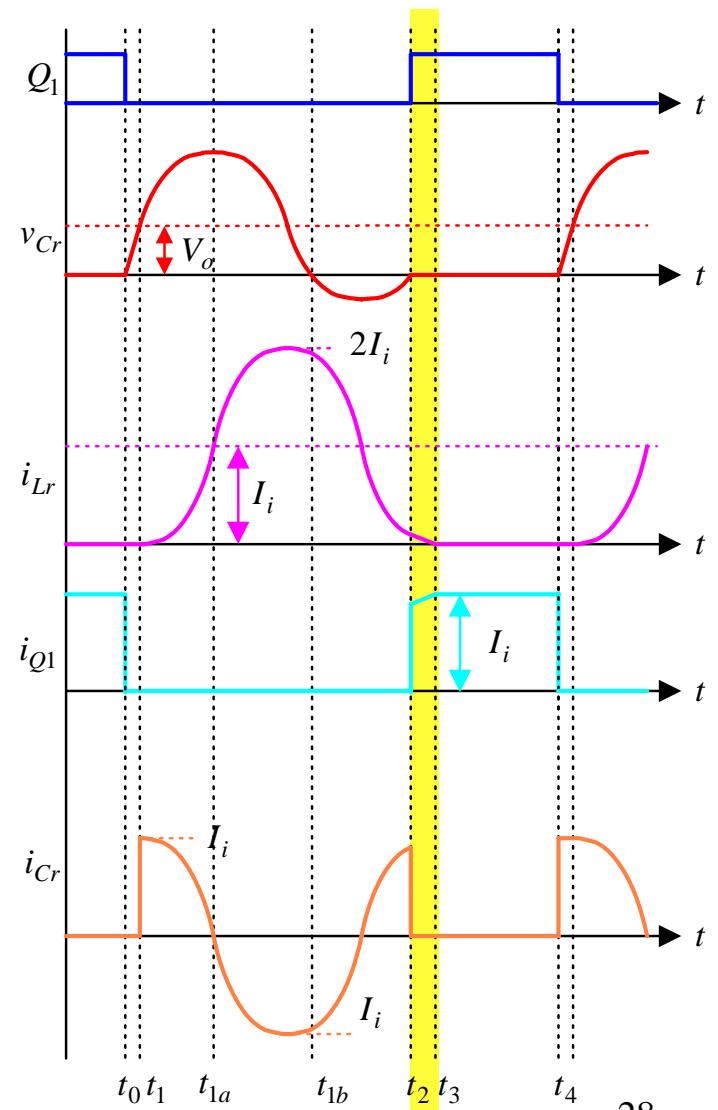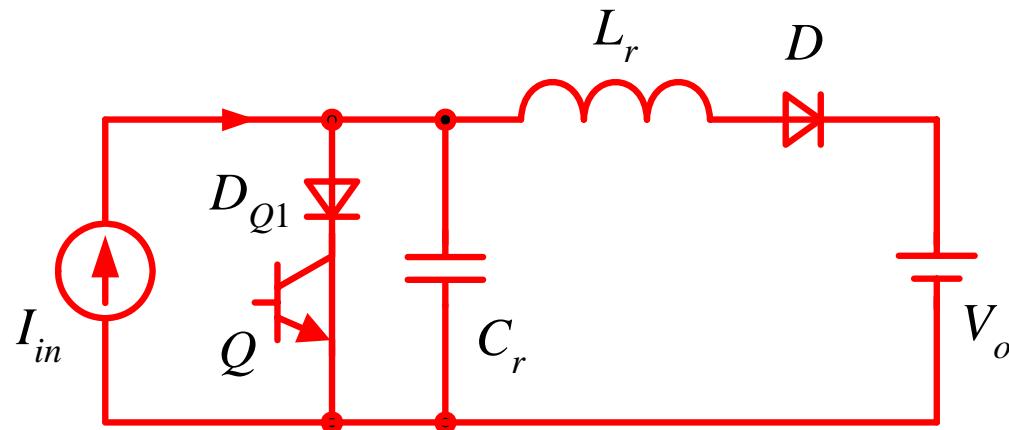


FW ZVS QRC: Freewheel Stage

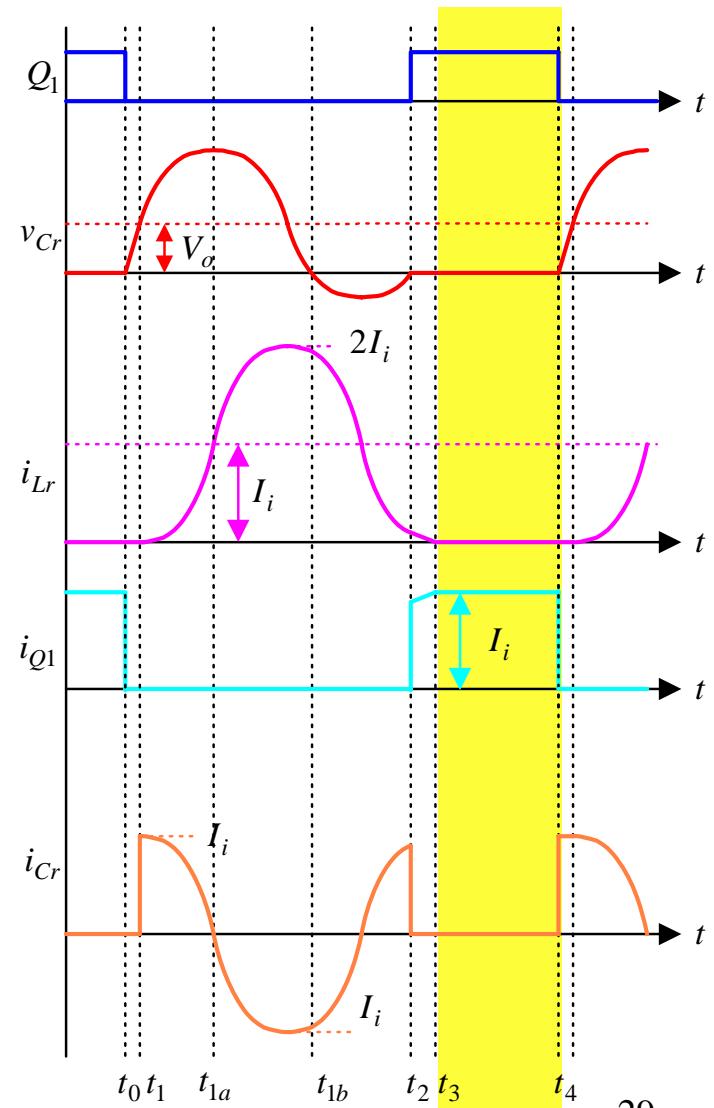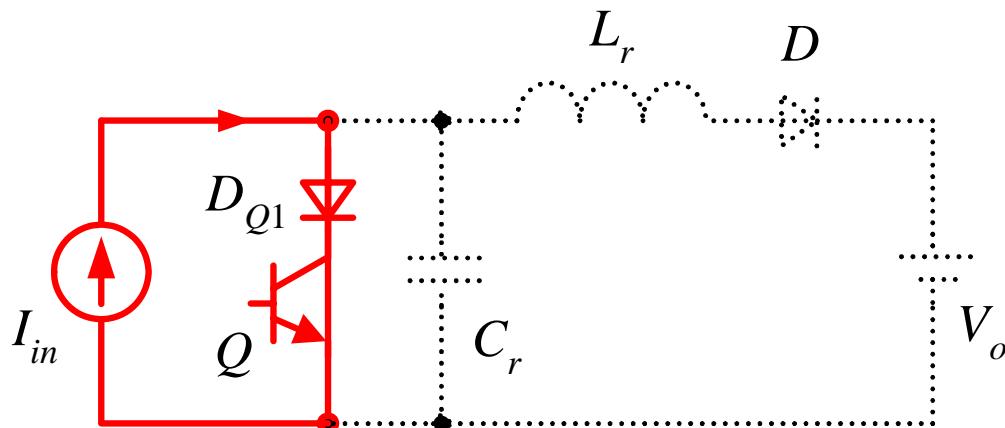

Comparison of ZVS QRC: HW vs FW

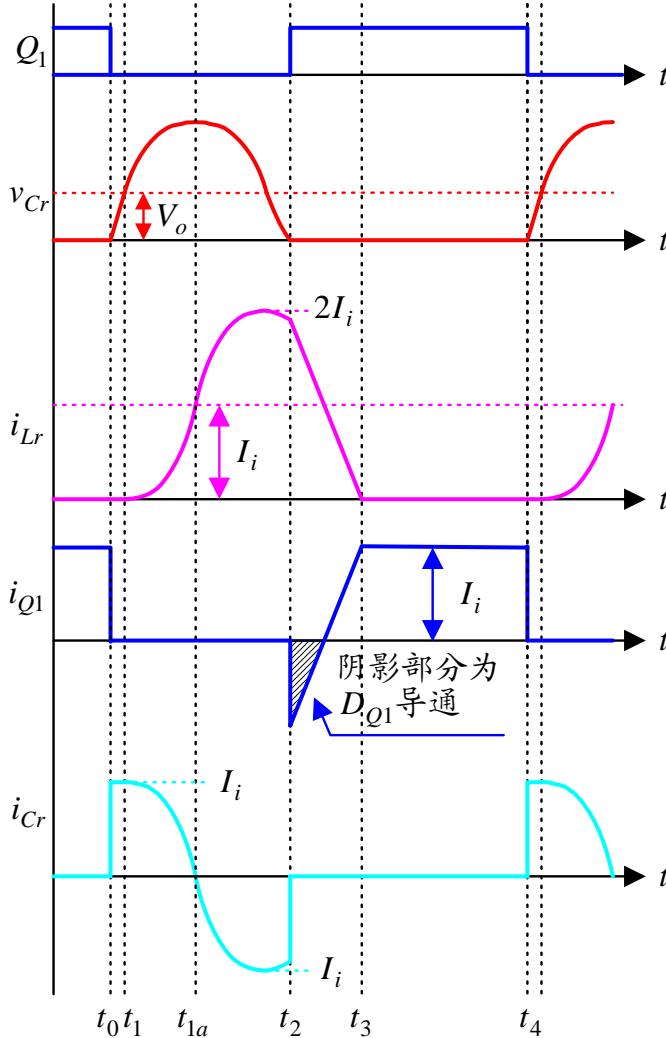


2011 Half-wave mode

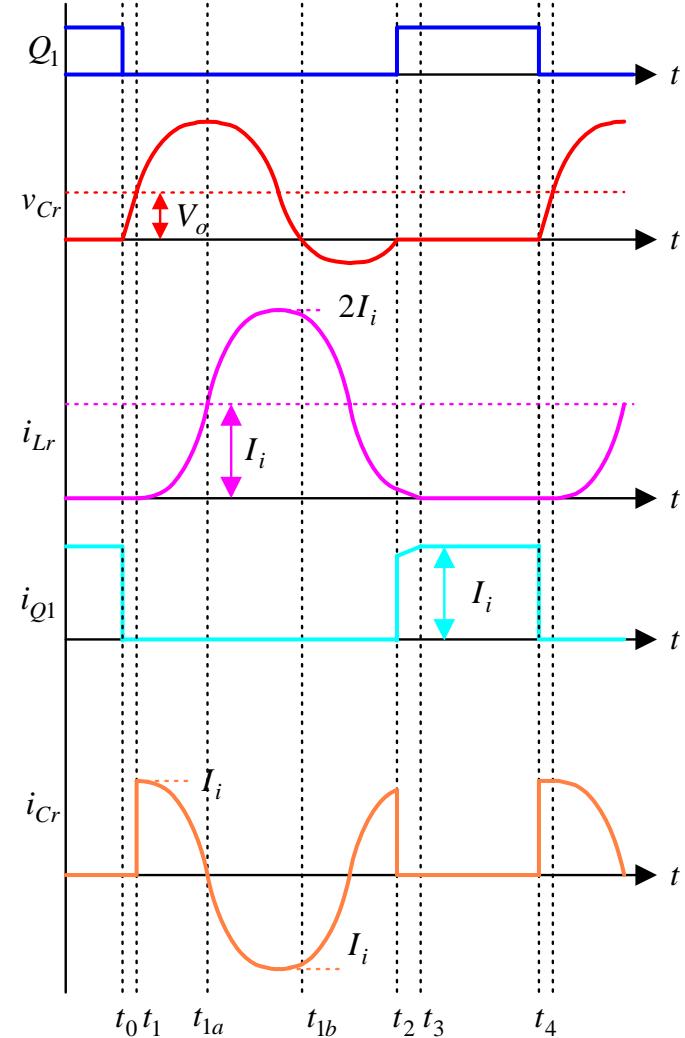


Full-wave mode

Output Characteristics of ZVS QRC

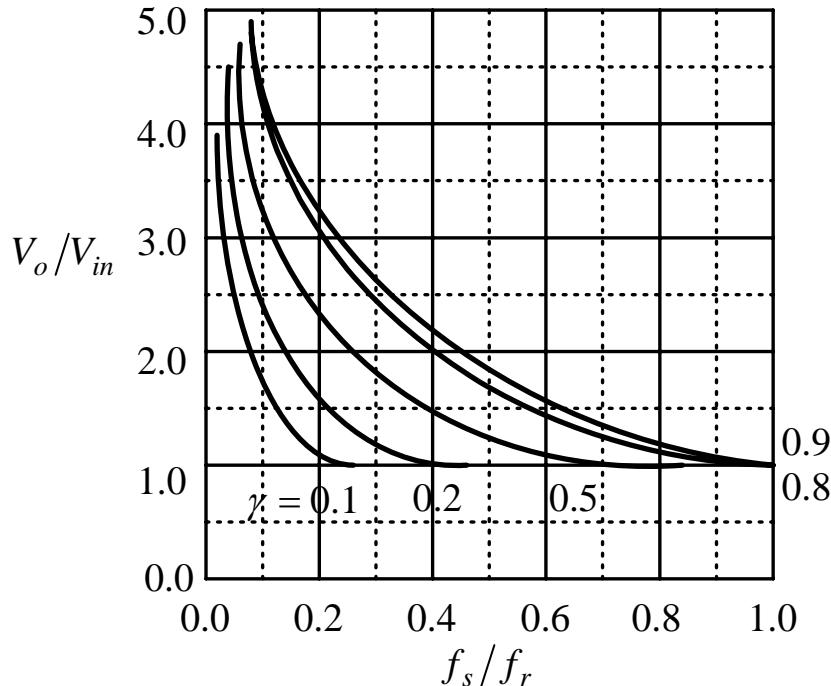


Half-wave mode

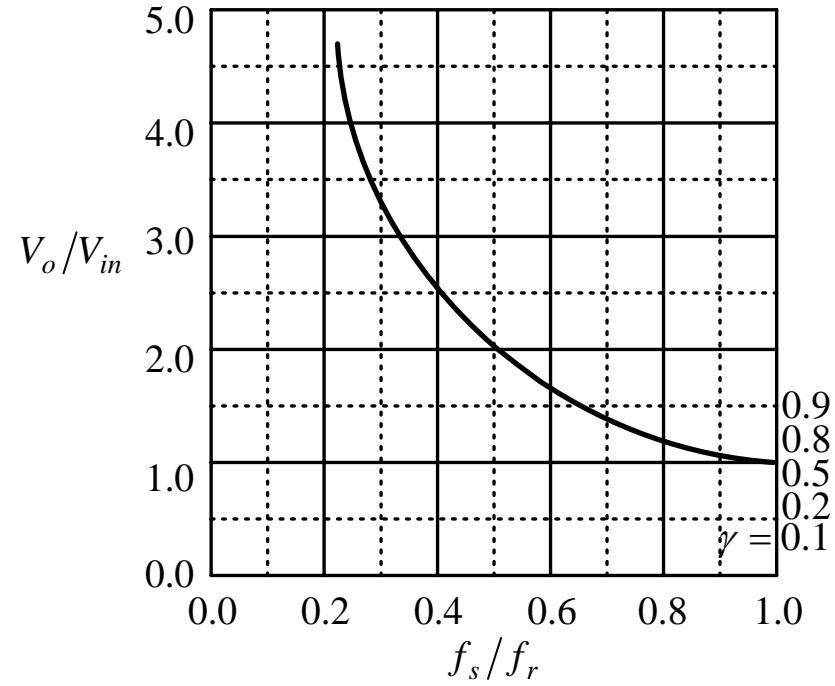


Full-wave mode


A Family of ZVS QRCs (1)

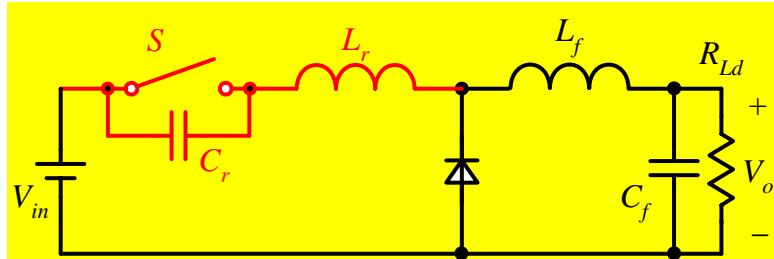


Buck

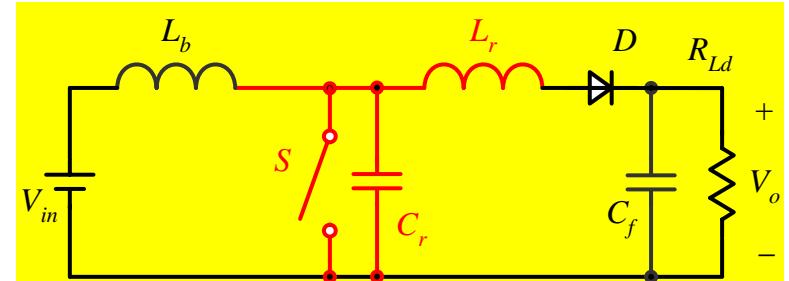


Boost

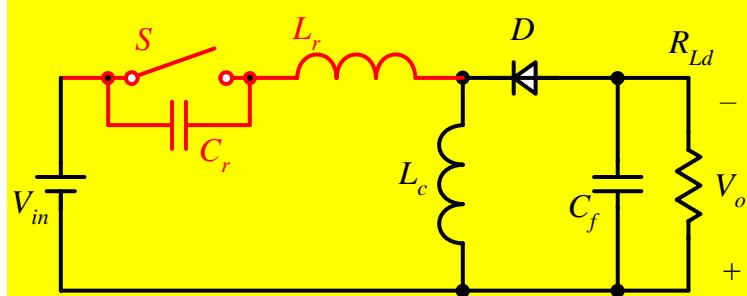


Buck-Boost

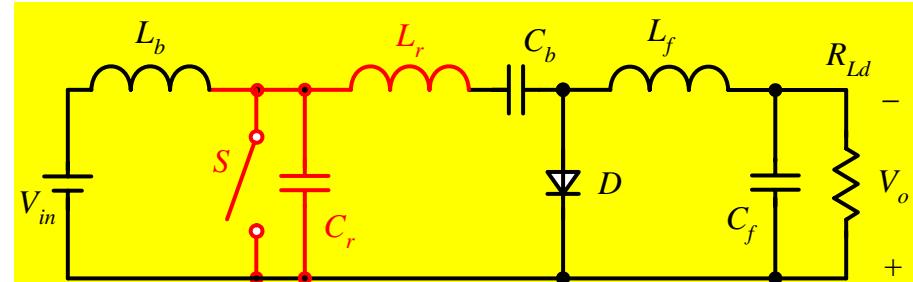


Cuk

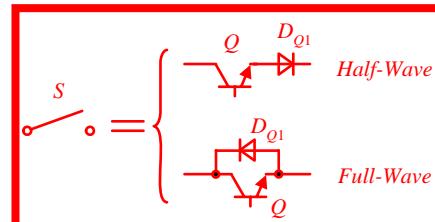


A Family of ZVS QRCs (2)

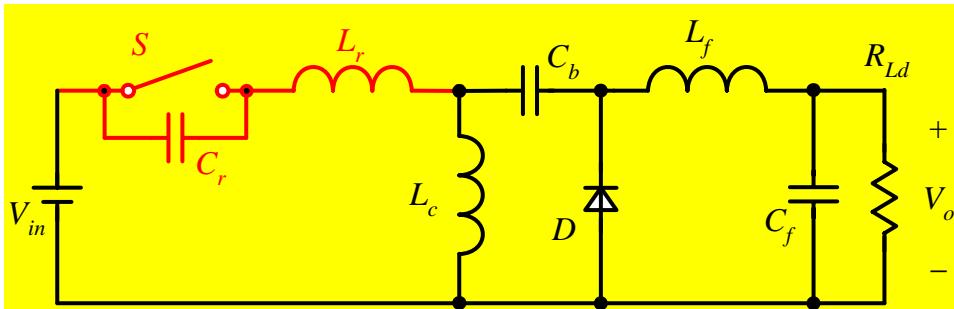


Zeta

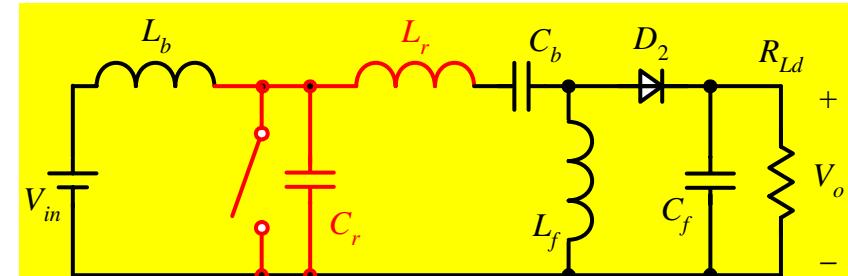

Sepic

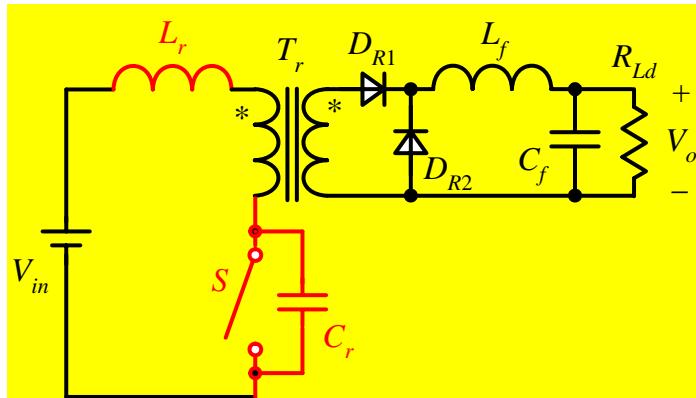

Forward

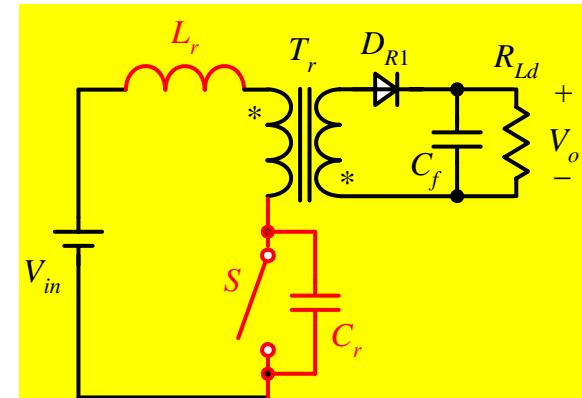

Flyback

Thanks for your attention !

Questions? / Answer!