


# Secondary Rectifier For Buck-Derived Converters

*Presented by*


*Xinbo Ruan*

**Aero-Power Sci-tech Center  
Nanjing University of Aeronautics & Astronautics**

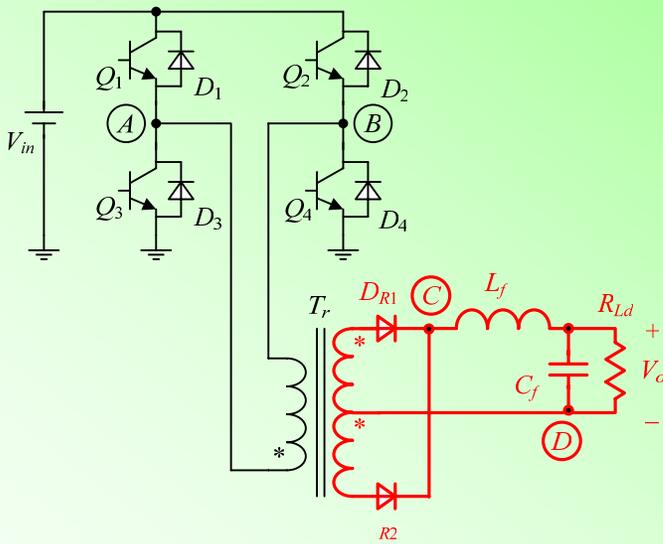
# Full-wave, Full-Bridge and Current Doubler Rectifier




Full-Wave

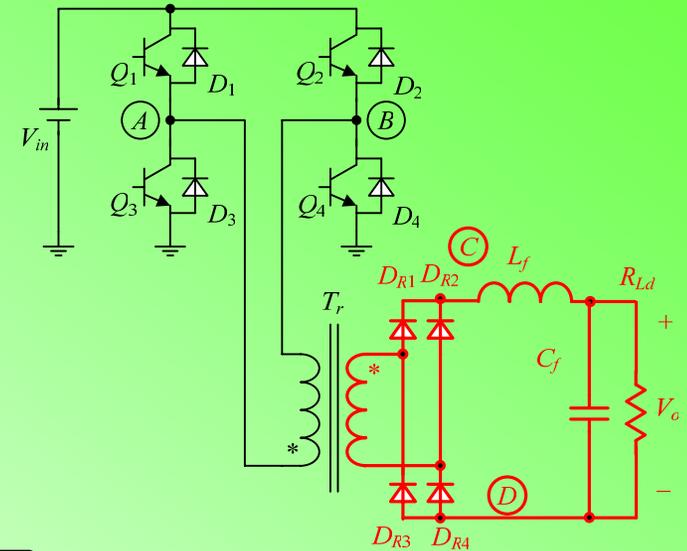


Full-Bridge

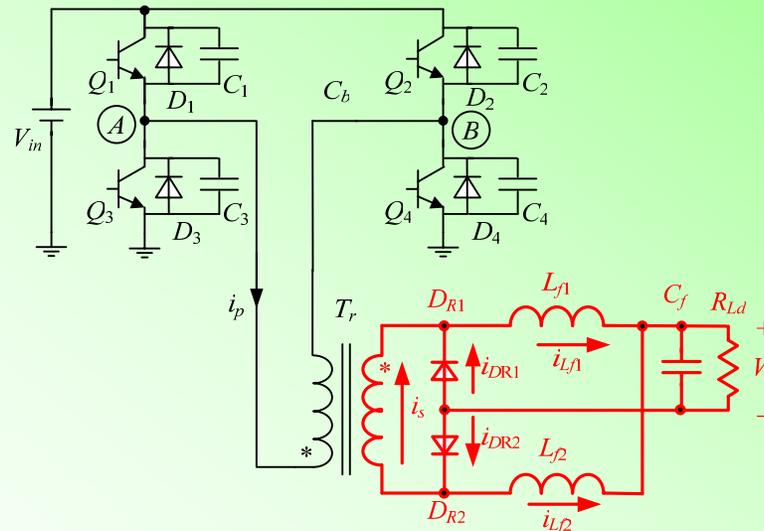


Current Doubler Rectifier

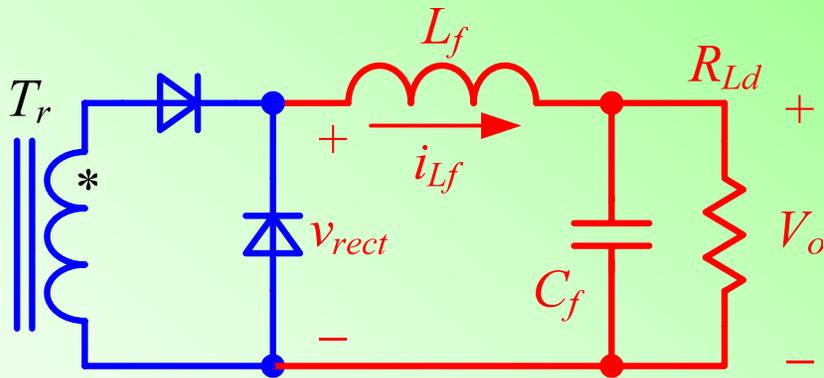

Positive cycle

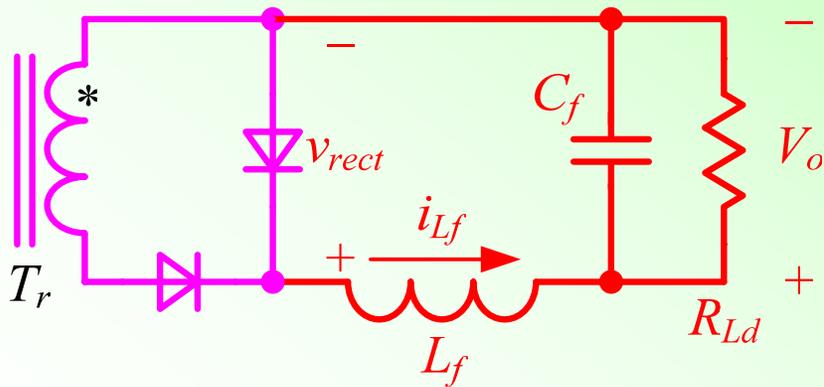


Negative cycle

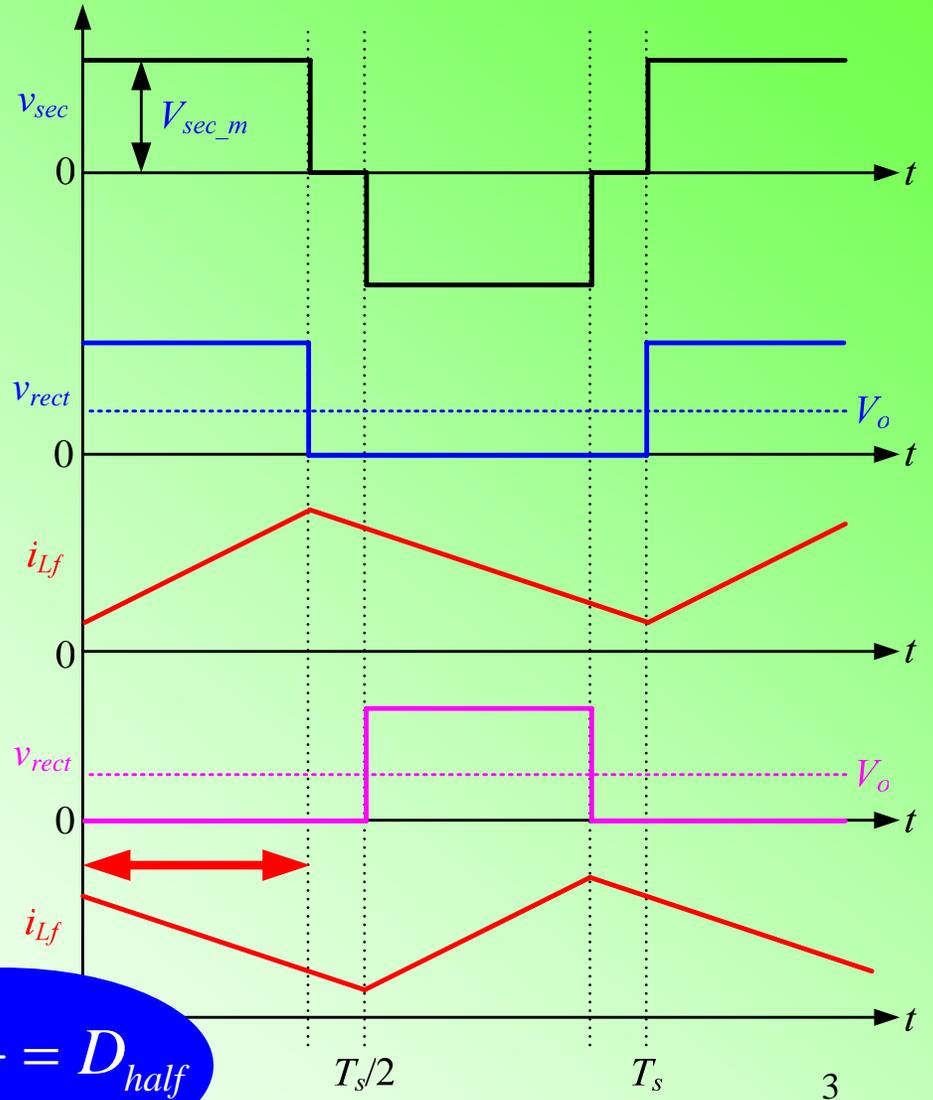


$$\frac{V_o}{V_{sec\_m}} = D_{half}$$

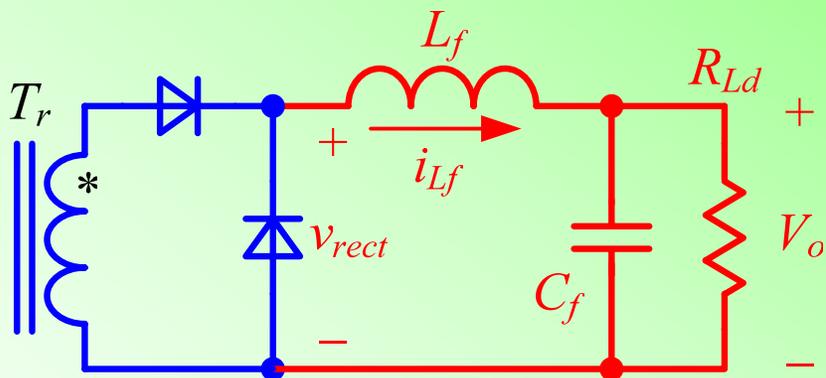
Two rectifiers with two coupled windings share the filter.







Positive cycle


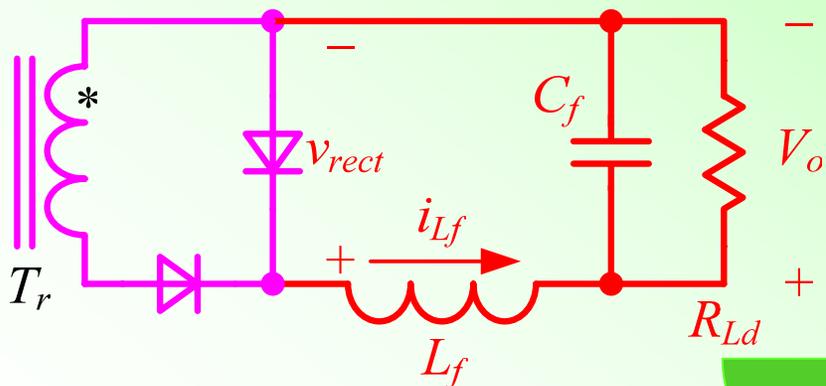




Negative cycle


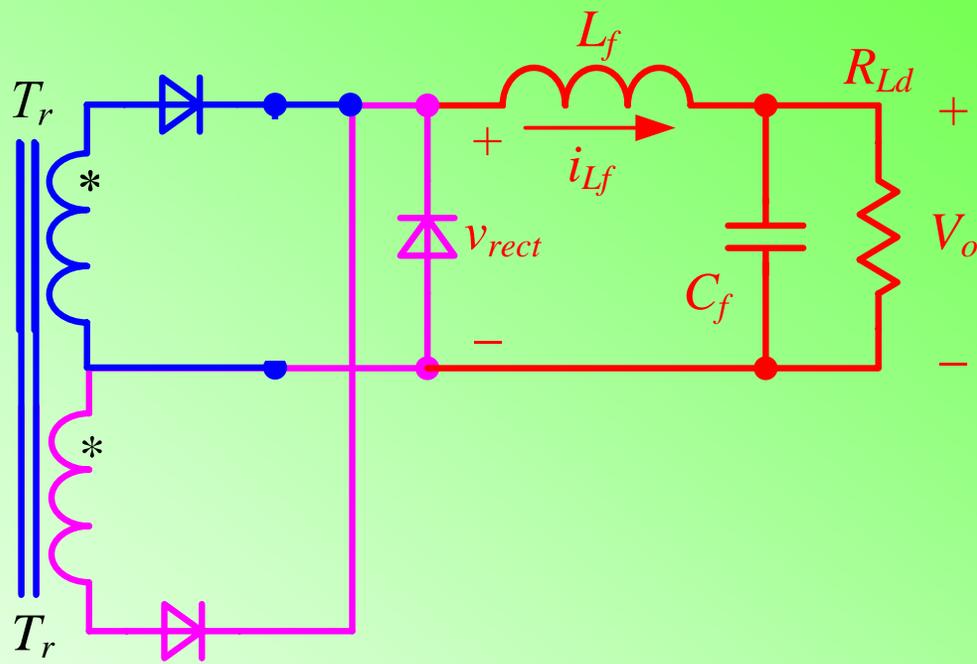


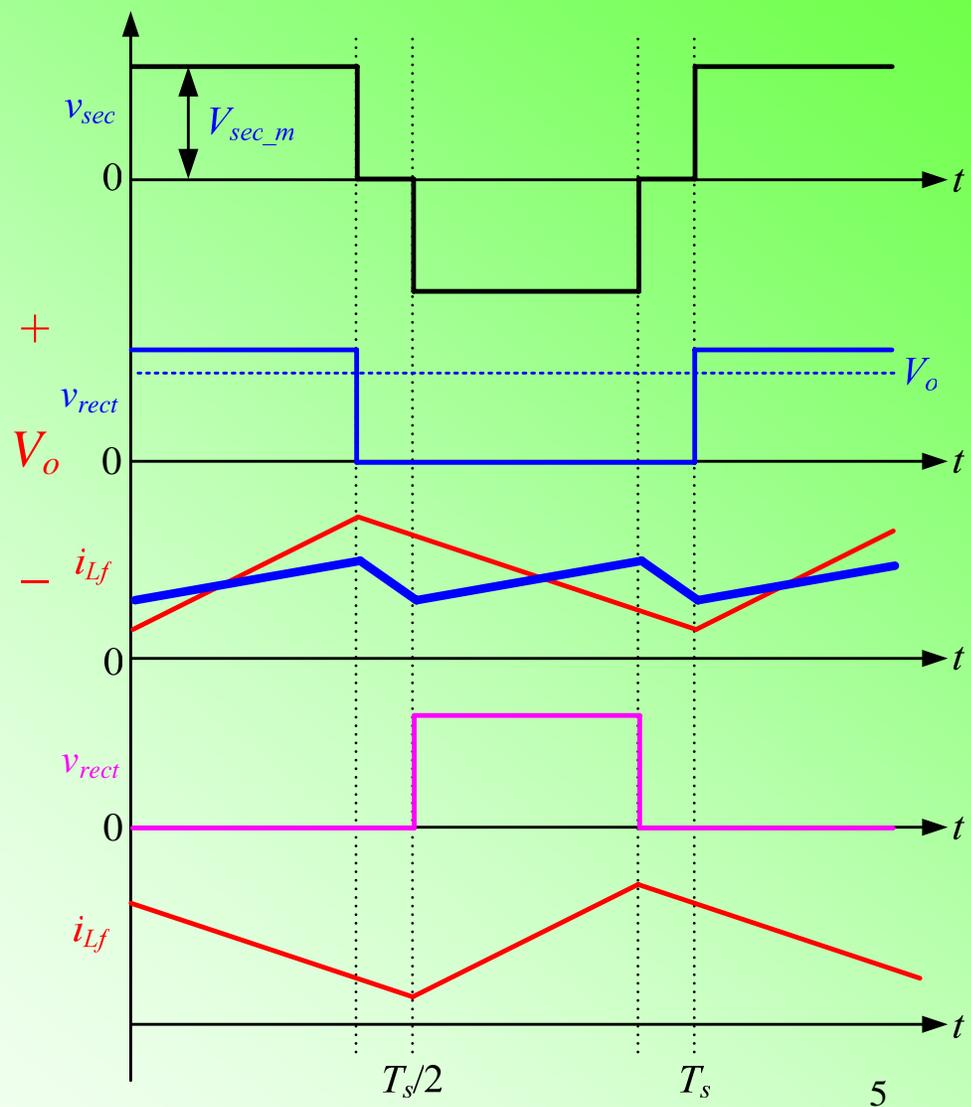
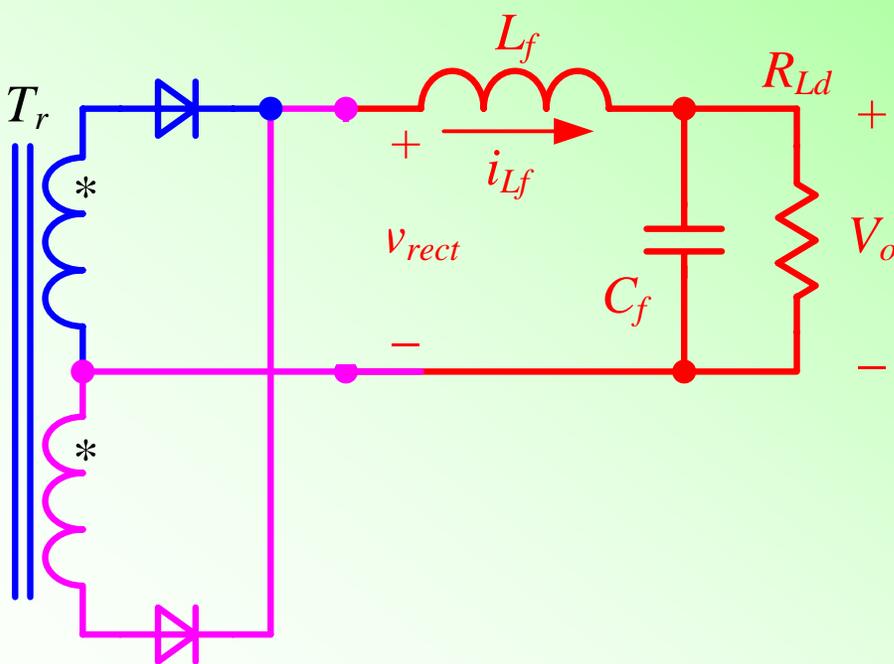


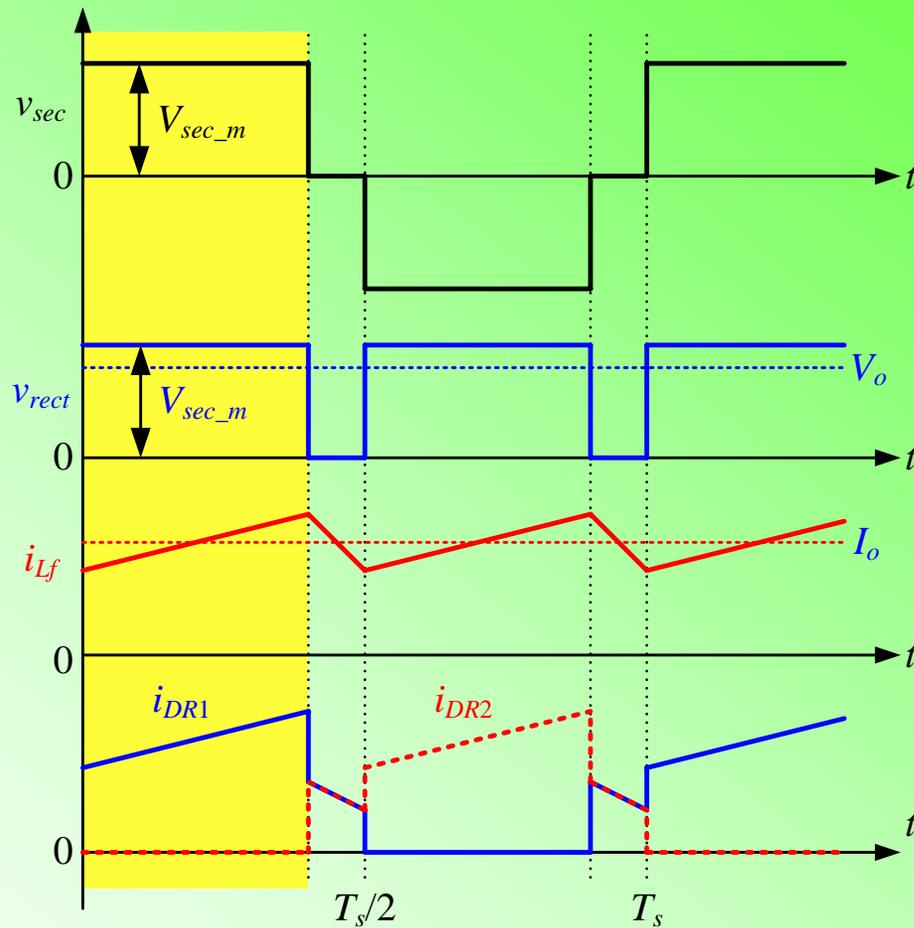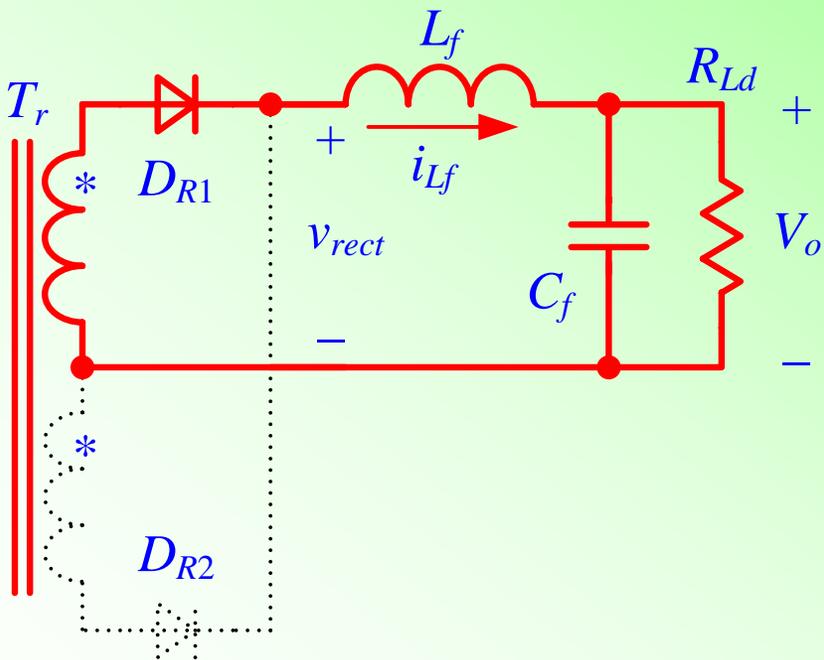

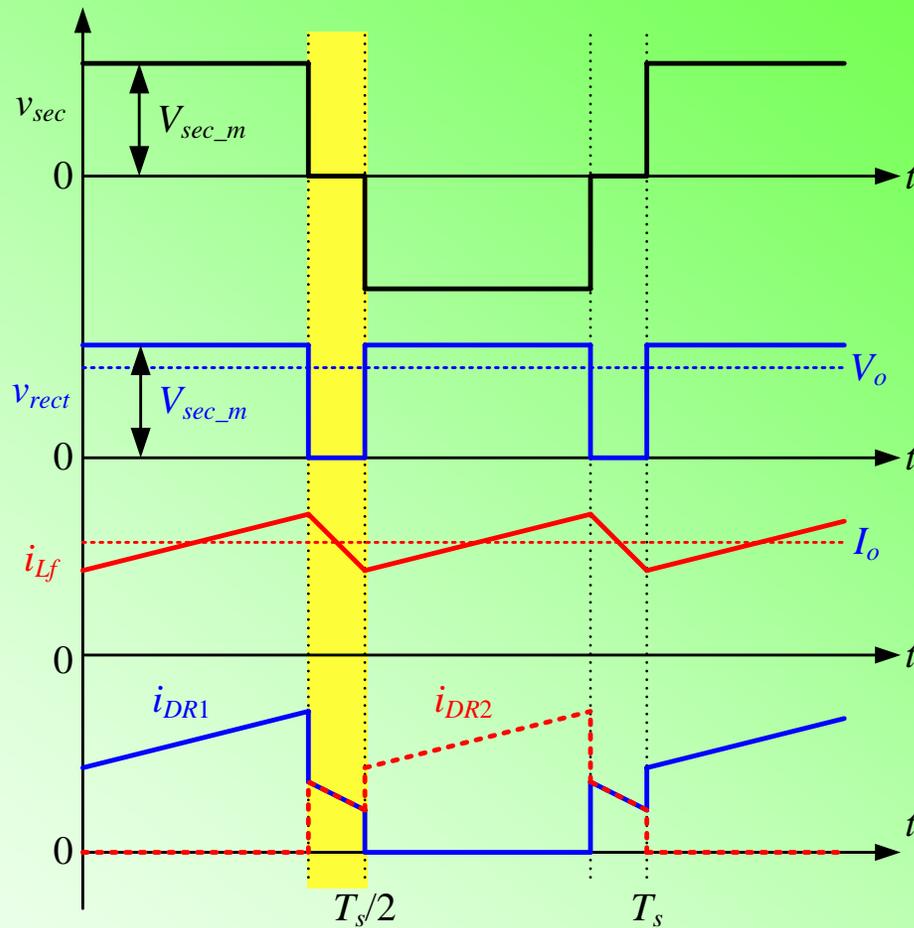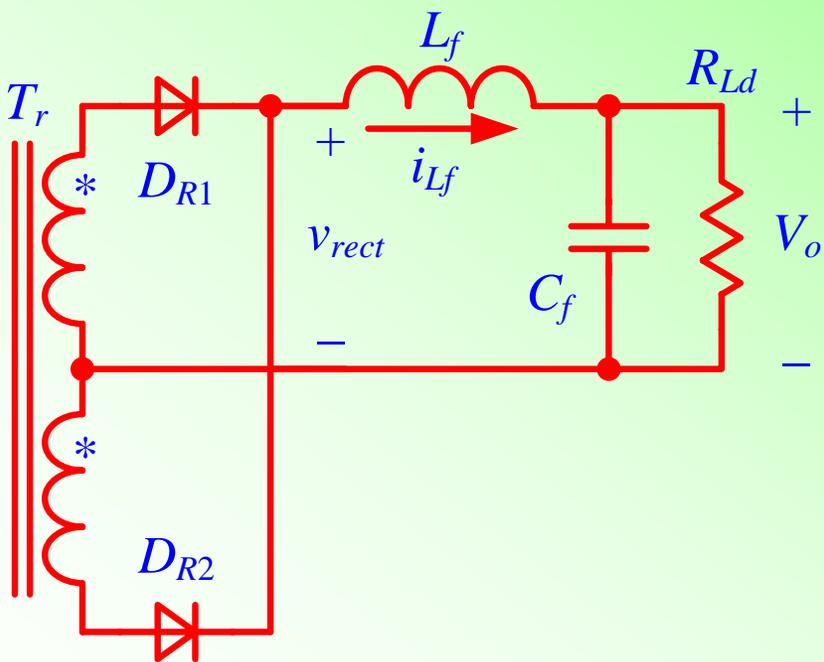

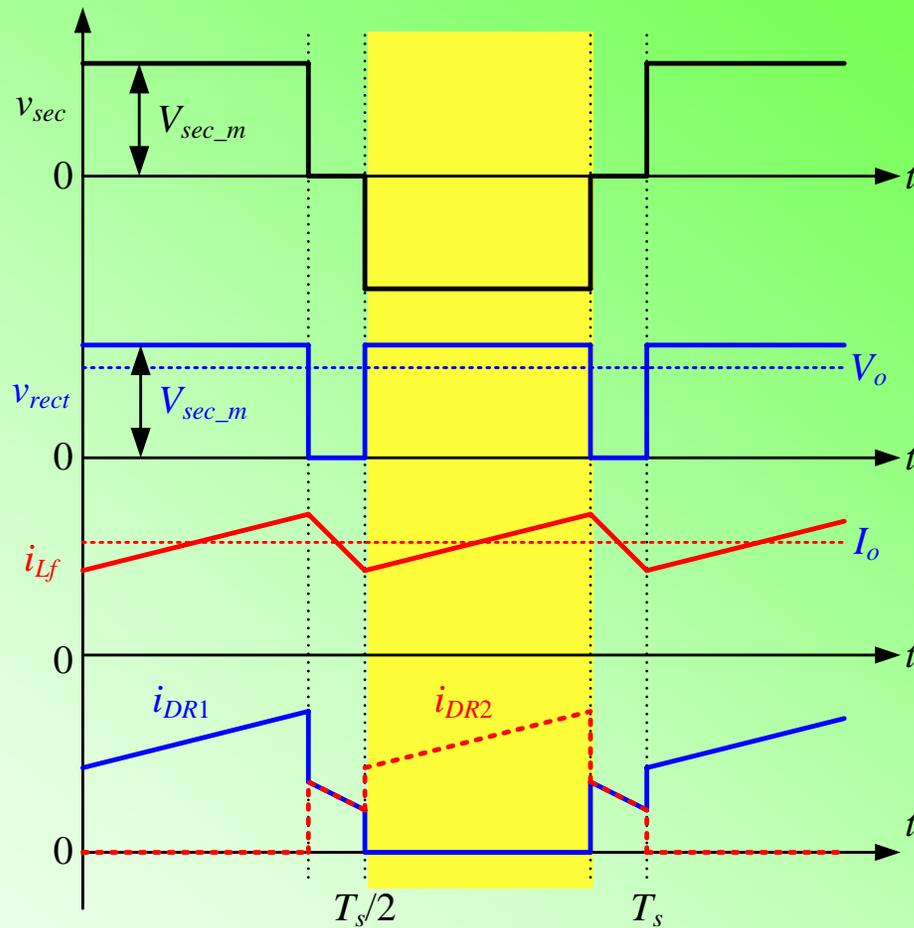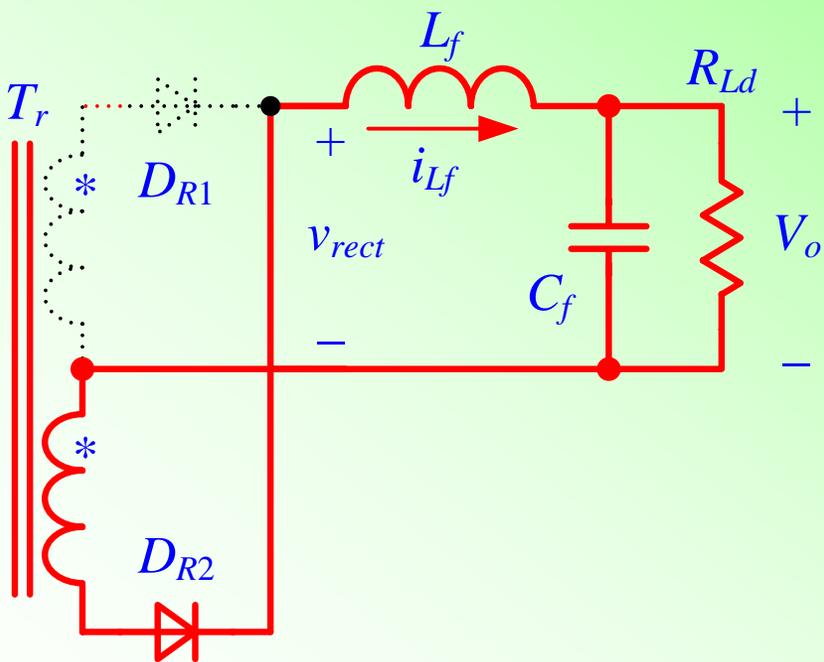

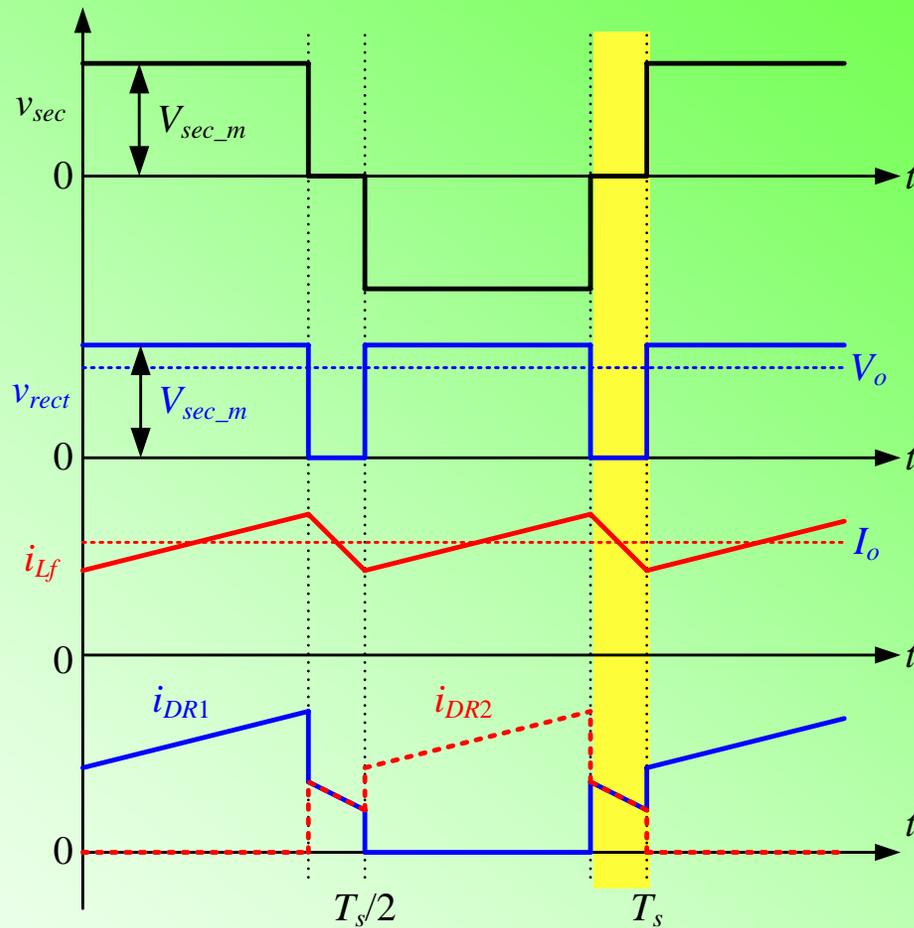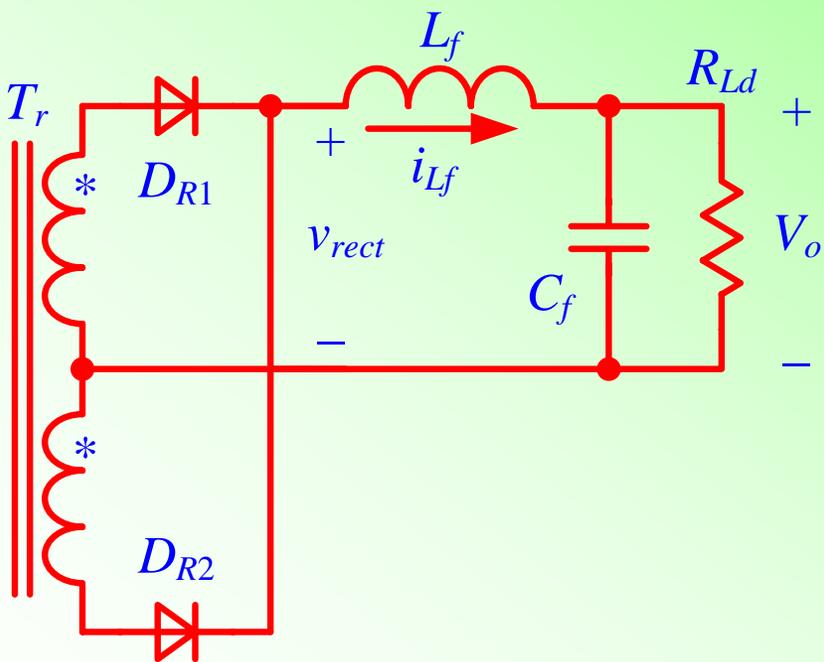

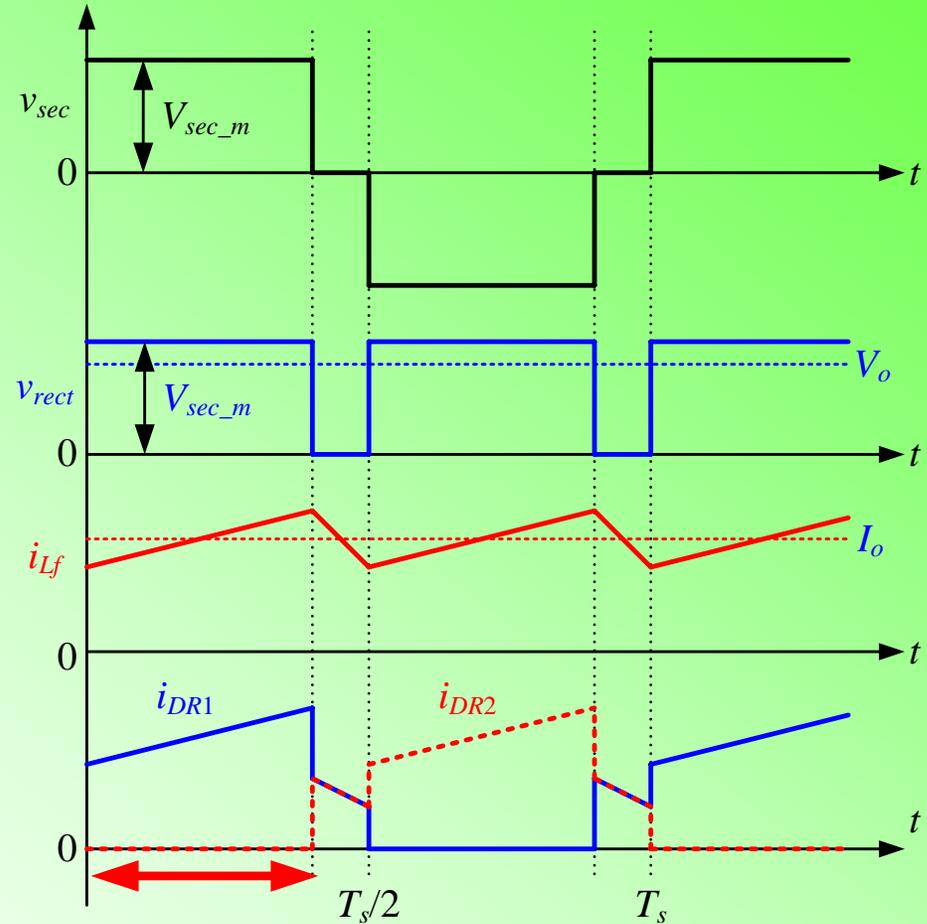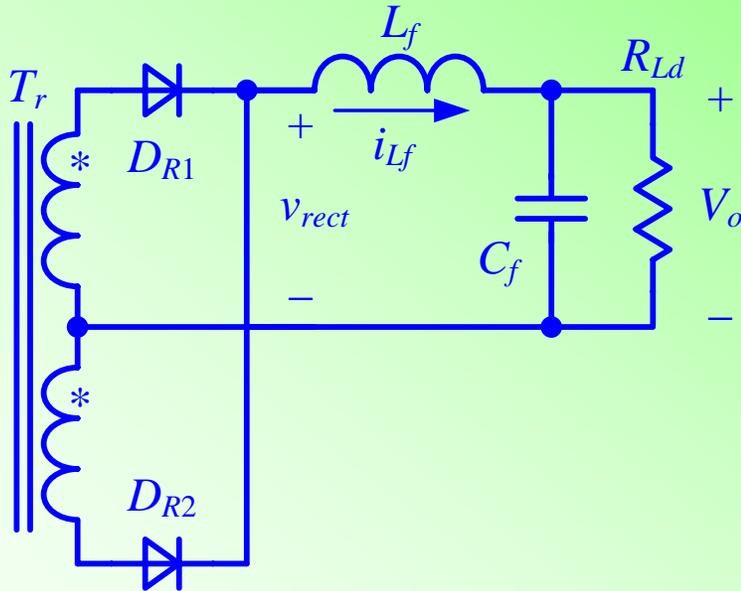




$$\frac{V_o}{V_{sec\_m}} = D_{eq} = 2D_{half}$$


$$V_{DR1} = V_{DR2} = 2V_{sec\_m}$$



$$I_{DR1} = I_{DR2} = \frac{1}{2} I_o$$



Inductor current can not flow in the negative direction.

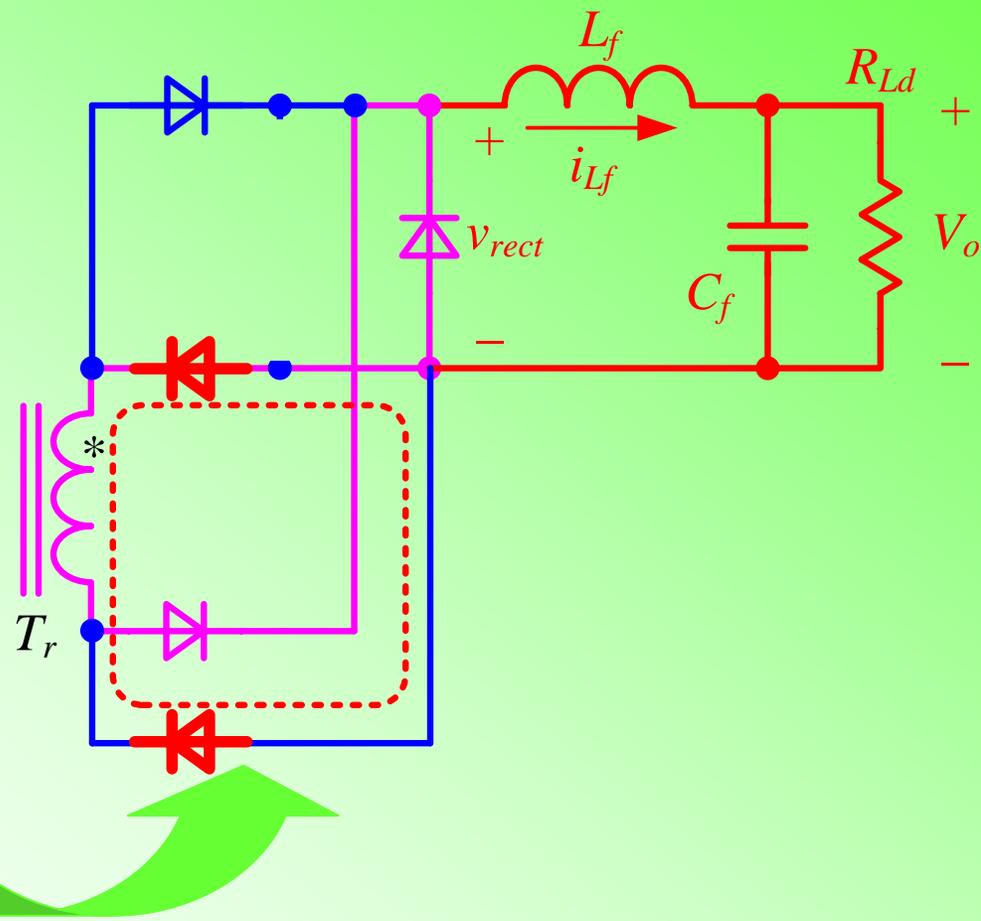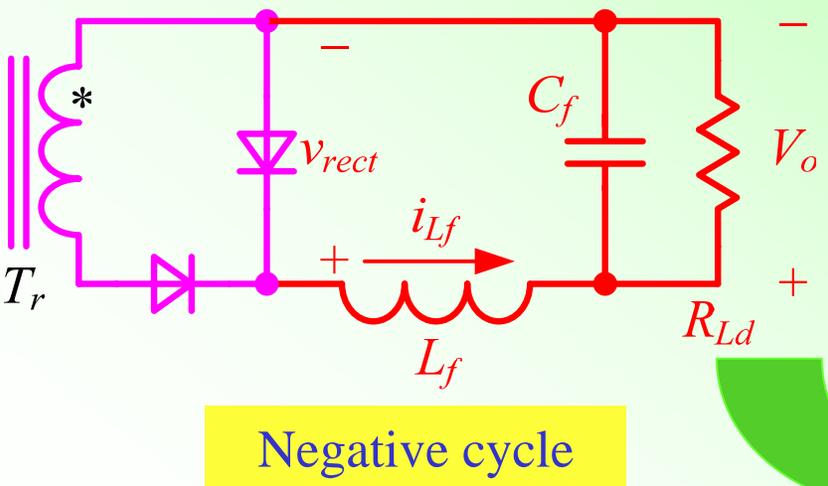
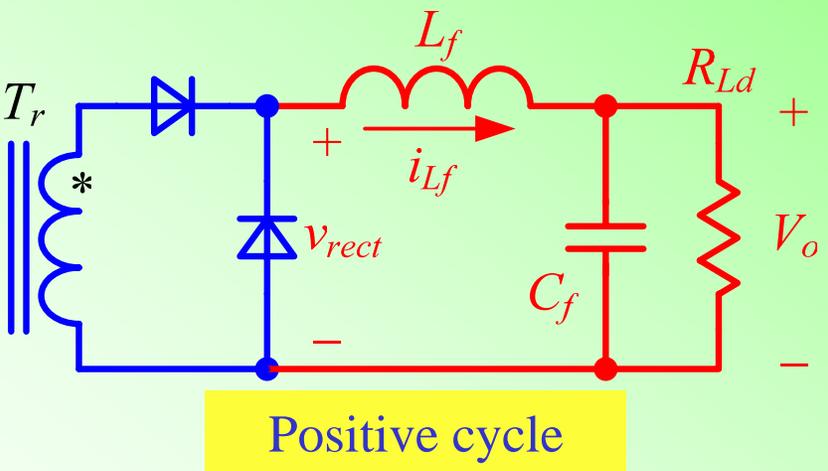
Two rectifiers share both the winding and the filter.






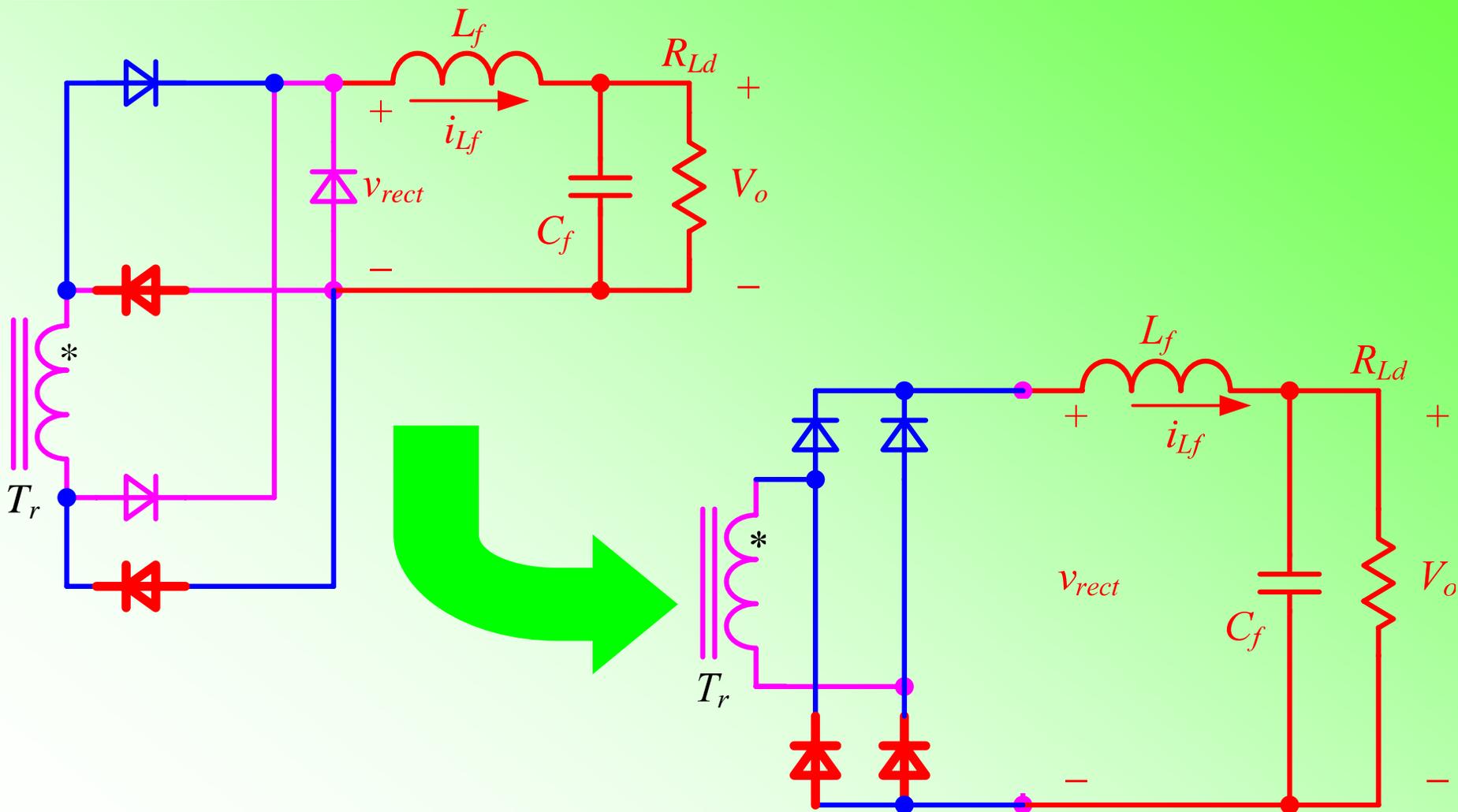


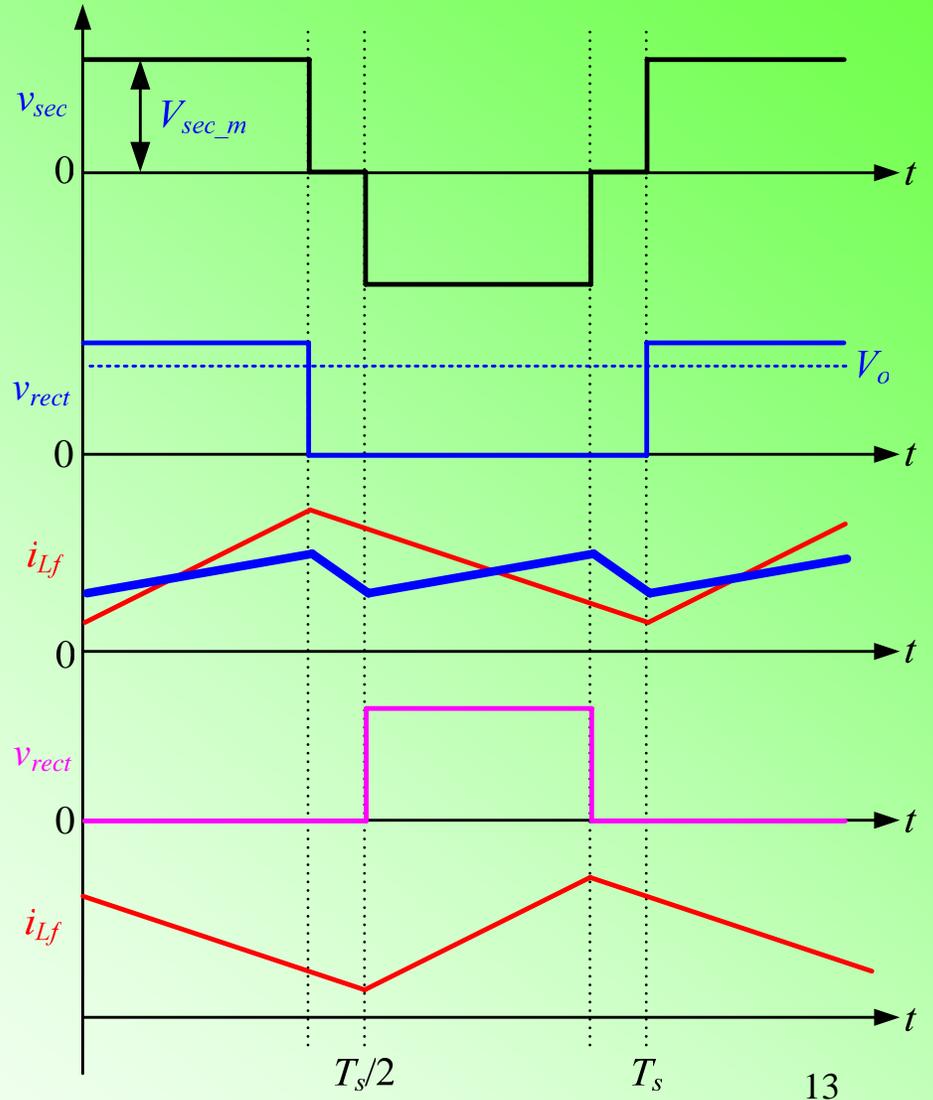
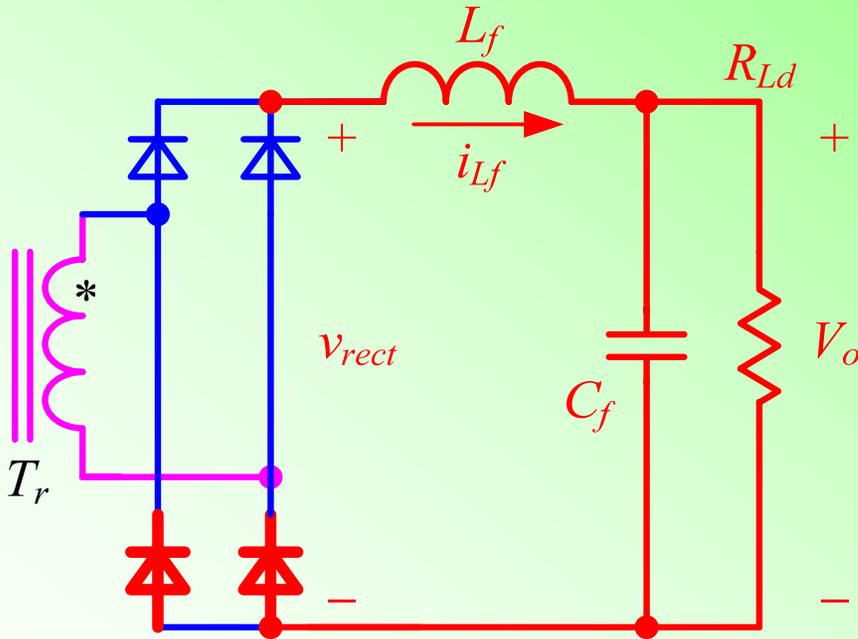


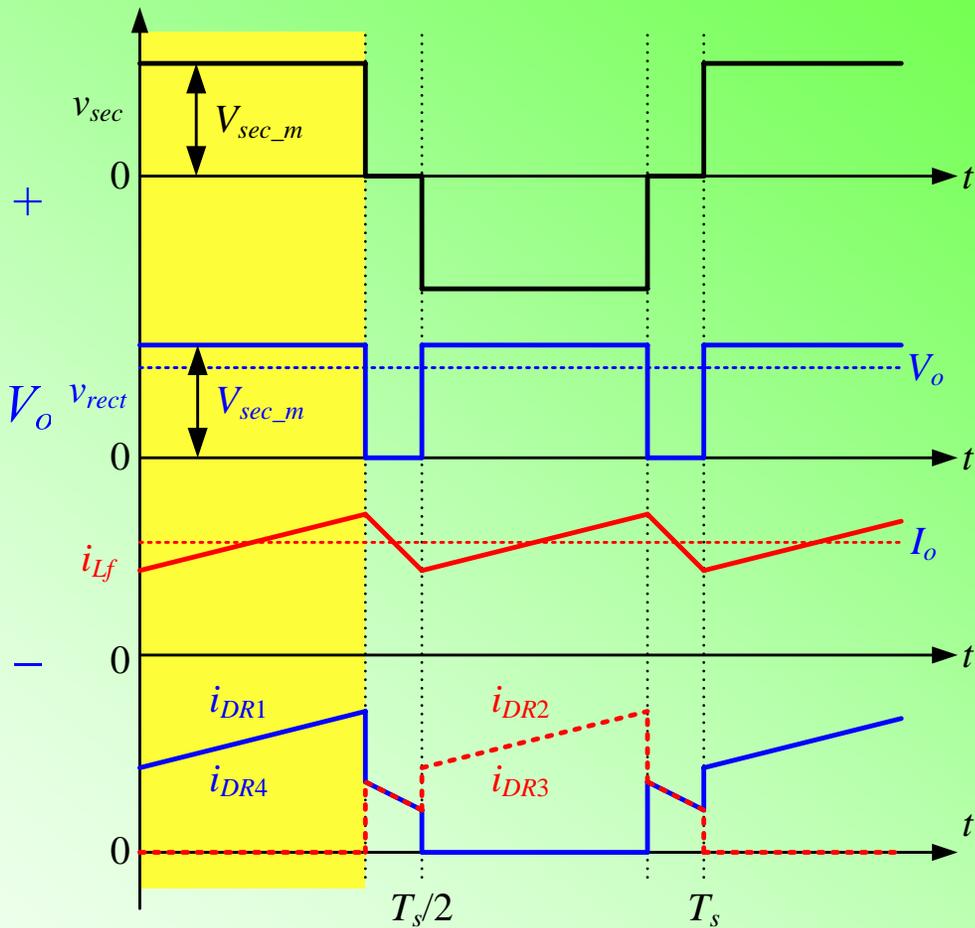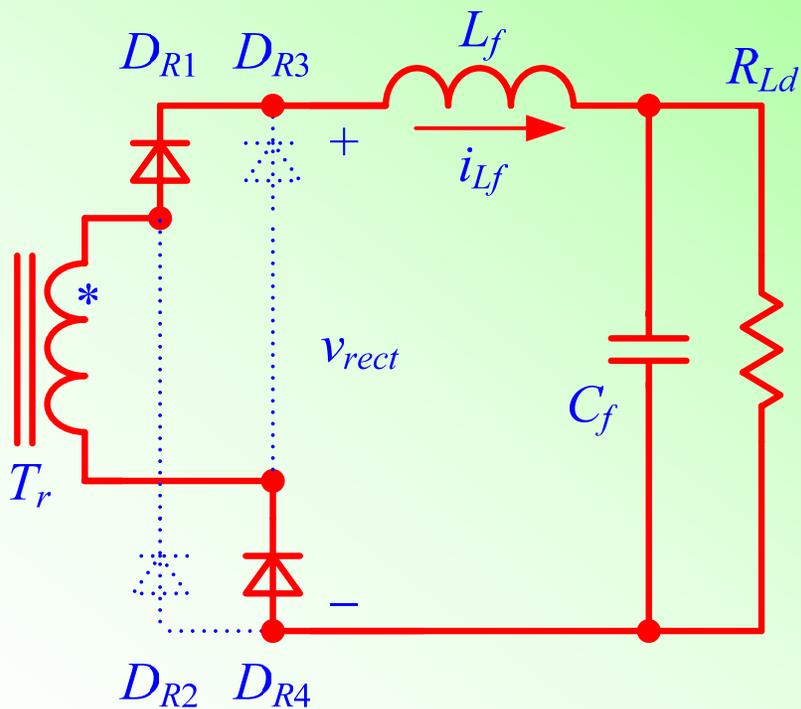

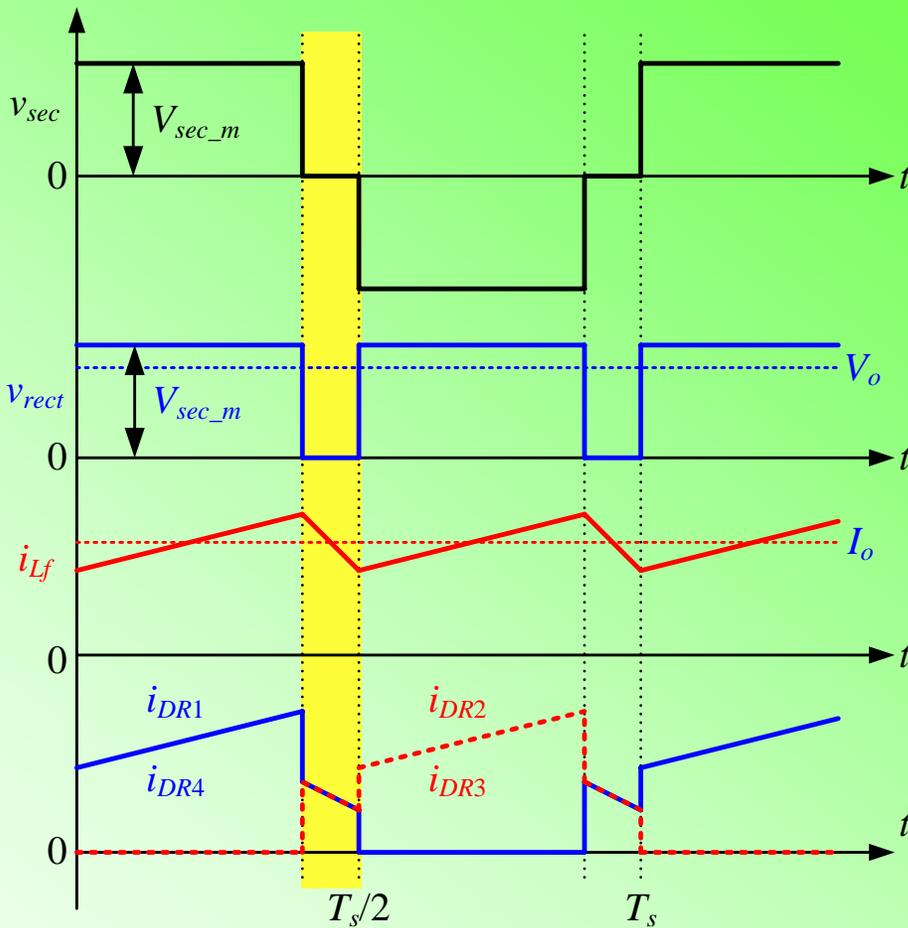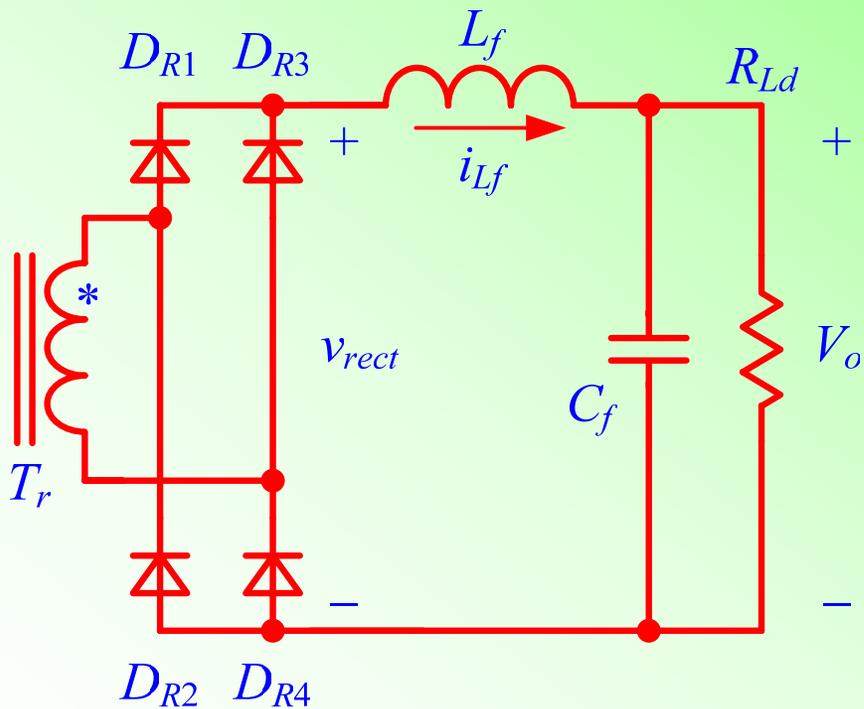

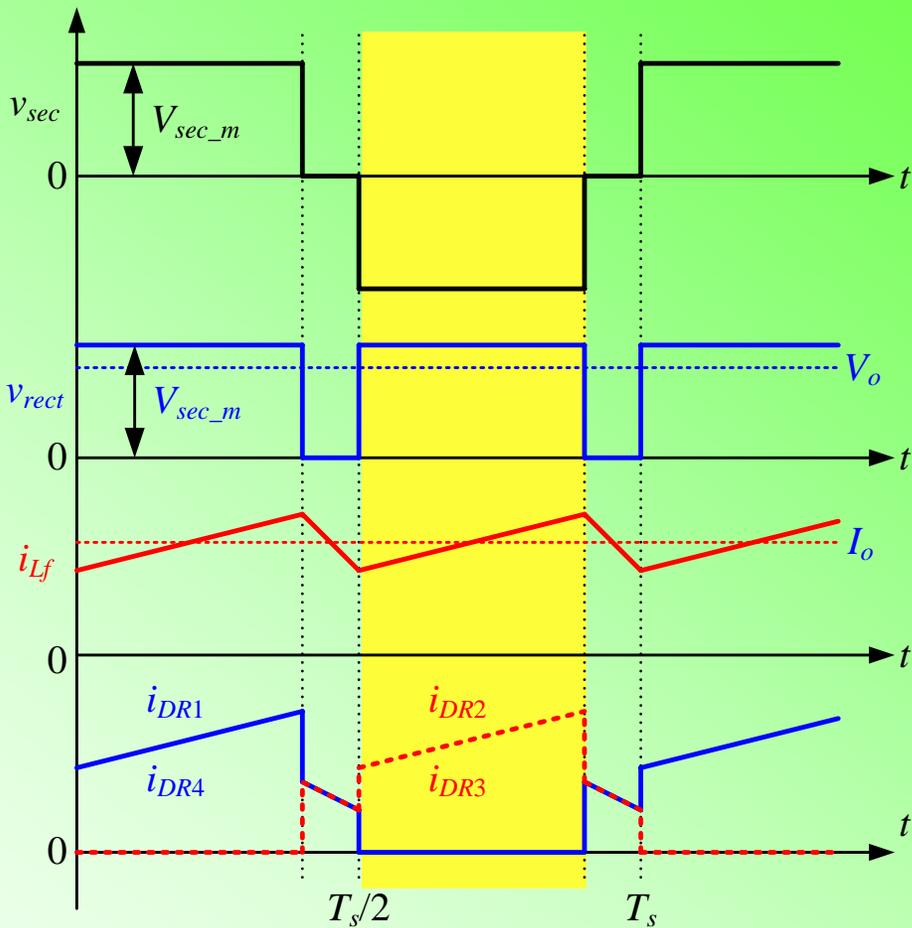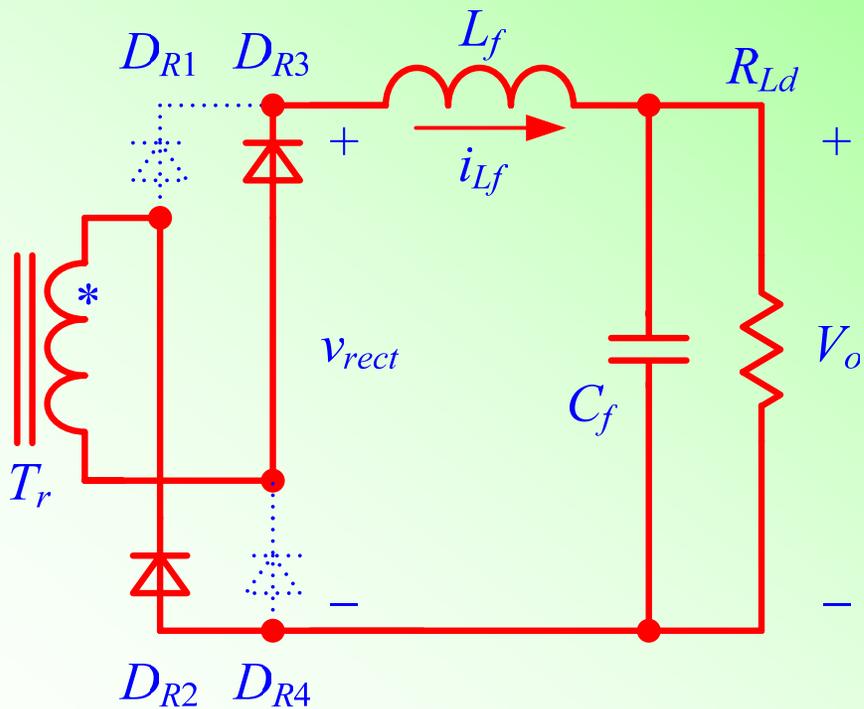

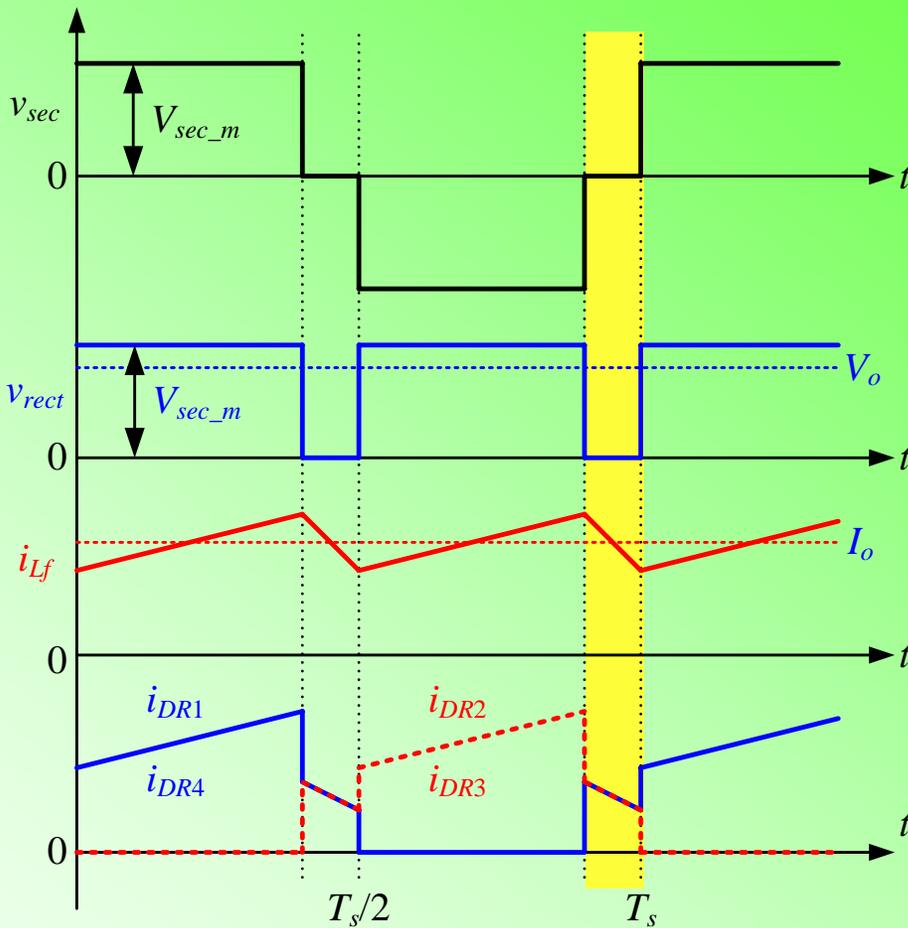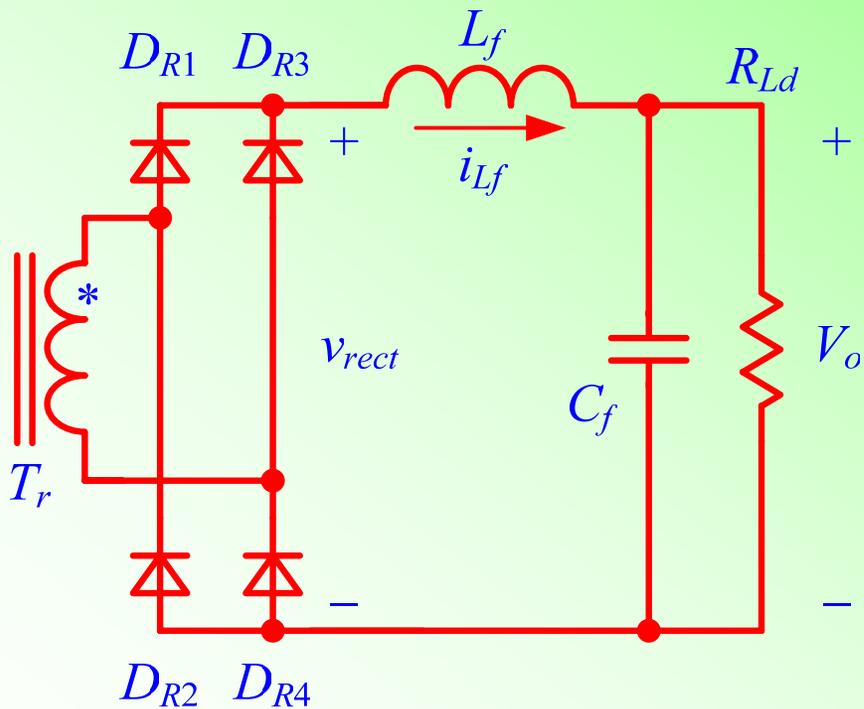

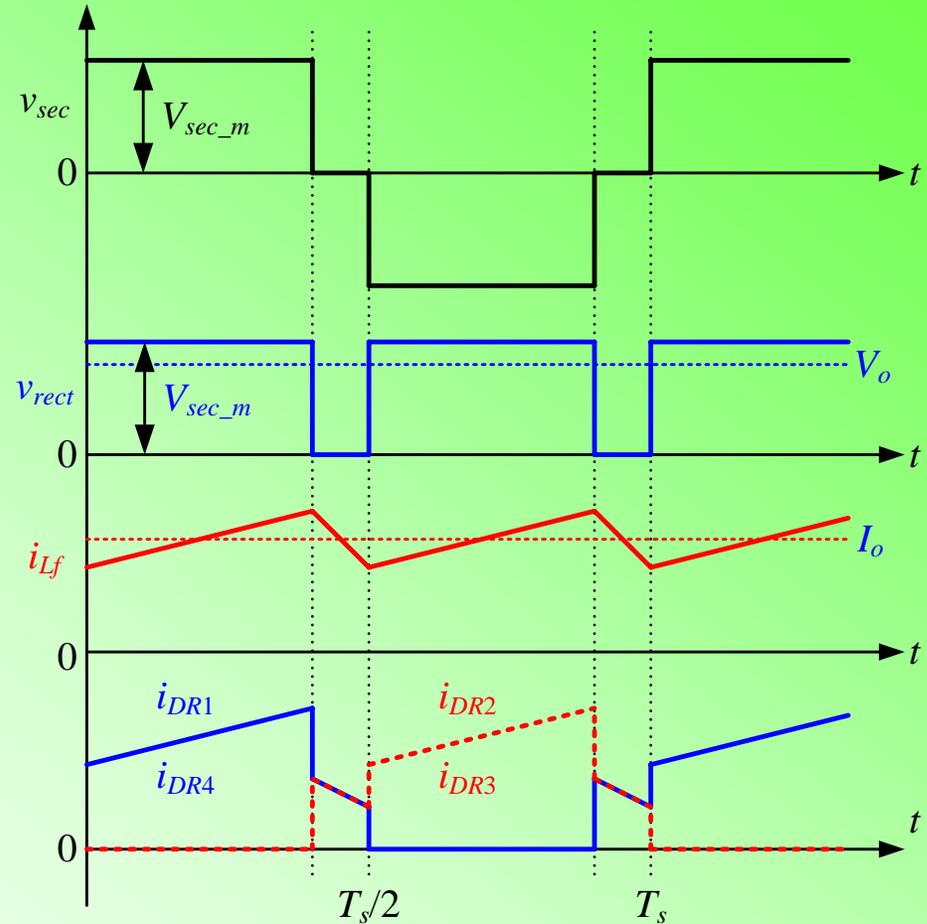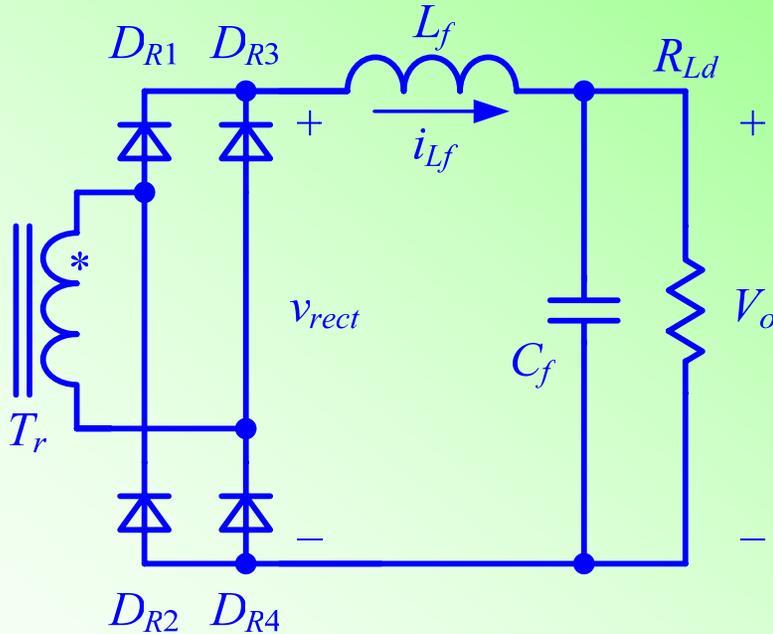






$$\frac{V_o}{V_{sec\_m}} = D_{eq} = 2D_{half}$$

$$V_{DR1} = V_{DR2} = V_{sec\_m}$$




$$I_{DR1} = I_{DR2} = \frac{1}{2} I_o$$

Inductor current can not flow in the negative direction.





Positive Cycle

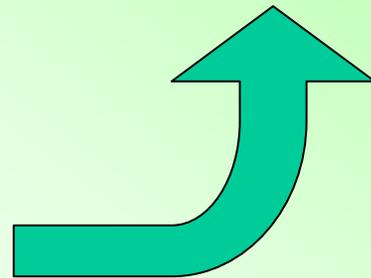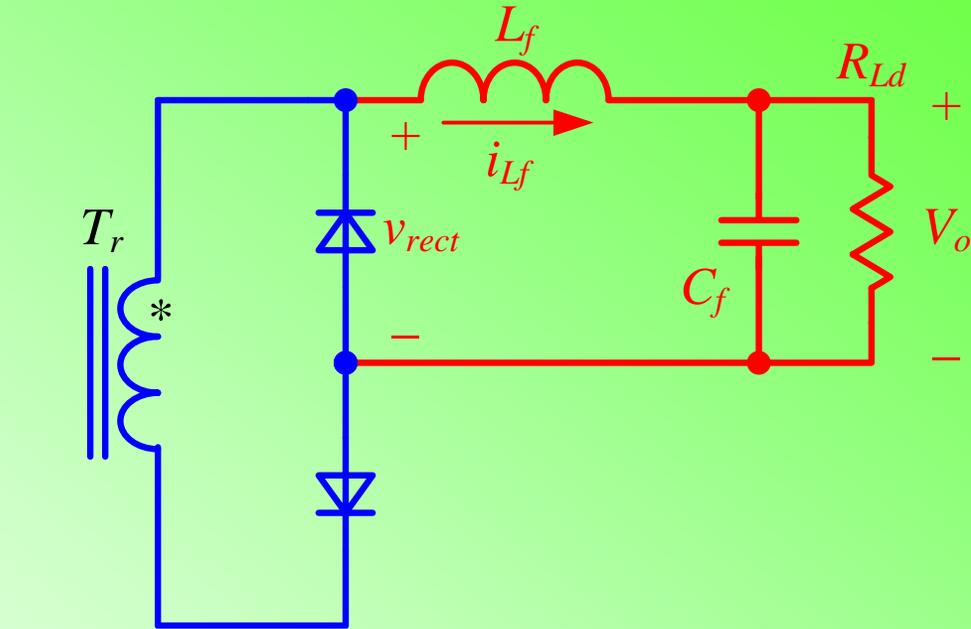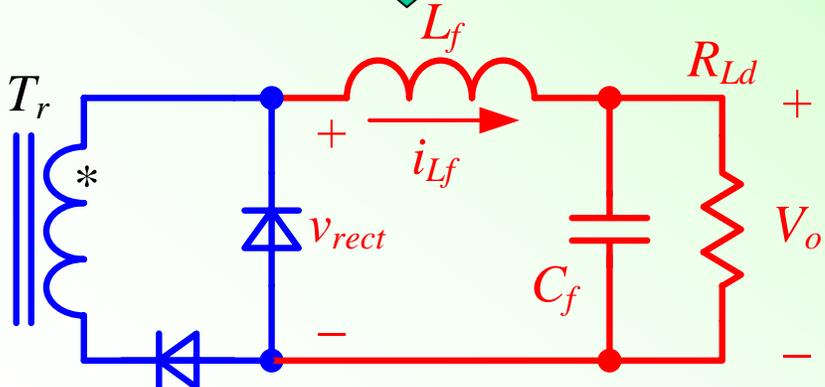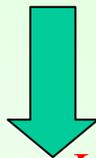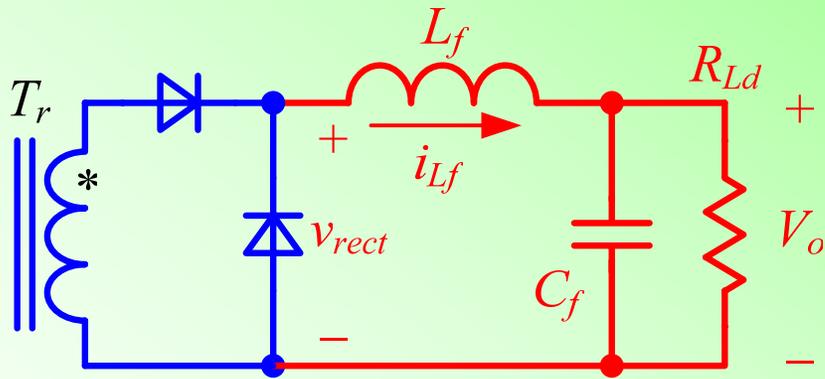


Negative Cycle

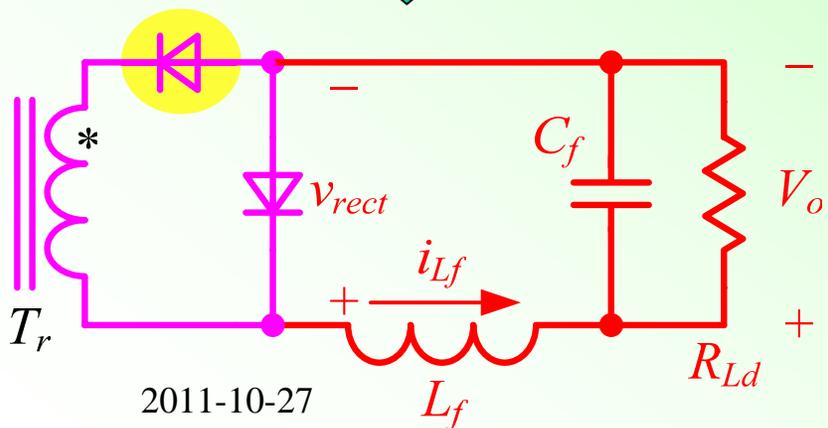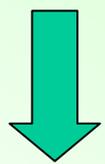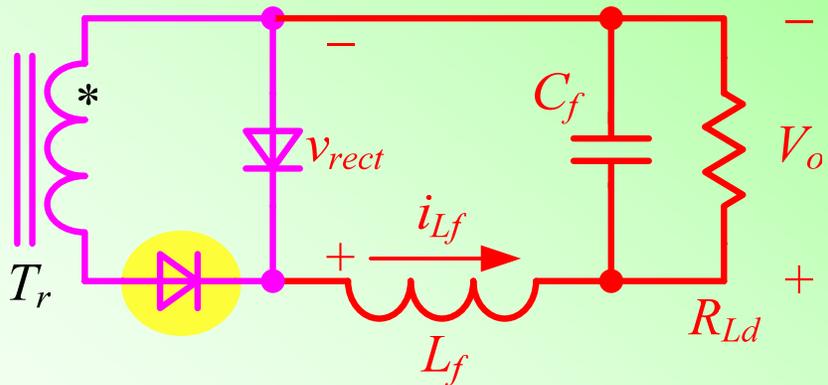


2011-10-27

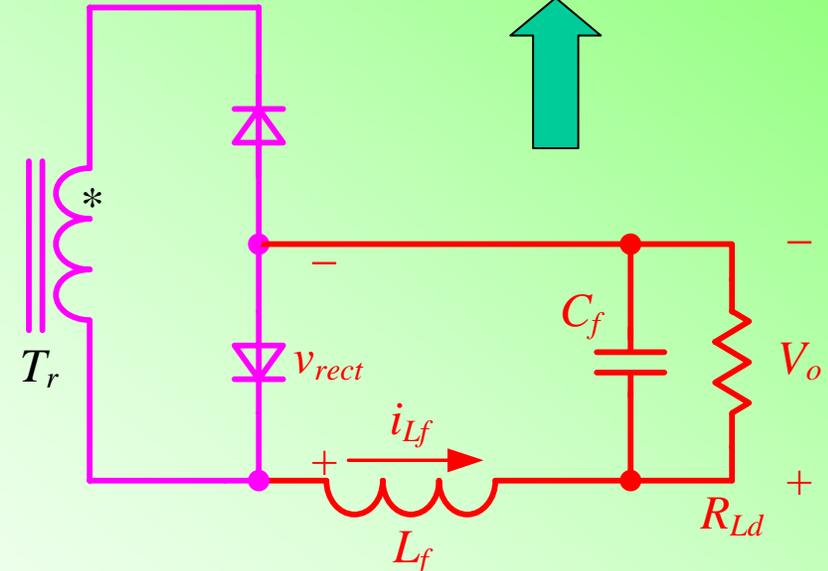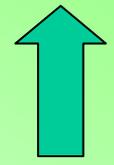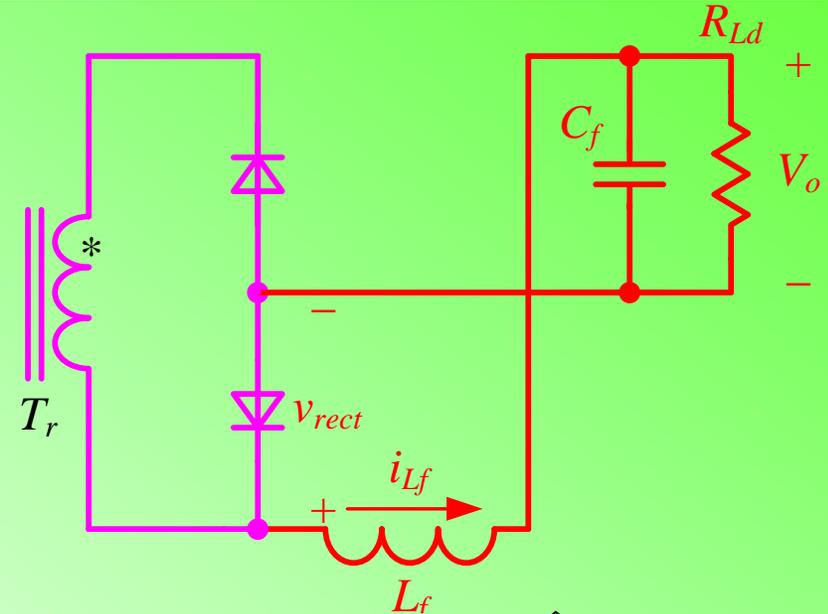
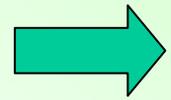



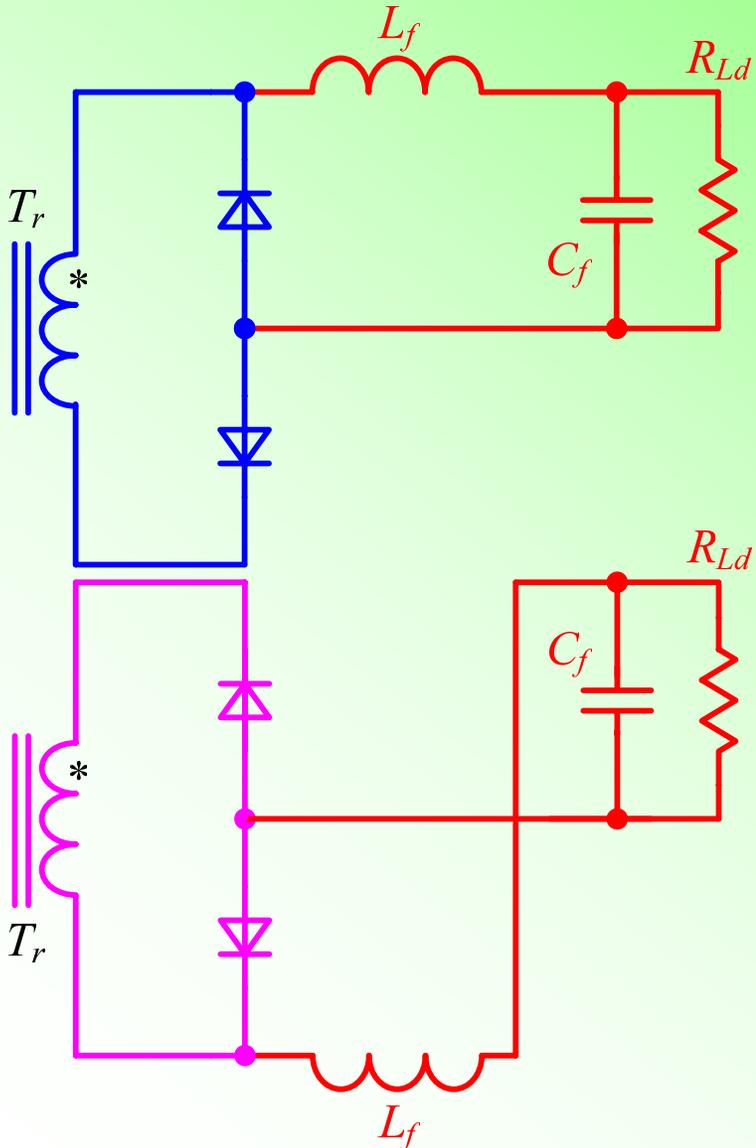



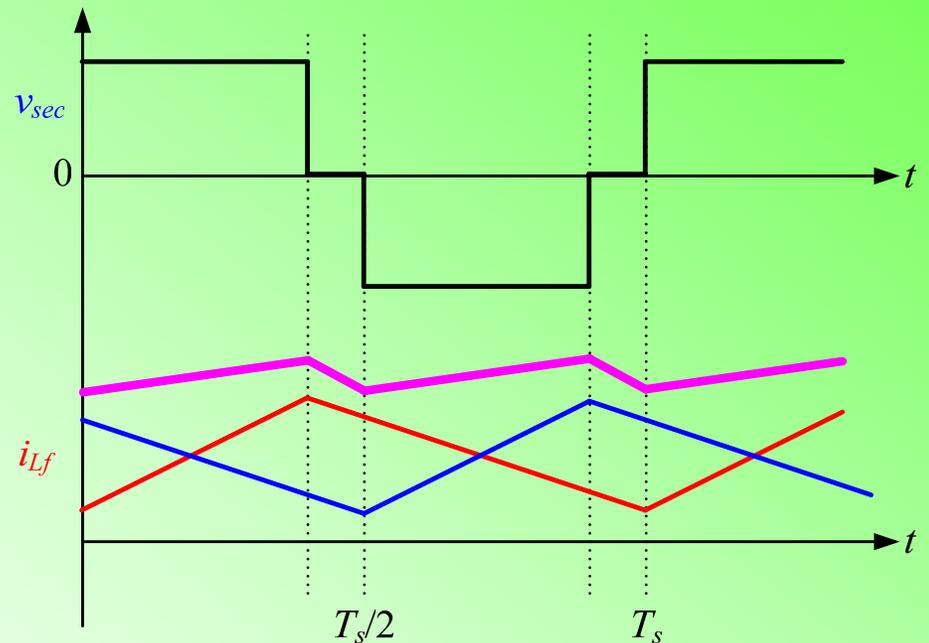
Two rectifiers share the winding and filter capacitor.






$$\frac{V_o}{V_{sec\_m}} = D_{half}$$

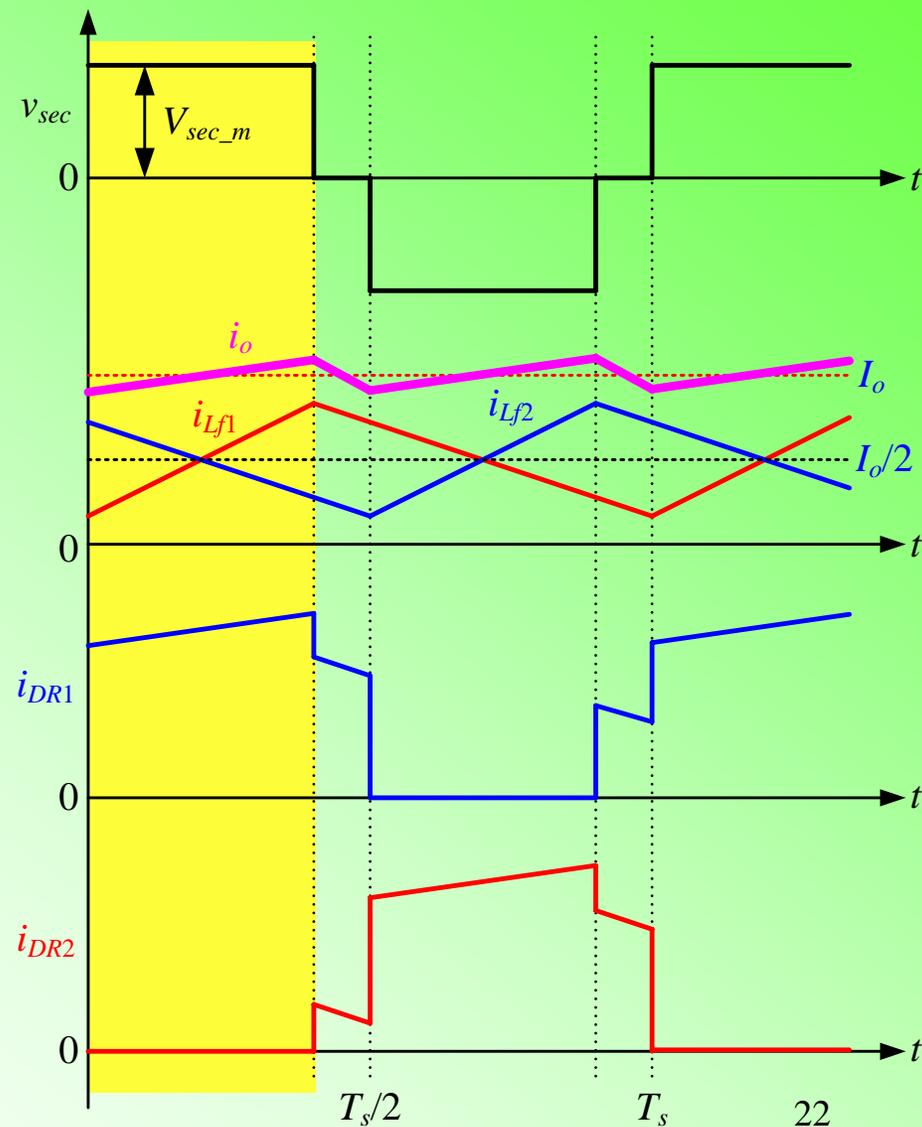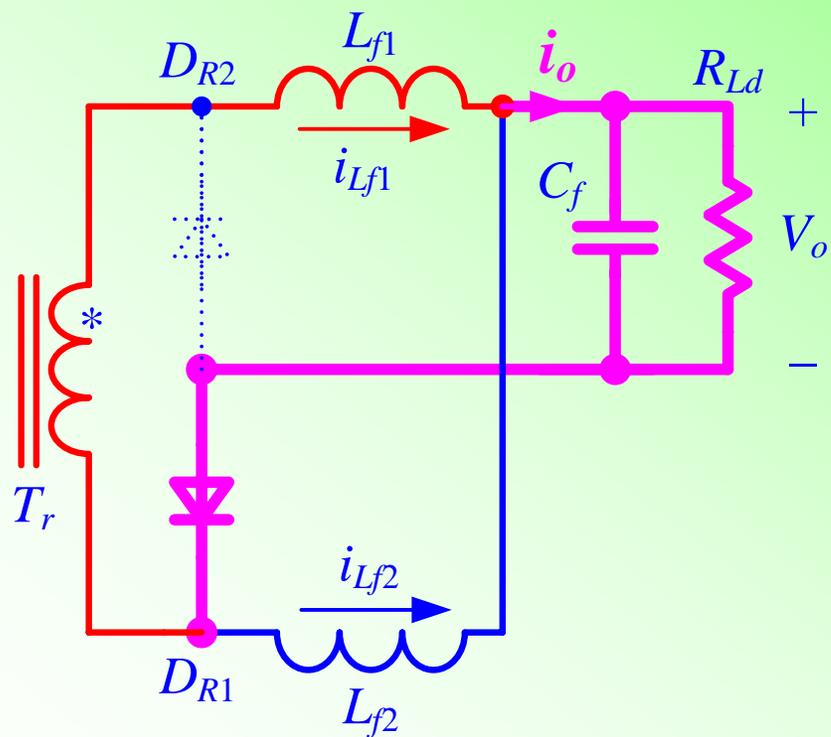

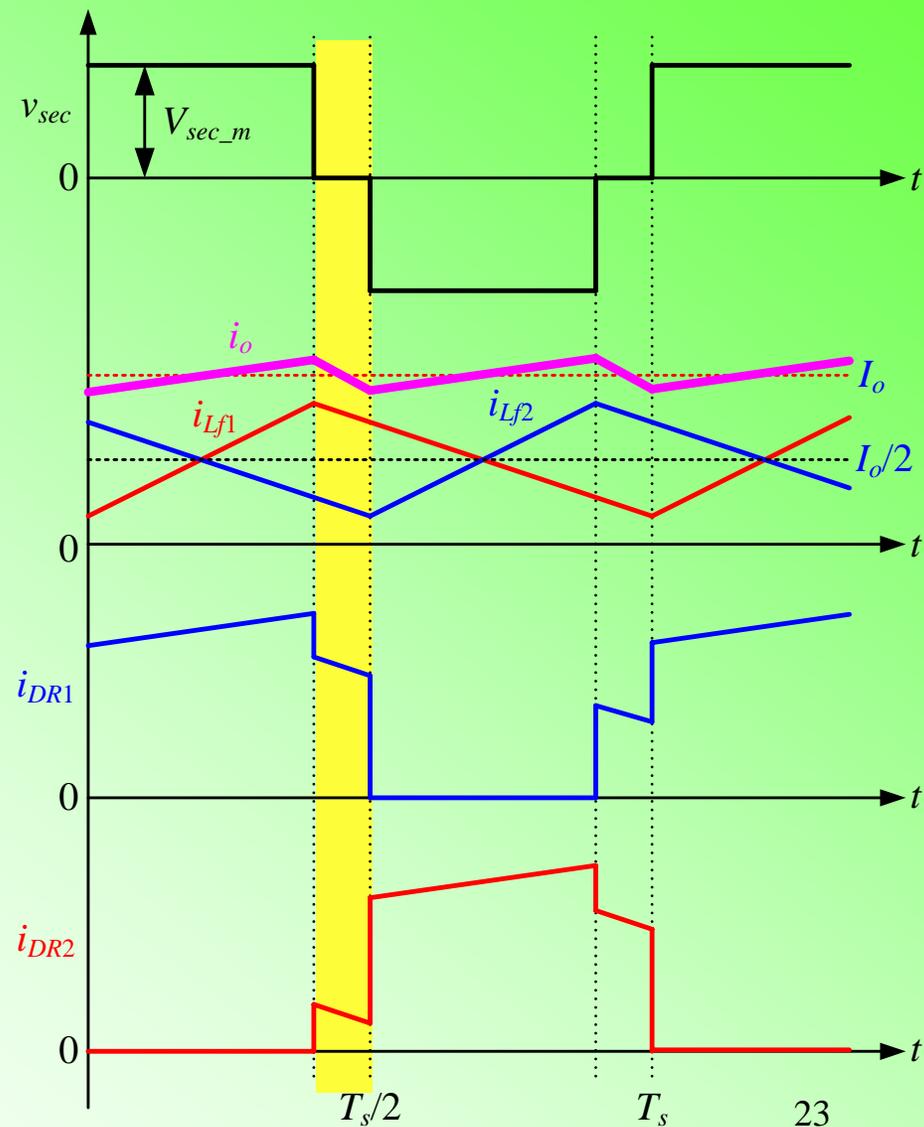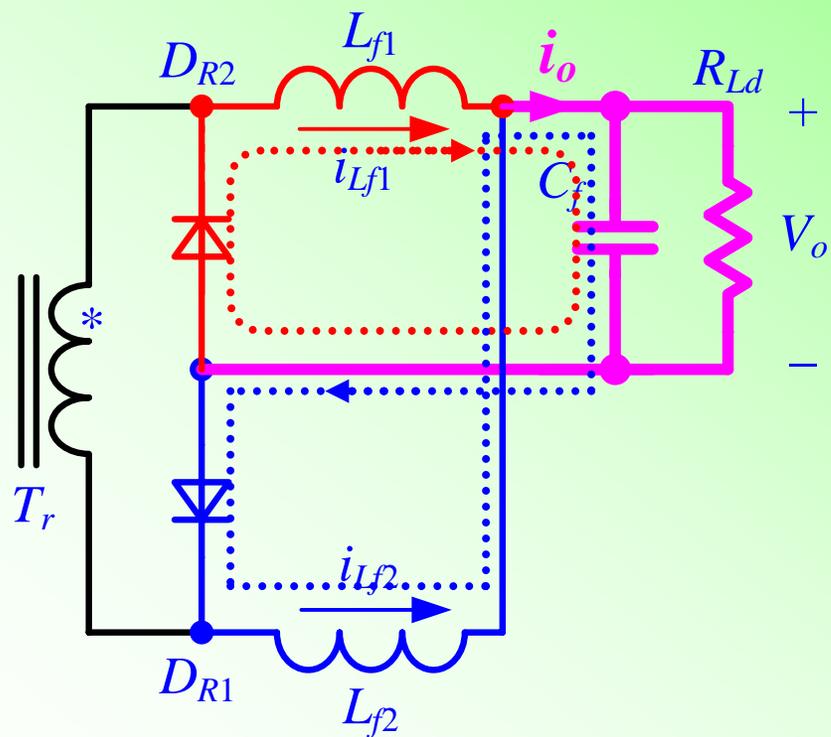

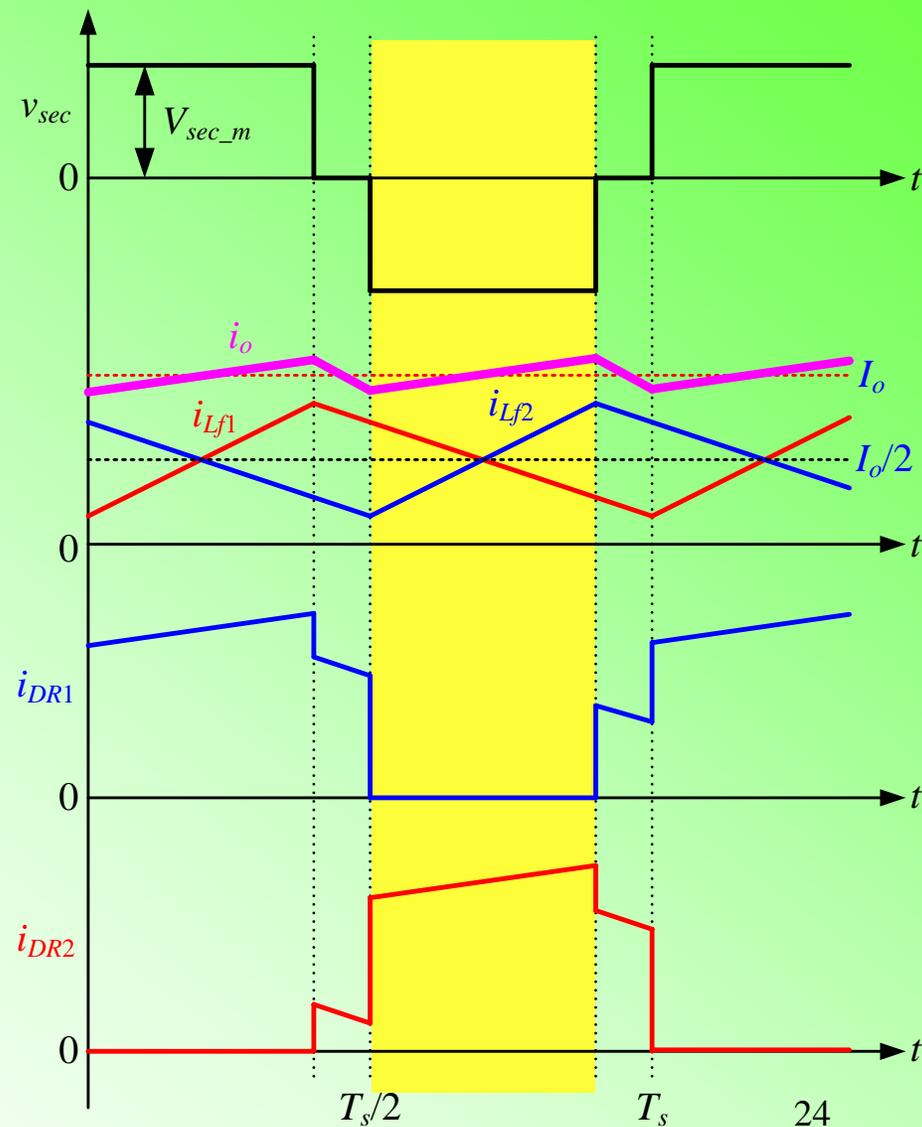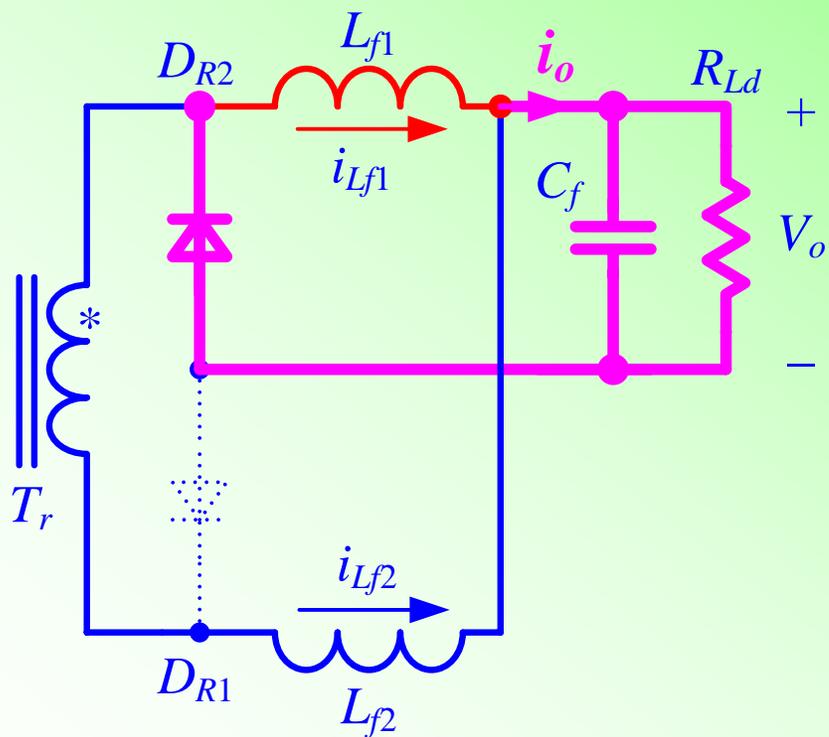

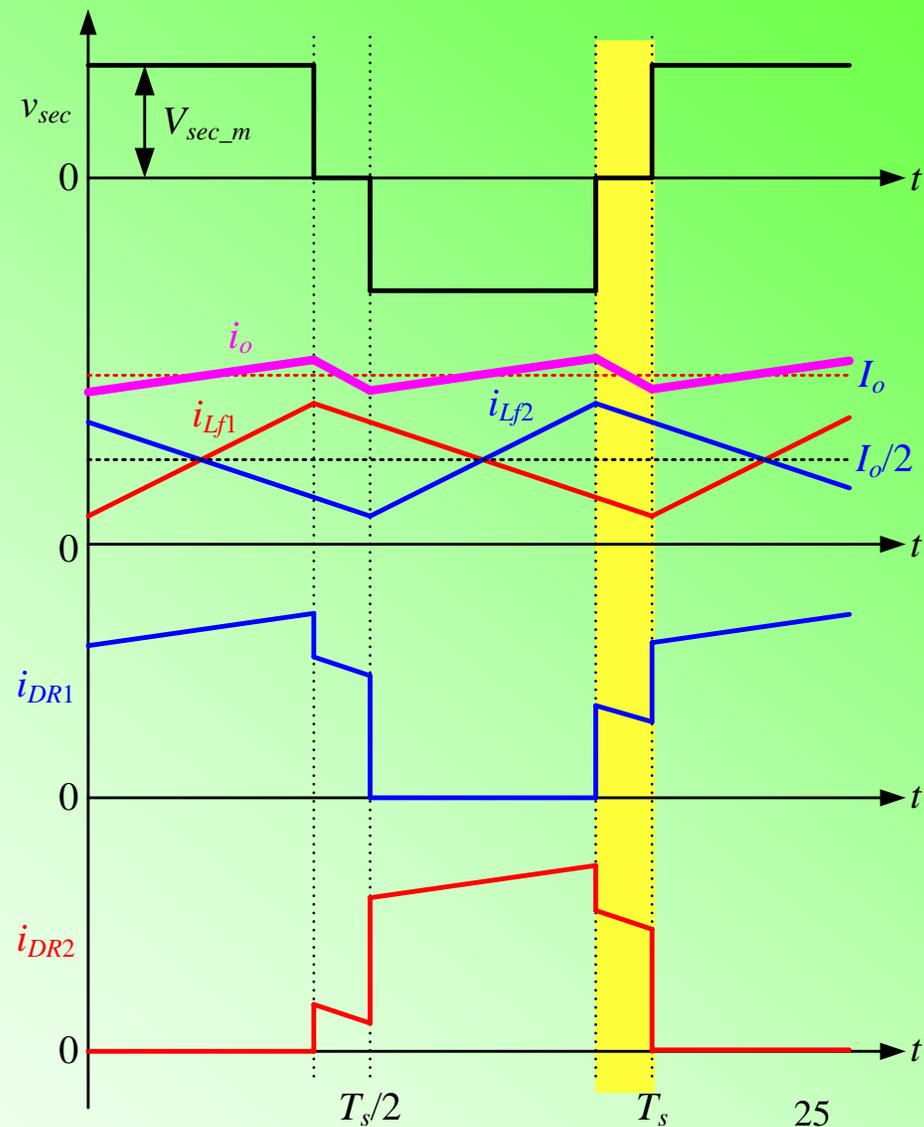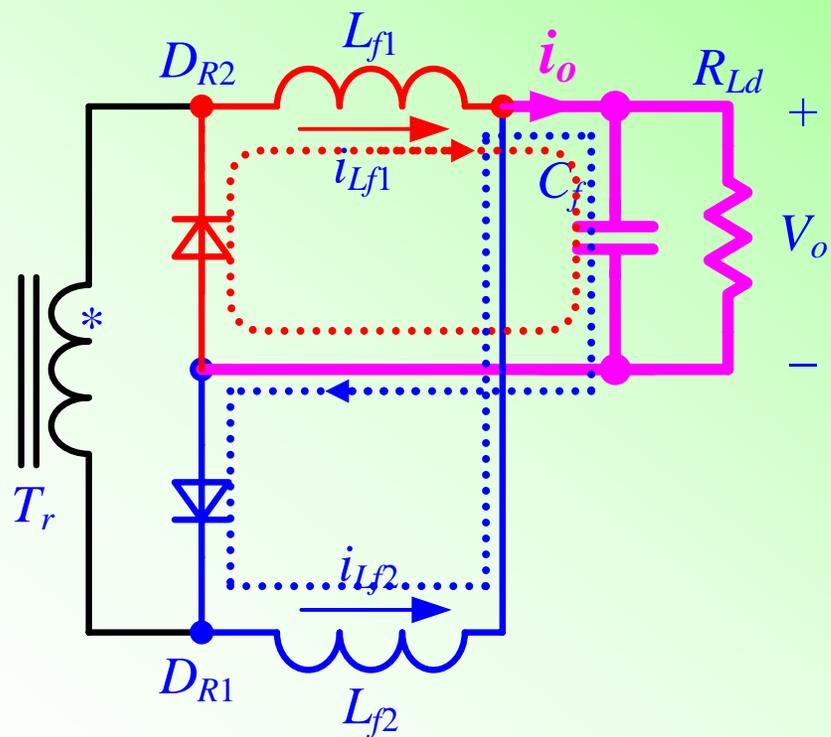



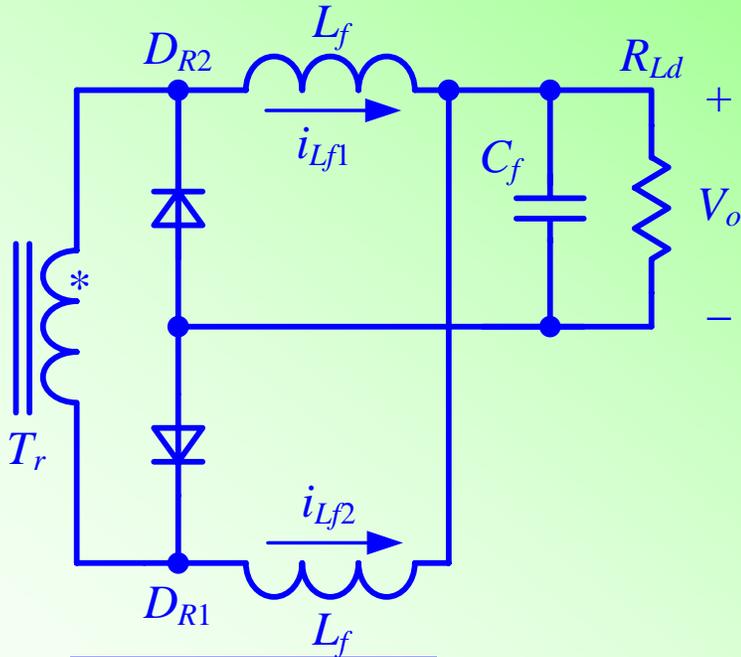


$$\frac{V_o}{V_{sec\_m}} = D_{half}$$



$$V_{DR1} = V_{DR2} = V_{sec\_m}$$



$$I_{DR1} = I_{DR2} = \frac{1}{2} I_o$$

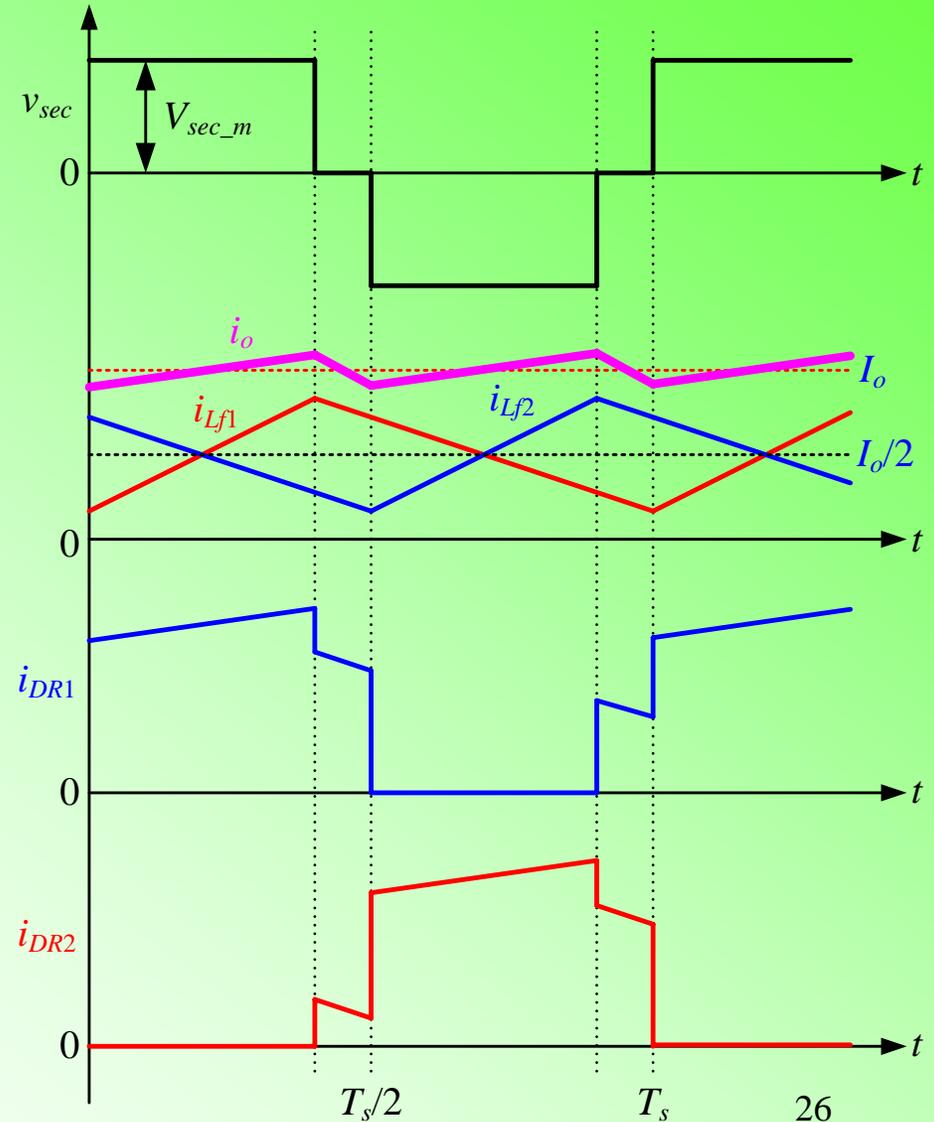

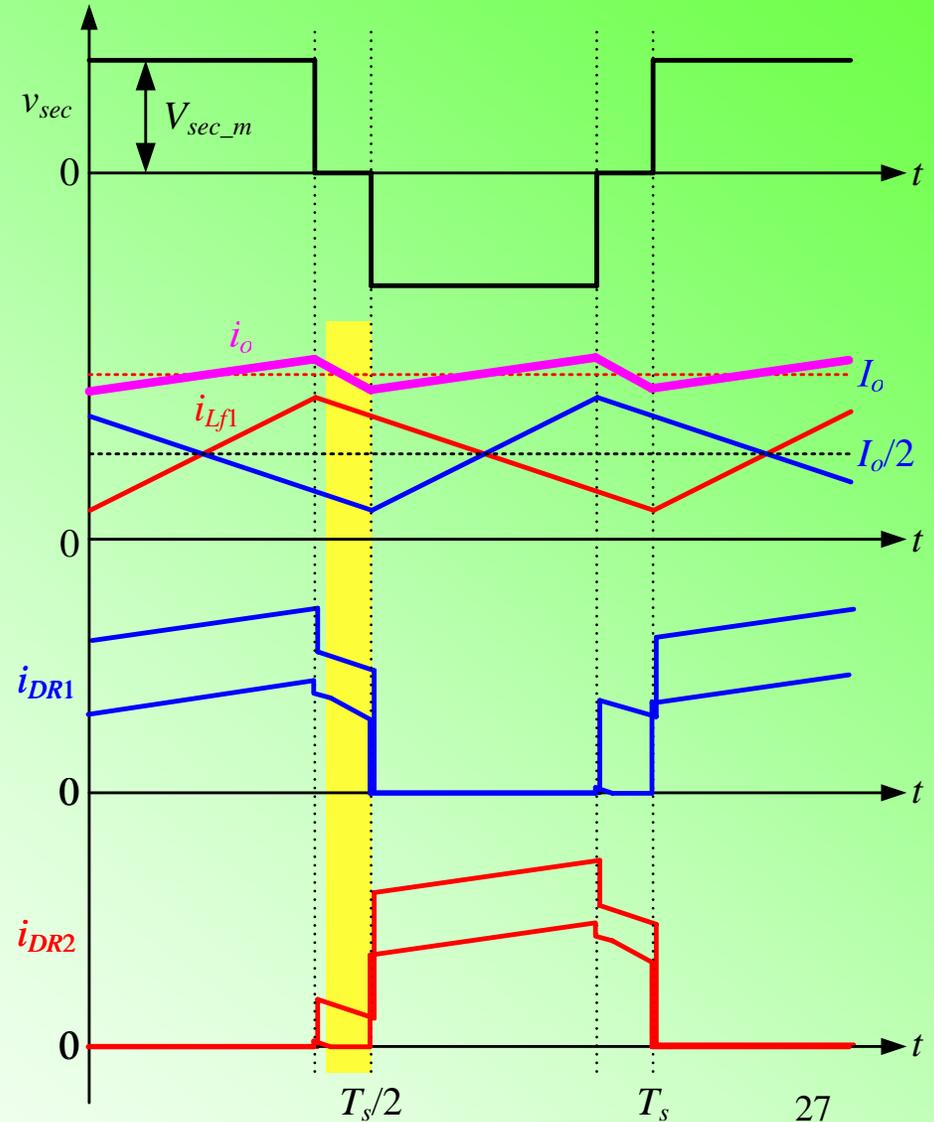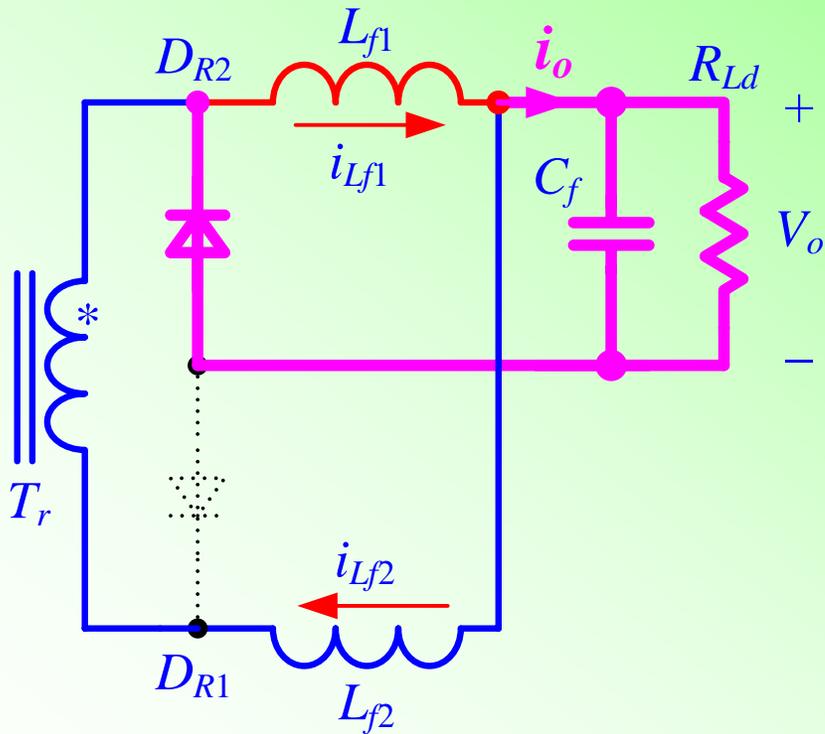

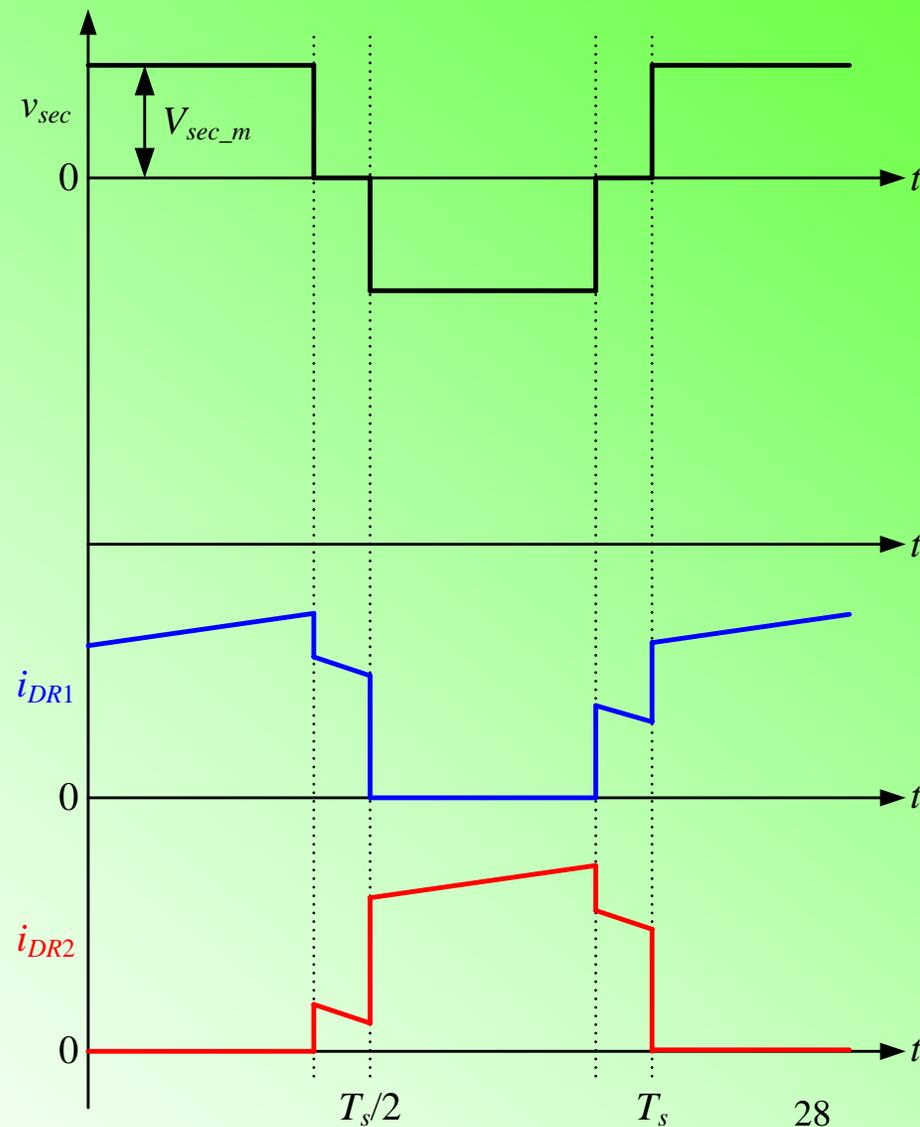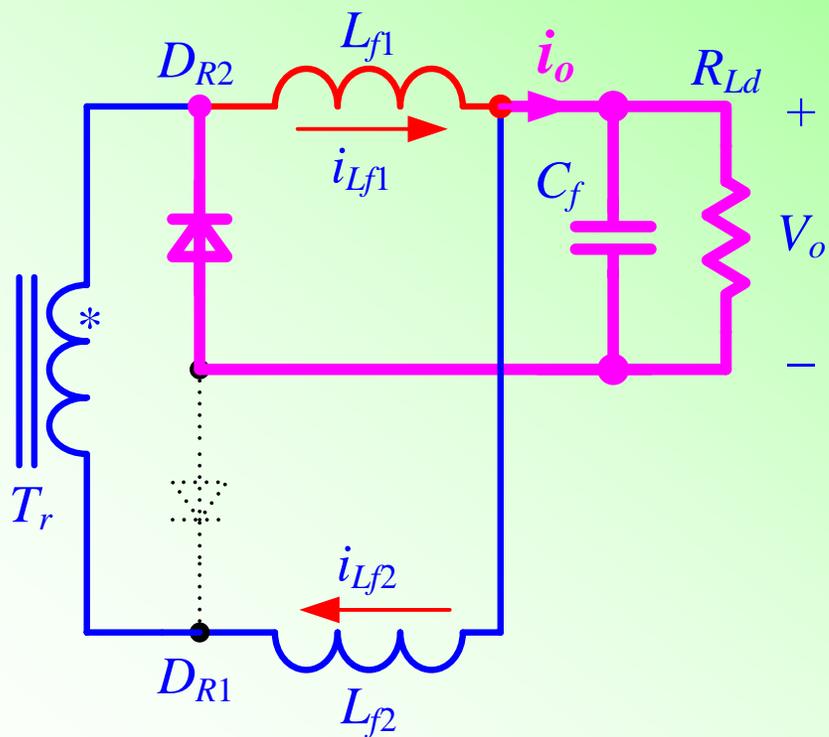Inductor current can flow in the negative direction.




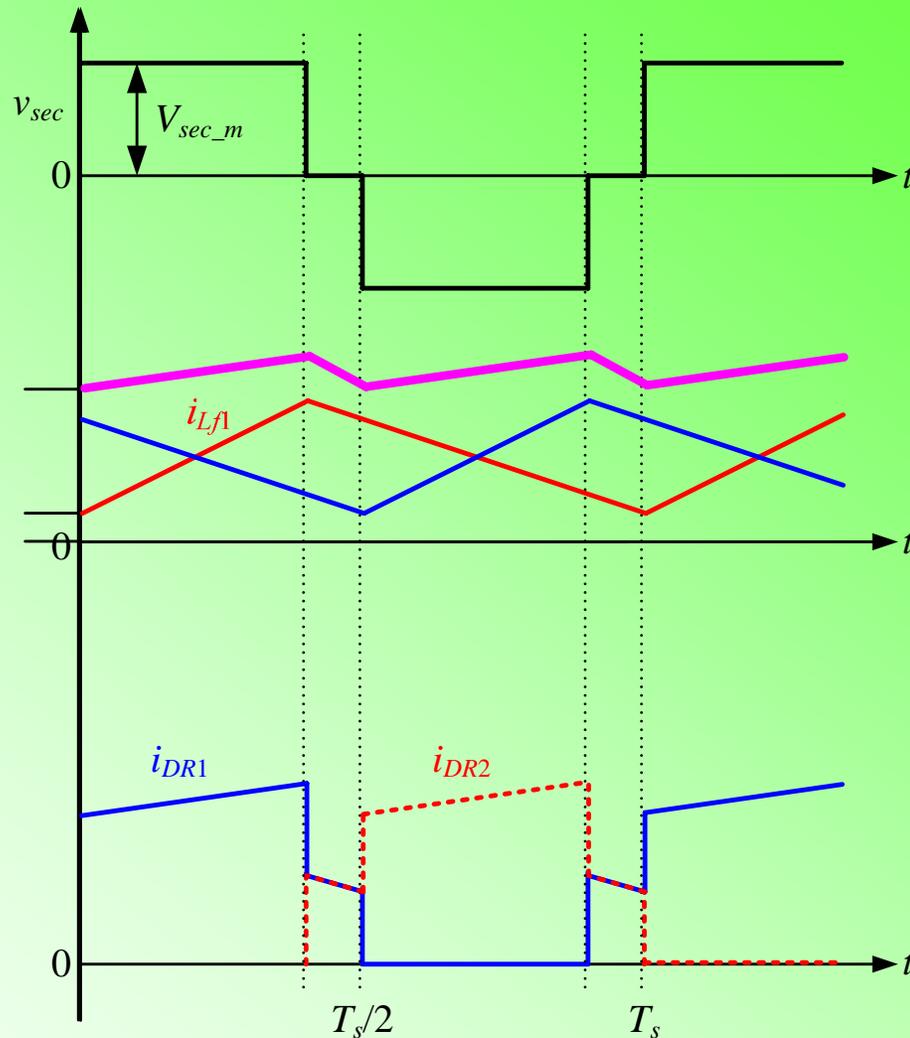
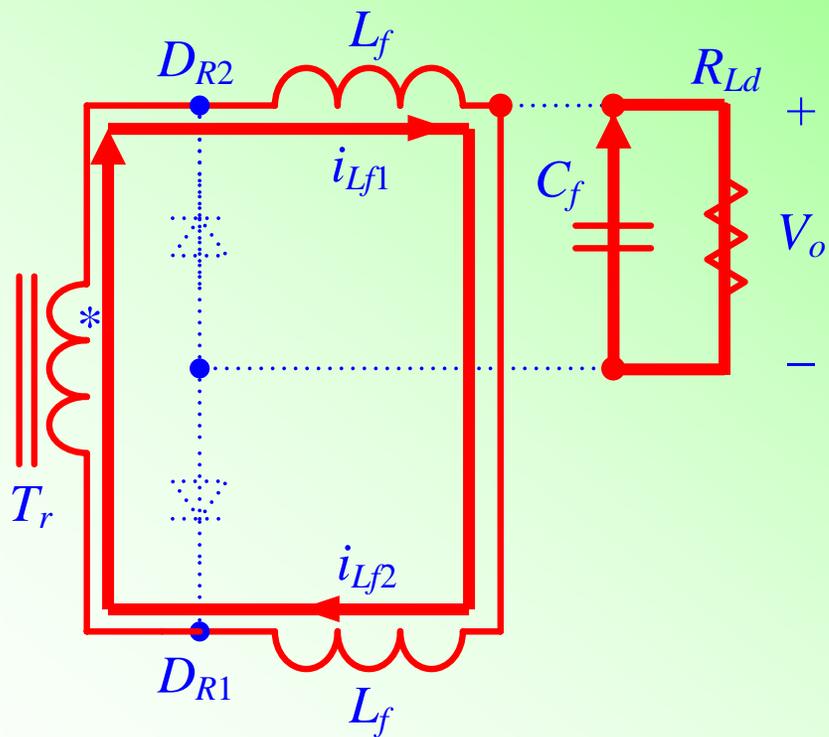


Inductor current can flow in the negative direction.

## Design a DC/DC converter

- Input Voltage:  $V_{in}$
- Output Voltage:  $V_o$
- Output Current:  $I_o$

Given the duty cycle of all the switches be 0.5

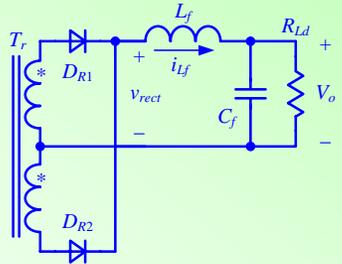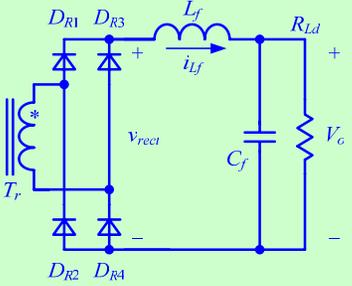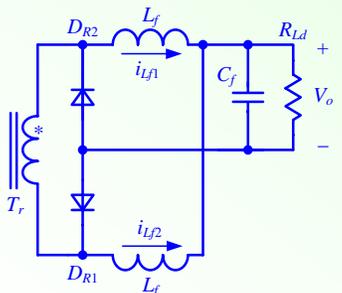Rectifier	Topology	Winding Ratio	Current Stress	Voltage Stress	No. of Diodes	Total Power of Diodes	Applications
Full-Wave		$K_0$	$I_o$	$2V_{in}/K_0$	2	$4V_{in}I_o$	Low output voltage
Full-Bridge		$K_0$	$I_o$	$V_{in}/K_0$	4	$4V_{in}I_o$	High output voltage
CDR		$K_0/2$	$I_o$	$2V_{in}/K_0$	2	$4V_{in}I_o$	Low output voltage, high current