

Six Basic DC/DC Converters

Presented by

Xinbo Ruan

Aero-Power Sci-tech Center
Nanjing University of Aeronautics & Astronautics

1. DC/DC
2. DC/AC
3. AC/DC
4. AC/AC

■ Non-Isolated DC-DC Converter: single-switch, dual-switch, and four-switch

◎ Single-switch: Buck, boost, buck-boost, Cuk, Zeta, and SEPIC;

◎ Dual-switch: Dual-switch buck-boost;

◎ Four-switch: Full-bridge converter.

■ Isolated DC-DC Converter: Single-Switch, Dual-Switch, and Four-Switch

◎ Single-switch: Forward, Flyback;

◎ Dual-switch: Forward, Flyback;


◎ Four-switch: Full-bridge converter.

Specifications:

■ $V_{in} = 100 \text{ V}$

■ $V_o = 50 \text{ V}$

■ $I_o = 10 \text{ A}$

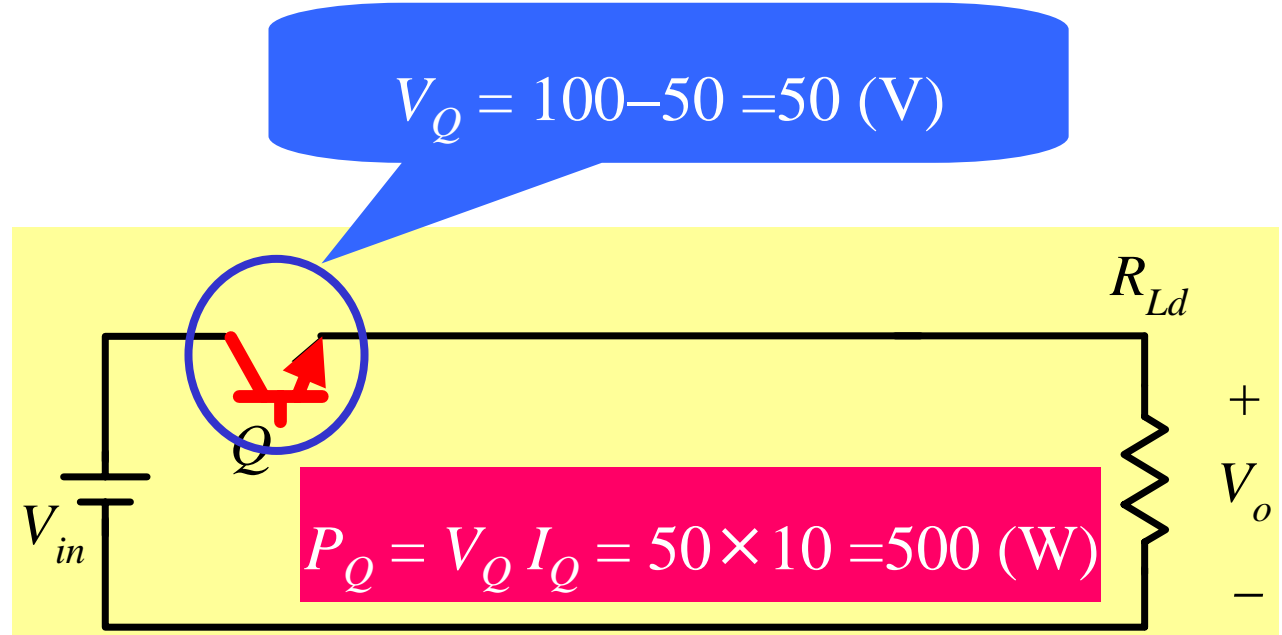

Too ***Low***
Efficiency!!!

$$\eta = V_o I_o / V_{in} I_o = V_o / V_{in}$$

$$= 50 / 100 = 50\%$$

Switching-Mode DC Converter

Specifications:


■ $V_{in} = 100 \text{ V}$

■ $V_o = 50 \text{ V}$

■ $I_o = 10 \text{ A}$


Q on: $P_{Q(on)} = V_{ces} I_o \cong 0$

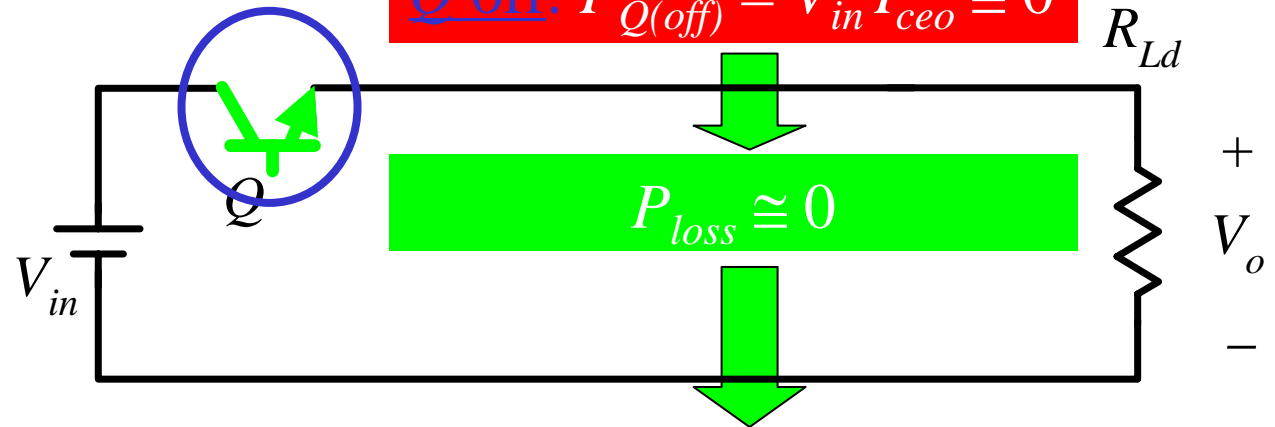Q off: $P_{Q(off)} = V_{in} I_{ceo} \cong 0$




$\eta \cong 100\%$


High Efficiency!!!

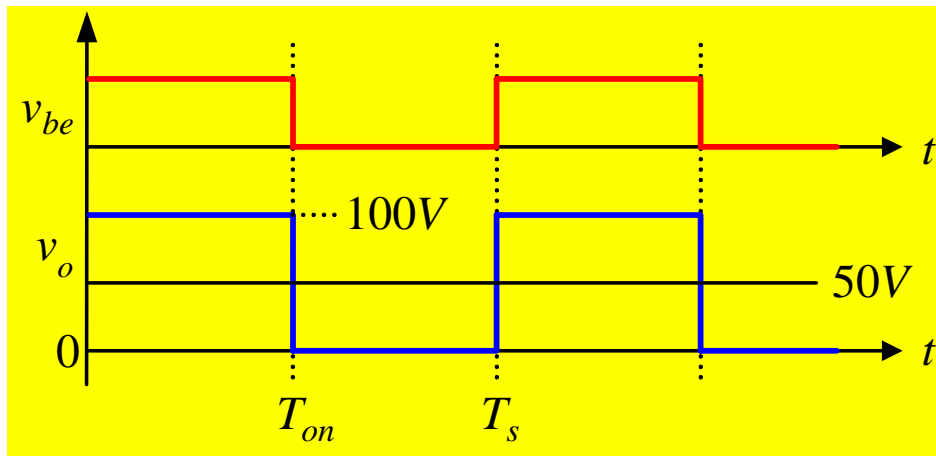


Derivation of Buck Converter

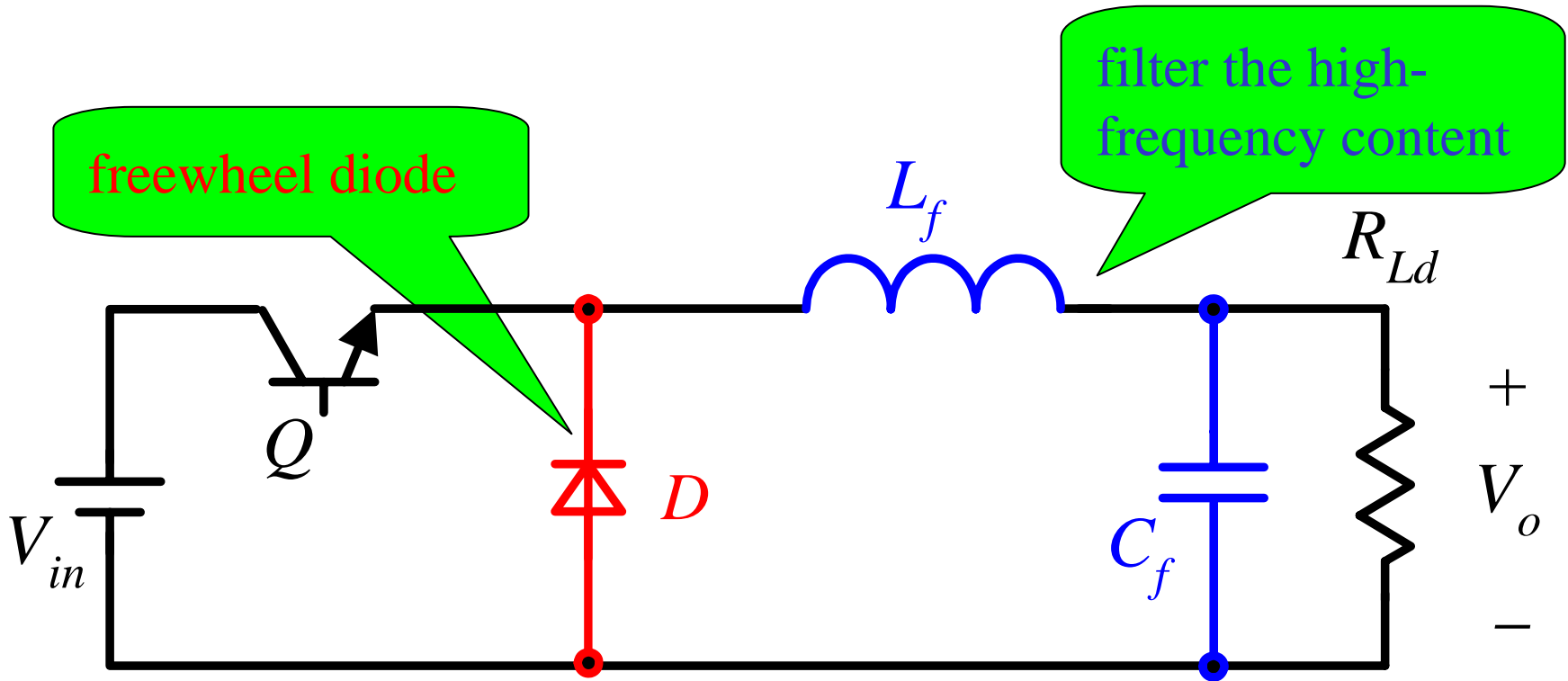

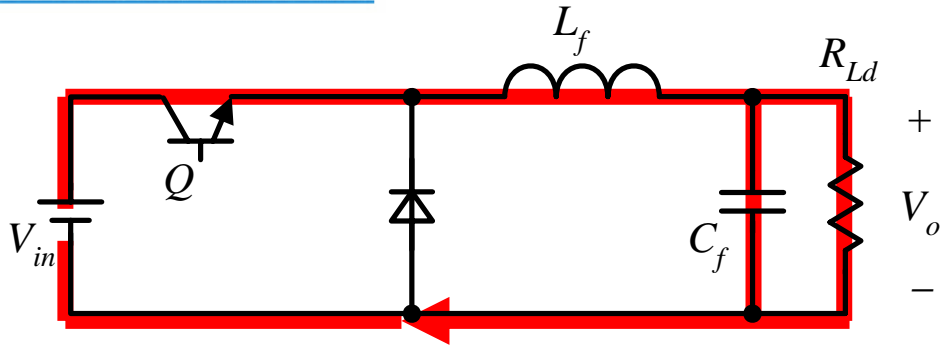Operation Principle of Buck Converter: CCM




Q ON




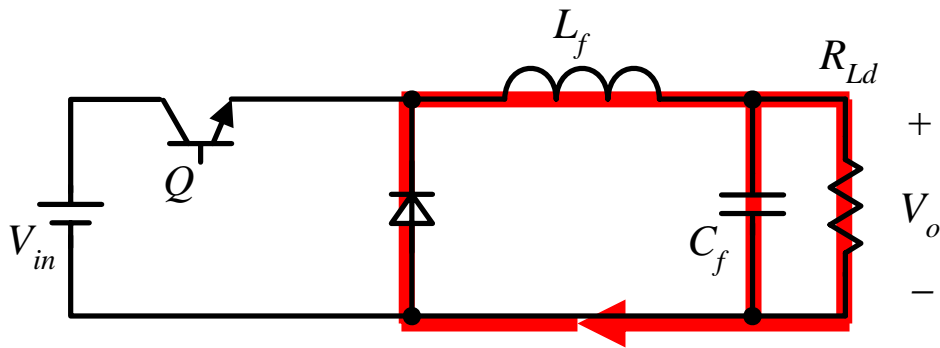


Q OFF


$$V_o / V_{in} = D$$

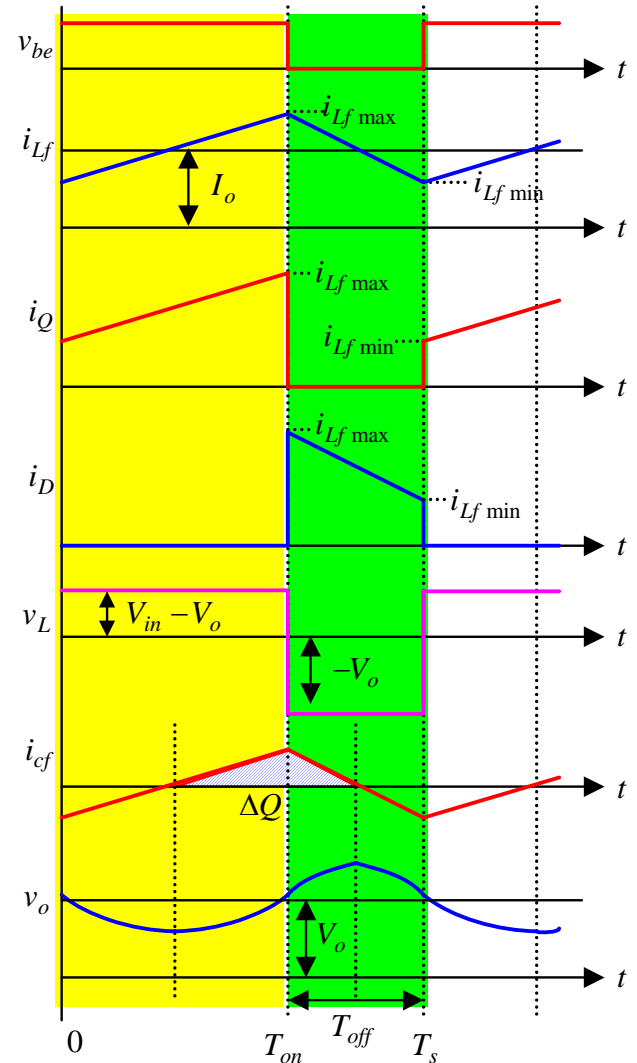

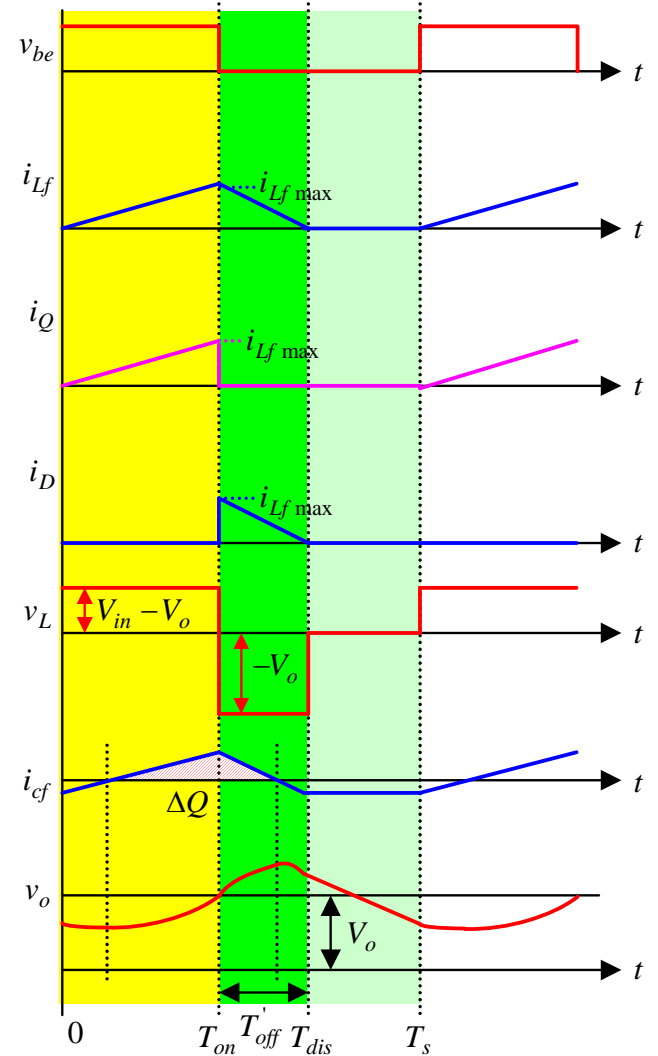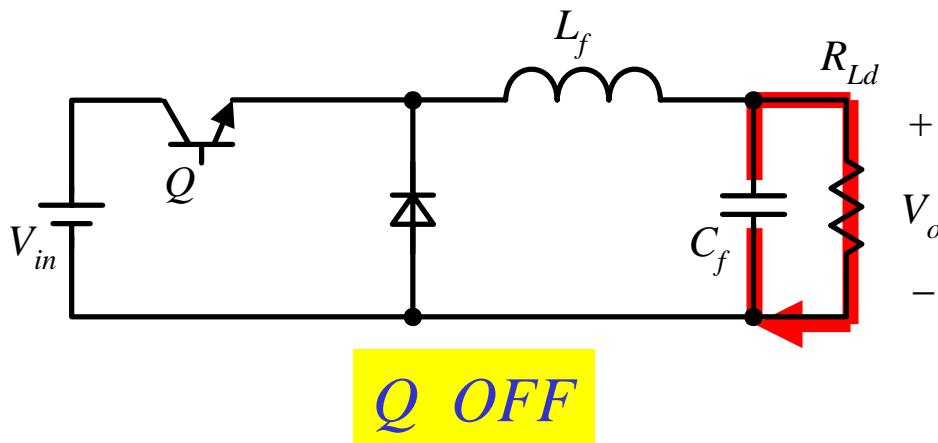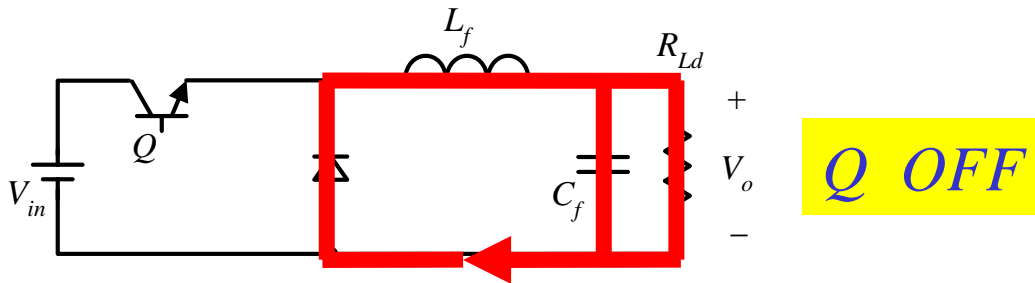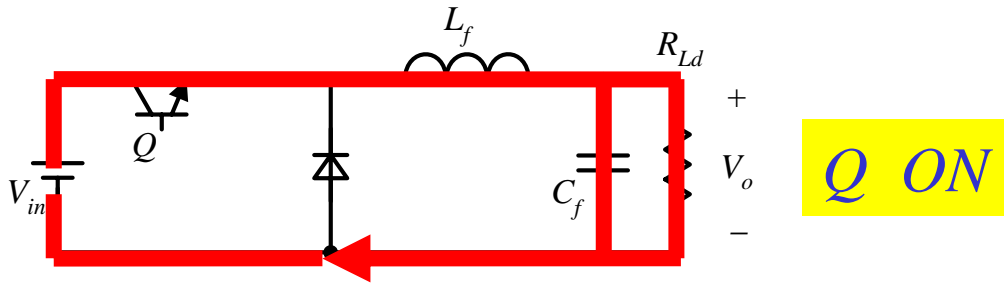
Operation Principle of Buck Converter: DCM




Voltage Conversion Ratio

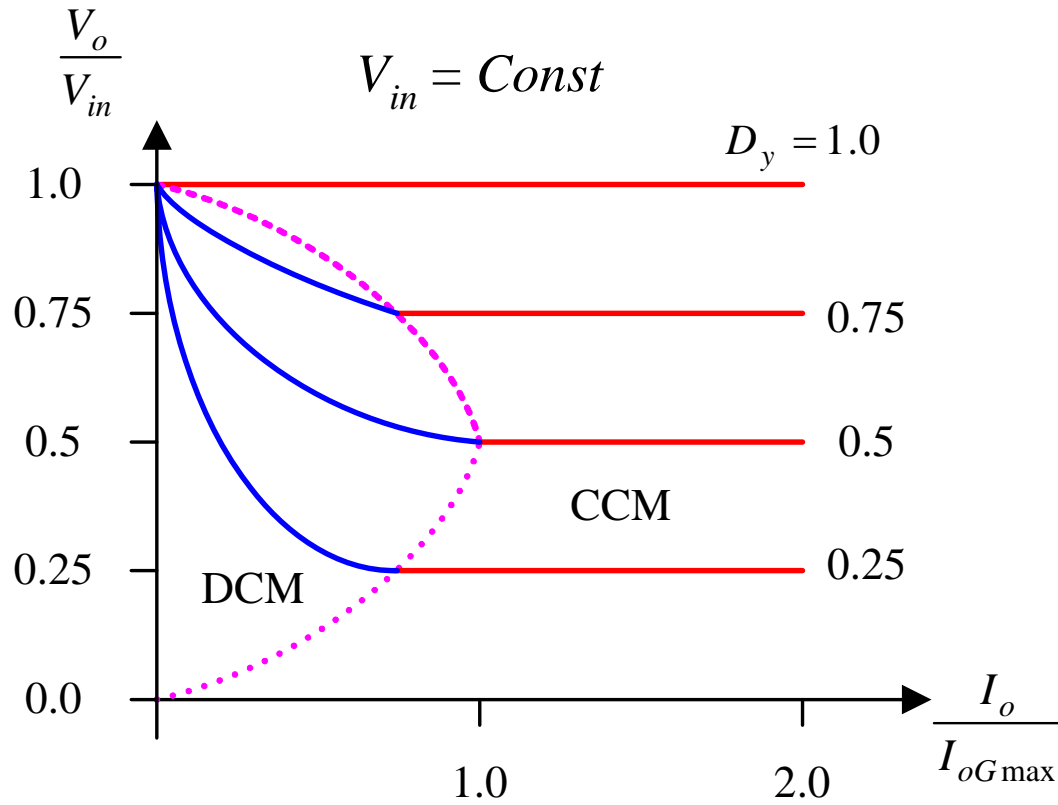

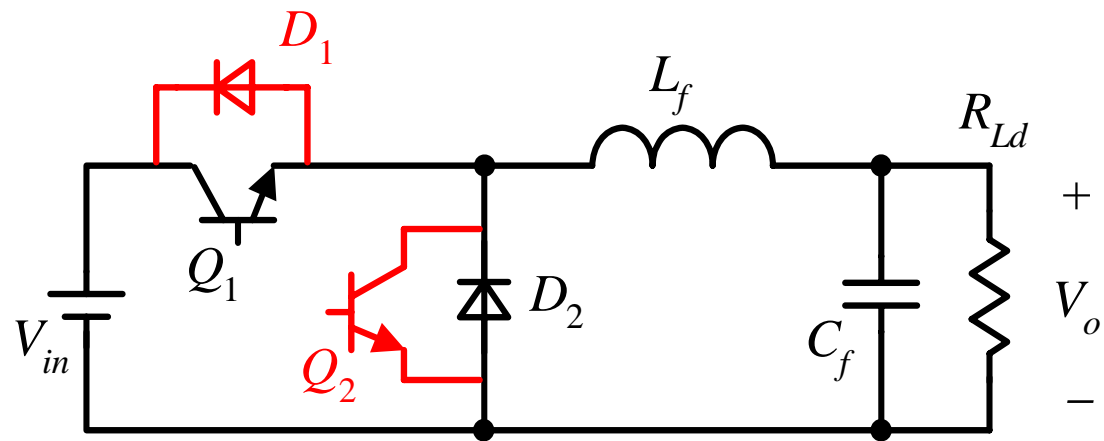
Buck Converter with Bi-Direction Switches



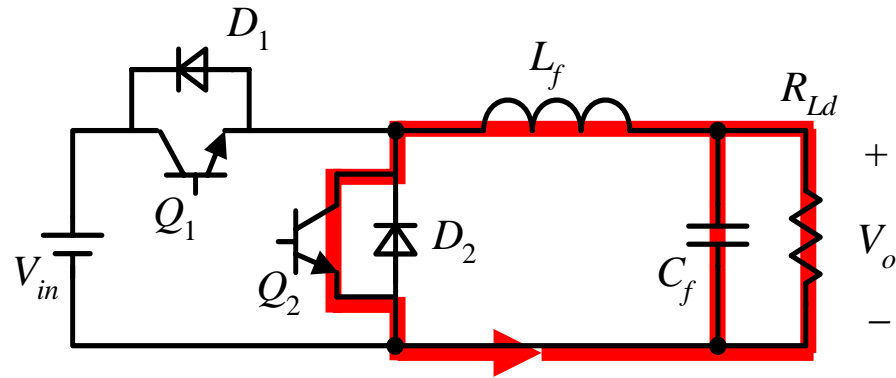
Buck Converter with Bi-Direction Switches




Q_1 OFF;
 Q_2 ON.

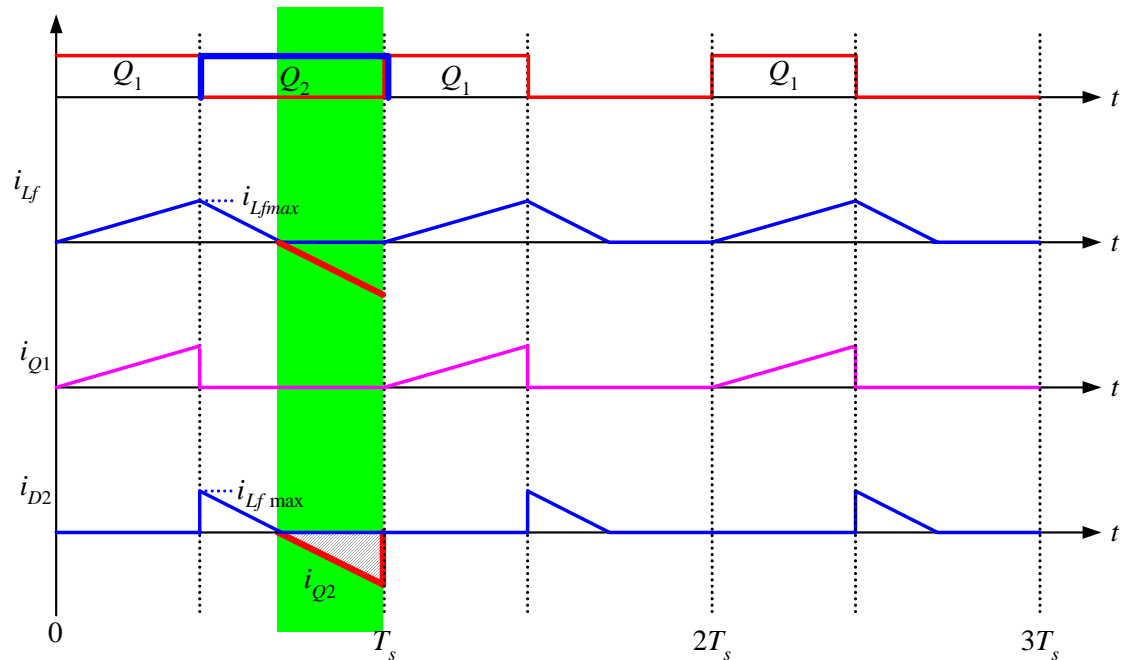

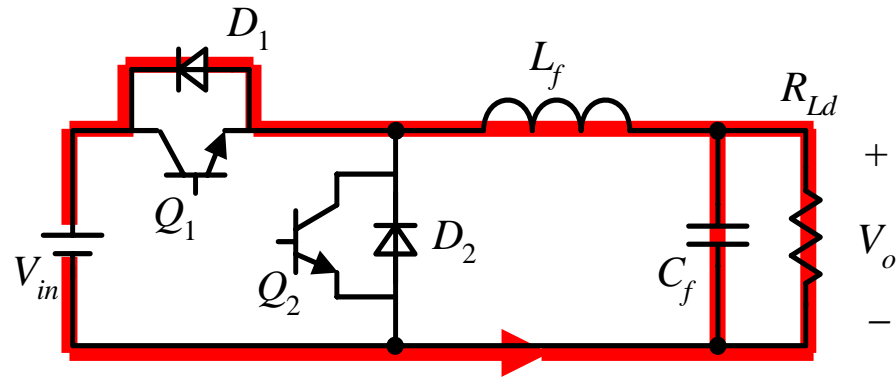
Buck Converter with Bi-Direction Switches




Q_1 ON
(D_1 Conduct);
 Q_2 OFF.

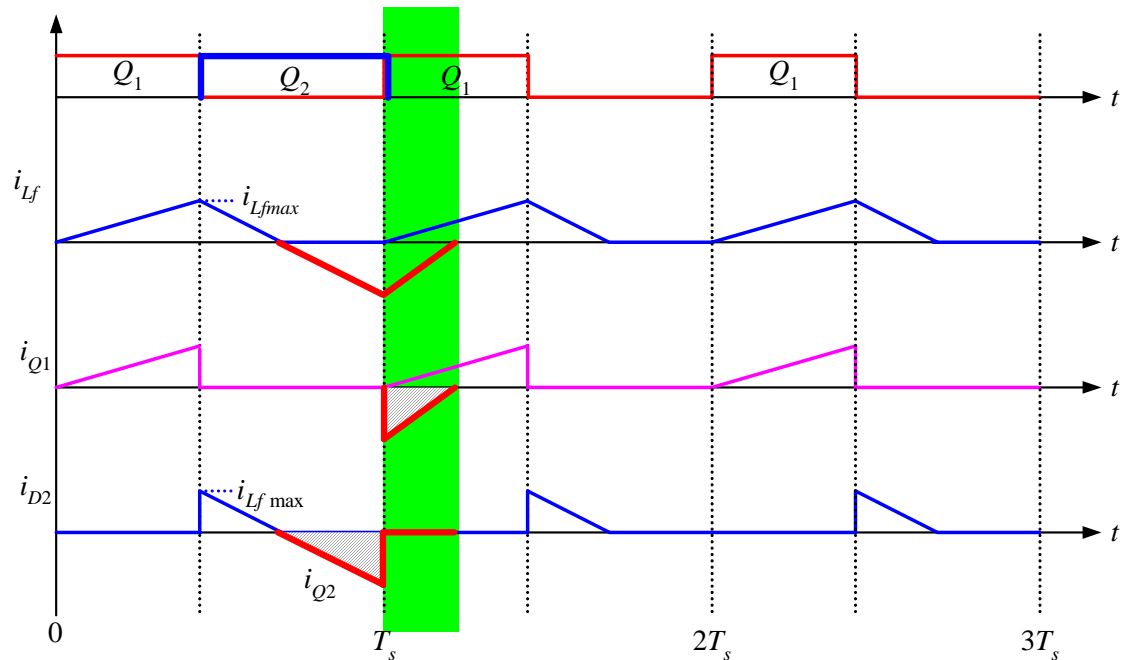


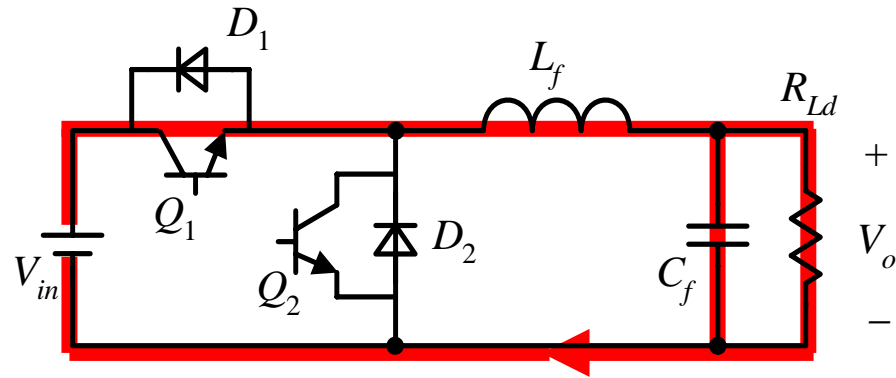
Buck Converter with Bi-Direction Switches







Q_1 ON;
 Q_2 OFF.

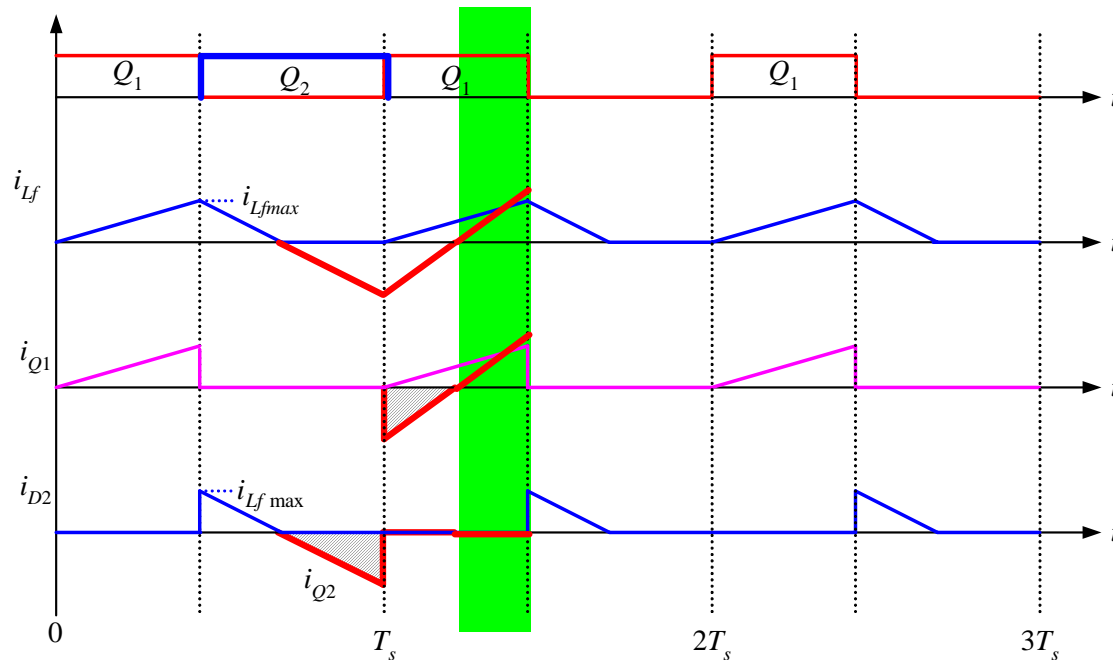

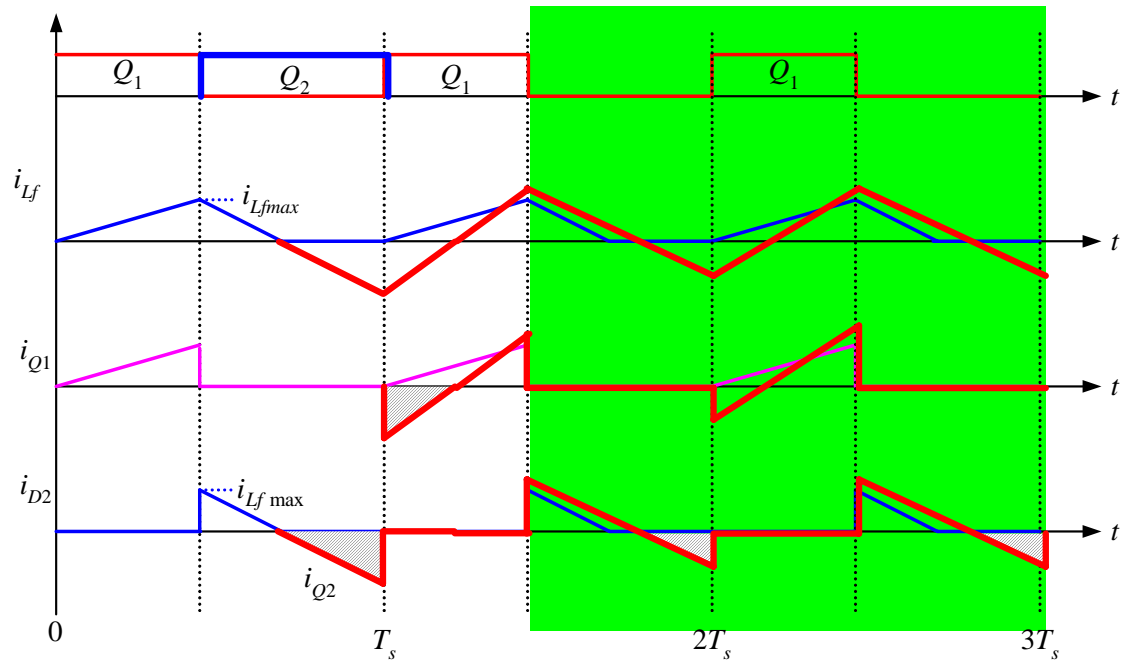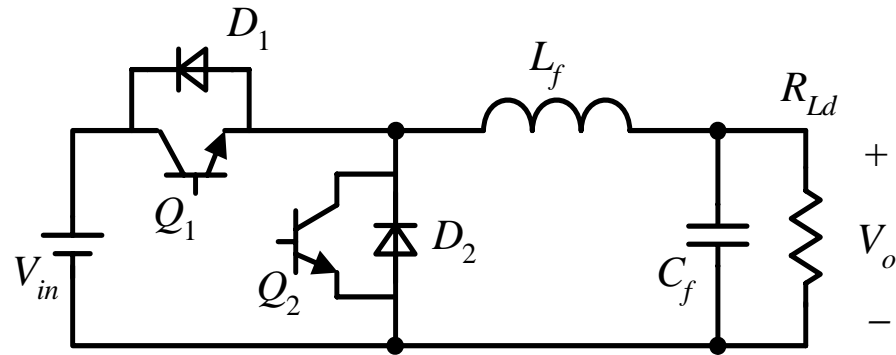
Buck Converter with Bi-Direction Switches



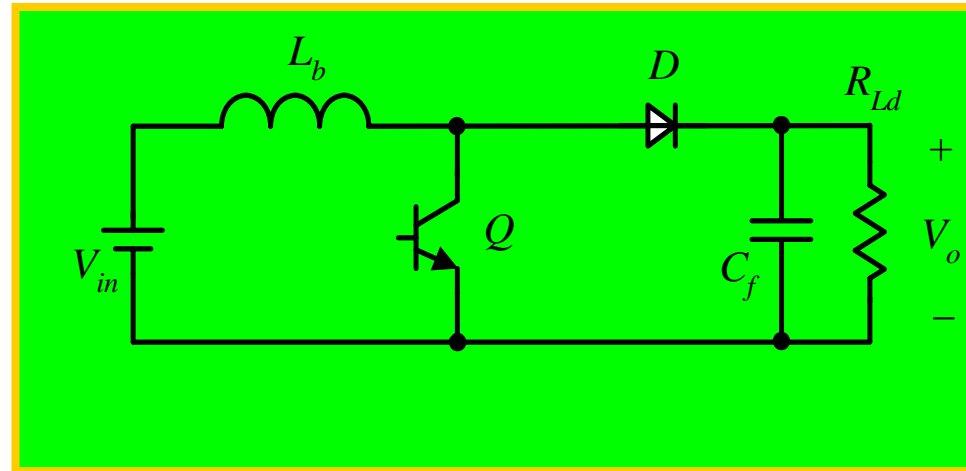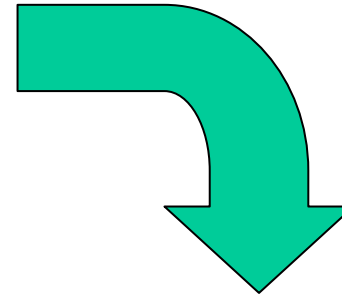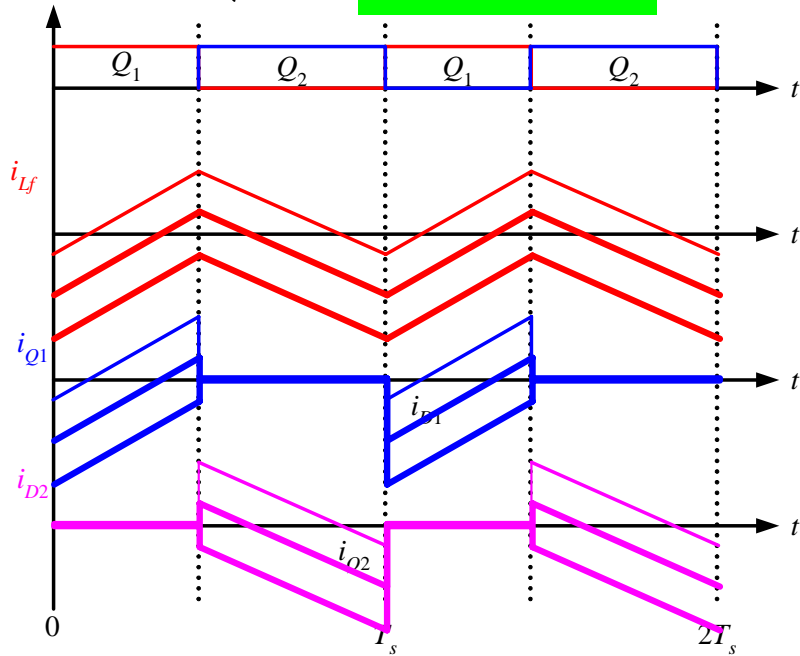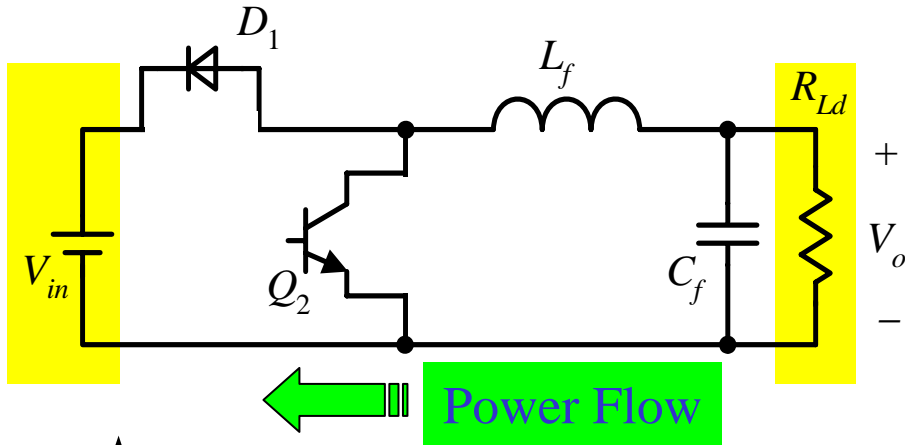Buck Converter with Bi-Direction Switches




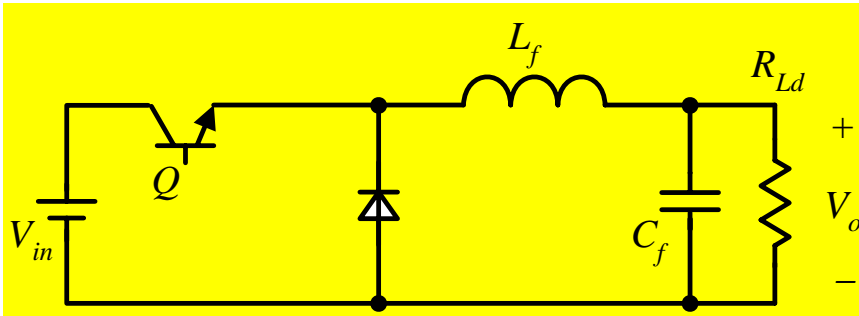Voltage Conversion Ratio of Boost Converter




$$\frac{V_o}{V_{in}} = D$$

D is the duty cycle of Q_1

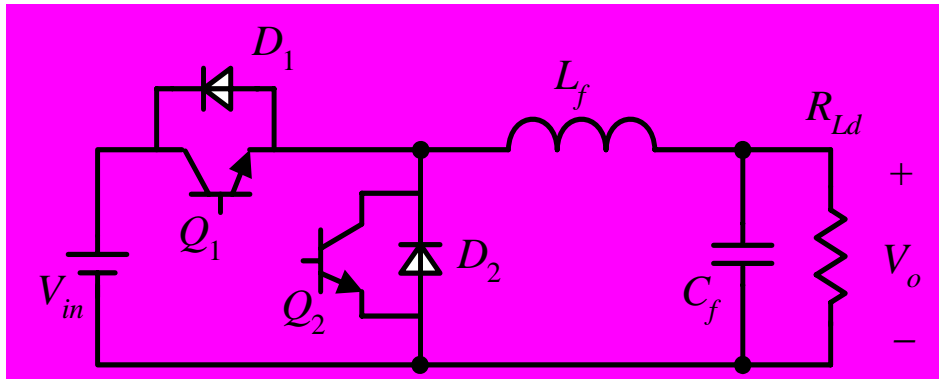


$$\frac{V_o}{V_{in}} = D$$

D is the duty cycle of Q_1

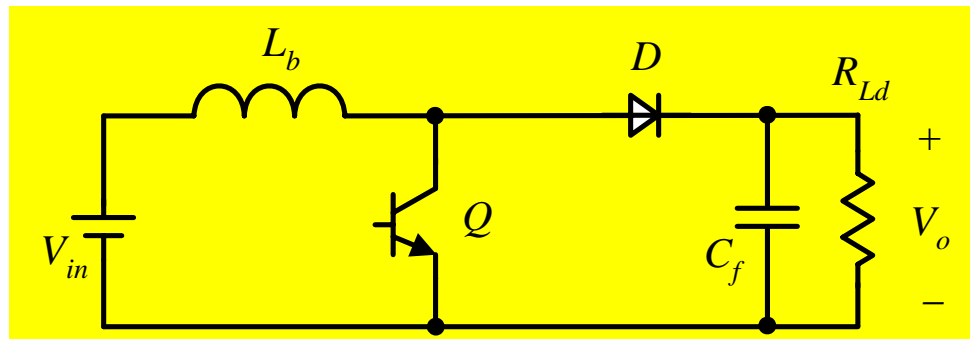


$$\frac{V_{in}}{V_o} = 1 - D$$

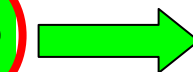


$$\frac{V_o}{V_{in}} = \frac{1}{1 - D}$$

D is the duty cycle of Q_2


Why Buck-Boost Converter?

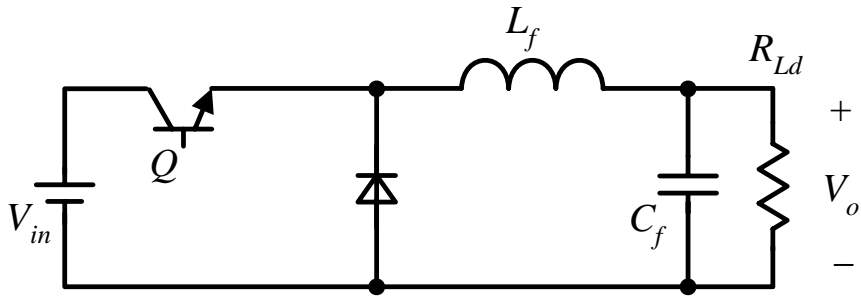

$$V_o < V_{in}$$


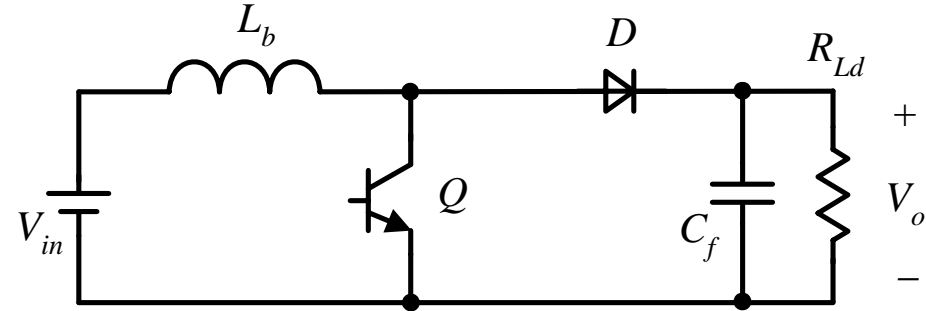


$$V_o > V_{in}$$





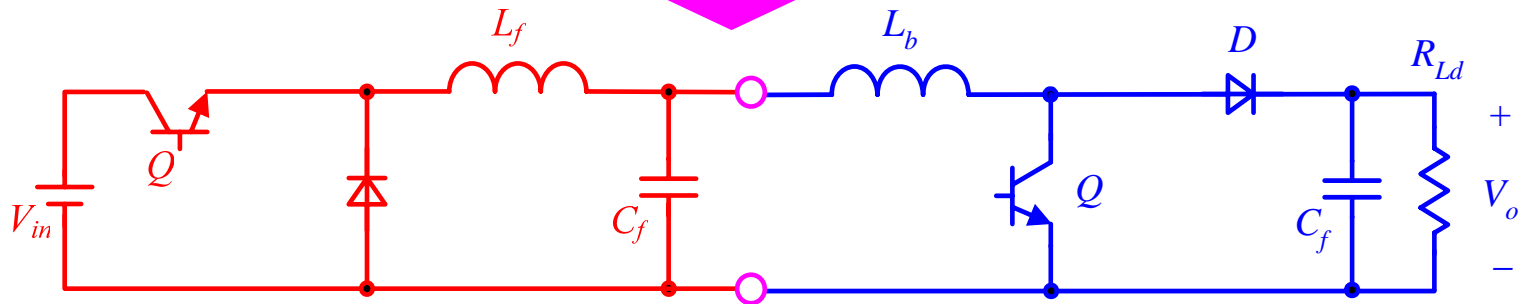


$$\frac{V_o}{V_{in}} = \frac{D_1}{1 - D_2}$$


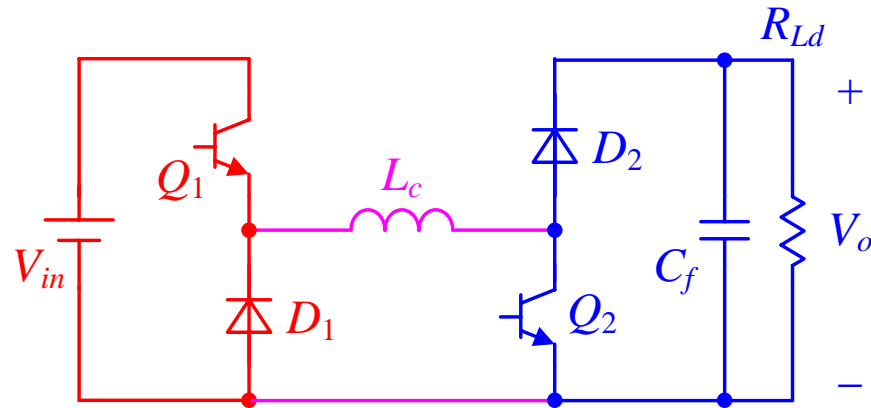
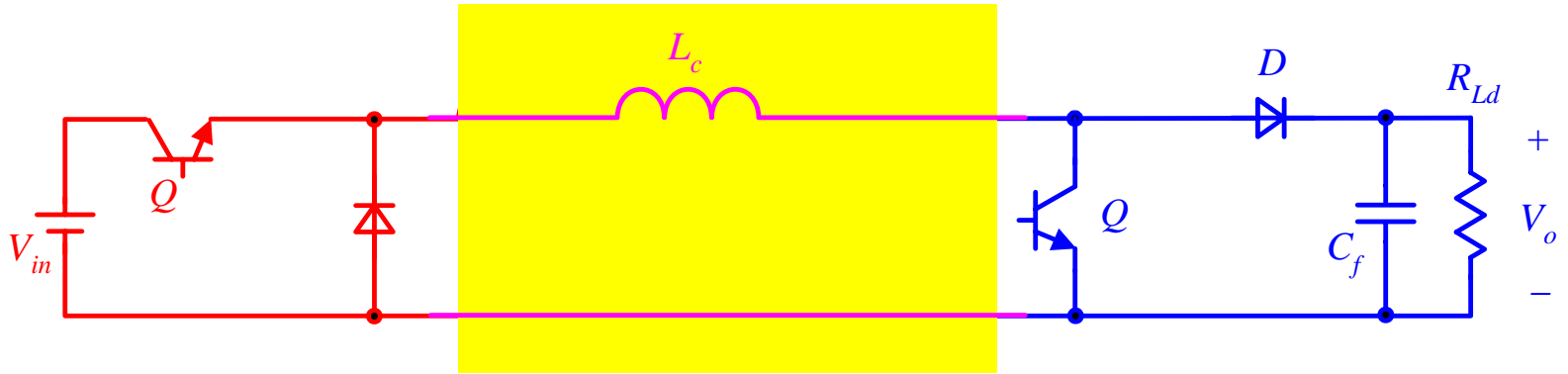
Simplification of Buck-Boost Converter (1)



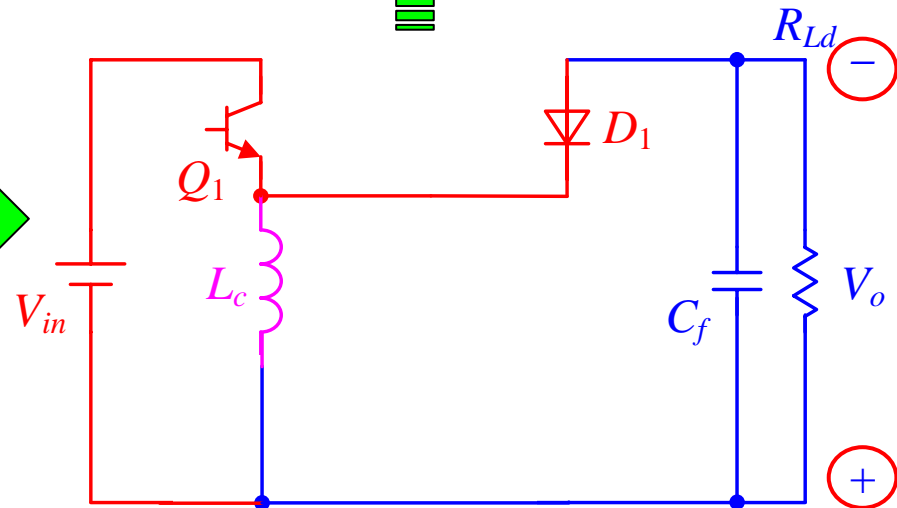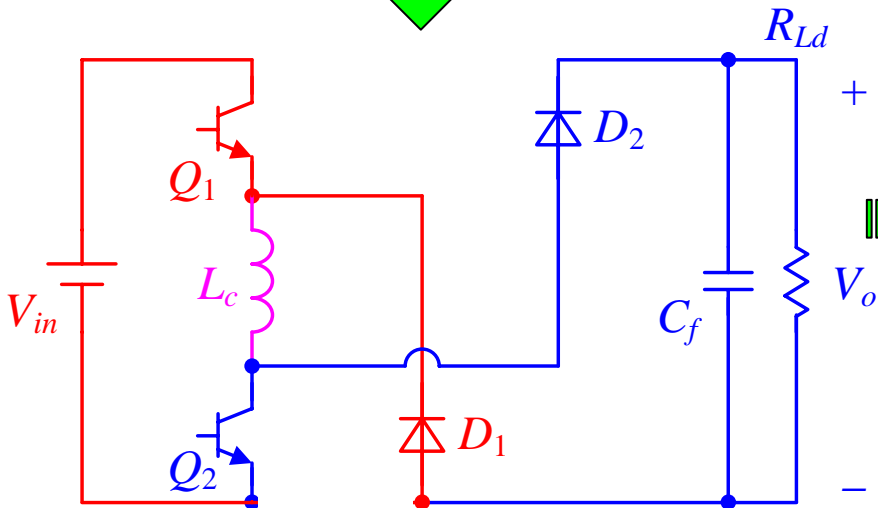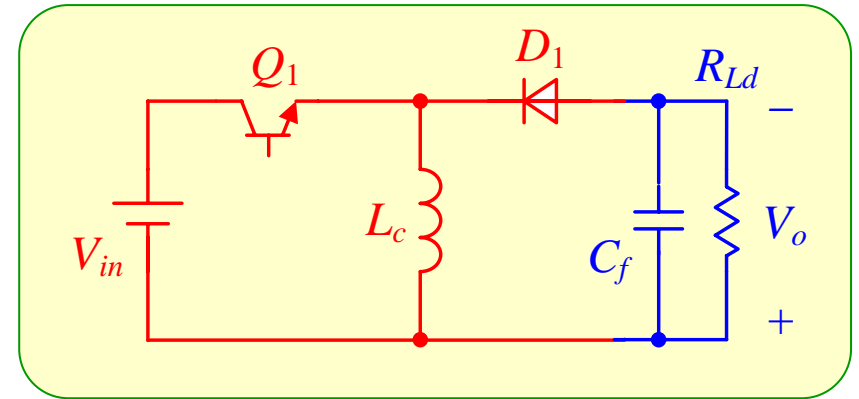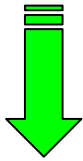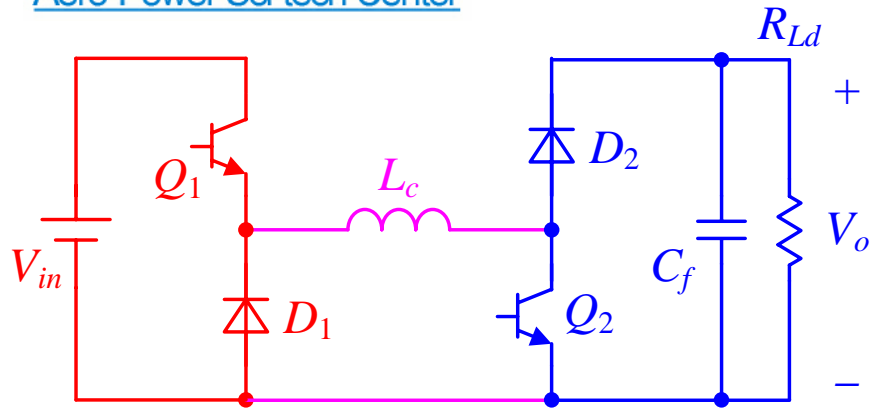Simplification of Buck-Boost Converter (2)






How to get Cuk?

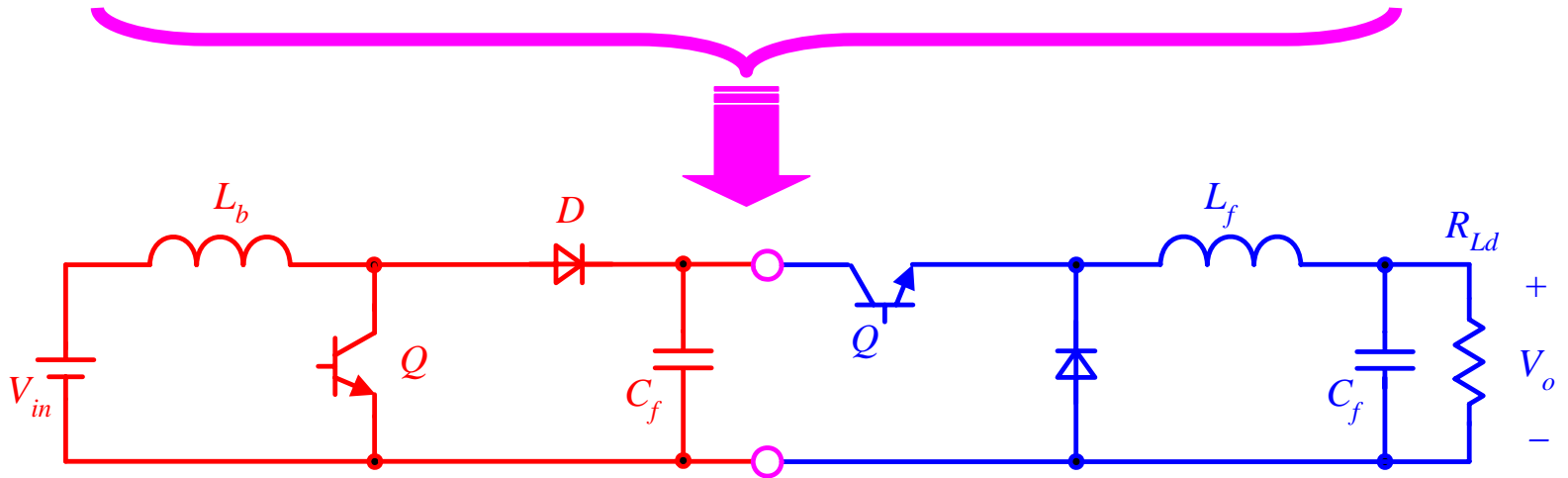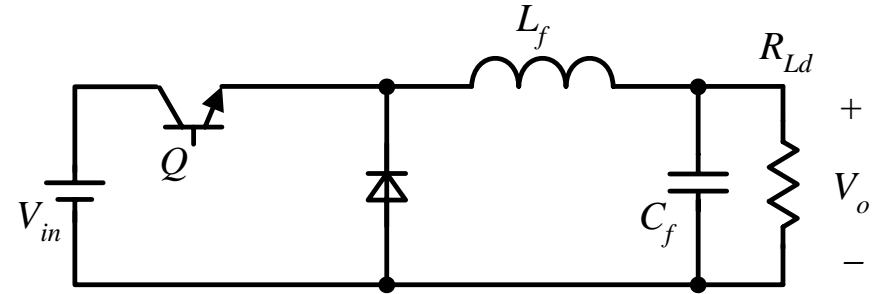
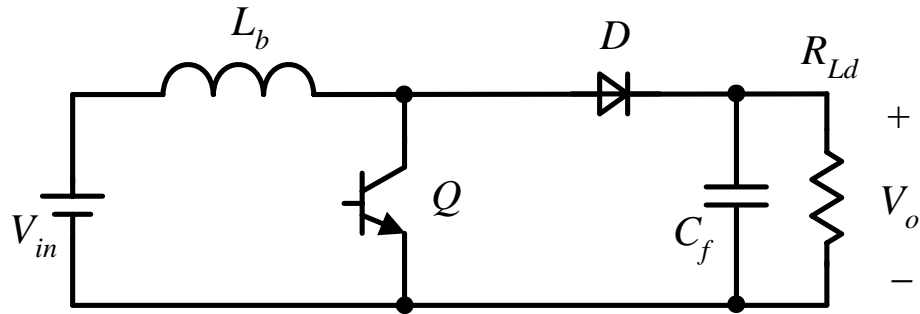


$$\frac{V_o}{V_{in}} = \frac{D_1}{1 - D_2}$$

Derivation of Cuk

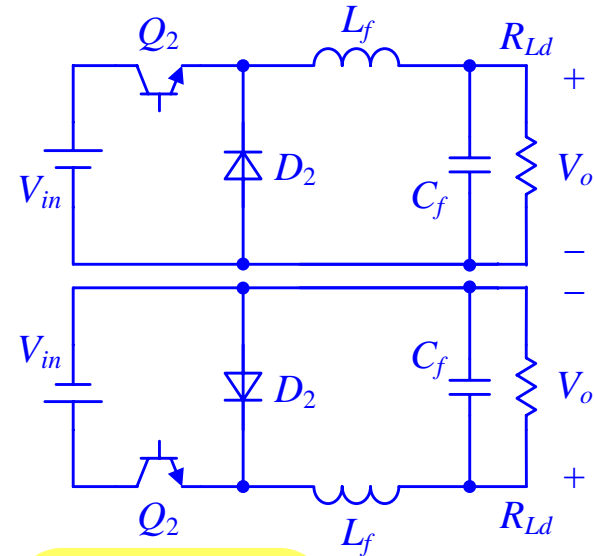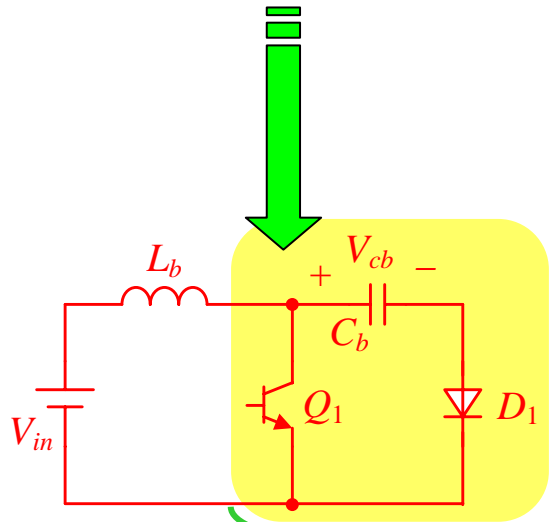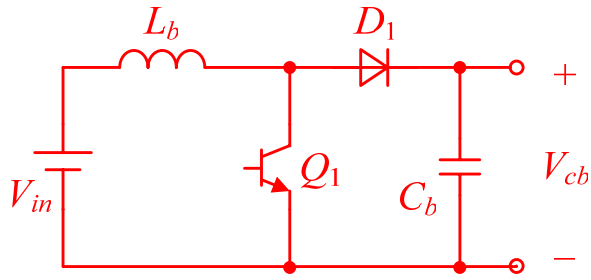


镜像翻转

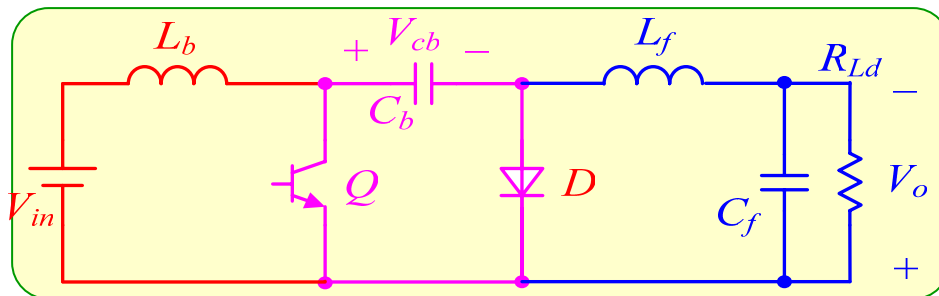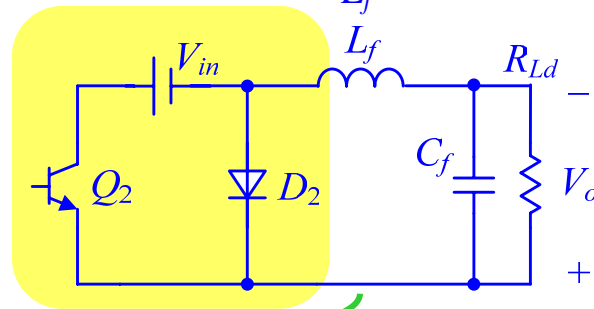

Derivation of Zeta

☹ Negative output voltage



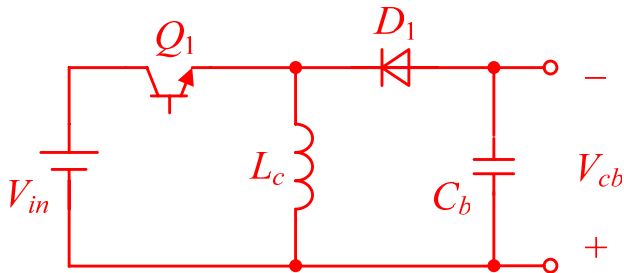


$$\frac{V_{cb}}{V_{in}} = \frac{D}{1-D}$$

☺ Positive output voltage

$$V_o = \frac{D}{1-D} V_{in} = \left(1 + \frac{D}{1-D}\right) D V_{in}$$
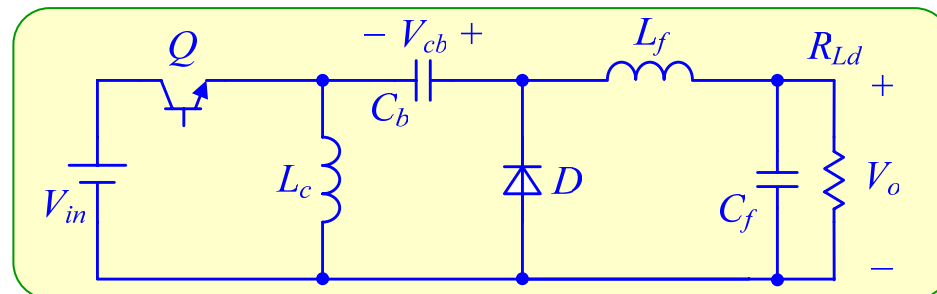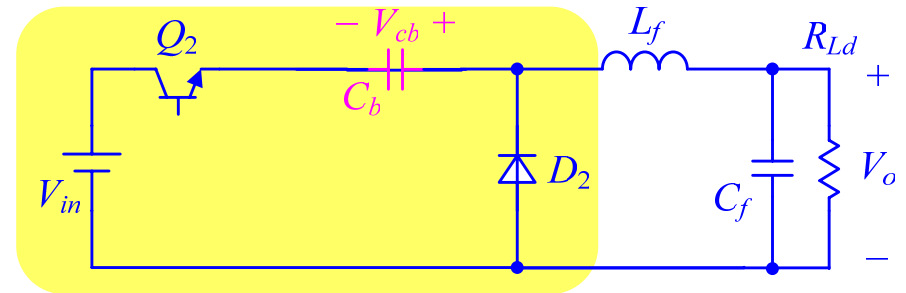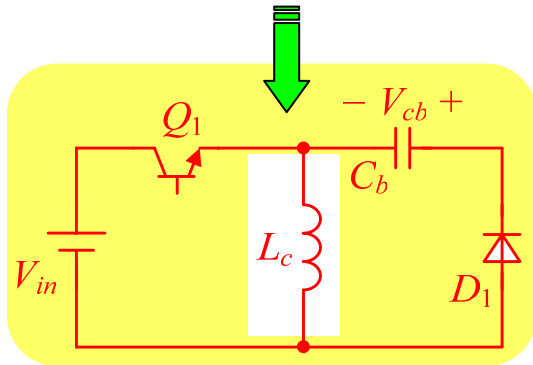
$$= D \left(V_{in} + \frac{D}{1-D} V_{in} \right)$$






Derivation of SEPIC

☹ Negative output voltage







☺ Positive output voltage

$$\frac{V_{cb}}{V_{in}} = \frac{D}{1-D}$$
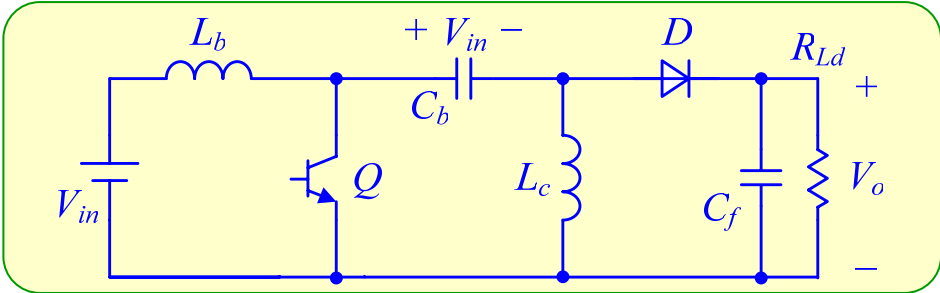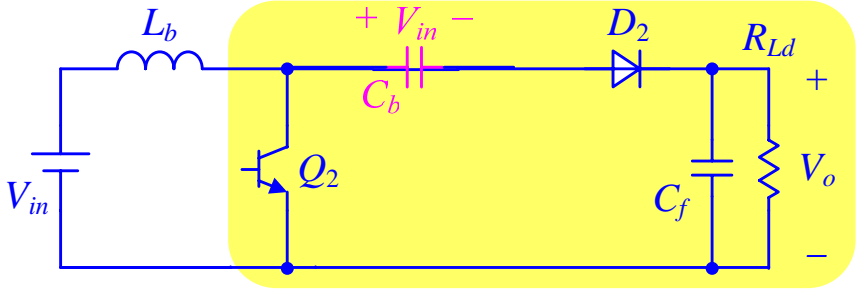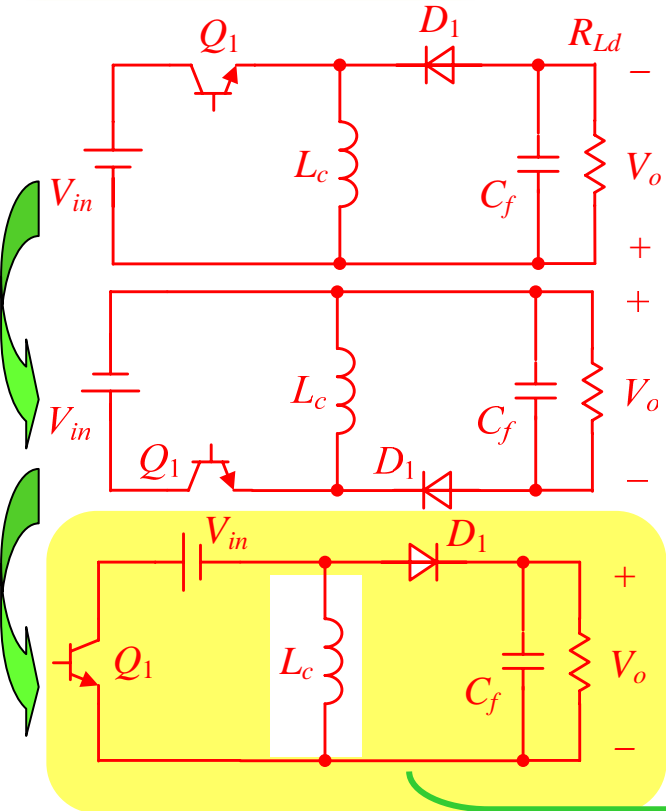
$$V_o = \frac{D}{1-D} V_{in} = \frac{1}{1-D} V_{in} - V_{in}$$



Comparison of the Six Converters

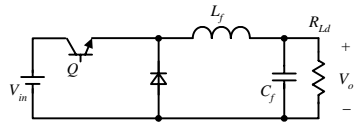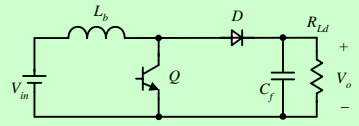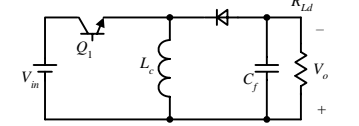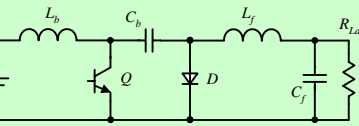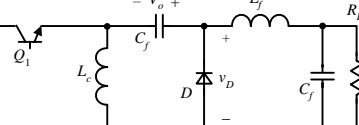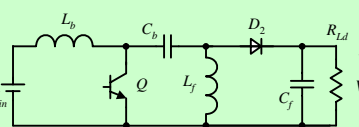Converter	Topology	Voltage Conversion Ratio	Output Voltage Polarity	Input Current Ripple	Output Current Ripple	Configuration
Buck		$\frac{V_o}{V_{in}} = D$ ↓	+	Large	Small	Simple
Boost		$\frac{V_o}{V_{in}} = \frac{1}{1-D}$ ↑	+	Small	Large	Simple
Buck-Boost		$\frac{V_o}{V_{in}} = \frac{D}{1-D}$ ↓↑	-	Large	Large	Simple
Cuk		$\frac{V_o}{V_{in}} = \frac{D}{1-D}$ ↓↑	-	Small	Small	Complex
Zeta		$\frac{V_o}{V_{in}} = \frac{D}{1-D}$ ↓↑	+	Large	Small	Complex
Sepic		$\frac{V_o}{V_{in}} = \frac{D}{1-D}$ ↓↑	+	Small	Large	Complex

Thanks for your attention !

Questions? / Answer!